



Lecture 3

Review on Digital Logic (Part 2)

Xuan 'Silvia' Zhang

Washington University in St. Louis

<http://classes.engineering.wustl.edu/ese461/>

Circuit Optimization



- Simplest implementation
- Cost criterion
 - literal cost (L)
 - gate input cost (G)
 - gate input cost with NOTs (GN)
- Examples (all the same function):
 - $F = BD + AB'C + AC'D'$ L =
 - $F = BD + AB'C + AB'D' + ABC'$ L =
 - $F = (A + B)(A + D)(B + C + D')(B' + C' + D)$ L =
 - Which solution is best?

Half Adder



- Truth Table


X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- Expression

- $S = X \oplus Y$

- $C = X \cdot Y$

- Logic Implementation

 

Full Adder




- Expression

- $S_i = A_i \oplus B_i \oplus C_i$
- or $C_{i+1} = A_i B_i + (A_i \oplus B_i) C_i$
- $C_o = AB + (A \oplus B) C_i$


Alternatively

- G = generate (=AB) and
- P = propagate (=A \oplus B)


 
- $C_{i+1} = G_i + P_i \cdot C_i$
- or $C_o = (G = \text{Generate}) \text{ OR } (P = \text{Propagate AND } C_i = \text{Carry In})$




Propagation Delay

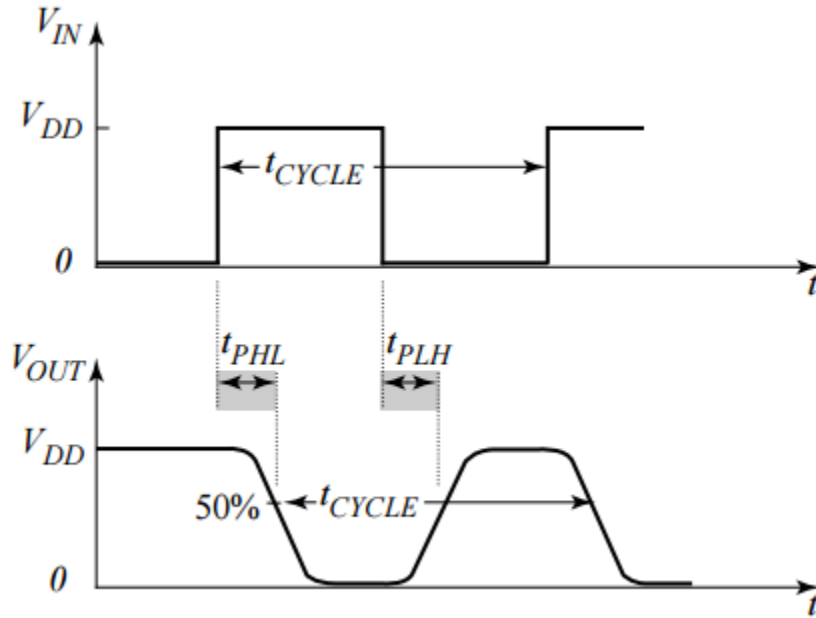

  
$$t_p = \frac{1}{2} (t_{PHL} + t_{PLH})$$



$t=0^-$

 

$t=0^+$

 

$t \rightarrow \infty$

Delay of a Full Adder




- Delay of the Sum and Carry bit

- $S_0 = A_0 \oplus B_0 \oplus C_0$
2 delays
2+2=4 delays

- $C_1 = A_0 B_0 + (A_0 \oplus B_0) C_0$
@2
@3
2+2=4 delays

- $C_n?$



- $S_n?$

 

Ripple Carry Adder




- Cascade four 1-bit full adders

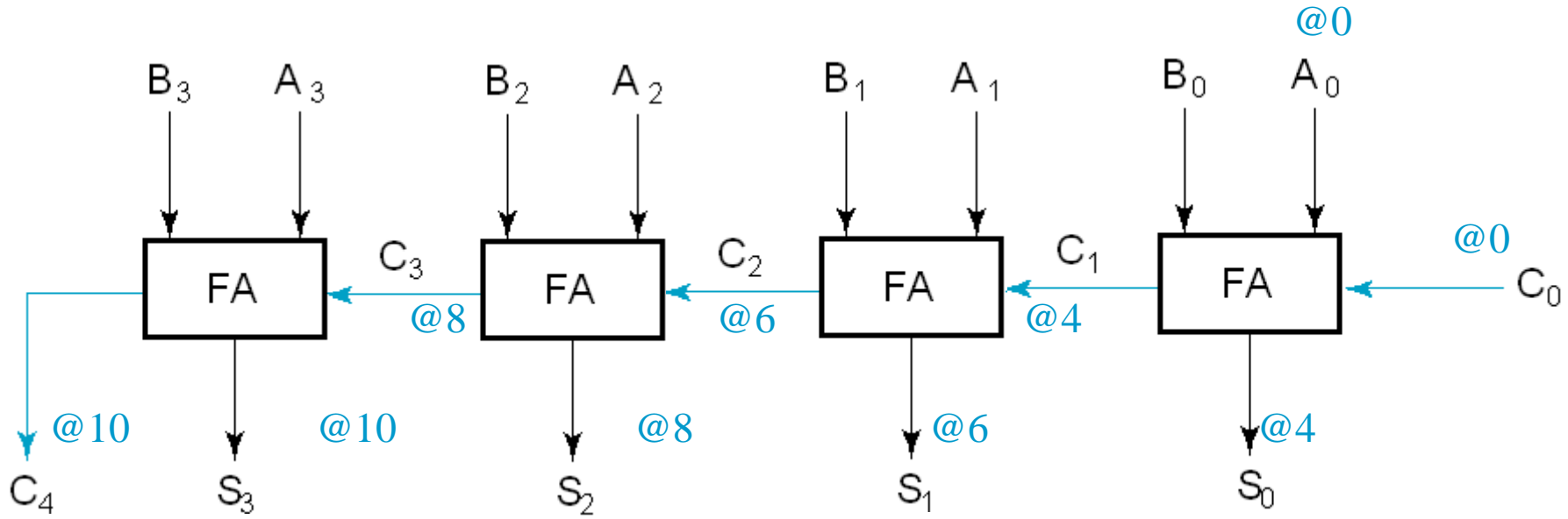 

Carry Lookahead Adder



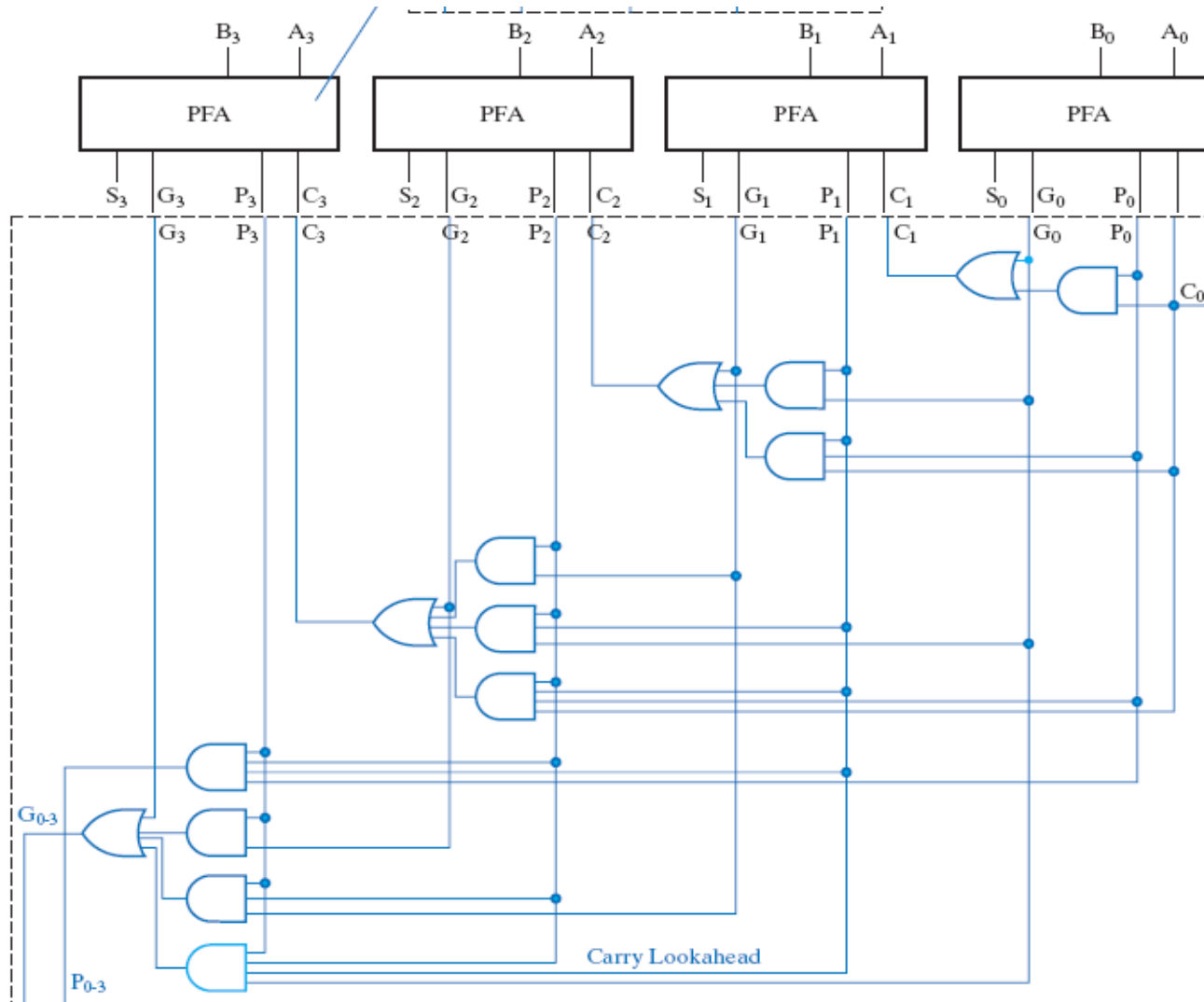- Separate circuit to calculate the carry



Revisit Number Representation



- Represent real numbers in hardware
 - accuracy
 - implementation complexity
 - robustness to errors
- Fixed-point
 - e.g. $(11.0101)_2$
 - 2's complement fractional binary number

Fract. binary format	Number of integer bits (including sign bit)	Number of fractional bits	Maximum positive decimal value	Maximum negative decimal value	Lsb decimal value
8.0	8	0	127.0	-128.0	1.0
7.1	7	1	63.5	-64.0	0.5
6.2	6	2	31.75	-32.0	0.25
5.3	5	3	15.875	-16.0	0.125
4.4	4	4	7.9375	-8.0	0.0625
3.5	3	5	3.96875	-4.0	0.03125
2.6	2	6	1.984375	-2.0	0.015625
1.7	1	7	0.9921875	-1.0	0.0078125

Fractional Binary Numbers



- 16-bit DSP
 - digital signal processor (DSP)
 - 1.15 (Q15) format

16-bit binary format	Decimal value	Binary	Hex
Two's complement	0.9999694824...	0 _◇ 111 1111 1111 1111	7FFF
1.15 (Q15) format	0.5	0 _◇ 100 0000 0000 0000	4000
	0.25	0 _◇ 010 0000 0000 0000	2000
resolution →	0.0000305175...	0 _◇ 000 0000 0000 0001	0001
	0	0 _◇ 000 0000 0000 0000	0000
	-0.0000305175...	1 _◇ 111 1111 1111 1111	FFFF
	-0.25	1 _◇ 110 0000 0000 0000	E000
	-0.5	1 _◇ 100 0000 0000 0000	C000
	-1.0	1 _◇ 000 0000 0000 0000	8000

- Two Q15 number multiply = Q30 (2.30 format)

Fixed Point Multiplication



- Two Q15 number multiply
 - $Q15 \times Q15 = Q30$
 - 2.30 format, 32 bits, two sign bits
 - MSB: extended sign bit
 - need to truncate back to 1.15 format
 - left shift by one bit, storing upper 16 bits
 - right shift by 15 bits, storing lower 16 bits
- Dynamic range
 - in a b-bit system

$$\text{dynamic range}_{\text{linear}} = \frac{\text{largest positive word value}}{\text{smallest positive word value}}$$
$$= \frac{2^b - 1}{1} = 2^b - 1.$$



Arithmetic Logic


Sequential Logic

Memory Circuit

Sequential Logic



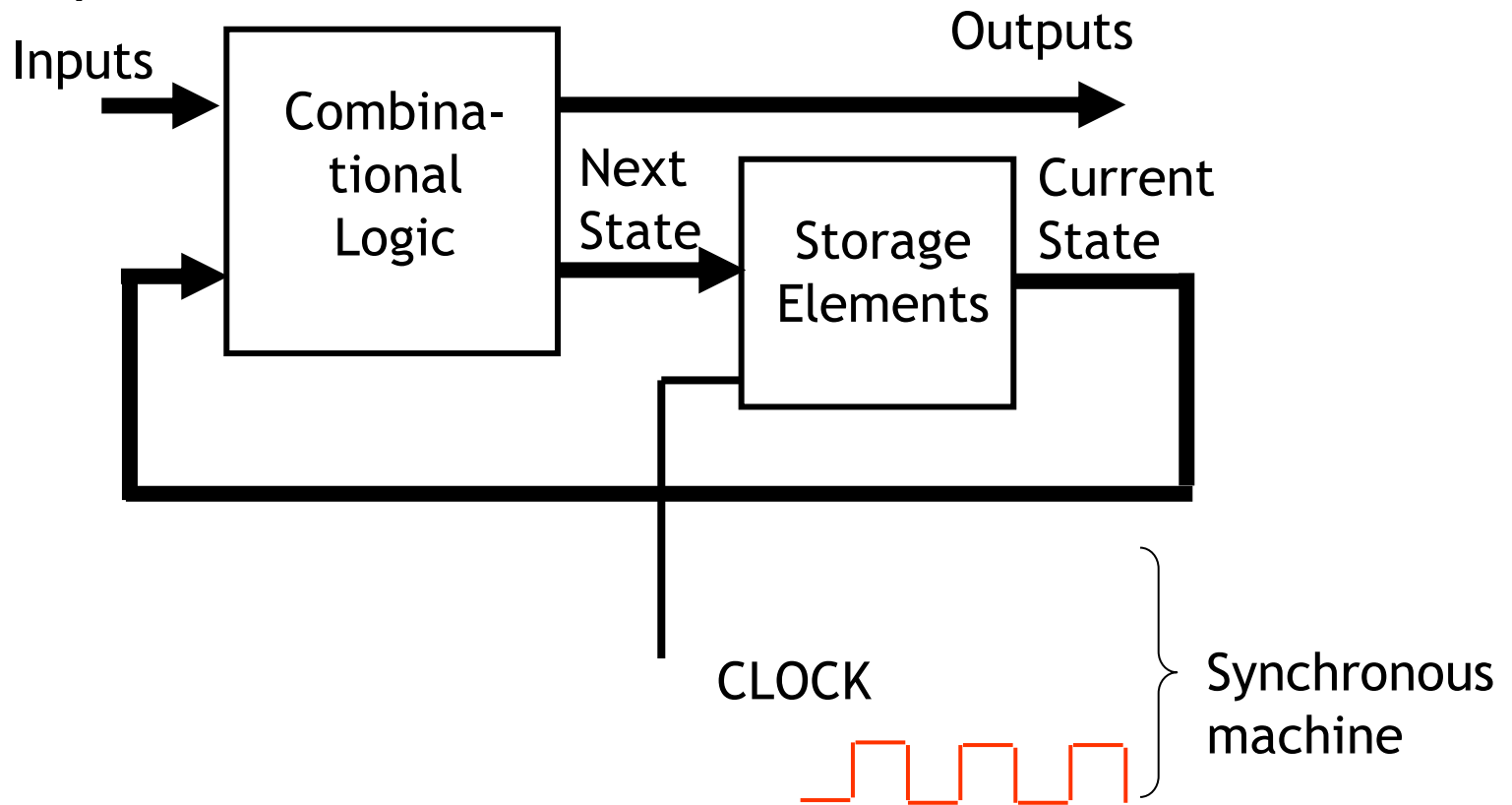
- Next state function
 - Next State = $f(\text{Inputs}, \text{State})$
- Output function




Finite State Machine (FSM)



 - Mathematical model of computation
 - consist of a finite number of “states”
 - only one state at a time (Current State)
 - change state at a triggering event or condition
- Mealy machine
 - $\text{Outputs} = g(\text{Inputs}, \text{State})$



 
- Moore machine
 - $\text{Outputs} = h(\text{State})$



SR Latch




- Basic NOR latch

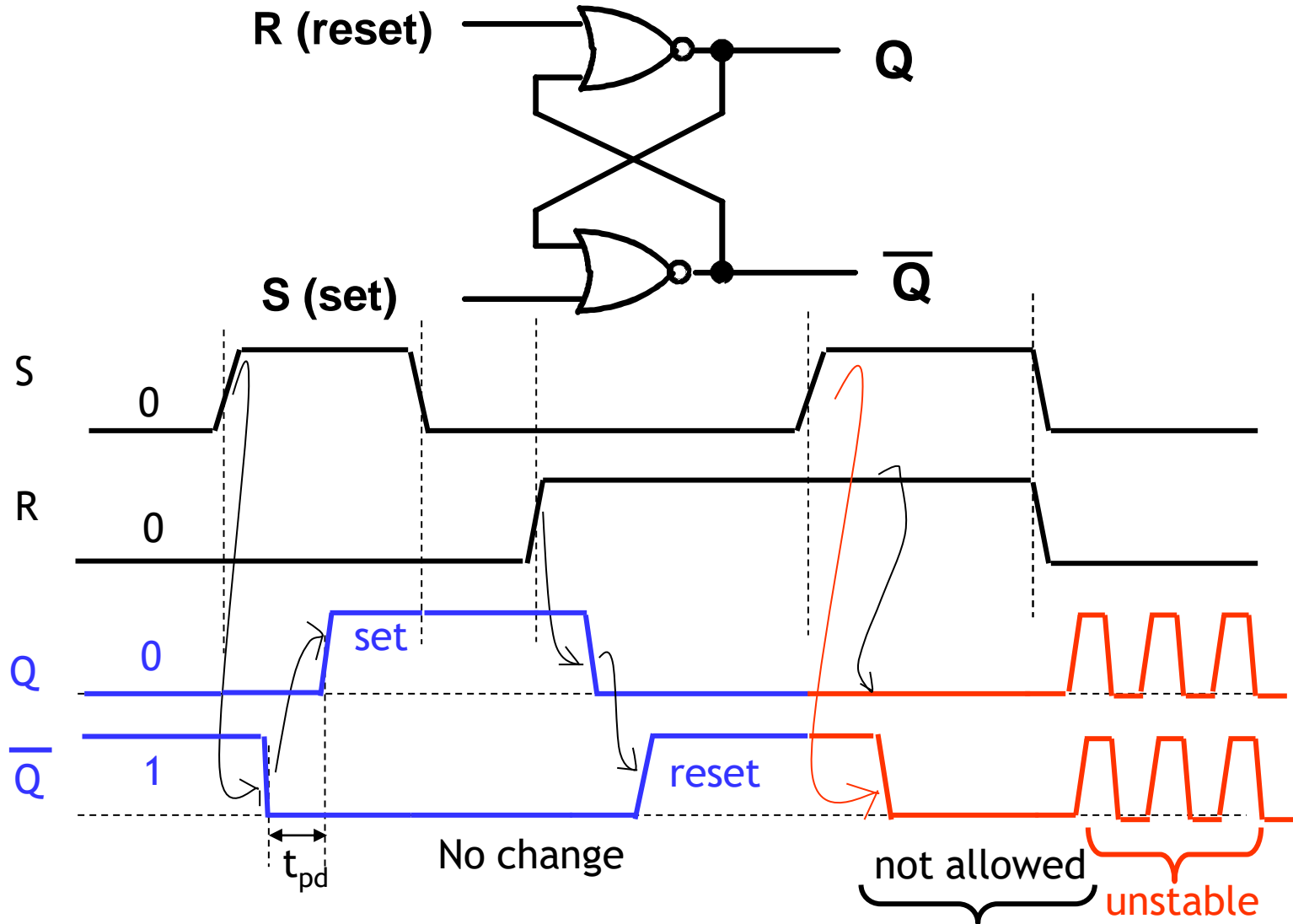



Other SR Latches



- Clocked

 

- NAND SR latch

  


D Latch



- Truth table


SR latch:

S	R	Q^+	\bar{Q}^+
0	0	hold,	
0	1	0	1
1	0	1	0
1	1	0	0

 


D latch


D	$Q(t+1)$
0	0
1	1

 

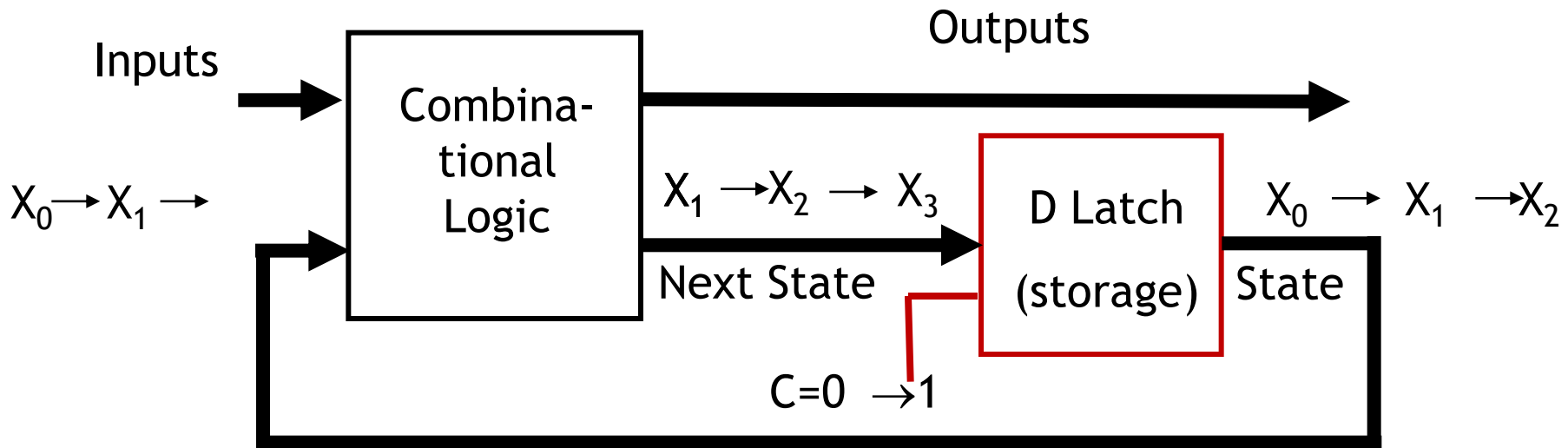- Latch timing issue
 - transparent when $C = 1$
 - state should change only once every new clock cycle




 
- Master-slave flip flop
 - break feedthrough



Flip-Flop Timing Issue



- 1' catching

 
 


wrong output should have been 0

Edge-Triggered D Flip-Flop (DFF)



  
- Why edge trigger?
- D replace S and R input



Sequential Circuit Analysis



 - Design steps
 - word description
 - state diagram
 - state table
 - select flip-flop types
 - input to FF and output
 - verification
- Reverse engineering




Input Equations



- To flip-flops
 - $D_A = A(t)x(t) + B(t)x(t)$
 - $D_B = A(t)x(t)$

- Output y
 - $y(t) = x(t)(B(t) + A(t))$

 

State Table



- For the example: $A(t+1) = A(t)x(t) + B(t)x(t)$
 $B(t+1) = \bar{A}(t)x(t)$
 $y(t) = \bar{x}(t)(B(t) + A(t))$

Inputs of the table Outputs of the table

Present State		Input	Next State		Output
A(t)	B(t)	x(t)	A(t+1)	B(t+1)	y(t)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

2^3 rows
 (2^{m+n}) rows


m : no. of FF
 n : no. of inputs

State Diagram




- Conventions

Moore Machine

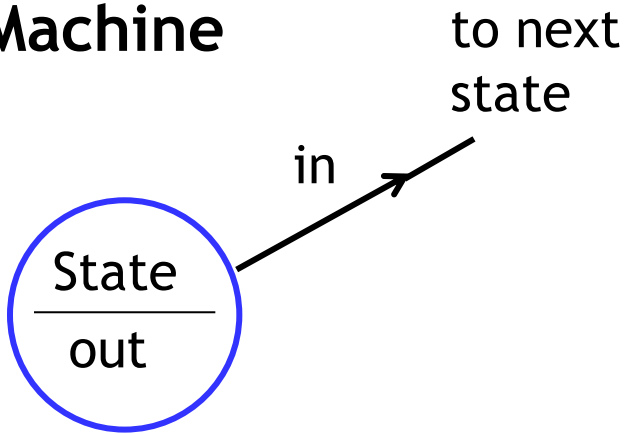


Example:

 

Moore type output depends only on state

Mealy Machine

 

Mealy type output depends on state and input



Arithmetic Logic

Sequential Logic



Memory Circuit

- Applications
 - CPU register file, cache, embedded memory, DSP
- Characteristics
 - 6 transistor per cell, other topologies
 - no need to refresh
 - access time ~ cycle time
 - no charge to leak
 - faster, more area, more expensive

SRAM Operation



 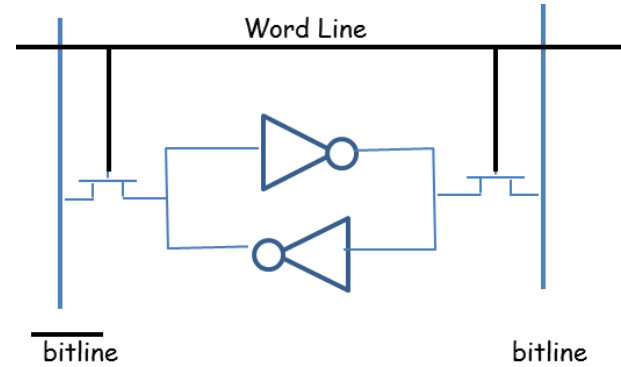- Standby
 - word line de-asserted
- Read
 - precharge bit lines
 - assert WL
 - BL rise/drop slightly
- Write
 - apply value to BL
 - assert WL
 - input drivers stronger



Summary



Number Representation

Boolean Logic and Gates

Combinational Logic

Arithmetic Logic

Sequential Logic

Memory Circuit



Questions?

Comments?

Discussion?

Homework #2



- Download problem sets from class website
- Due 09/12 (Monday) in class
- 2-day grace period