



Lecture 12

Timing Analysis, Part 1

Xuan 'Silvia' Zhang
Washington University in St. Louis

<http://classes.engineering.wustl.edu/ese461/>

Types of Simulation



- Behavioral simulation
 - black box with inputs and outputs
- Functional simulation
 - unit-delay simulation; ignore timing
- Static timing analysis
 - derive the longest delay path
- Gate-level simulation
 - aka. logic simulation; check ASIC timing performance
 - logic cell as black box modeled by functions with input signal as variables
- Switch-level simulation
- Transistor or circuit-level simulation

higher level
less accurate
faster



lower level
more accurate
slower

- “What is the longest delay in my circuit?”
 - critical path delay
 - determines the max clock frequency
- Dynamic analysis
 - vector-based simulation
 - find the input vector that activates the longest path
 - false path example
- Static timing
 - worst case analysis
 - no consideration of the input vector

- Timing vs delay model
 - timing model: delay outside the logic cells
 - delay model: delay inside the logic cells
- Types of delays
 - pin-to-pin: input pin to output pin, excluding interconnect
 - pin delay: delay lumped to pin
 - net/wire delay: interconnect
- Linear delay model
 - prop-ramp delay model

$$t_{PD} = R (C_{out} + C_p) + t_q$$



- standard cell library data book

$$\text{pin I (input)} = 0.060 \text{ pF} \quad \text{pin ZN (output)} = 0.038 \text{ pF}$$

Timing in Digital Logic




- Setup time
- Hold time

  

Timing in Digital Logic




- Launch edge and latch edge

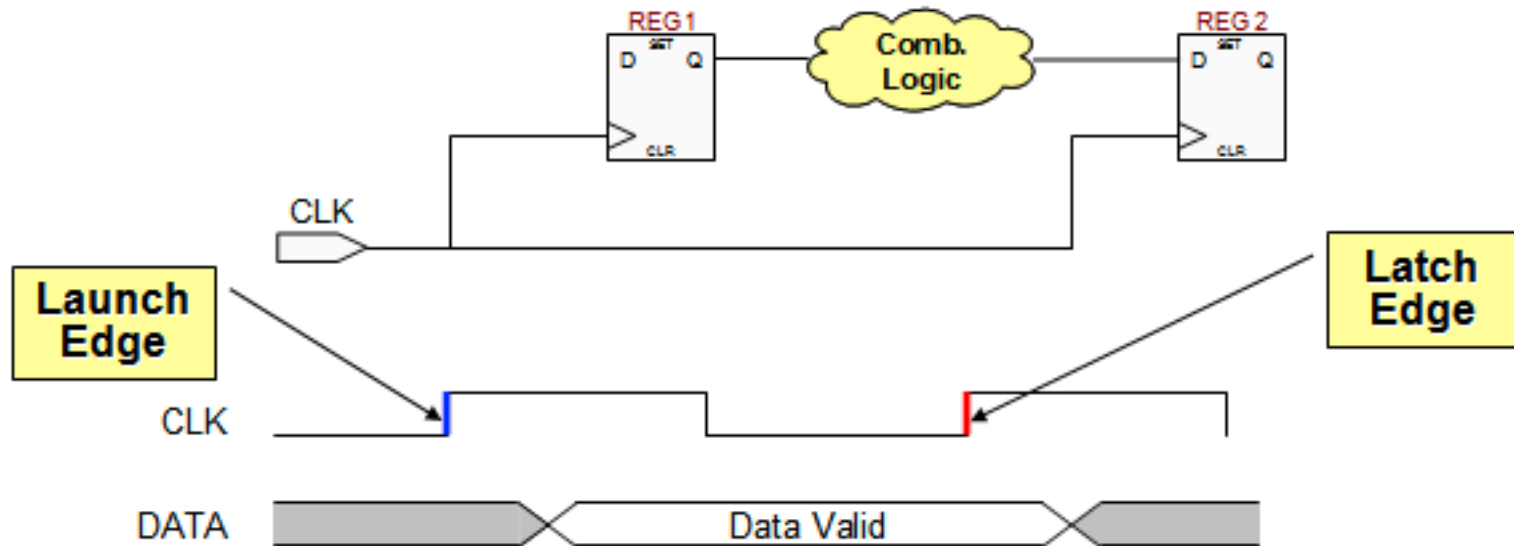

Timing in Digital Logic



- Data arrival time: using launch edge

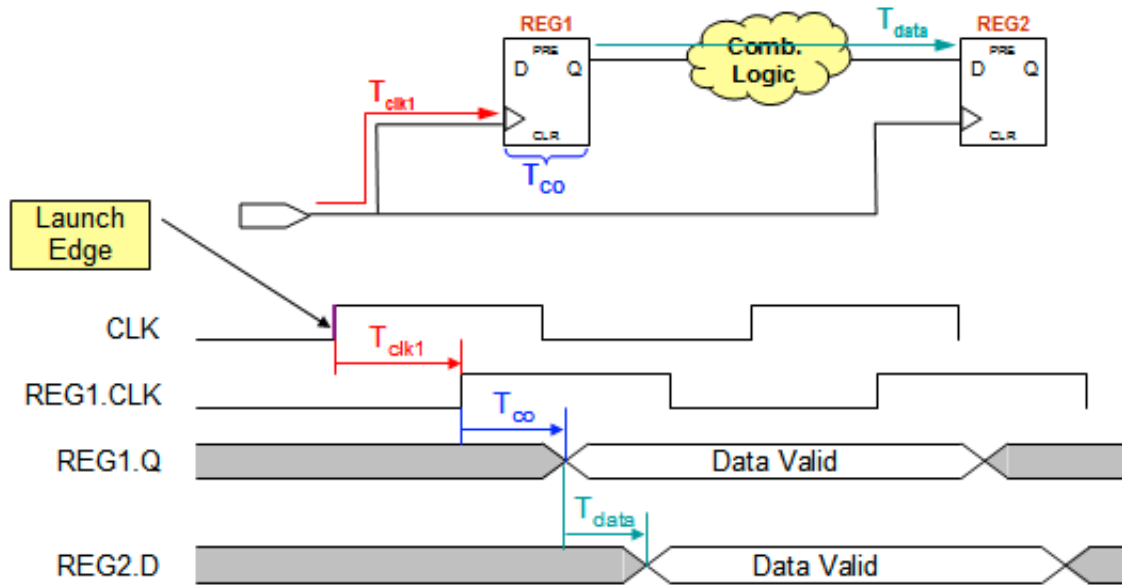


Data Arrival Time = launch edge + T_{clk1} + T_{co} + T_{data}

Tclk	Clock Skew	Tco	FF Clock-> Output	Tdata	Logic Delay
------	------------	-----	-------------------	-------	-------------

Timing in Digital Logic



- Clock arrival time

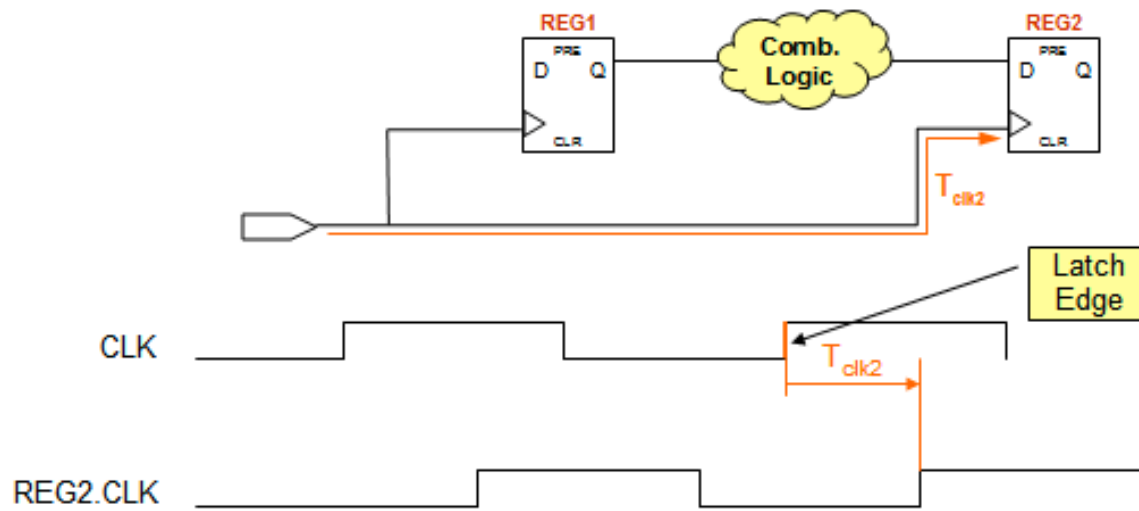


Clock Arrival Time = latch edge + T_{clk2}

Timing in Digital Logic



- Data required time (setup): latch edge

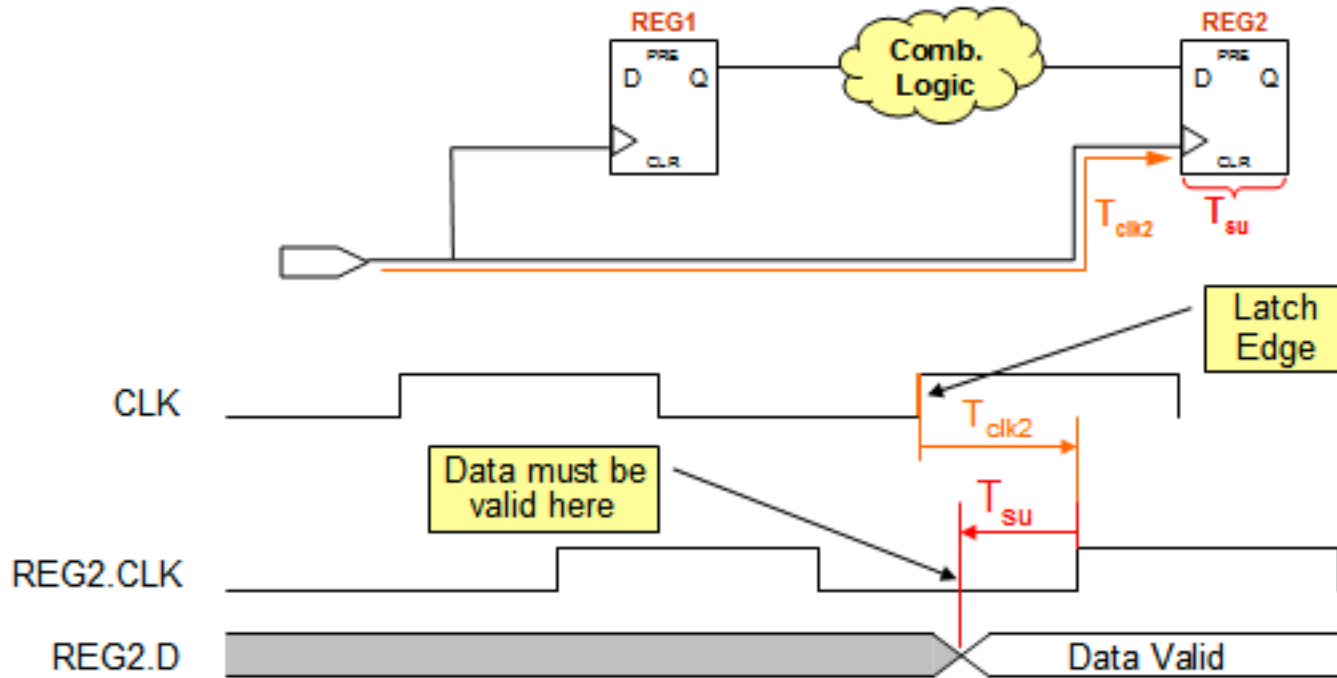


Data Required Time = Clock Arrival Time - T_{su} - Setup Uncertainty

Timing in Digital Logic



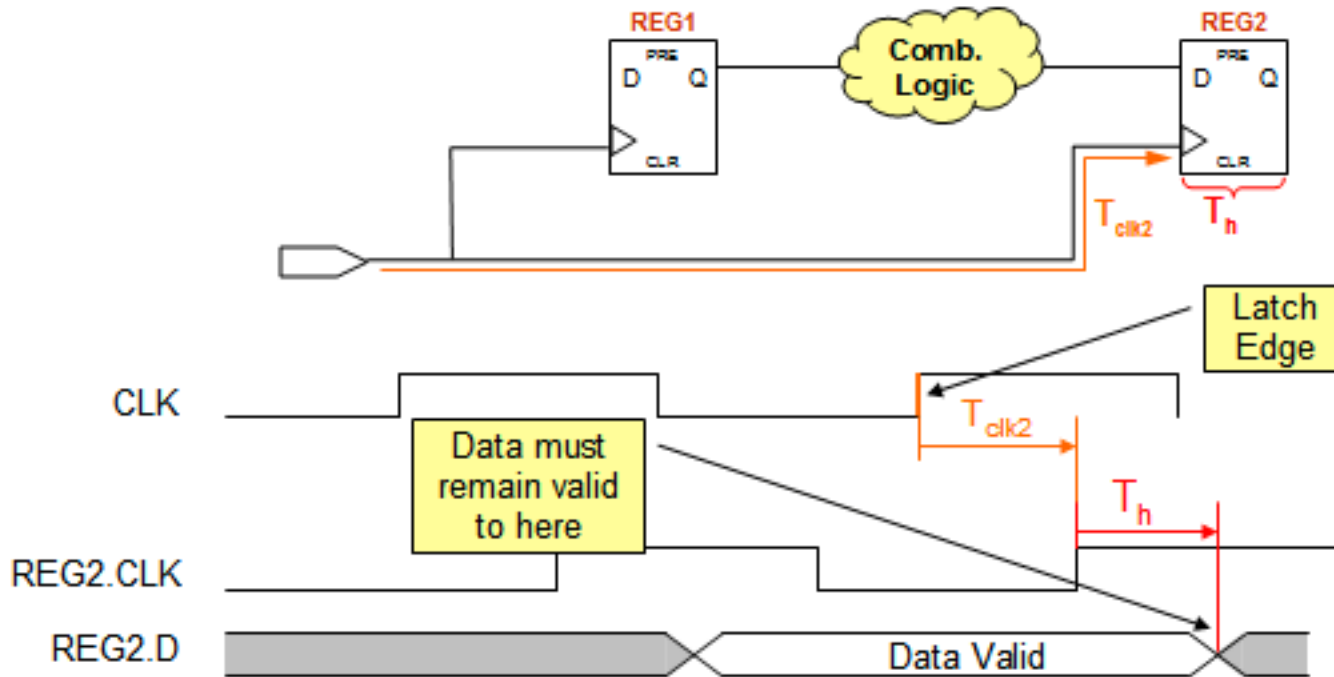- Data required time (hold): next launch = latch




Data Required Time = Clock Arrival Time + T_h + Hold Uncertainty

Timing in Digital Logic



- Setup slack

 

Setup Slack = Data Required Time – Data Arrival Time


Positive slack
Timing requirement met

Negative slack
Timing requirement not met

Timing in Digital Logic



- Hold slack

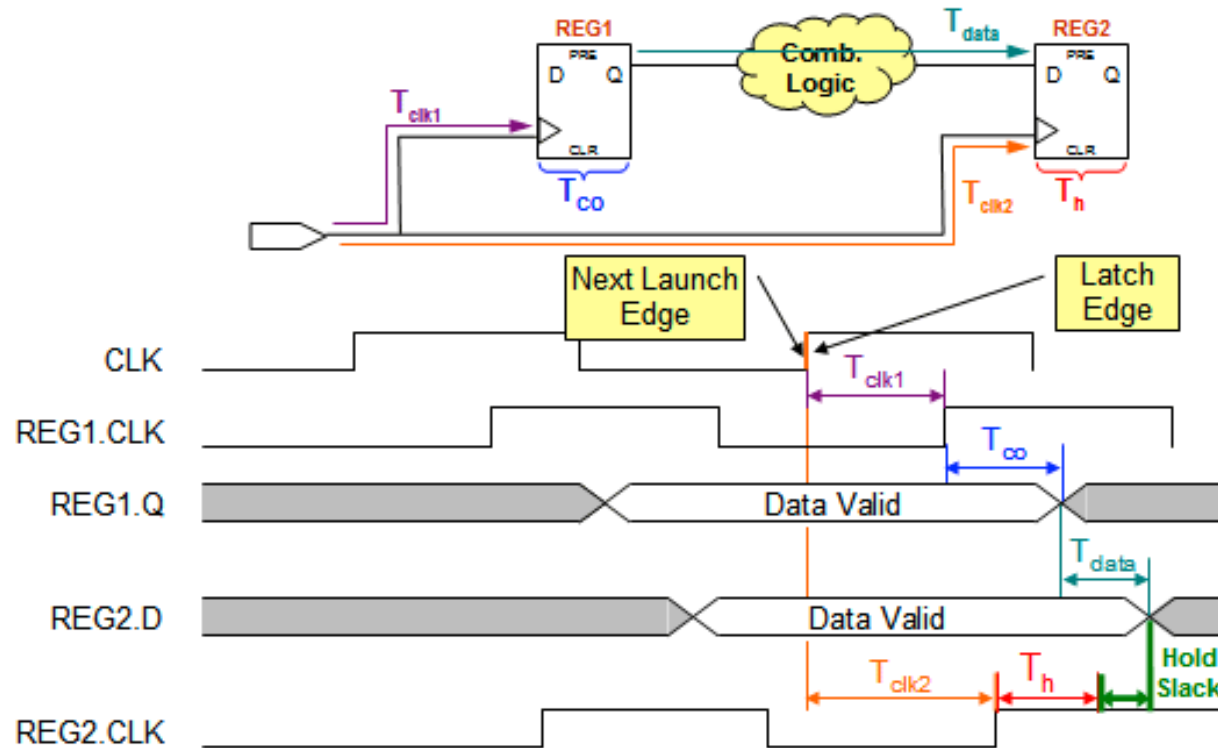

$$\text{Hold Slack} = \text{Data Arrival Time} - \text{Data Required Time}$$


Positive slack
Timing requirement met

Negative slack
Timing requirement not met

Static Timing Analysis



 
- Timing Model and Timing Constraint
- Arrival Time (AT) and Required Time (RT)



Static Timing Analysis



- Library Data

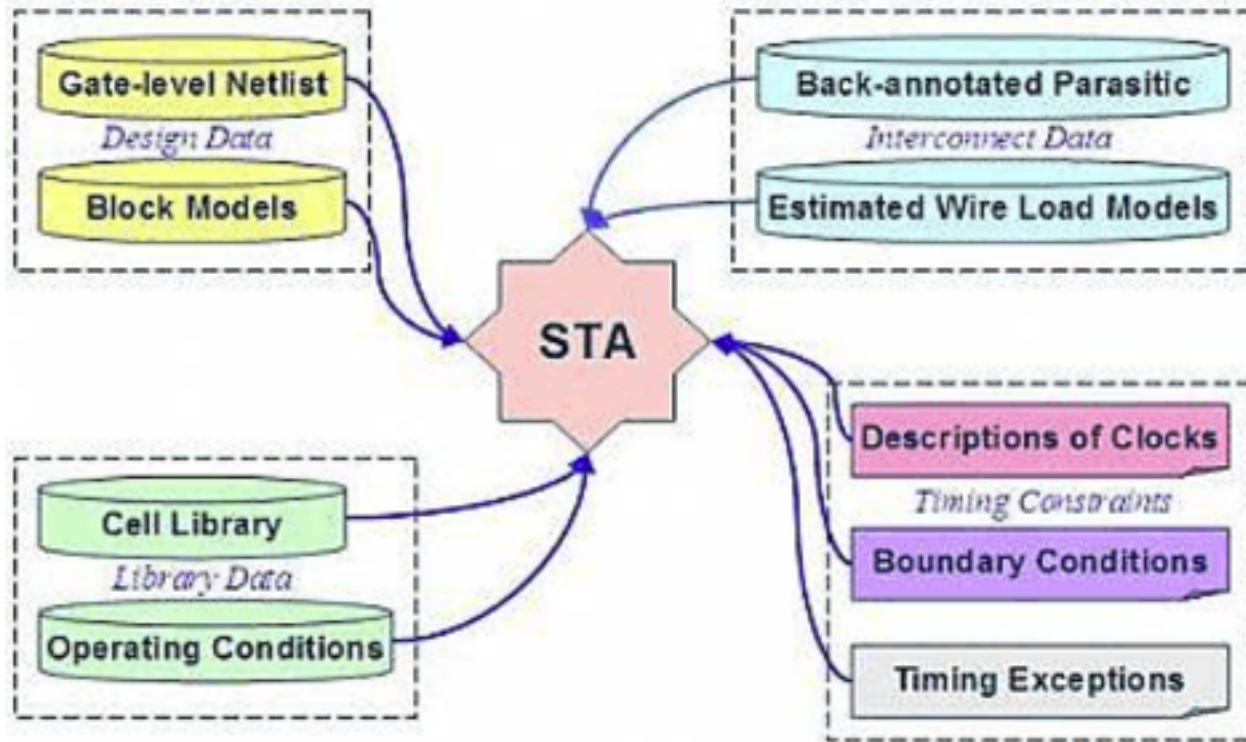


- Timing type
 - Combinational Timing (Delay)
 - Setup Timing (Check)
 - Hold Timing (Check)
 - Edge Timing (Delay)
 - Present and Clear Timing (Delay)
 - Recovery Timing (Check)
 - Removal Timing (Check)
 - Three State Enable & Disable Timing (Delay)
 - Width Timing (Check)

Static Timing Analysis




- Combinational Timing (Delay)

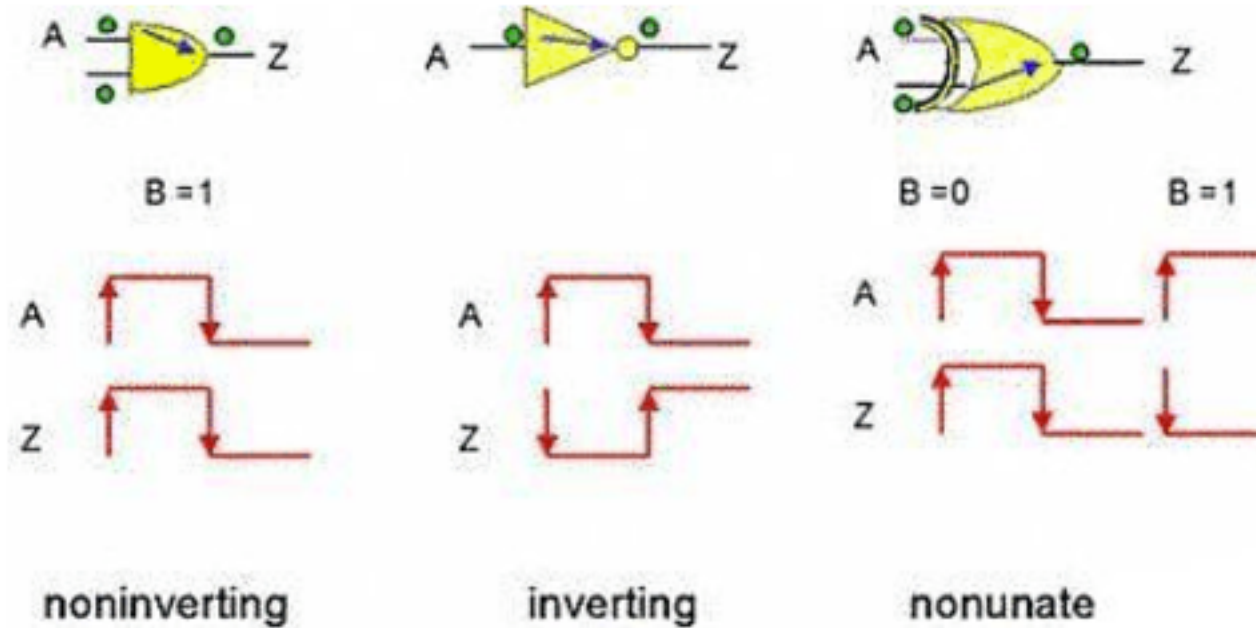


Static Timing Analysis



- Setup Timing (Check)

 


- Hold Timing (Check)

 


Static Timing Analysis



- Edge Timing (Delay)

 



- Preset and Clear Timing (Delay)

 



Static Timing Analysis



- Recovery Timing (Check)

  



- Removal Timing (Check)

  



Static Timing Analysis



  - Three State Enable & Disable Timing (Delay)



- Width Timing (Check)

  



- Interconnect Delay
 - Depends on P&R (Place and Routing)
 - Wireload Model: Fan-out
 - RC Extraction
 - Back-annotate for STA

Reference



- Chapter 13 from the ASIC book



Questions?

Comments?

Discussion?