



Lecture 13

Timing Analysis, Part 2


Xuan 'Silvia' Zhang
Washington University in St. Louis

<http://classes.engineering.wustl.edu/ese461/>

Review: Timing in Digital Logic



- Setup slack

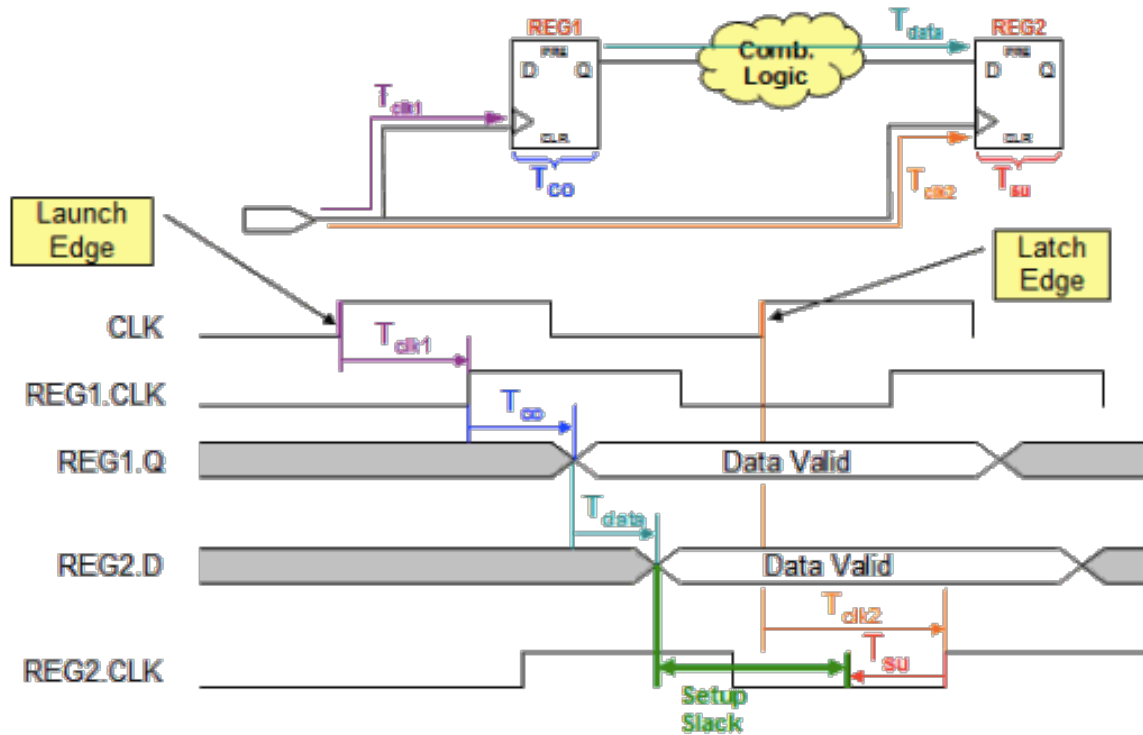

$$\text{Setup Slack} = \text{Data Required Time} - \text{Data Arrival Time}$$


Positive slack
Timing requirement met

Negative slack
Timing requirement not met

Review: Timing in Digital Logic



- Hold slack

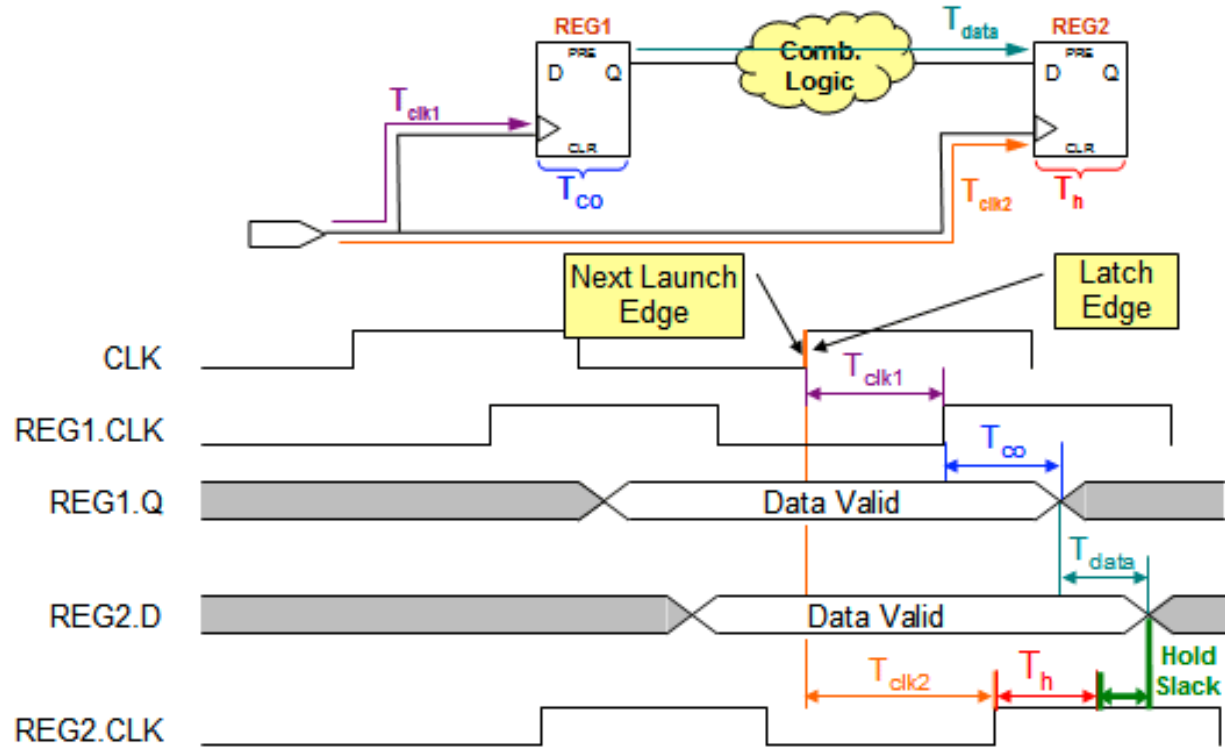

$$\text{Hold Slack} = \text{Data Arrival Time} - \text{Data Required Time}$$

Positive slack
Timing requirement met

Negative slack
Timing requirement not met

Review: Static Timing Analysis




- Timing Type
 - Combinational Timing (Delay)
 - Setup Timing (Check)
 - Hold Timing (Check)
 - Edge Timing (Delay)
 - Present and Clear Timing (Delay)
 - Recovery Timing (Check)
 - Removal Timing (Check)
 - Three State Enable & Disable Timing (Delay)
 - Width Timing (Check)
- Interconnect Delay

Static Timing Analysis



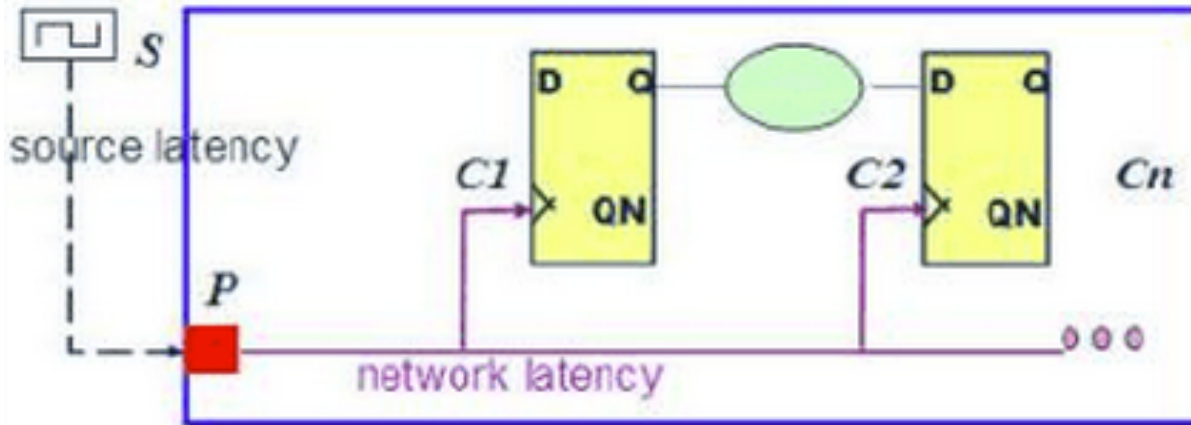- Timing Constraints
 - path delay between two flip-flops must be less than one clock period
 - once clock specification is fixed, timing constraint is fixed between all flip flops




Static Timing Analysis



- Clock Specification

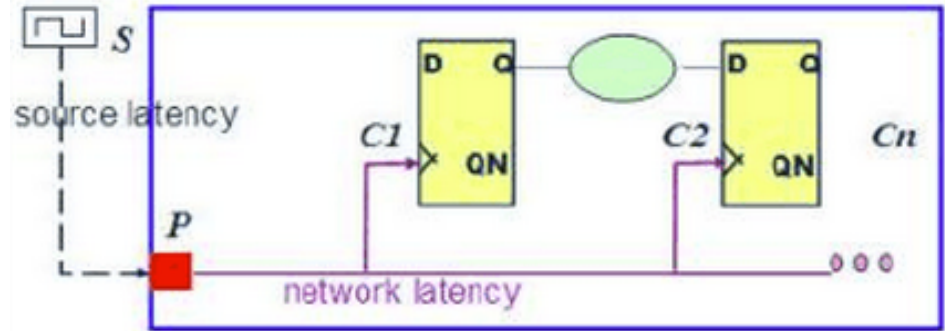
- period
- source latency
- network latency
- uncertainty
- skew



Ideal Clock Source



C1 / C2 (after P&R)

 

C1 (after P&R)




C2 (after P&R)



Static Timing Analysis




 
- Path
 - FF Clock to FF Input
 - PI (Primary Input) to FF Input
 - FF Clock to PO (Primary Output)
 - PI to PO



Static Timing Analysis



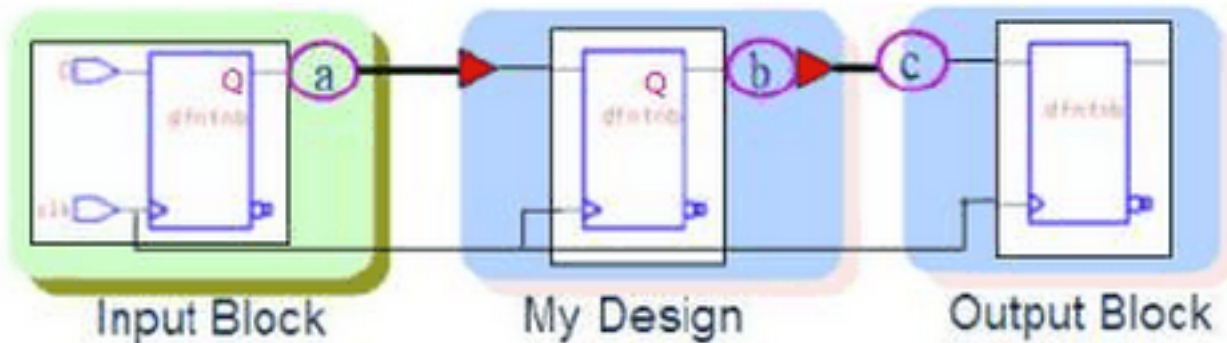 
- Boundary Conditions: External Environment
 - driving cell
 - input transition time
 - output capacitance load
 - input delay
 - output delay




Static Timing Analysis



 - Once boundary condition is defined, all four types of paths can be converted into the 1st type of path



STA Example

 


- Timing Model

Gate 0-1	3ns	FF Setup	1ns	Clock N.L. (Dclkn)	3ns
Gate 1-0	2ns	FF Hold	1ns	Clock Uncertainty (Dclku)	1ns
Net	2ns	Clock	14ns	Input Delay (Da, Db, Dc)	1ns
FF CLK-Q	3ns	Clock S.L. (Dclks)	2ns	Output Delay (DY)	3ns

STA Example



- Find Timing Path

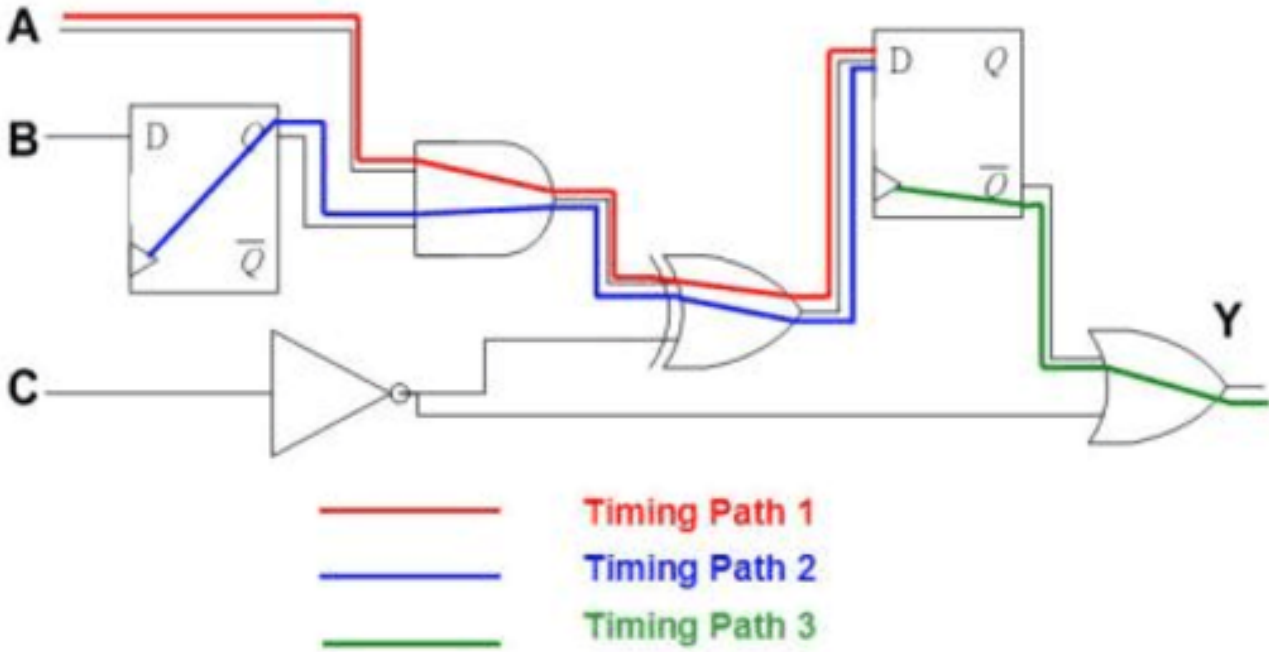


STA Example



- Path 1: Arrival Time when A: 0->1

$$AT = D_a + 2 + 3 + 2 + 3 + 2 = 13ns$$

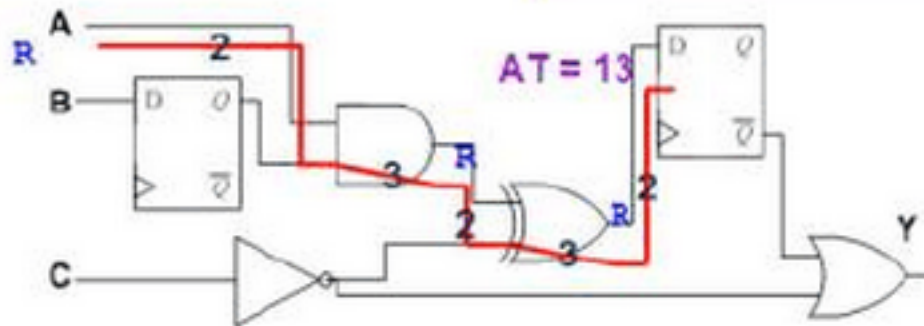


STA Example



- Path 1: Required Time

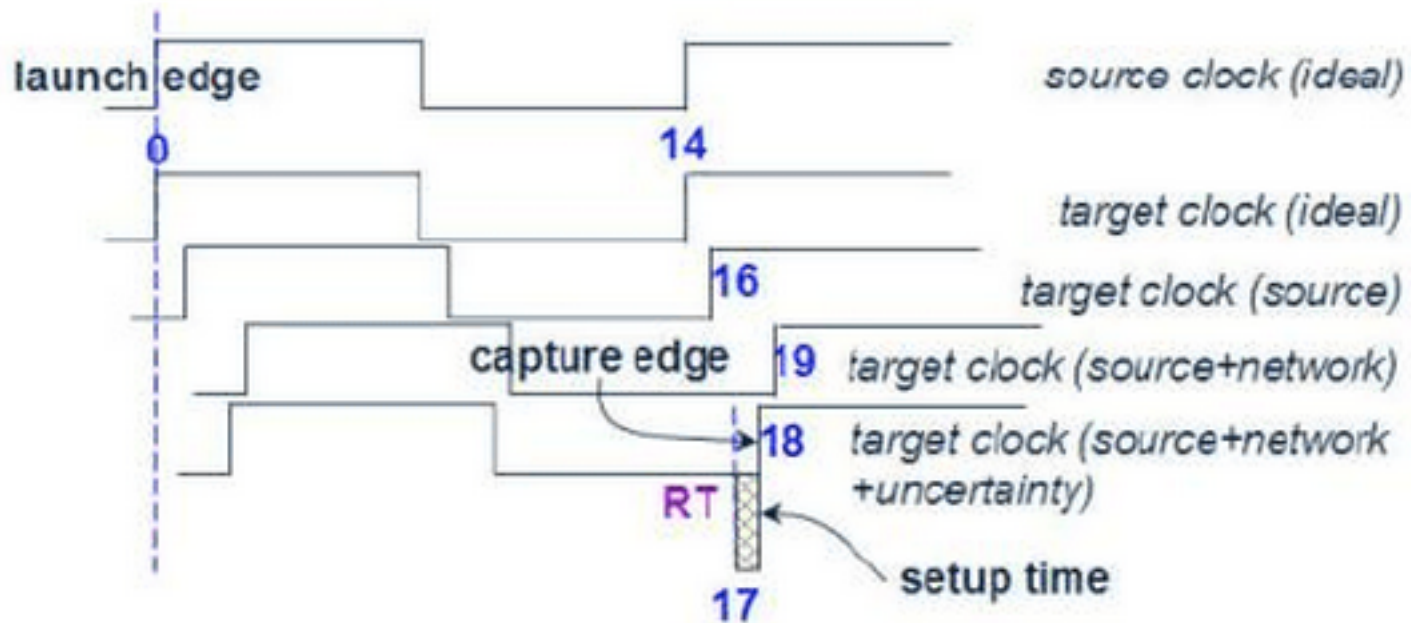
$$RT = D_{clkq} + D_{clks} + D_{clkt} - D_{clku} - T_s = 14 + 2 + 3 - 1 - 1 = 17ns$$



STA Example




- Path 1:
 - Slack 0->1
 - “+” = GOOD

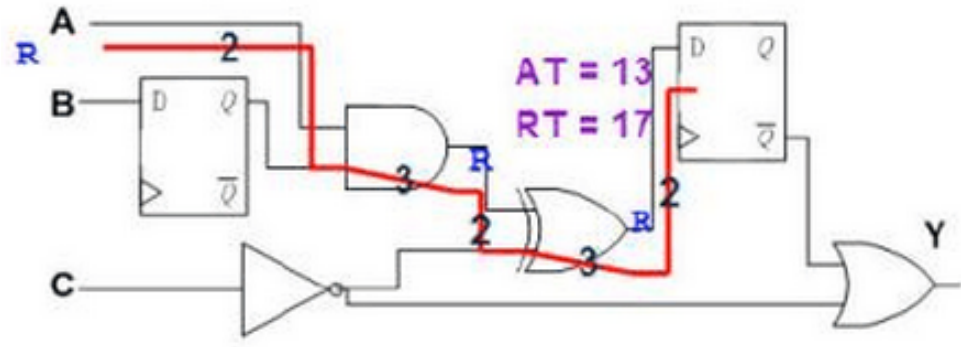

$$\text{Slack} = RT - AT = 17 - 13 = 4ns$$

- Slack 1->0
- “+” = GOOD

 


$$\text{Slack} = RT - AT = 17 - 12 = 5ns$$

STA Example



- Path 2: Arrival Time when B: 0->1
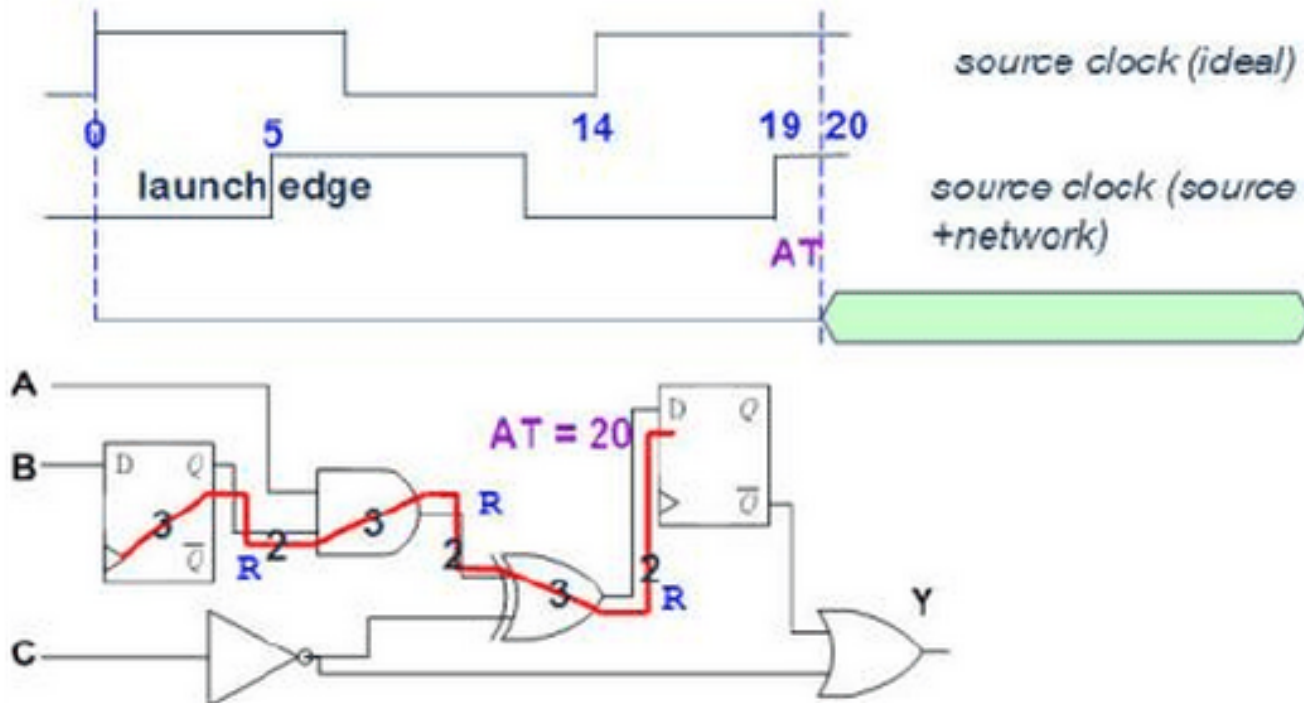
$$AT = D_{clk_s} + D_{clk_n} + 3 + 2 + 3 + 2 + 3 + 2 = 20ns$$





STA Example



- Path 2: Arrival Time when B: 1->0
 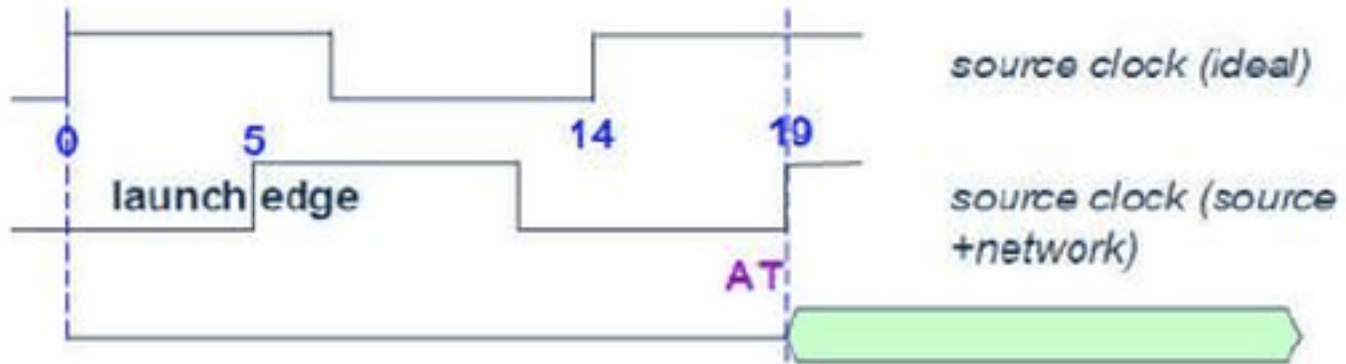
$$AT = D_{clk} + D_{clk} + 3 + 2 + 2 + 2 + 3 + 2 = 20ns$$




STA Example



- Path 2: Required Time

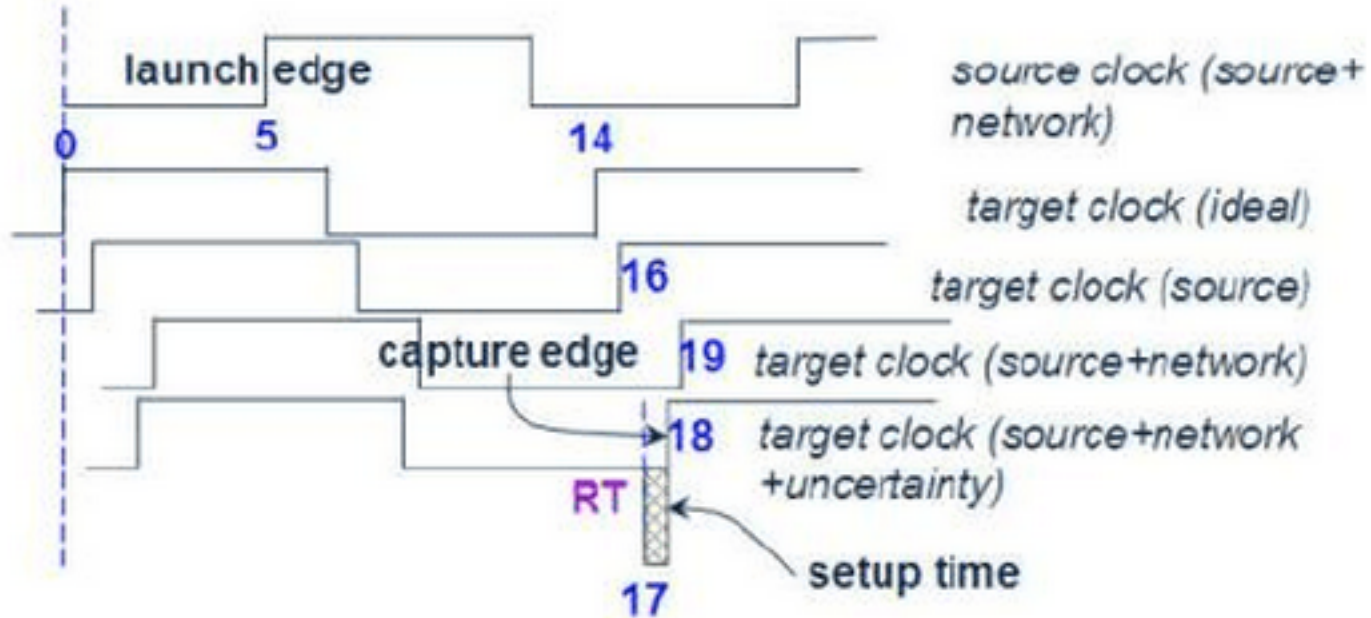
$$RT = D_{clkp} + D_{clks} + D_{clkt} - D_{clkd} - T_s = 14 + 2 + 3 - 1 - 1 = 17ns$$




STA Example



- Path 2:
 - Slack 0->1
 - “—” = BAD

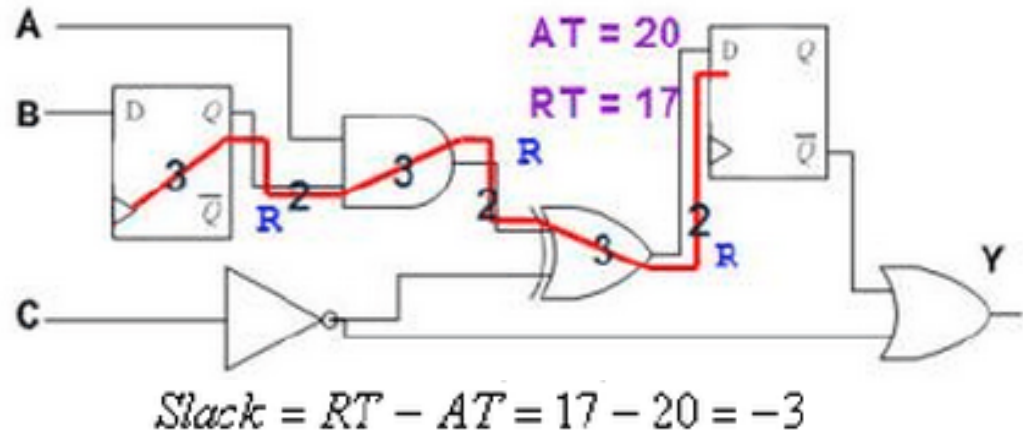

- Slack 1->0
- “—” = BAD

 


STA Example



- Path 3: Arrival Time: 0->1
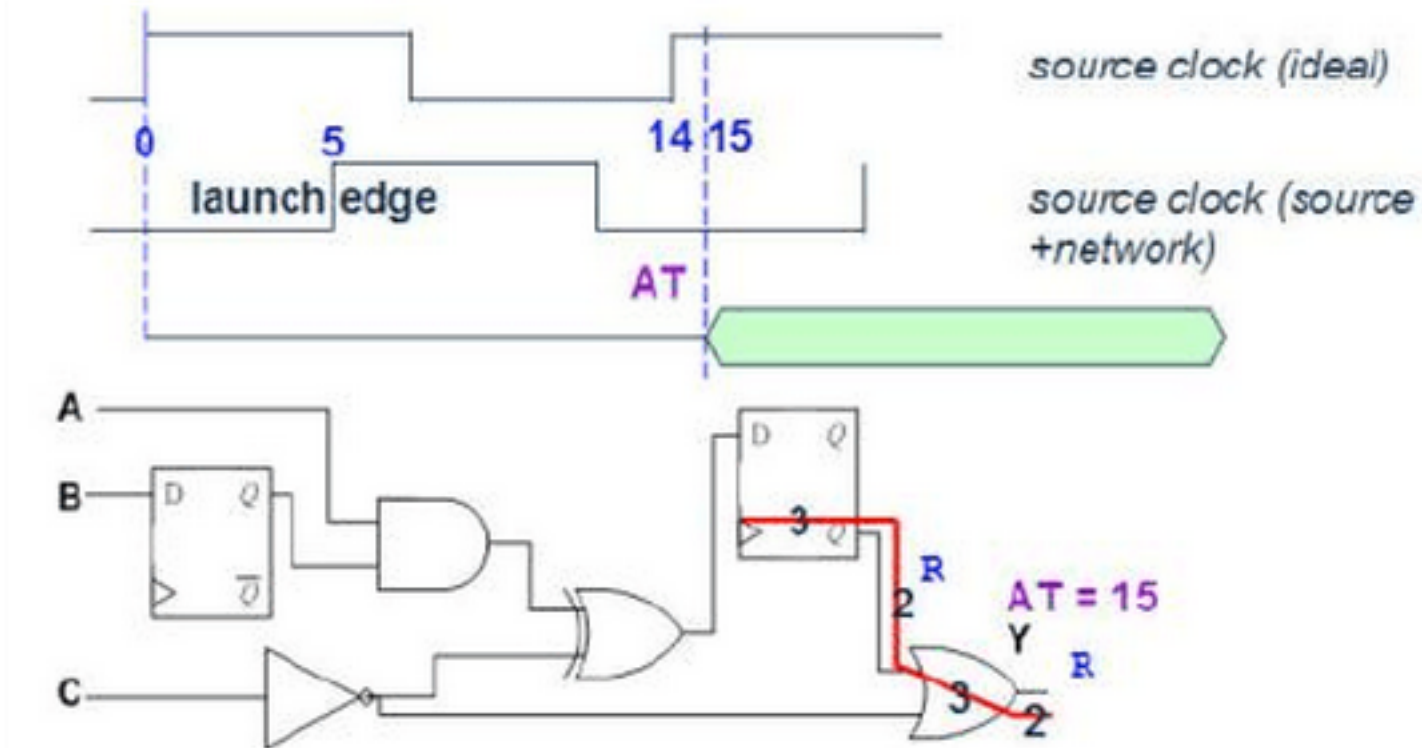
$$AT = D_{clk_s} + D_{clk_n} + 3 + 2 + 3 + 2 = 15ns$$




STA Example



- Path 3: Arrival Time: 1->0
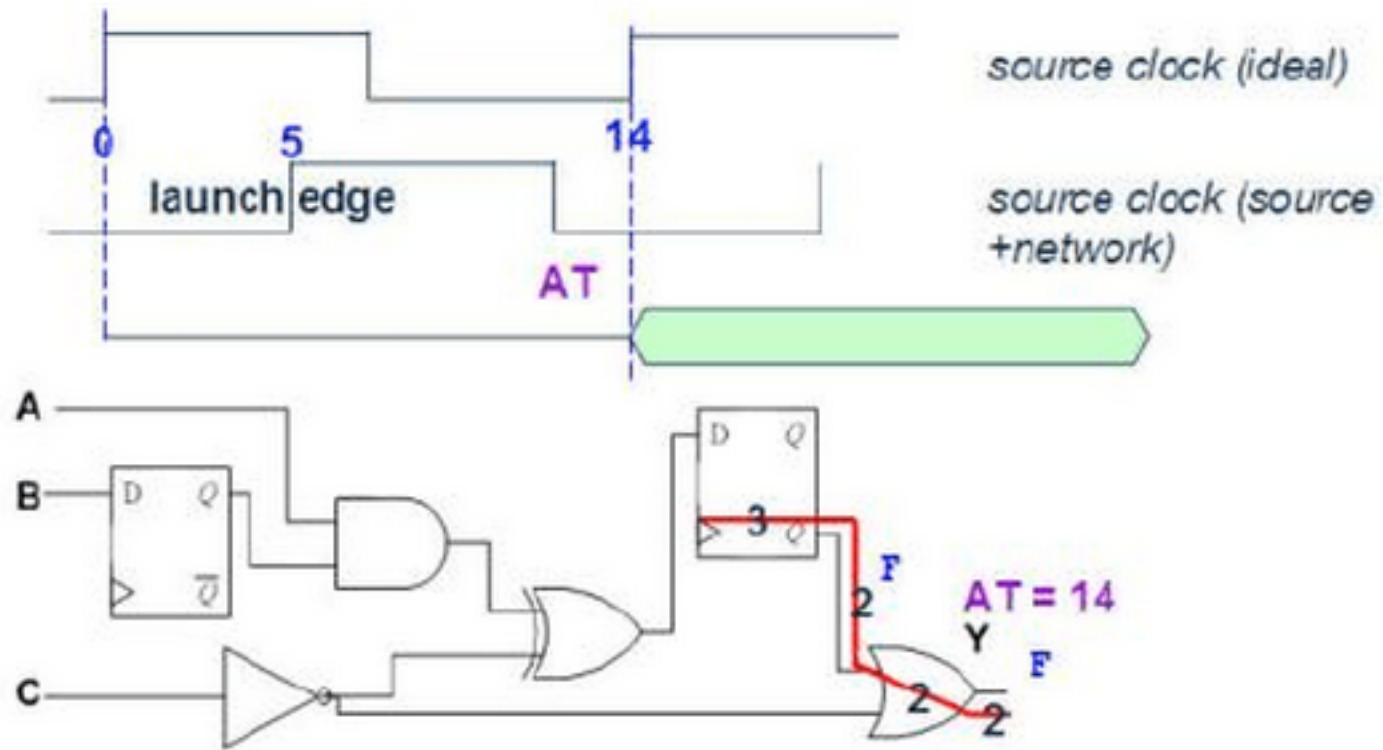
$$AT = D_{clk_s} + D_{clk_n} + 3 + 2 + 2 + 2 = 14ns$$





STA Example



- Path 3: Required Time


$$RT = D_{clk} - D_Y = 14 - 3 = 11ns$$

  

STA Example




- Path 3:
 - Slack 0->1
 - “—” = BAD

 

$$\text{Slack} = RT - AT = 11 - 15 = -4$$

- Slack 1->0
- “—” = BAD

 


$$\text{Slack} = RT - AT = 11 - 14 = -3$$

Timing Violation



 - Setup violations
- Hold violations
- Transition violations



Setup Time Violation



- Data path too slow compared to the clock speed at the latch edge
- Fix setup violations
 - reduce delay in data path
 - increase delay in clock
 - reduce number of buffers in the path
 - increase the size of buffers
 - reduce capacitance
 - reduce clock uncertainty
 - insert buffers for the clock
 - reduce clock speed (fix violation after tapeout)

Hold Time Violation




- Data not held long enough after latch edge
 - new data is too fast compared to the clock speed
- Fix hold time violations
 - adding buffers to the data path
 - reduce buffer size in the data path
 - add more capacitance to the buffer output
 - time borrowing from setup time margin

After tapeout, no way to save hold time violation!

Transition Violations



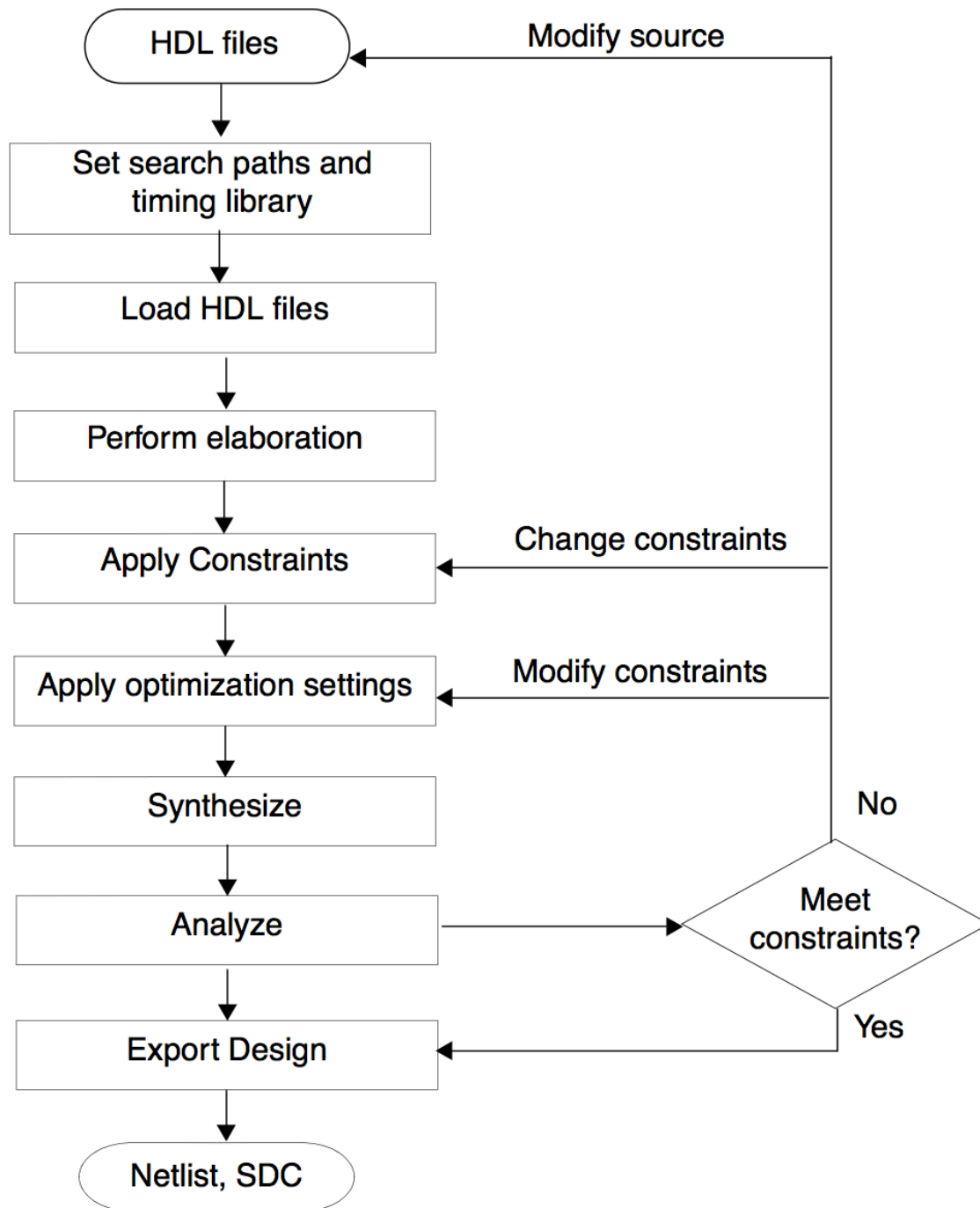- Signal takes too long transiting from one logic level to another
 - meta-stable
- Fix transition violations
 - modify data path, instead of adjusting register location, or adding buffers to the global clock; otherwise you cause more violations than you fix
 - reducing capacitance
 - adding a buffer
 - using more powerful device
 - reduce resistance (increase width of route)





Questions?

Comments?

Discussion?