

# ESE 566A: Modern System-on-Chip Design

## Homework 1

Due: Jan 23, 2:30 pm


---

---


1. Write a Boolean SOP expression for this truth table and then simplify it.

Input				Output
A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

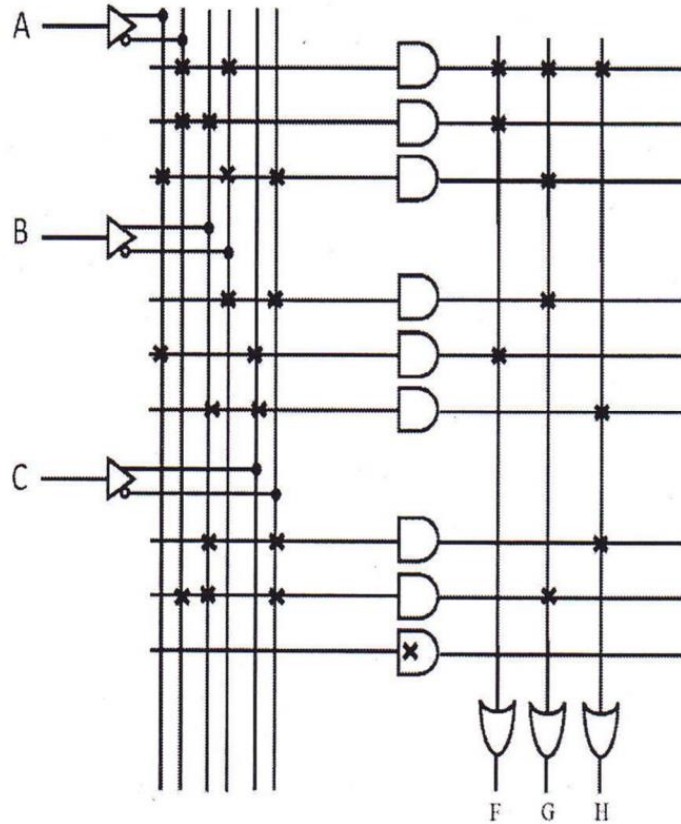2. For the following programmable Logic Array (PLA), find the function expressions for all outputs and draw the Karnaugh-Maps for function "F".



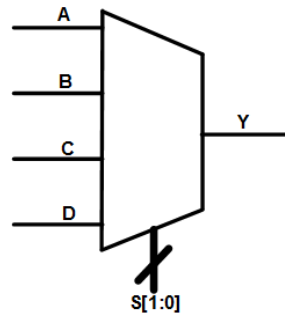3. Draw a circuit diagram for a 4-input multiplexer using NOT, AND, and OR.



4-input multiplexer


**4. Design a 3 FlipFlop counter which transitions through states  $Q_2Q_1Q_0 = 000, 100, 110, 111, 011, 001$  and then repeats.**

**a. Draw the state diagram and state transition table.**



**b. Draw the Karnaugh maps, clearly indicating the implicants that you use in your covers of the next-state functions.**

**c. Implement the counter using D flip flops and whatever gates you like.**

**5. Construct a circuit for this FSM**

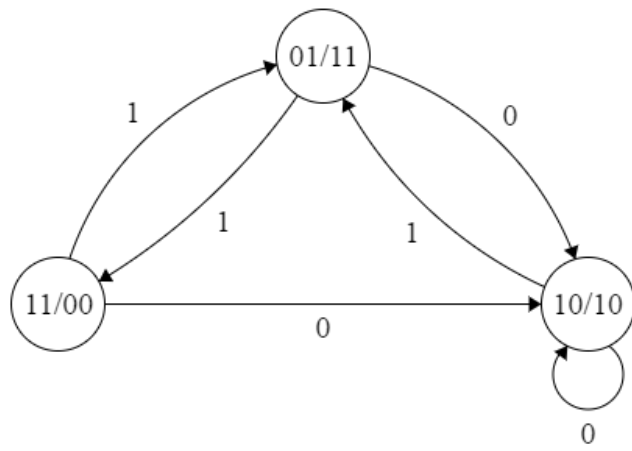

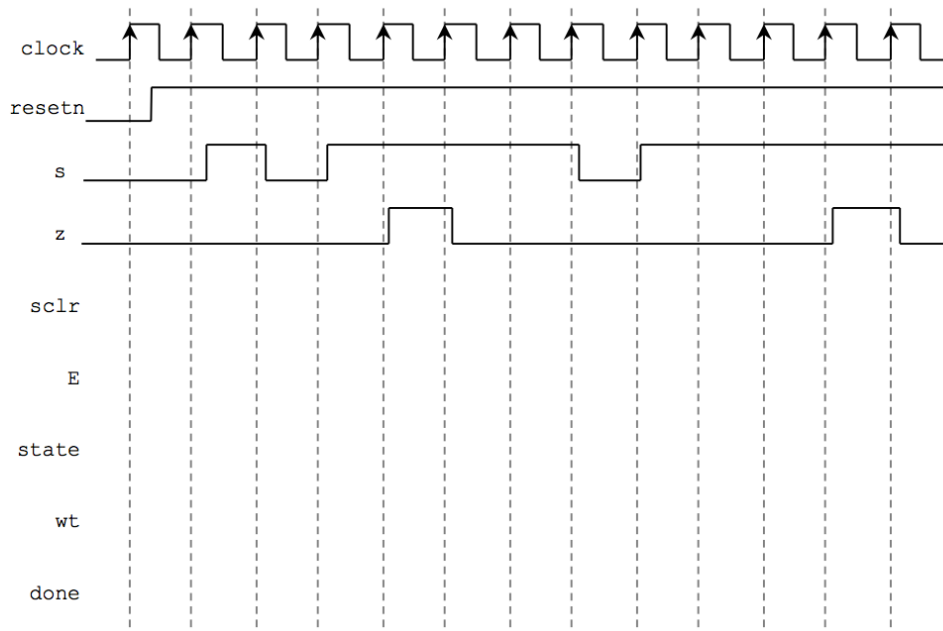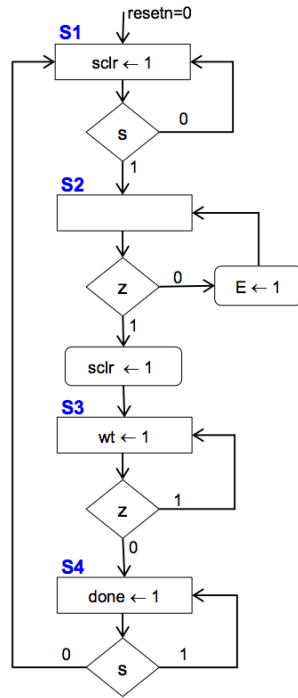6 Complete the timing diagram of the following FSM (represented as an ASM chart).



**7. Design a finite state machine that recognizes the particular pattern "111". The input to a finite state machine (FSM) is a sequence of binary bits in series. When the FSM sees three 1's in a row, it it should output "1" - otherwise it should output a "0".**

## **8. Finite state machine design:**

**A vending machine sells candy for 30 cents. It accepts nickels, dimes and quarters and provides no change if more than 30 cents is deposited.**

**Design a finite state machine to control the vending machine. The inputs to the machine are two signals indicating which coin has been deposited or that a coin release is requested. The 4 possible inputs are encoded by the two signals as:**

- 00: nickel deposited**
- 01: dime deposited**
- 10: quarter deposited**
- 11: coin release**

**Assume that your machine will receive a clock only when there is an input (a coin has been deposited or the coin release has been pulled). These two signals are synchronized with a clock. The outputs of your machine are two signals: one releasing the candy and the other releasing the coins.**