




Sequential Logic Design: Controllers

Controller Design,
Flip Flop Timing

Standard Controller Architecture

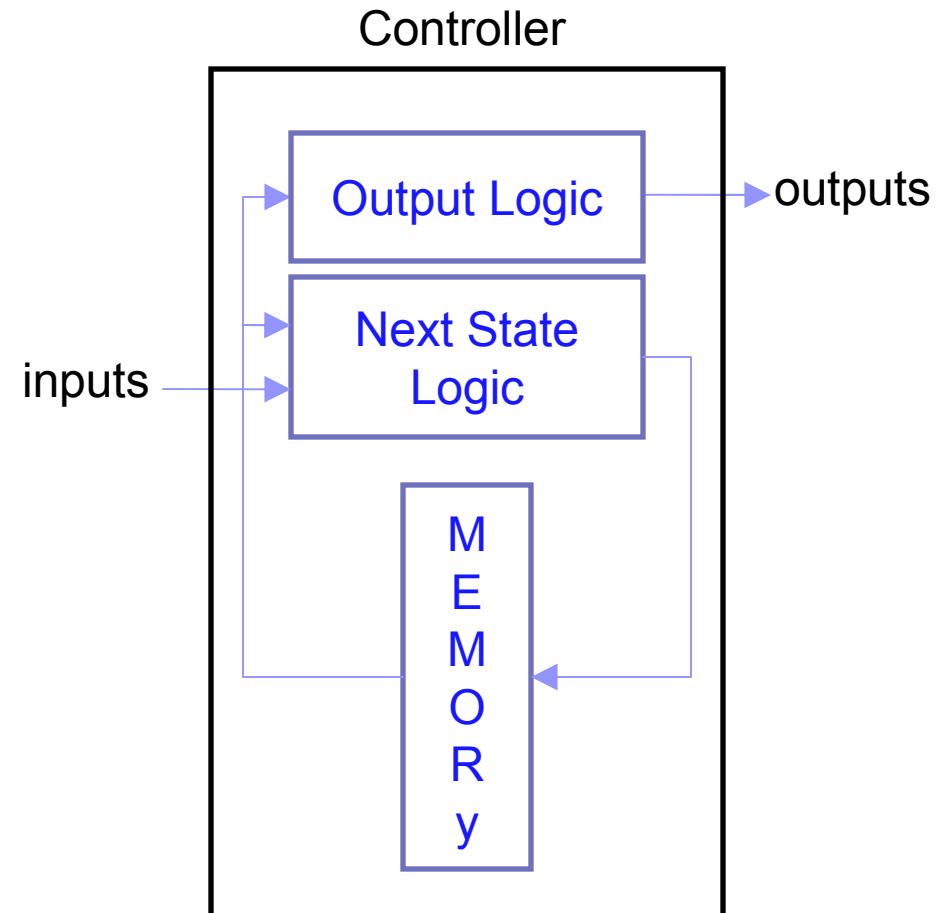- A circuit that implements a FSM is referred to as a controller
 - A controller is made up of
 - Combinational Logic
 - Calculate next state
 - Calculate outputs
 - State Registers





Controller Design Process

1. Capture FSM behavior
 - Create a state diagram to describe the intended behavior
2. Convert to a Circuit
 1. Set up the standard architecture
 - Choose the width of the of the state registers
 - Determine number of inputs and outputs for the combinational logic
 - # circuit inputs
 - # of state bits
 2. Encode the states
 - Assign unique binary numbers to each state
 3. Translate the state diagram into a truth table for the combinational logic.
 - Order the truth table with state bits first to make it easier to follow
 4. Implement the combinational logic from the truth table




Guidelines for Encoding States

- Intelligent selecting of state encodings can simplify the design and/or make it easier to understand and debug.
- Suggested Guidelines:
 1. Choose an initial code that can be easily forced by a reset (I,e. 000)
 2. Minimize the number of state bits that change between transitions.
 3. Maximize the number of state bits that don't change in a group of related transitions.
 4. Exploit symmetries in the design
 - If there are two groups of similar transitions, they should have similar encodings.
 5. If there are unused states, choose the best subset to meet the previous goals.
 6. Decompose state variables into individual bits or fields, where each field has a well defined meaning with respect to circuit outputs.
 7. Consider using more than the minimum number of state variables to make a decomposed assignment possible.

Controller Design Example: Sequence Detector

 1. Capture the desired behavior
 - Use the FSM from last lecture.





Controller Design Example: Sequence Detector

2. Convert to a circuit.
 1. Set up standard architecture
 - 5 states → Need at least 3 state bits
 - 1 output, F
 - 1 input, X
 2. Encode the states

State	Bit Encoding
0	000
1	001
1-0	010
1-0-1	011
1-0-1-1	100

Controller Design Example: Sequence Detector

2. Convert to a circuit
3. Convert the FSM to a truth table.

S2	S1	S0	X	F	N2	N1	N0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	0	1
0	1	0	0	0	0	0	0
0	1	0	1	0	0	1	1
0	1	1	0	0	0	1	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	1	0
1	0	0	1	1	0	0	1
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Note: The X's in the truth table indicate that we don't care about the value.
i.e. it can be either 0 or 1 without effecting our function.

Controller Design Example: Sequence Detector

2. Convert to a circuit
4. Design a circuit that implements the logic from the truth table.


$$F = S_2 \cdot S_1' \cdot S_0' \cdot X + S_2 \cdot S_1' \cdot S_0' \cdot X'$$

$$= S_2 \cdot S_1' \cdot S_0'$$

$$N_2 = S_2' \cdot S_1 \cdot S_0 \cdot X$$

$$N_1 = S_2' \cdot S_1' \cdot S_0 \cdot X' + S_2' \cdot S_1 \cdot S_0' \cdot X + S_2' \cdot S_1 \cdot S_0' \cdot X' + S_2 \cdot S_1' \cdot S_0' \cdot X'$$
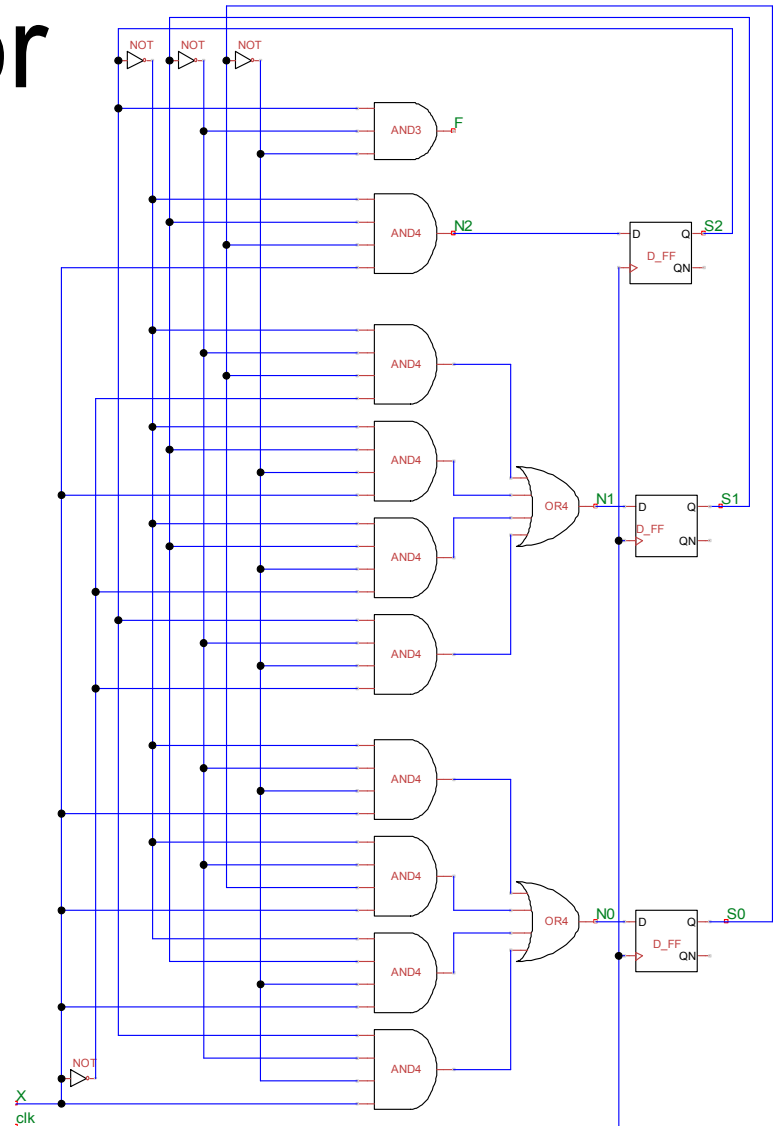
$$N_0 = S_2' \cdot S_1' \cdot S_0' \cdot X + S_2' \cdot S_1' \cdot S_0 \cdot X + S_2' \cdot S_1 \cdot S_0' \cdot X + S_2 \cdot S_1' \cdot S_0' \cdot X$$






Reverse Engineering a Circuit

- A FSM can be reverse engineered from a circuit
 1. Determine excitation functions from the circuit.
 2. Complete a truth table using the excitation functions.
 3. Create a FSM from the truth table.
 - Use generic state names if the operation of the FSM isn't immediately apparent.


Reverse Engineering Example

- Reverse Engineer the following circuit

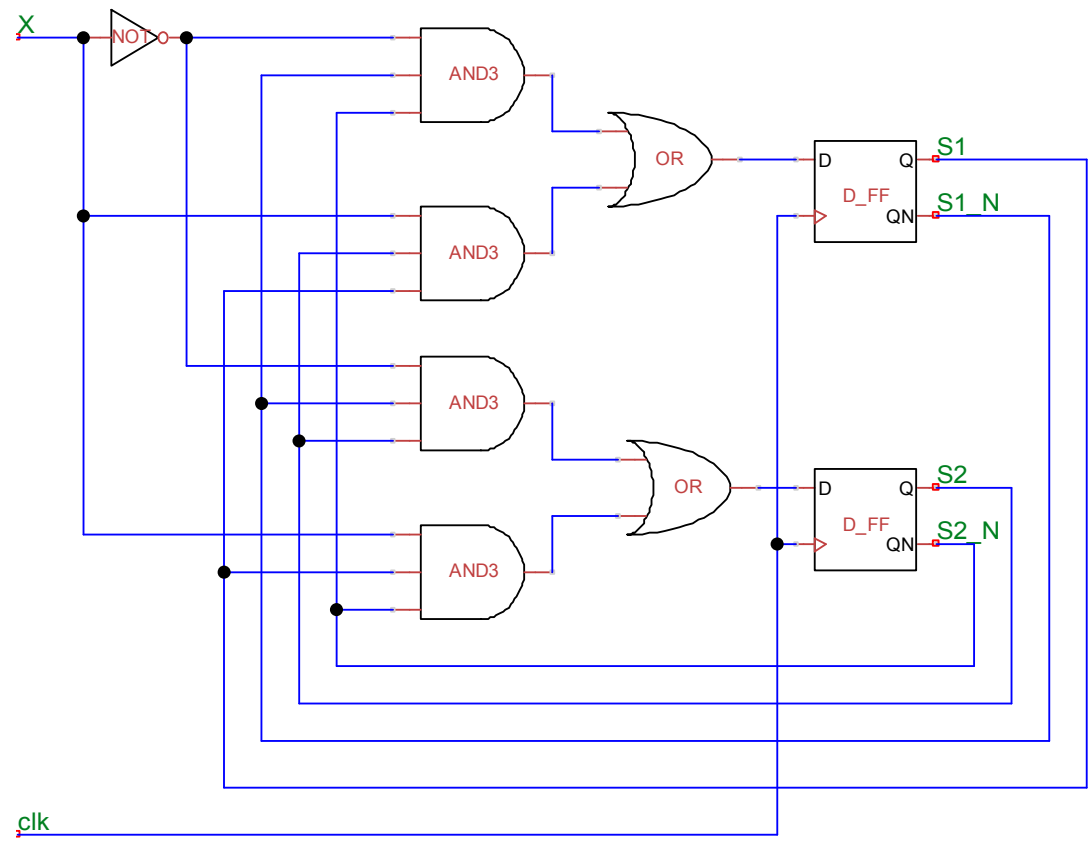


Bi-stable Elements

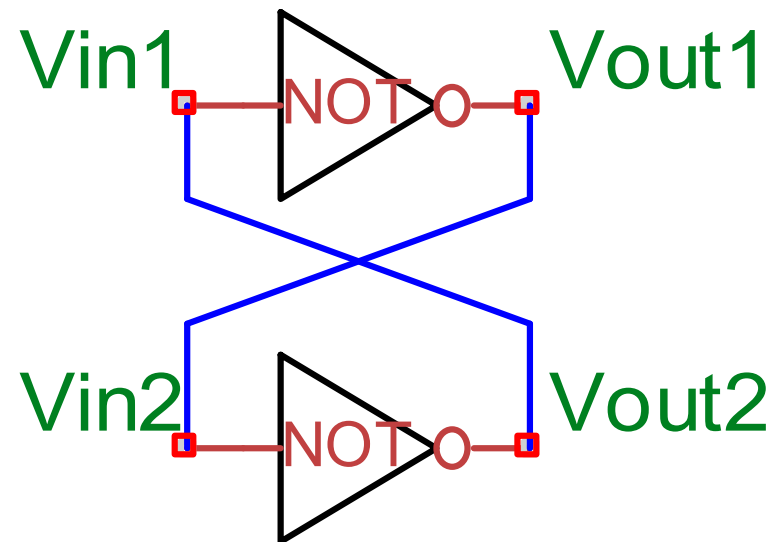- All bit storage elements are bi-stable.
 - Can stably hold two values: 0 or 1
- However, there is actually a third state.
 - Consider the simplest bi-stable element



Simple Bi-stable Response

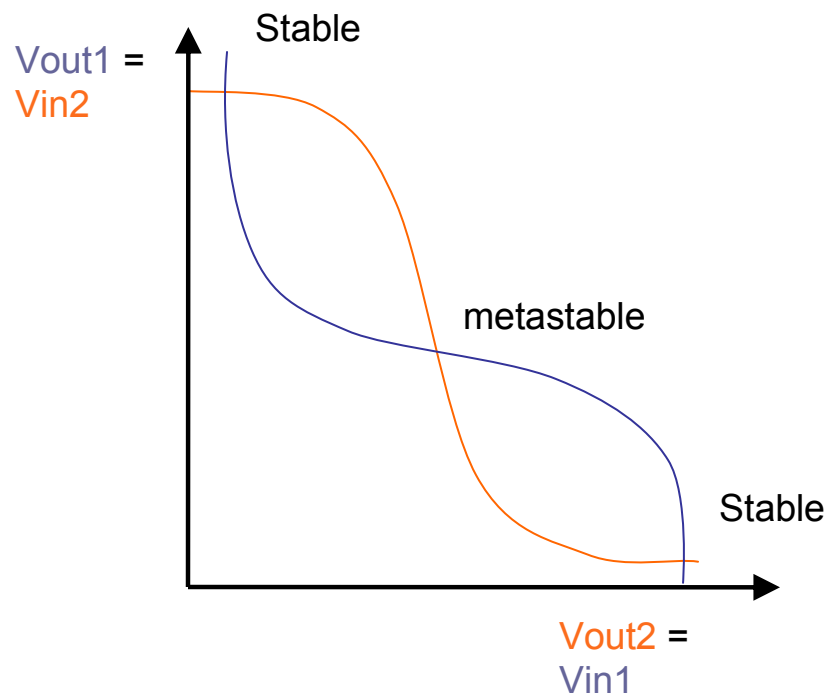

If Q is low, Q_L is high and vice versa. Since there are no inputs, the state will be held forever.

$$V_{out1} = T(V_{in1}) = V_{in2}$$

$$V_{out2} = T(V_{in2}) = V_{in1}$$

$$V_{in1} = V_{out2}$$

$$= T(V_{in2})$$

$$= T(V_{out1})$$

$$= T(T(V_{in1}))$$

Each spot where the two graphs cross is stable. A small amount of noise can push it out of stability.

Note that there are 3 stable points!




Metastability

- The stable point in the center of the curve is known as metastable
 - Only slightly stable
 - Small amounts of noise cause the outputs to rapidly converge on the truly stable points.
- Because of metastability, it is important to drive a signal beyond the linear range of the inverter
 - Means we have timing requirements for driving gates

Metastability Example

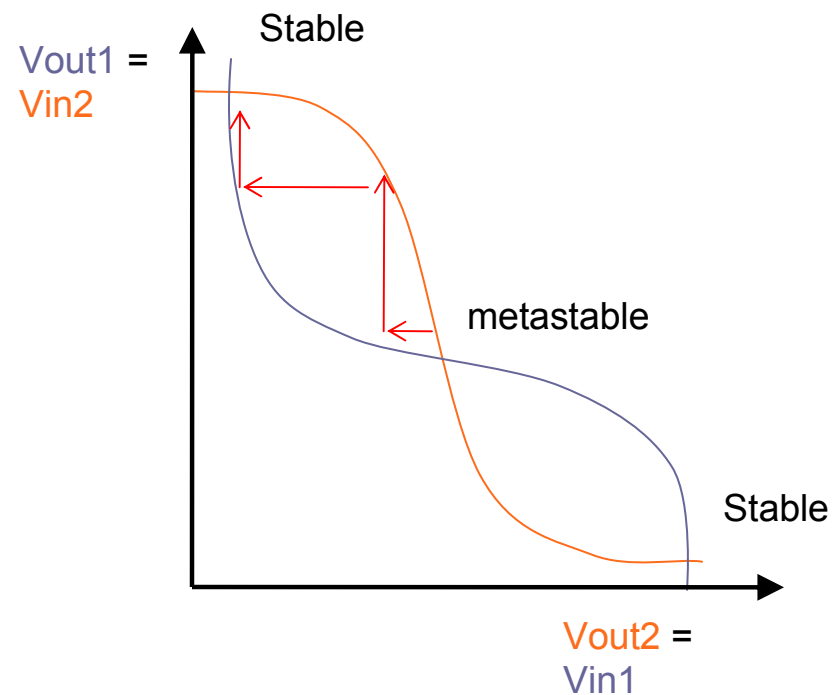- Assume the circuit is at the metastable point and apply a small amount of noise to reduce V_{in1} .
 - Increases $V_{out1} = V_{in2}$
 - Which decreases $V_{out2} = V_{in1}$
 - Which increases $V_{out1} = V_{in2}$
 - Which repeats until V_{in2} is HIGH and V_{in1} is LOW.
 - This can take longer than a clock cycle!






Latch & Flip Flop Timing Requirements

- For flip flops to operate properly, timing constraints must be met
 - Setup Time (t_{setup})
 - Minimum amount of time a signal level must be present before the active clock edge.
 - Hold Time (t_{hold})
 - Minimum amount of time signal level must be present after the active clock edge.
 - These are properties of a particular gate based on how it is design. The designer will provide these values.
- Latches also have a minimum pulse width.

Sequential Circuit Timing

 




Determining Clock Frequency

- Remember that frequency, $f = 1 / T$
 - Higher frequencies mean that you can do more work in less time.
 - Higher frequencies mean shorter clock periods.
 - Shorter periods mean that you have less time to accomplish your task.
 - The smallest period (and highest frequency) is constrained by your circuit's ***critical path***.
 - The longest delay path from a register output or circuit input to a register input.

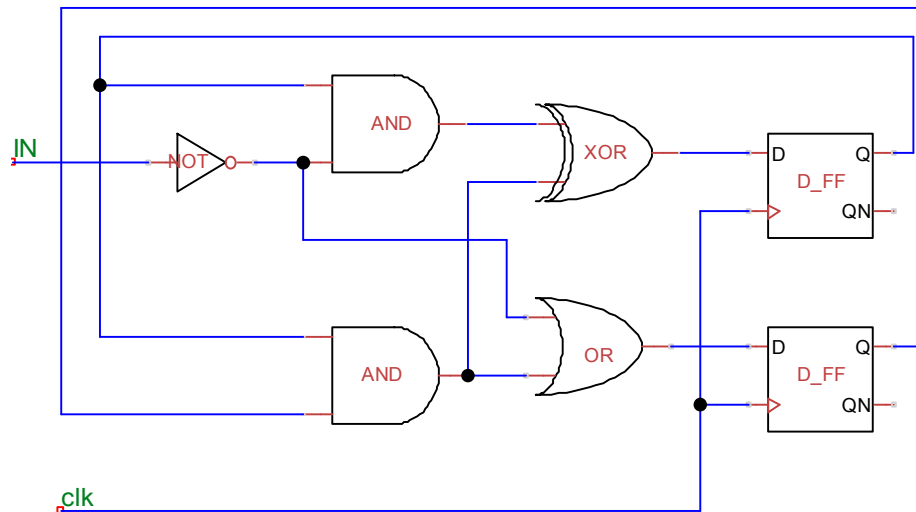Example: Minimal Clock Frequency

- Using the following propagation delays, what is the critical path of the following circuit?
 - $T_{pdff} = 3 \text{ ns}$
 - $T_{pd,AND} = 1.5 \text{ ns}$
 - $T_{pd,OR} = 2 \text{ ns}$
 - $T_{pd,XOR} = 2.5 \text{ ns}$
 - $T_{pd,NOT} = 1 \text{ ns}$
 - $T_{setup} = 2 \text{ ns}$
 - $T_{hold} = 1 \text{ ns}$
- What is the fastest clock frequency at which this circuit can operate?






Sequential Timing Margins

- Timing margins indicate how much “slop” we have in our timing requirements.
 - Well designed systems have positive, non-zero margins
 - Allows for unexpected timing errors
 - Negative margins may lead to metastability.
- Setup-time margin = $t_{\text{clk}} - t_{\text{comb(max)}} - t_{\text{setup}} - t_{\text{pd,ff(max)}}$
- Hold-time margin = $t_{\text{ffpd(min)}} + t_{\text{comb(min)}} - t_{\text{hold}}$
 - t_{ffpd} is almost always larger than t_{hold} , so designers rarely evaluate the hold time margin
- Setup-time margins are evaluated for the circuit's **critical** path, the longest delay path in the circuit to a flip flop input.

Sequential Circuit Timing

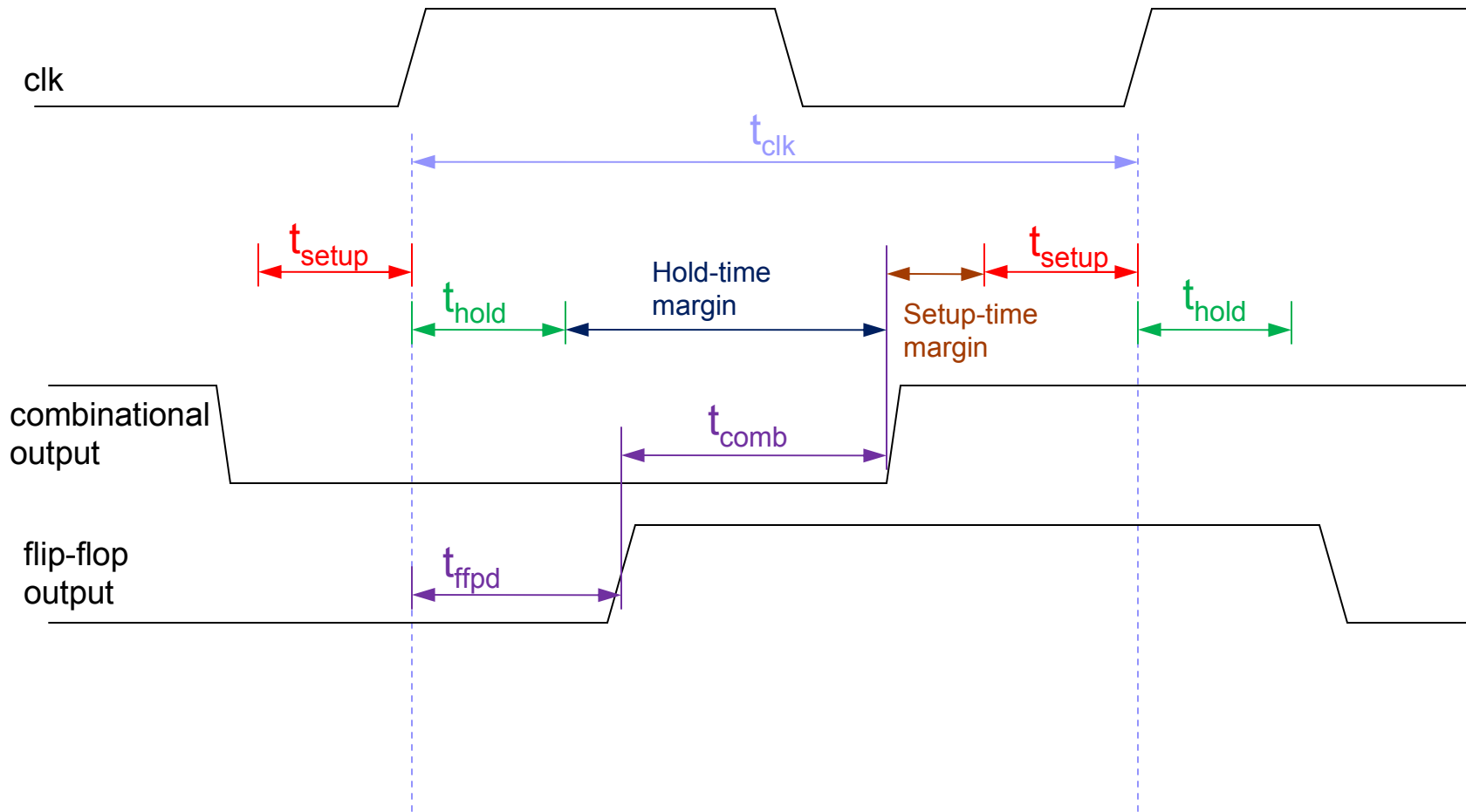





Timing Diagrams in Sequential Circuits

- Timing diagrams are done the same as with combinational logic, but you must evaluate the circuit for each clock cycle.



Sequential Timing Diagram Example

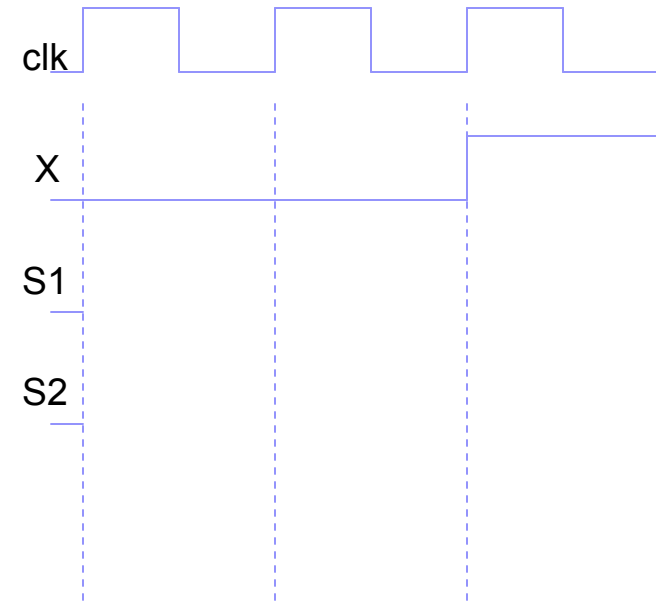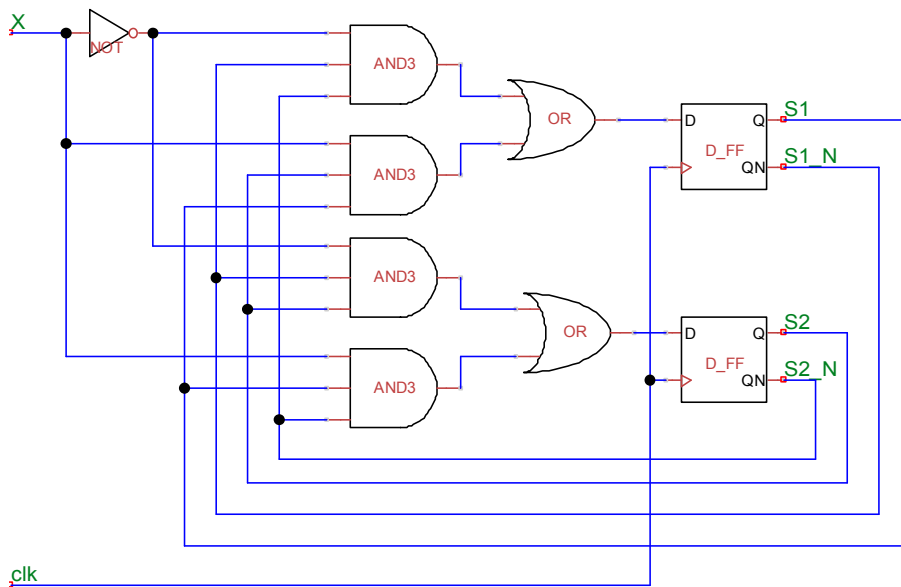- Evaluate the following timing diagram
 - Use ideal timing
 - Assume setup and hold times have been met



Sequential Timing Diagram Example

  - Evaluate the following timing diagram
 - Repeat the previous example incorporating delays in the timing.
 - $t_{\text{clk}} = 15\text{ns}$,
 - $t_{\text{pd,AND}} = t_{\text{pd,OR}} = 3\text{ ns}$
 - $t_{\text{ffpd}} = 1.5\text{ ns}$
 - $t_{\text{setup}} = 3\text{ ns}$, $t_{\text{hold}} = 2\text{ ns}$





Synchronous vs. Asynchronous

- A synchronous circuit is one where all elements operate using the same clock
 - All registers in a circuit can only store a value at the same clock edge.
- An asynchronous circuit is one where there is no clock, or there are two or more clocks of different frequencies.
 - Asynchronous circuits must account for metastability because there is no guarantee that setup or hold times will be met.
 - Asynchronous inputs need to be synchronized.





Impediments to Synchronous Design

■ Clock Skew

- The difference between the arrival times of a clock edge at different devices/gates
 - Subtracts from the hold-time margin
 - Hold-time margin = $t_{\text{ffpd}(\text{min})} + t_{\text{comb}(\text{min})} - t_{\text{hold}} - t_{\text{skew}(\text{max})}$
- Can be caused by
 - Long paths
 - Gated clocks
- Clock skew can cause incorrect values to be sampled, or even metastability!

Clock Skew Example

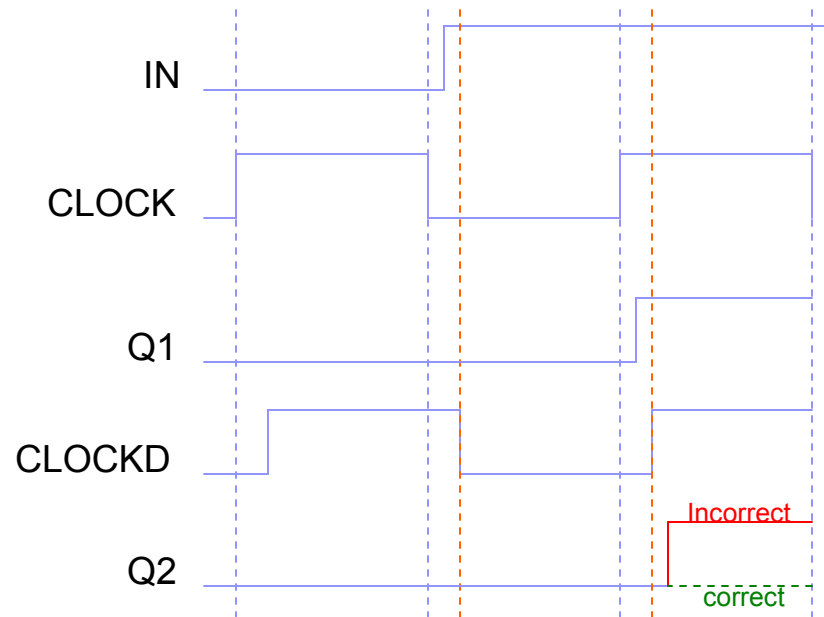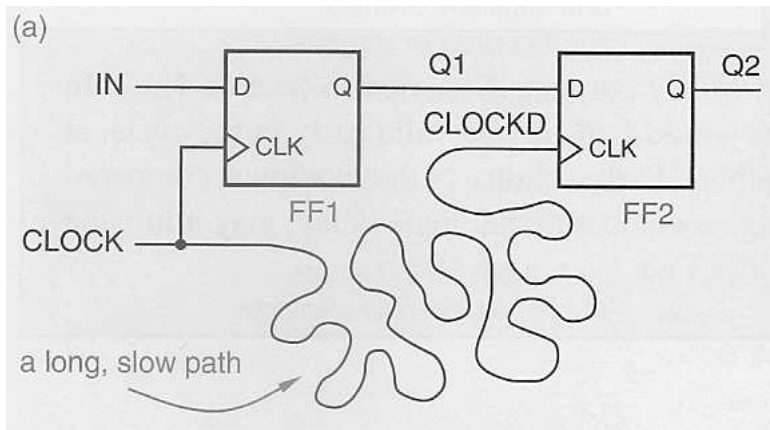




Impediments to Synchronous Design

- Asynchronous Inputs
 - The input is not in sync with the clock of the synchronous circuit
 - Will undoubtedly cause metastability
 - The input must be synchronized.

Synchronizer

 - A ***synchronizer*** is a flip flop that samples the asynchronous input before it is used by a synchronous circuit.
 - Won't the synchronizer suffer from metastability?
 - YES! However, it provides time for the output to settle before it is sampled by the synchronous circuit.
 - The more flip flops in series, the more time metastable inputs have to settle.





Synchronizer Failure

- Failure is said to occur if a synchronizer output is sampled when still in a metastable state.
- To avoid metastability
 - Wait “long enough” before sampling the synchronizer output.
 - The output must settle within the ***Resolution Time***
 - $t_r = t_{\text{clk}} - t_{\text{comb}} - t_{\text{setup}}$
 - So, what is a good Resolution Time?



Mean Time Between Failures (MTBF)

- MTBF is a measure of the mean time between failures caused by metastability
- $MTBF(tr) = \exp(tr/\tau) / (T_0 * f * a)$
 - **Tr** – Resolution Time, must be greater than the flip flop propagation delay.
 - **T₀** & **τ** -- constants that depend on the electrical characteristics of the flip flop.
 - In our examples, these will be given to you.
 - **f** – frequency of the flip flop clock.
 - **a** – the number of asynchronous input changes per second
- An MTBF of 100 years or more isn't unreasonable!
- To improve MTBF
 - Use better flip flops
 - Slow down the clock (more time to resolve)



MTBF Example


- What resolution time is required to ensure a synchronizer with two flip flops doesn't experience a failure for 100 years, on average. Use the following parameters:
 - $\tau = 1.5$ nano seconds
 - $T_0 = 0.4$ seconds
 - $f = 10$ MHz
 - $A = 10$ KHz

$$100 \cdot 365 \cdot 24 \cdot 60 \cdot 60 = \exp(\tau_r / 1.5) / (0.4 \cdot 10^7 \cdot 10^4)$$

$$\tau_r = 69.43 \text{ ns}$$

Reliable Synchronizers

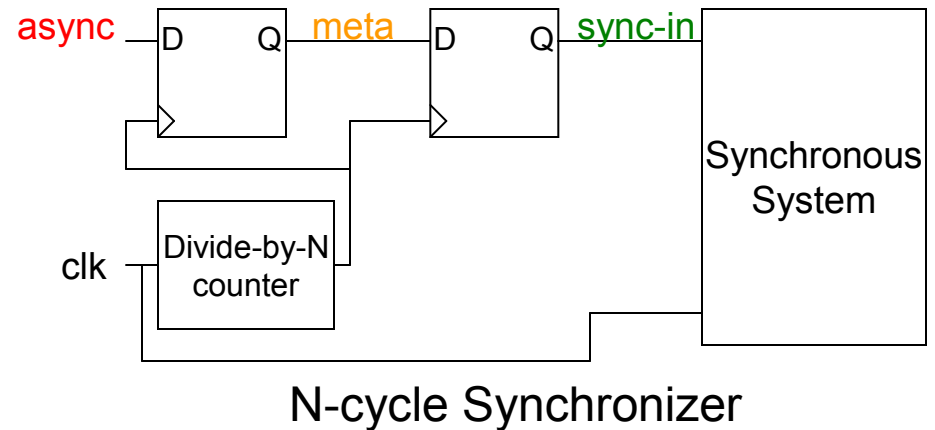- To make a reliable synchronizer, methods of lengthening the resolution time, t_r , must be devised
- For a system with the simplest synchronizer, the best t_r can be is
 - $t_r = t_{\text{clk}} - t_{\text{setup}}$



- We will discuss two ways to increase t_r :
 - N-cycle synchronizer
 - The synchronizer's clock frequency is smaller than the synchronous system.
 - $t_r = n \cdot \text{clk} - t_{\text{setup}}$
 - Limited by clock skew at higher frequencies
 - Cascading synchronizer
 - Adding more flip flops adds more resolution time
 - $t_r = n \cdot (\text{clk} - t_{\text{setup}})$

