
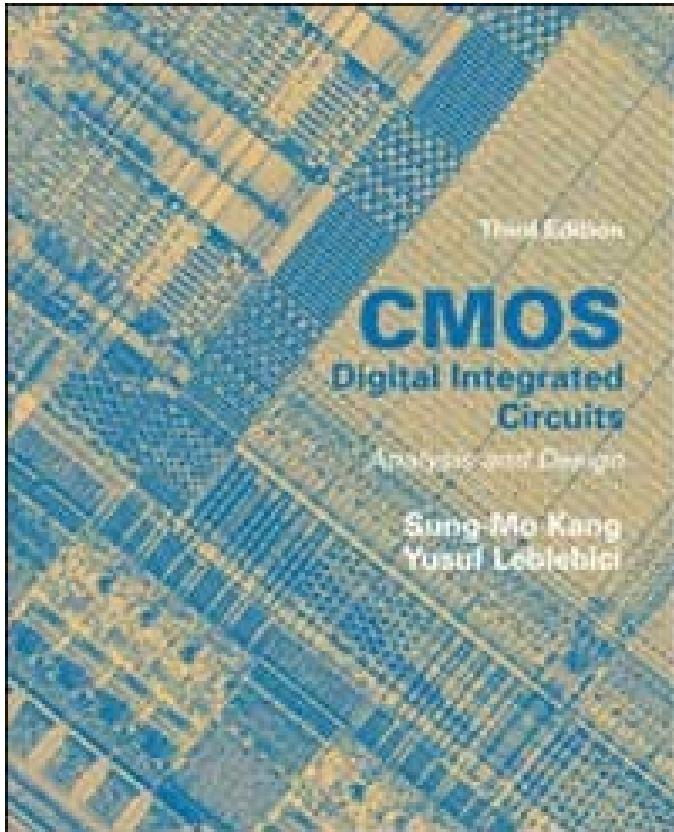


Digital IC Design and Architecture

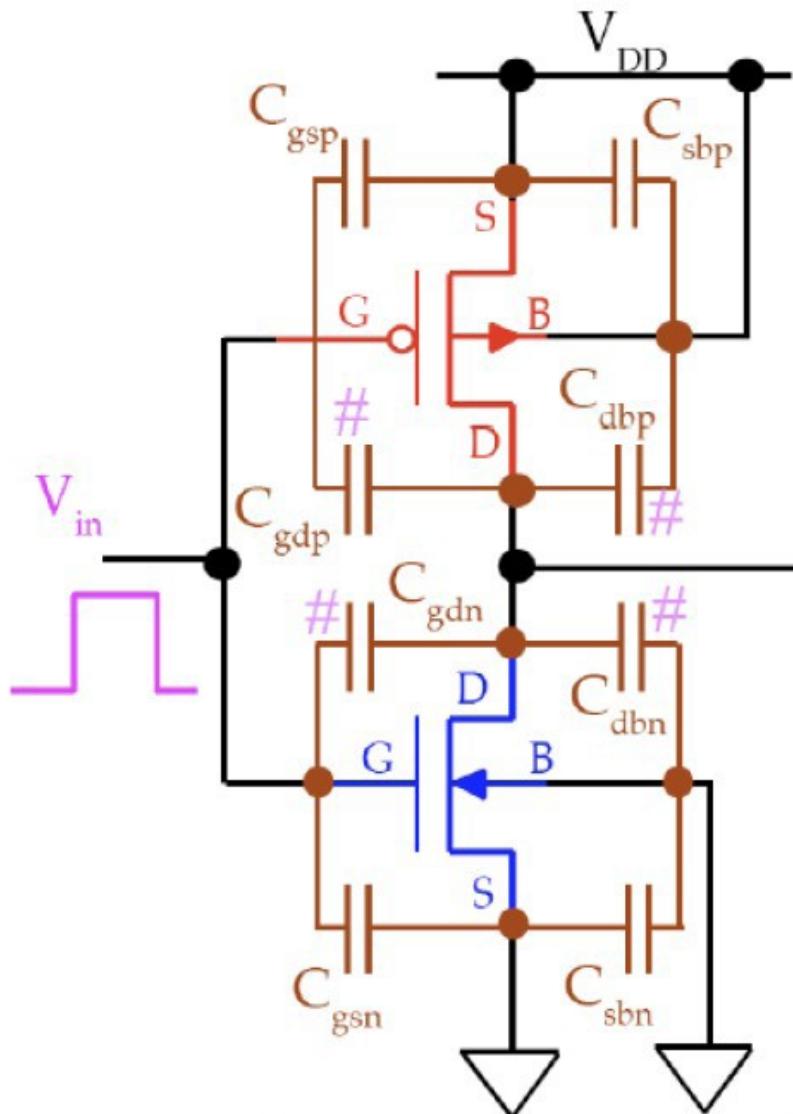

MOS Inverter
Dynamic Behavior




$$C_{\text{load}} = C_{\text{dbn}}^{\#} + C_{\text{dbp}}^{\#} + C_{\text{gdn}}^{\#} + C_{\text{gdp}}^{\#} + C_{\text{int}}^{\#} + C_{\text{gb}}^{\#} \approx C_{\text{dbn}} + C_{\text{dbp}} + C_{\text{int}} + C_{\text{gb}}$$


$C_{\text{gd}'} \ C_{\text{gs}'} \ C_{\text{gb}'} \rightarrow$ Oxide Caps
 $C_{\text{db}'} \ C_{\text{sb}'} \rightarrow$ Junction Caps
 C_{int} → Inteconnect Cap

Usually
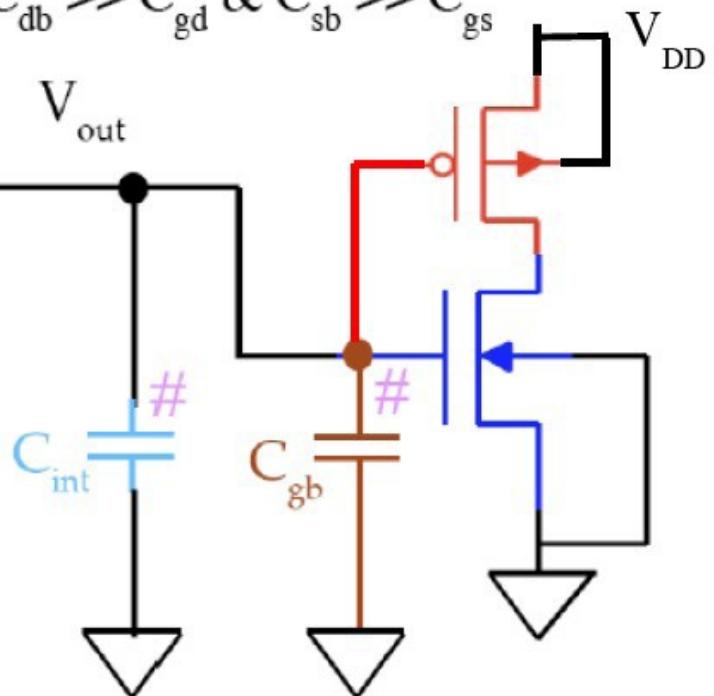
$$C_{\text{db}} \gg C_{\text{gd}} \ \& \ C_{\text{sb}} \gg C_{\text{gs}}$$




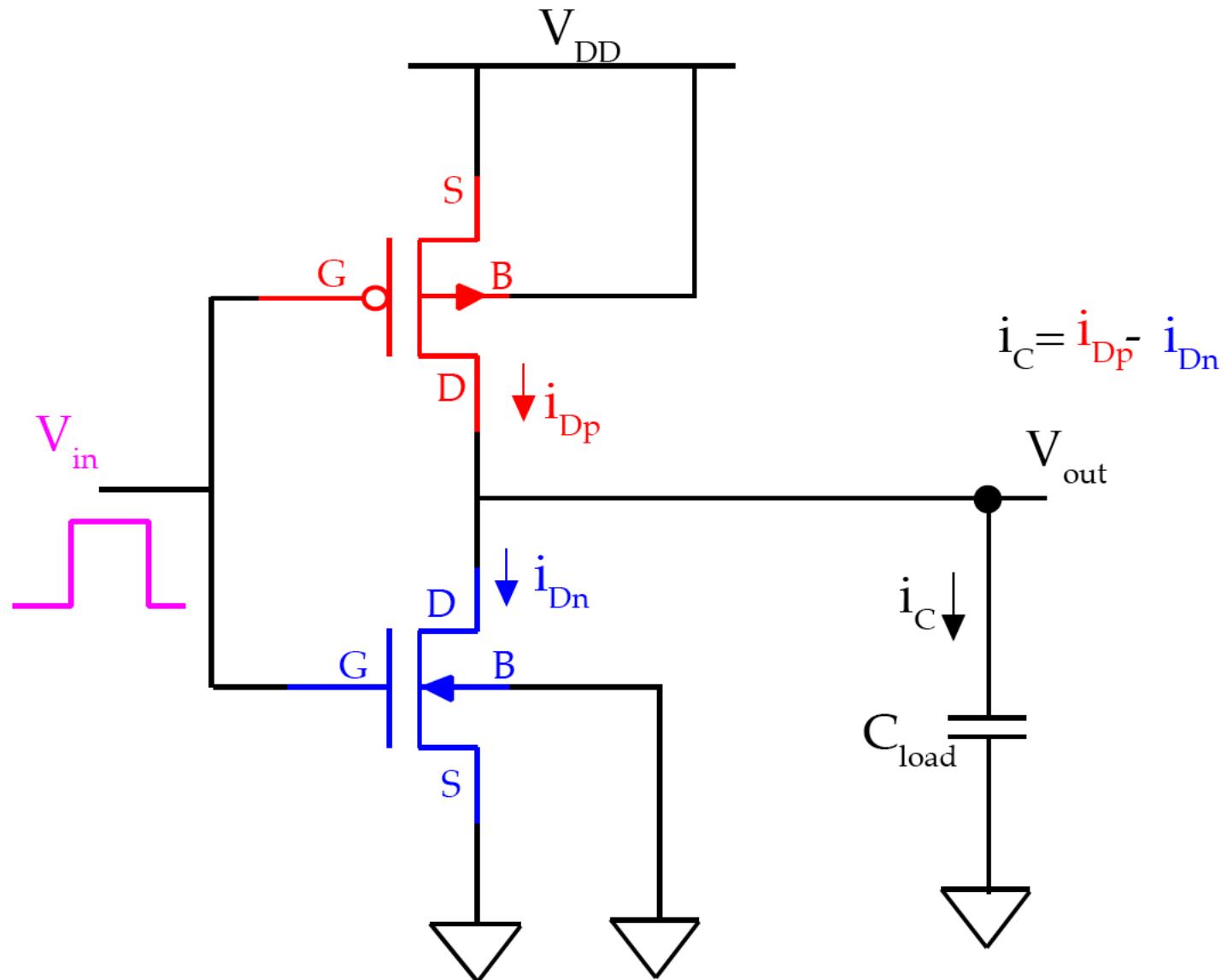where $C_{\text{gb}} = C_{\text{gbn}} + C_{\text{gbp}}$




$$C_{load} = C_{gdn} + C_{gdp} + C_{dbn} + C_{dbp} + C_{int} + C_{gb}$$

PROPAGATION DELAY DEFINITIONS


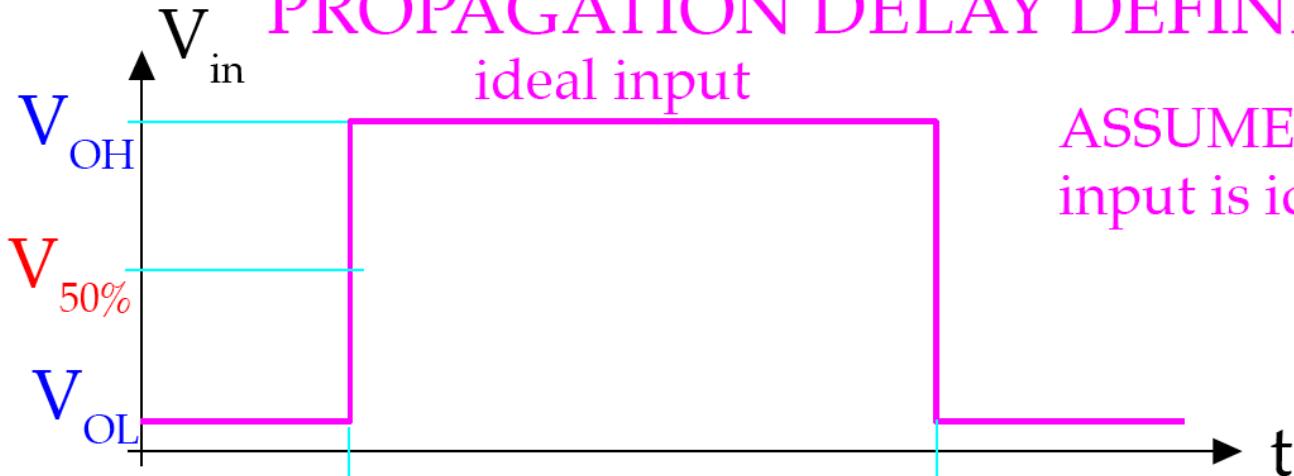


ASSUME: Initially the input is ideal.

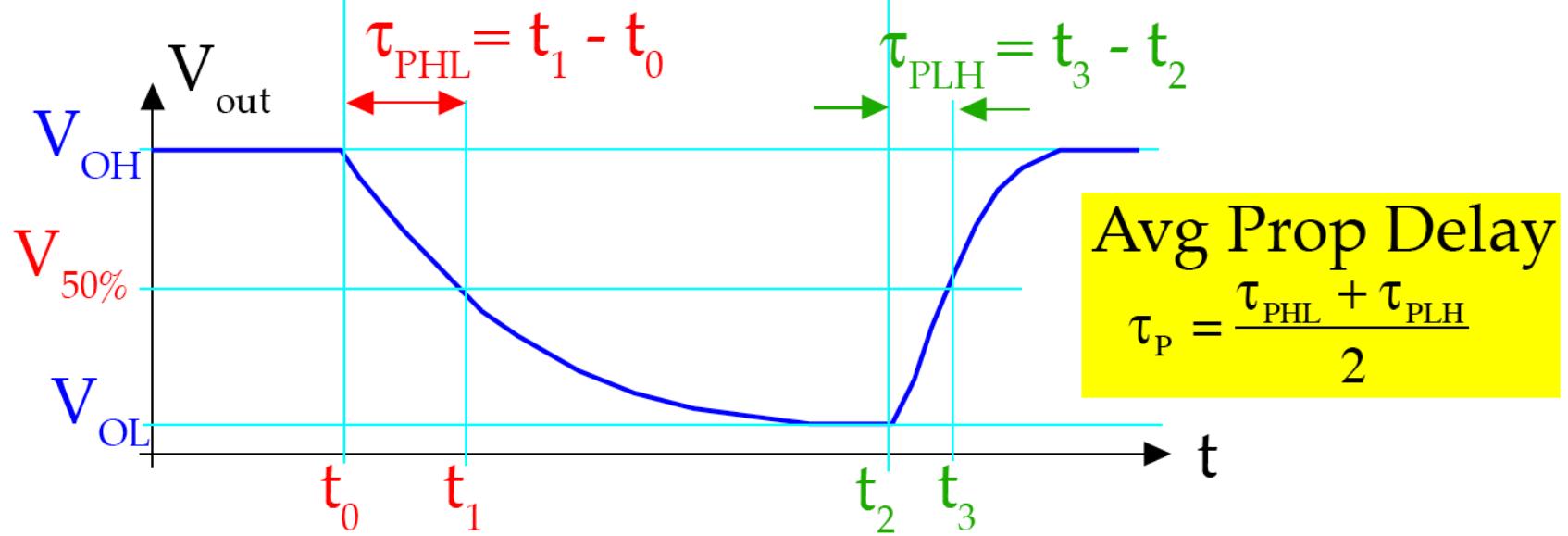


$$V_{50\%} = V_{OL} + 0.5 [V_{OH} - V_{OL}] = 0.5 [V_{OL} + V_{OH}]$$

PROPAGATION DELAY DEFINITIONS

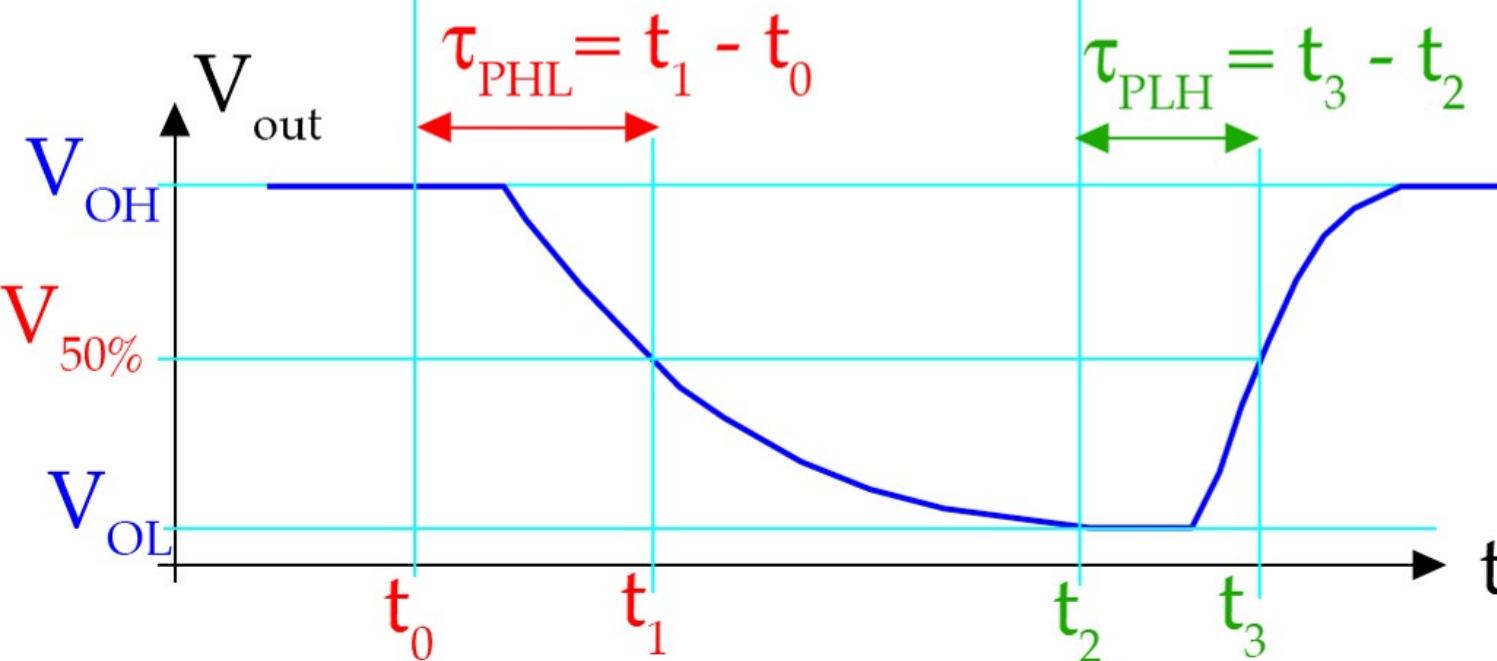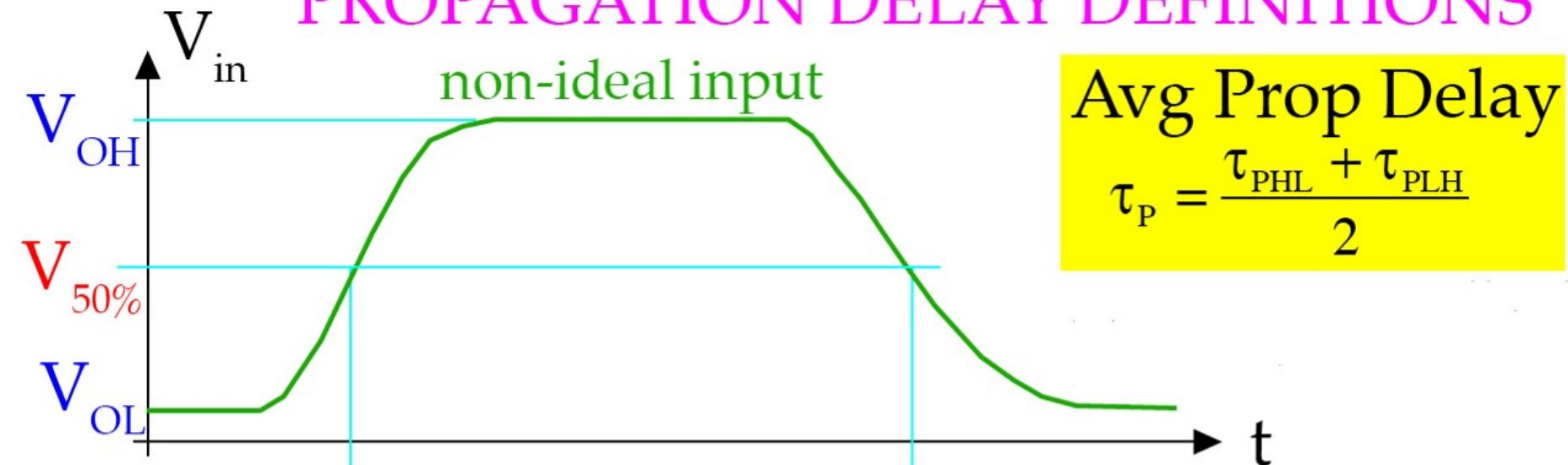

$$V_{50\%} = V_{OL} + 0.5 [V_{OH} - V_{OL}] = 0.5 [V_{OL} + V_{OH}]$$

OUTPUT VOLTAGE RISE & FALL TIMES

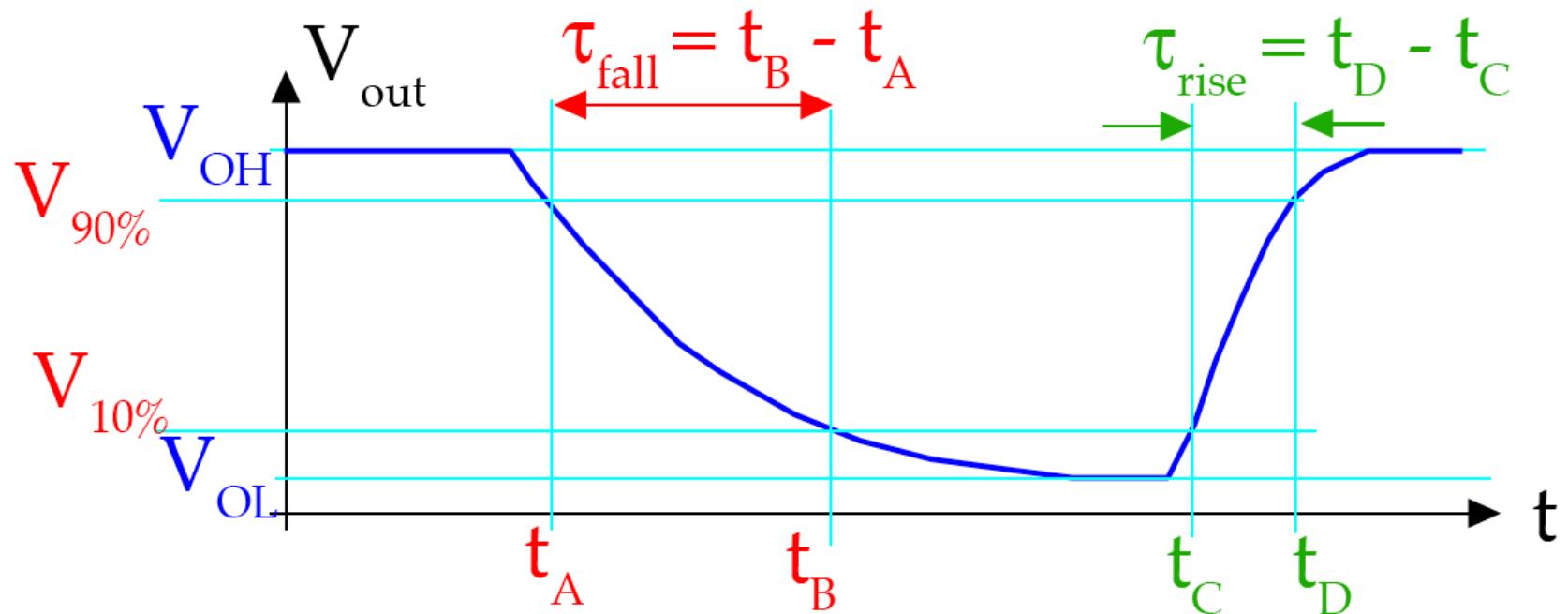

$$V_{10\%} = V_{OL} + 0.1 [V_{OH} - V_{OL}]$$

$$V_{90\%} = V_{OL} + 0.9 [V_{OH} - V_{OL}]$$

$$I = C \frac{\Delta V}{\Delta t}$$

CALCULATION OF DELAY TIMES

QUICK ESTIMATES:

$$\tau_{PHL} = \frac{C_{load} \Delta V_{HL}}{I_{avg,HL}} = \frac{C_{load} (V_{OH} - V_{50\%})}{I_{avg,HL}}$$

$$\tau_{PLH} = \frac{C_{load} \Delta V_{LH}}{I_{avg,LH}} = \frac{C_{load} (V_{50\%} - V_{OL})}{I_{avg,LH}}$$


$I_{avg,HL}$ -> approximate average C_{load} current during high-to-low V_{out} transition


$$I_{avg,HL} = \frac{1}{2} [i_C(V_{in} = V_{OH}, V_{out} = V_{OH}) + i_C(V_{in} = V_{OH}, V_{out} = V_{50\%})]$$

$I_{avg,LH}$ -> approximate average C_{load} current during low-to-high V_{out} transition

$$I_{avg,LH} = \frac{1}{2} [i_C(V_{in} = V_{OL}, V_{out} = V_{OL}) + i_C(V_{in} = V_{OL}, V_{out} = V_{50\%})]$$

$$i_C = i_{Dp} - i_{Dn}$$

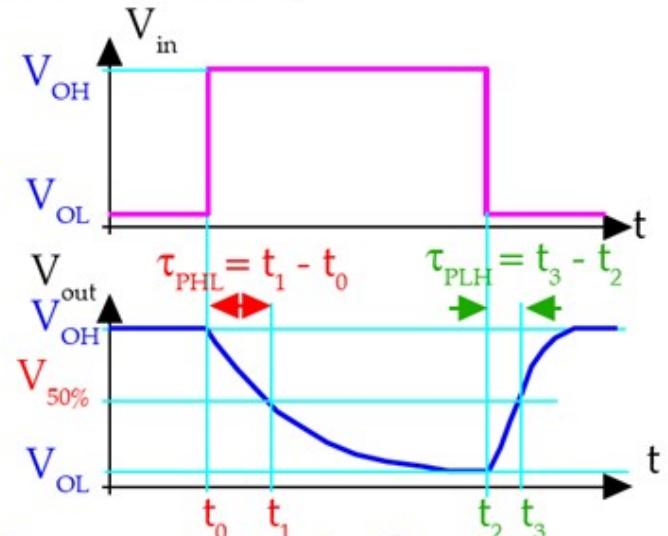

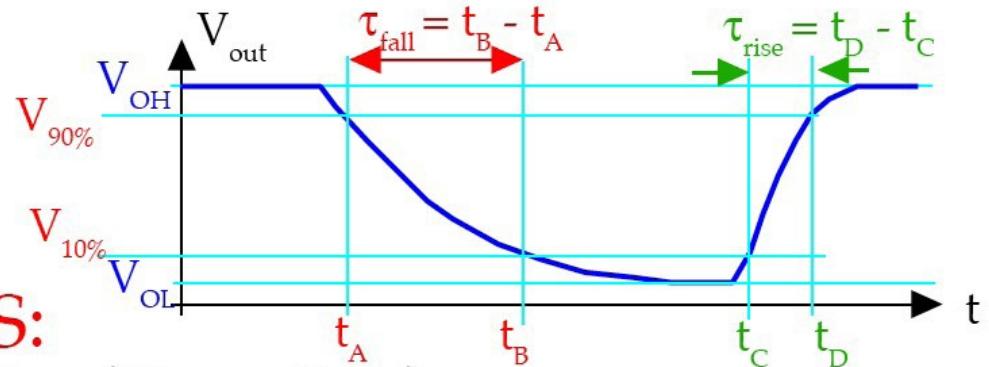

QUICK ESTIMATES:

$$\tau_{\text{fall}} = \frac{C_{\text{load}} \Delta V_{90\text{-to-}10\%}}{I_{\text{avg,90-to-10\%}}} = \frac{C_{\text{load}} (V_{90\%} - V_{10\%})}{I_{\text{avg,90-to-10\%}}}$$

$$\tau_{\text{rise}} = \frac{C_{\text{load}} \Delta V_{10\text{-to-}90\%}}{I_{\text{avg,10-to-90\%}}} = \frac{C_{\text{load}} (V_{90\%} - V_{10\%})}{I_{\text{avg,10-to-90\%}}}$$

$I_{\text{avg,90-to-10\%}}$ -> approximate average C_{load} current during 90%-to-10% V_{out} transition


$$I_{\text{avg,90-to-10\%}} = \frac{1}{2} [i_C(V_{\text{in}} = V_{\text{OH}}, V_{\text{out}} = V_{90\%}) + i_C(V_{\text{in}} = V_{\text{OH}}, V_{\text{out}} = V_{10\%})]$$

$I_{\text{avg,10-to-90\%}}$ -> approximate average C_{load} current during 10%-to-90% V_{out} transition

$$I_{\text{avg,10-to-90\%}} = \frac{1}{2} [i_C(V_{\text{in}} = V_{\text{OL}}, V_{\text{out}} = V_{10\%}) + i_C(V_{\text{in}} = V_{\text{OL}}, V_{\text{out}} = V_{90\%})]$$

Calculating Propagation Delays By Solving the Circuit Differential Equation

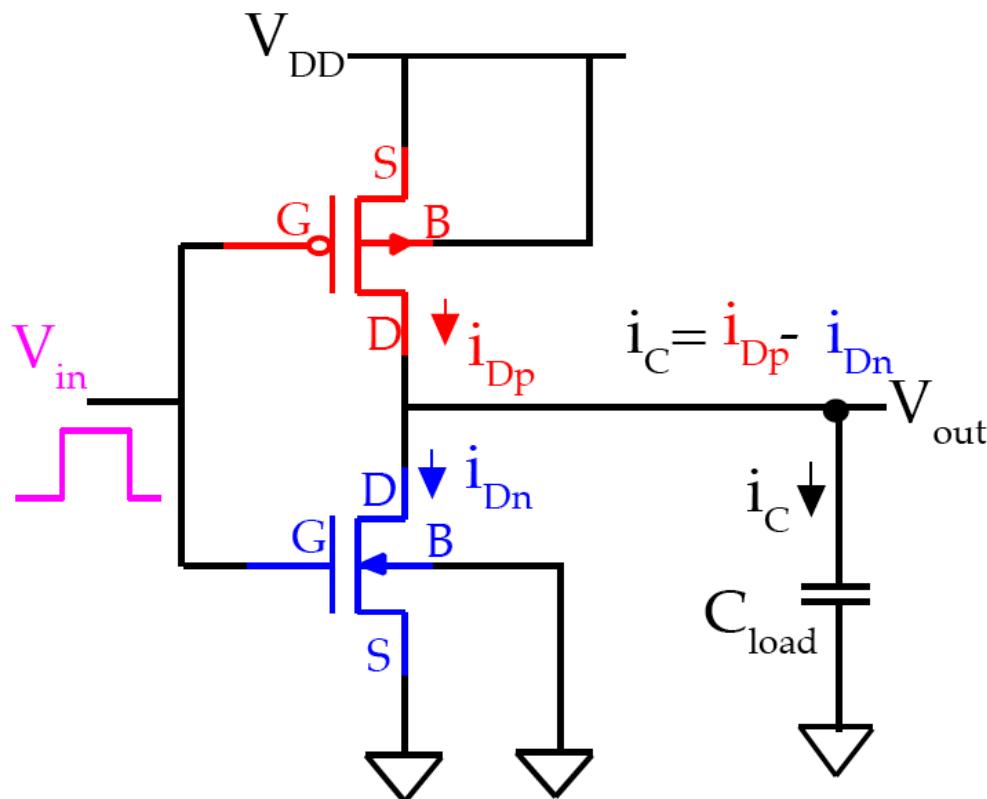MORE ACCURATE CALCULATION OF τ_{PHL} , τ_{PLH} :



$$i_C = i_{Dp} - i_{Dn}$$

$$i_C = C_{load} \frac{dV_{out}}{dt} = i_{Dp} - i_{Dn}$$


1) V_{in} - ABRUPTLY RISES CASE -> TPHL

1) V_{in} - ABRUPTLY RISES CASE:

IC: $V_{out} = V_{DD}$, $V_{in} = 0 \rightarrow V_{DD}$

nMOS - ON SAT $V_{out} \geq V_{DD} - V_{T0n}$

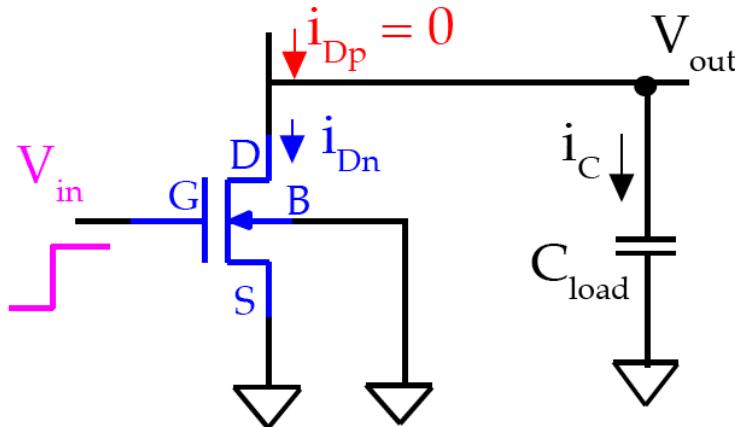
p-MOS OFF LIN $0 \leq V_{out} < V_{DD} - V_{T0n}$




$$C_{load} \frac{dV_{out}}{dt} = -i_{Dn}$$

NOTE THAT:

$|i_{Dp}| \ll |i_{Dn}|$ for all inverter types

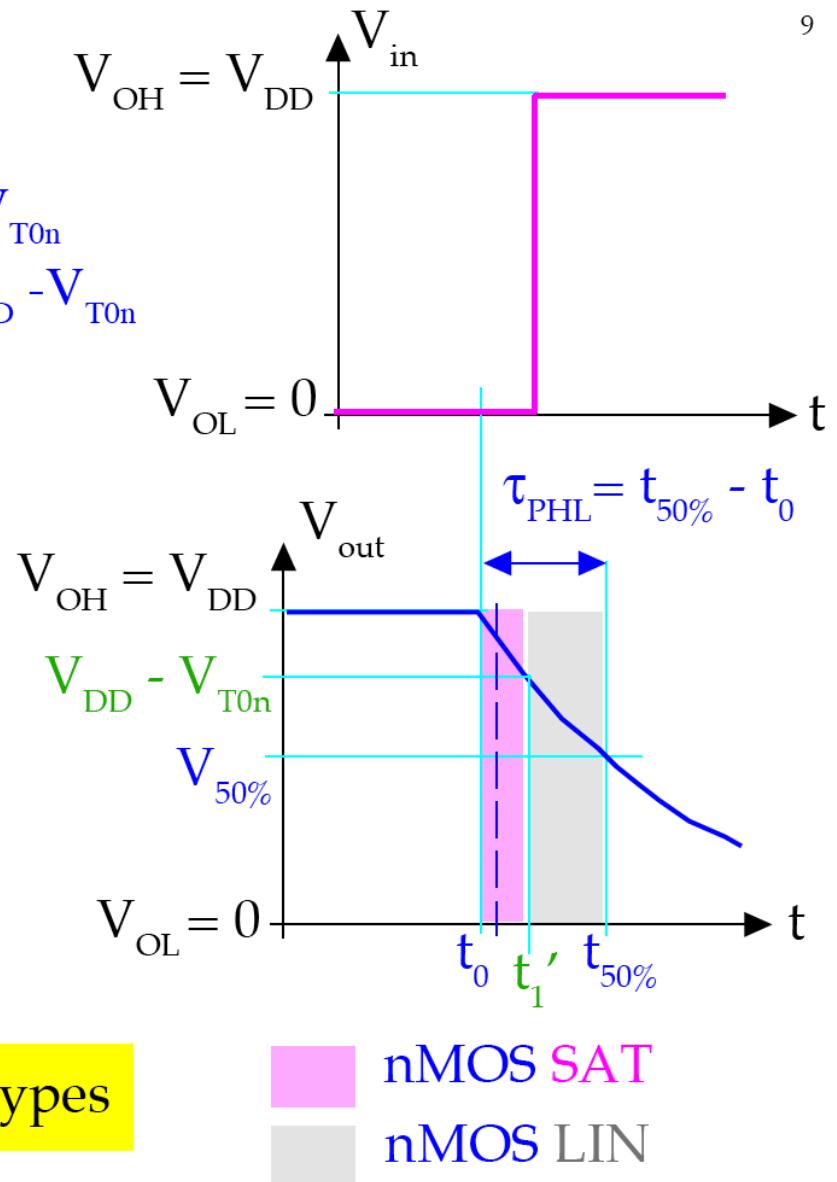



CMOS Inverter Revisited

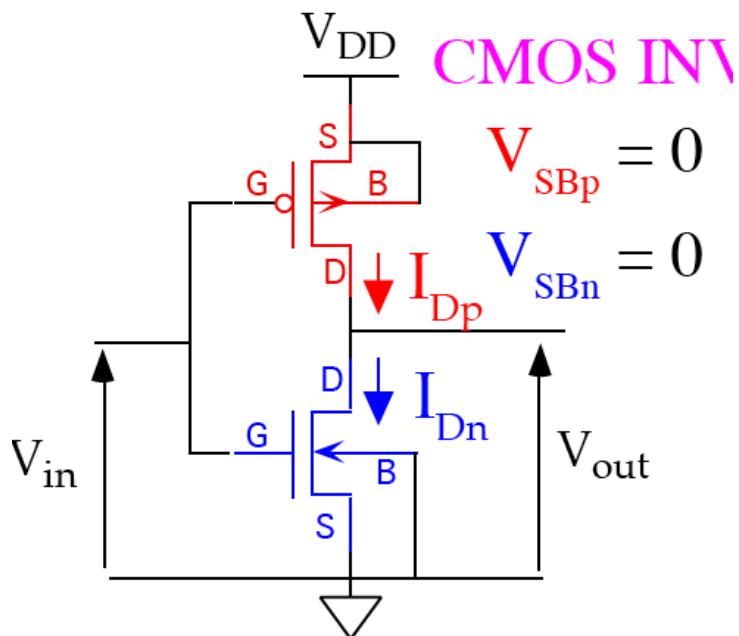

$$V_{in} = V_{GSn} = V_{GSp} + V_{DD}$$

$$V_{out} = V_{DSn} = V_{DSP} + V_{DD}$$

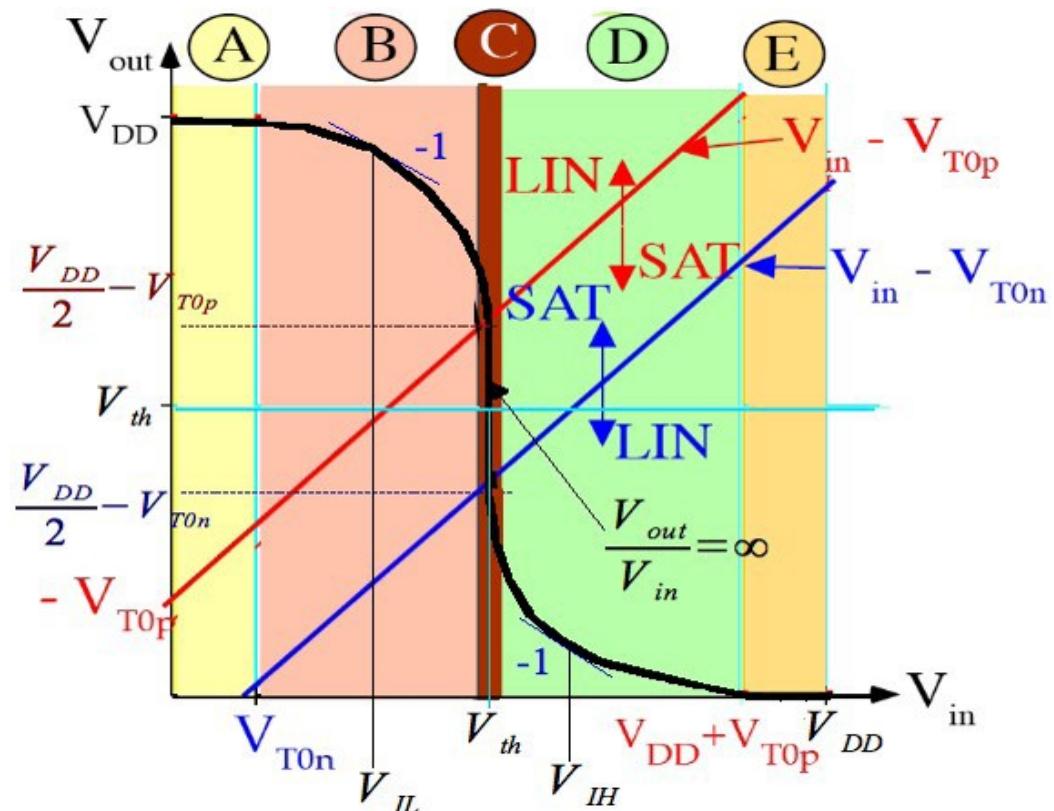

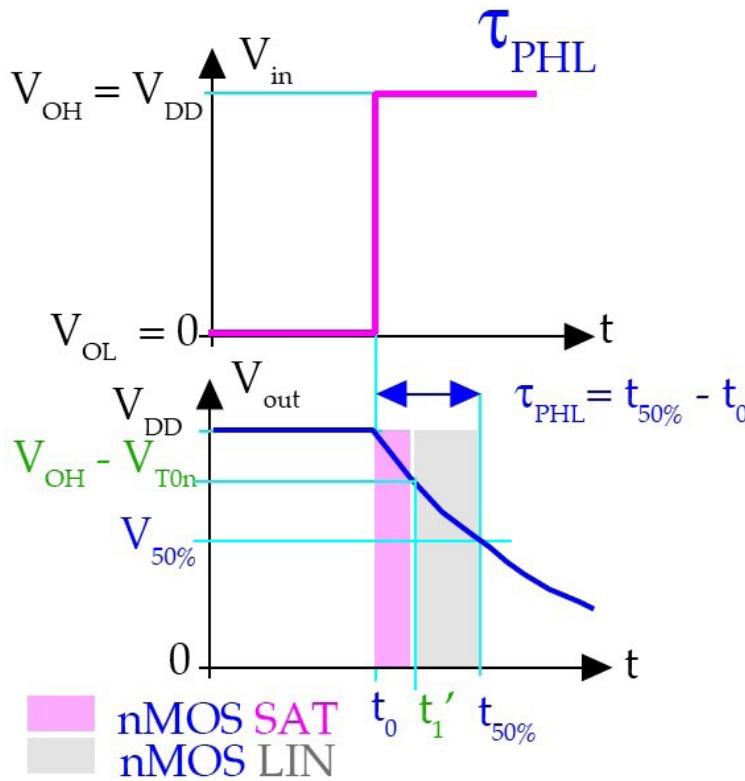

Since i_{Dn} is INDEP of V_{out}

$$\int_{t=t_0}^{t=t_1'} dt = - \frac{C_{load}}{\frac{k_n}{2}(V_{OH} - V_{T0n})^2} \quad \begin{aligned} V_{out} &= V_{OH} - V_{T0n} \\ &\int_{V_{out}=V_{OH}}^{V_{out}=V_{OH}-V_{T0n}} dV_{out} \end{aligned}$$

$$t_1' - t_0 = \frac{2C_{load}V_{T0n}}{k_n(V_{OH} - V_{T0n})^2}$$

$t_0 < t < t_1'$:


$$i_{Dn} = \frac{k_n}{2}(V_{in} - V_{T0n})^2 = -i_C$$

$$\frac{k_n}{2}(V_{OH} - V_{T0n})^2 = -C_{load} \frac{dV_{out}}{dt}$$

for $V_{OH} - V_{T0n} < V_{out} \leq V_{OH}$

$$i_{Dn} = -C_{load} \frac{dV_{out}}{dt} \Rightarrow dt = -\frac{C_{load}}{i_{Dn}} dV_{out}$$
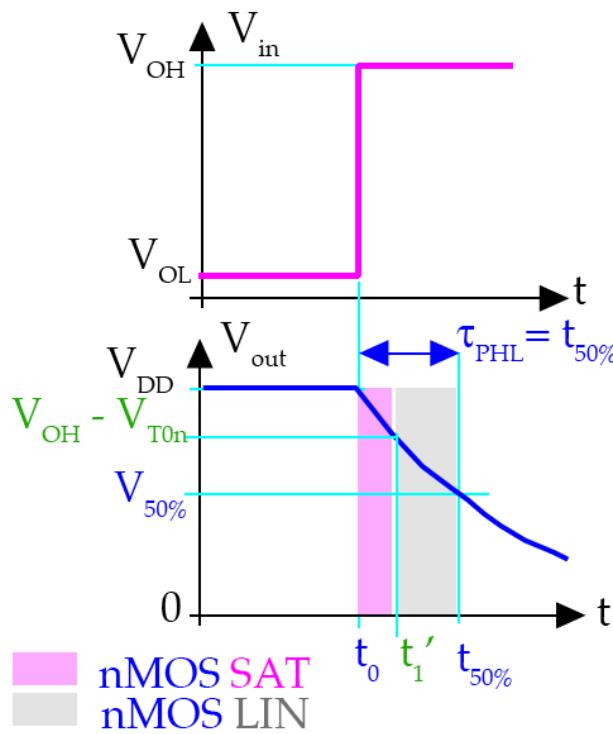
$$\int_{t=t_0}^{t=t_1'} dt = -C_{load} \int_{V_{out}=V_{OH}}^{V_{out}=V_{OH}-V_{T0n}} \left(\frac{1}{i_{Dn}} \right) dV_{out}$$



$t_1' < t < t_{50\%}$:

$$i_{Dn} = \frac{k_n}{2} [2(V_{in} - V_{T0n})V_{out} - V_{out}^2]$$

$$\tau_{PHL} = t_{50\%} - t_0 = \frac{k_n}{2} [2(V_{OH} - V_{T0n})V_{out} - V_{out}^2] = -C_{load} \frac{dV_{out}}{dt}$$

for $V_{out} \leq V_{OH} - V_{T0n}$

$$\int_{t=t_1'}^{t=t_{50\%}} dt = -C_{load} \int_{V_{out}=V_{OH}-V_{T0n}}^{V_{out}=V_{50\%}} \left(\frac{1}{\frac{dV_{out}}{dt}} \right) dV_{out}$$

$$\int_{t=t_1'}^{t=t_{50\%}} dt = -\frac{2C_{load}}{k_n} \int_{V_{out}=V_{OH}-V_{T0n}}^{V_{out}=V_{50\%}} \left(\frac{1}{2(V_{OH} - V_{T0n})V_{out} - V_{out}^2} \right) dV_{out}$$

$$t_{50\%} - t_1' = -\frac{2C_{load}}{k_n} \frac{1}{2(V_{OH} - V_{T0n})} \ln \left(\frac{V_{out}}{2(V_{OH} - V_{T0n}) - V_{out}} \right) \Big|_{V_{out}=V_{50\%}}^{V_{out}=V_{OH}-V_{T0n}}$$

$$t_{50\%} - t_1 = -\frac{2C_{load}}{k_n} \frac{1}{2(V_{OH} - V_{T0n})} \ln\left(\frac{V_{out}}{2(V_{OH} - V_{T0n}) - V_{out}}\right) \Bigg| \begin{array}{l} V_{out} = V_{50\%} \\ V_{out} = V_{OH} - V_{T0n} \end{array}$$

$$= \frac{C_{load}}{k_n(V_{OH} - V_{T0n})} \ln\left(\frac{2(V_{OH} - V_{T0n}) - V_{50\%}}{V_{50\%}}\right)$$

→ $t_1' - t_0 = \frac{2C_{load}V_{T0n}}{k_n(V_{OH} - V_{T0n})^2}$

$$\tau_{PHL} = t_{50\%} - t_1' + t_1' - t_0$$

$$\tau_{PHL} = \frac{2C_{load}V_{T0n}}{k_n(V_{OH} - V_{T0n})^2} + \frac{C_{load}}{k_n(V_{OH} - V_{T0n})} \ln\left(\frac{2(V_{OH} - V_{T0n}) - V_{50\%}}{V_{50\%}}\right)$$

$$= \frac{C_{load}}{k_n(V_{OH} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{OH} - V_{T0n}} + \ln\left(\frac{2(V_{OH} - V_{T0n}) - V_{50\%}}{V_{50\%}} - 1\right) \right]$$

$$\tau_{PHL} = \frac{C_{load}}{k_n(V_{OH} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{OH} - V_{T0n}} + \ln \left(\frac{2(V_{OH} - V_{T0n})}{V_{50\%}} - 1 \right) \right]$$


SUBSTITUTING $V_{50\%} = 0.5 [V_{OL} + V_{OH}]$

$$\tau_{PHL} = \frac{C_{load}}{k_n(V_{OH} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{OH} - V_{T0n}} + \ln \left(\frac{4(V_{OH} - V_{T0n})}{V_{OH} + V_{OL}} - 1 \right) \right]$$

WHERE for CMOS Inverters $V_{OL} = 0, V_{OH} = V_{DD}$

$$\tau_{PHL} = \frac{C_{load}}{k_n(V_{DD} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

Fall Time: τ_{fall}

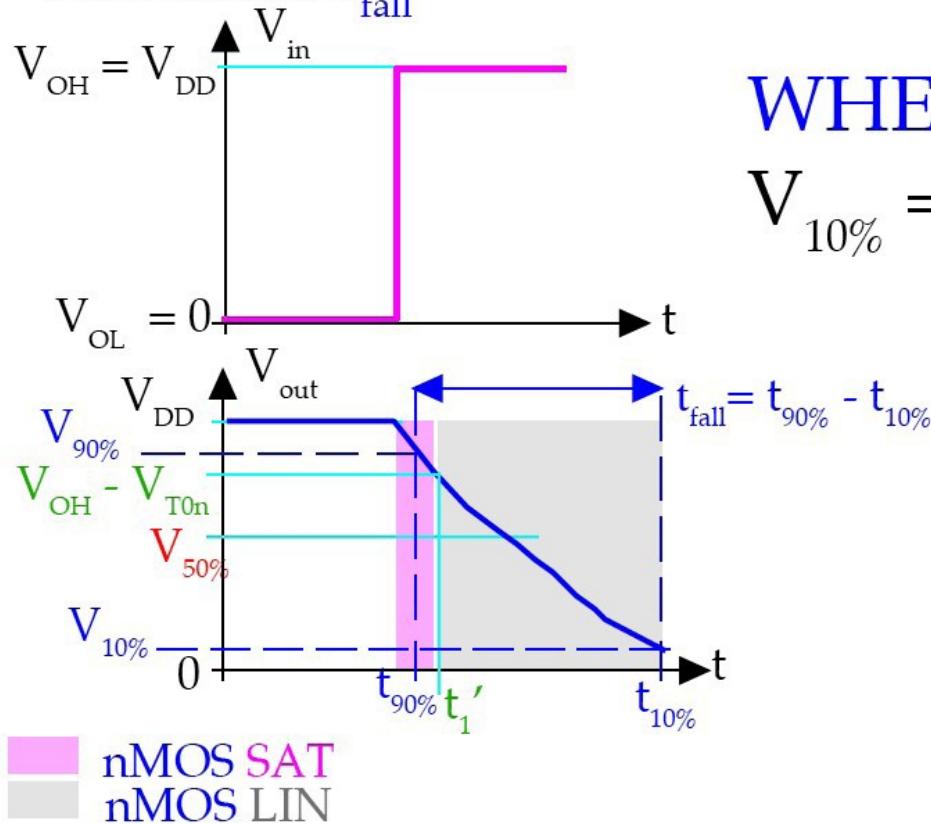

WHERE for CMOS Inverters

$$V_{\text{10\%}} = 0.1V_{\text{DD}}, V_{\text{90\%}} = 0.9V_{\text{DD}}$$

$$\tau_{\text{fall}} = \frac{C_{\text{load}}}{k_n(V_{\text{DD}} - V_{\text{T0n}})} \left[\frac{2(V_{\text{T0n}} - 0.1V_{\text{DD}})}{V_{\text{DD}} - V_{\text{T0n}}} + \ln \left(\frac{2(V_{\text{DD}} - V_{\text{T0n}})}{0.1V_{\text{DD}}} - 1 \right) \right]$$

$$\tau_{\text{PHL}} = \frac{C_{\text{load}}}{k_n(V_{\text{DD}} - V_{\text{T0n}})} \left[\frac{2V_{\text{T0n}}}{V_{\text{DD}} - V_{\text{T0n}}} + \ln \left(\frac{2(V_{\text{DD}} - V_{\text{T0n}})}{0.5V_{\text{DD}}} - 1 \right) \right]$$

EXAMPLE 6.1

Consider a CMOS inverter with $C_{\text{load}} = 1.0 \text{ pF}$, where the IV characteristics of the nMOS transistor driver are specified as follows:

$$V_{GSn} = 5 \text{ V} \text{ and } V_{DSn} \geq 4 \text{ V} \Rightarrow i_{Dn} = i_{Dnsat} = 5 \text{ mA}$$

Assume V_{in} is a step pulse that switches instantaneously from 0 to 5 V. Calculate the delay time necessary for the inverter output to fall from its initial value of 5 V to 2.5 V.

$$V_{50\%} = 0.5 [V_{OL} + V_{OH}] = 0.5 [0 + 5 \text{ V}] = 2.5 \text{ V}$$

1. FROM IV DATA: Determine V_{T0n} and k_n

$$\text{nMOS in SAT} \Rightarrow V_{DSn} = 5 \text{ V} - V_{T0n} = 4 \text{ V} \Rightarrow V_{T0n} = 1 \text{ V}$$

Using $i_{Dnsat} = \frac{k_n}{2} (V_{GS} - V_{T0n})^2 = 5 \text{ mA}$

$$k_n = \frac{2i_{Dnsat}}{(V_{GS} - V_{T0n})^2} = \frac{2 \times 5 \text{ mA}}{(4 \text{ V})^2} = 0.625 \times 10^{-3} \text{ A/V}^2$$

2. $t_0 < t < t_1'$:

where $i_{Dn} = I_{Dnsat} = 5\text{mA}$

$$\begin{aligned} t=t_1' \\ \int_{t=t_0}^{t=t_1'} dt = -C_{load} \int_{V_{out}=V_{OH}}^{V_{out}=V_{OH}-V_{T0n}} \left(\frac{1}{i_{Dn}} \right) dV_{out} \\ V_{OH} - V_{T0n} = 4 \text{ V} \\ V_{OH} = 5 \text{ V} \end{aligned}$$

$$t_1' - t_0 = -\frac{C_{load}}{i_{Dnsat}} \int_{V_{out}=5\text{V}}^{V_{out}=4\text{V}} dV_{out} = -\frac{1\text{pF}}{5\text{mA}} (-1\text{V}) = 0.2\text{nS}$$

UNITS

$$\frac{C_{Load}}{i_{Dnsat}} \Delta V = \frac{F}{A} V = \frac{C/V}{C/s} V = s$$

3. $t_1' < t < t_1$:

$$\begin{aligned} t_1 - t_1' &= \frac{C_{load}}{k_n(V_{OH} - V_{T0n})} \ln \left(\frac{2(V_{OH} - V_{T0n}) - V_{50\%}}{V_{50\%}} \right) \\ &= \frac{1\text{pF}}{(0.625 \times 10^3 \text{ A/V}^2)(5 - 1)\text{V}} \ln \left(\frac{2(5 - 1)\text{V} - 2.5\text{V}}{2.5\text{V}} \right) \end{aligned}$$

$$= \frac{1 \times 10^{-12} \text{ F}}{(0.625 \times 10^3 \text{ A/V}^2) 4 \text{ V}} \ln \left(\frac{5.5}{2.5} \right) = 1.26 \text{ ns}$$

$$\tau_{PHL} = 0.2 \text{ ns} + 1.26 \text{ ns} = 1.46 \text{ ns}$$

2) V_{in} - ABRUPTLY FALLS CASE:

IC: $V_{out} = V_{OL}$, $V_{in} = V_{OH} \rightarrow V_{OL} = 0$


nMOS - OFF

$$\text{SAT } V_{out} \leq V_{in} - V_{T0p} = 0$$


p-MOS ON

$$\text{LIN } V_{out} > -V_{T0p}$$
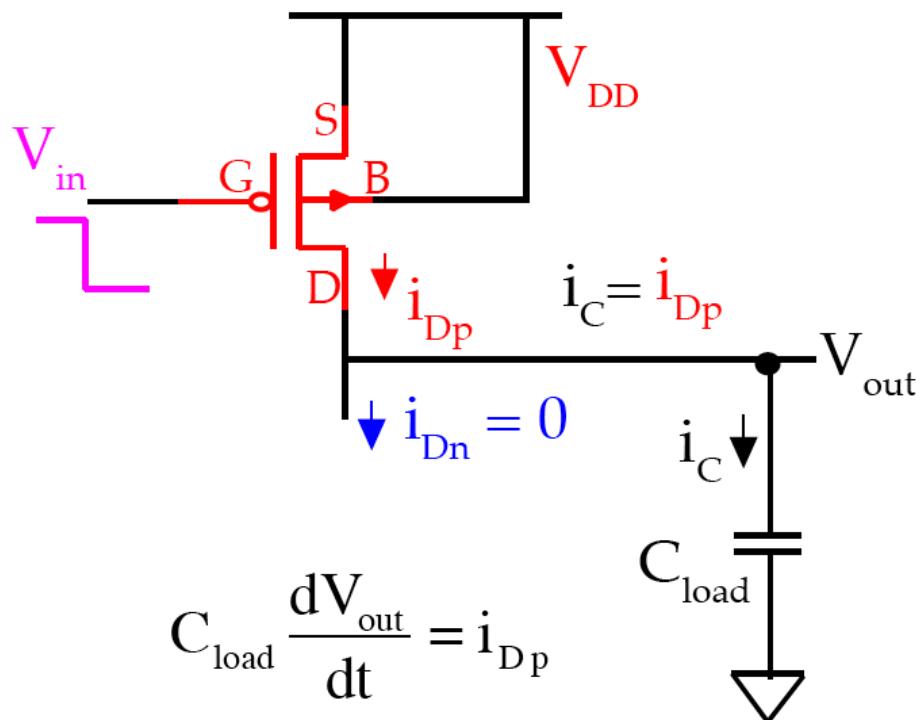
$$V_{GS} = V_{in} - V_{DD} \quad V_{DS} = V_{out} - V_{DD}$$


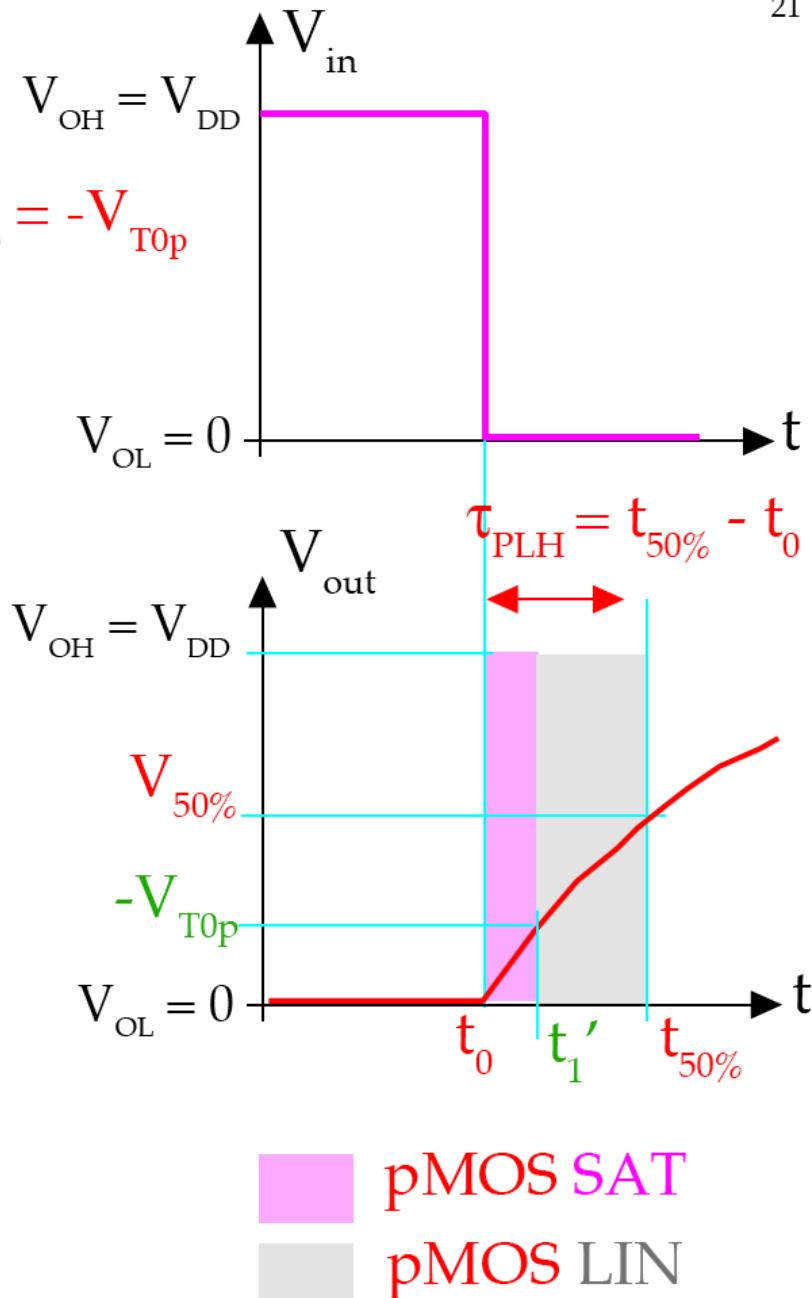
$$C_{load} \frac{dV_{out}}{dt} = i_{Dp}$$



$$\tau_{PLH} = \frac{C_{load}}{k_p(V_{OH} - V_{OL} - |V_{T0p}|)} \left[\frac{2|V_{T0p}|}{V_{OH} - |V_{T0p}|} + \ln \left(\frac{2(V_{OH} - V_{OL} - |V_{T0p}|)}{V_{OH} - V_{50\%}} - 1 \right) \right]$$

$V_{50\%} = 0.5 [V_{OL} + V_{OH}]$, FOR CMOS INV: $V_{OL} = 0$, $V_{OH} = V_{DD}$

$$\tau_{PLH} = \frac{C_{load}}{k_p(V_{DD} - |V_{T0p}|)} \left[\frac{2|V_{T0p}|}{V_{DD} - |V_{T0p}|} + \ln \left(\frac{4(V_{DD} - |V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

$$\tau_{rise} = \frac{C_{load}}{k_p(V_{DD} - |V_{T0p}|)} \left[\frac{2(|V_{T0p}| - 0.1V_{DD})}{V_{DD} - |V_{T0p}|} + \ln \left(\frac{2(V_{DD} - |V_{T0p}|)}{0.1V_{DD}} - 1 \right) \right]$$

FOR CMOS INV: $V_{OL} = 0$, $V_{OH} = V_{DD}$

$$\tau_{PHL} = \frac{C_{load}}{k_n(V_{DD} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

CONDITIONS FOR Balanced CMOS Inverter Propagation Delays, i.e. $\tau_{PHL} = \tau_{PLH}$

$$\tau_{PLH} = \frac{C_{load}}{k_p(V_{DD} - |V_{T0p}|)} \left[\frac{2|V_{T0p}|}{V_{DD} - |V_{T0p}|} + \ln \left(\frac{4(V_{DD} - |V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PHL} = \frac{C_{load}}{k_n(V_{DD} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

where $k_n = \mu_n C_{ox} \frac{W_n}{L_n}$ & $k_p = \mu_p C_{ox} \frac{W_p}{L_p}$

FOR $\tau_{PHL} = \tau_{PLH}$

$$V_{T0n} = |V_{T0p}| \quad \text{or} \quad \frac{\left(\frac{W}{L}\right)_n}{\left(\frac{W}{L}\right)_p} = \frac{\mu_p}{\mu_n}$$

$$k_n = k_p$$




OBSERVATIONS

$$\tau_{PHL} = \frac{C_{load} L_n}{\mu_n C_{ox} (V_{DD} - V_{T0n})} \left(\frac{1}{W_n} \right) \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH} = \frac{C_{load} L_p}{\mu_n C_{ox} (V_{DD} - |V_{Top}|)} \left(\frac{1}{W_p} \right) \left[\frac{2|V_{Top}|}{V_{DD} - |V_{Top}|} + \ln \left(\frac{4(V_{DD} - |V_{Top}|)}{V_{DD}} - 1 \right) \right]$$

- Calculation of τ_{PHL} , depends largely on NMOS driver, i.e. **nearly same for all INV types**.
- Calculation of τ_{PLH} , depends largely on the **load device** and its operation, i.e. **different for all INV types**.
- Options to reduce τ_{PHL} , τ_{PLH} :
 - Decrease C_{load}
 - Increase V_{DD}
 - Increase W/L ratio (which usually means increasing W)

Account for Input Waveform Slope

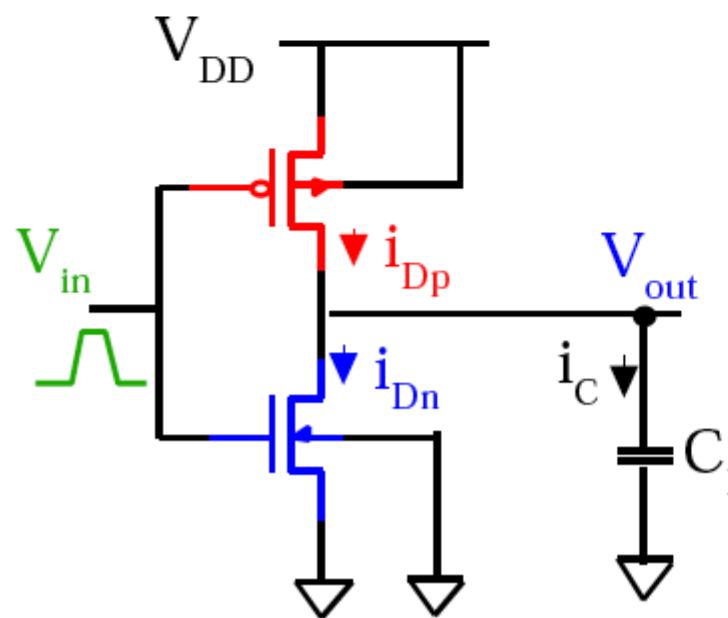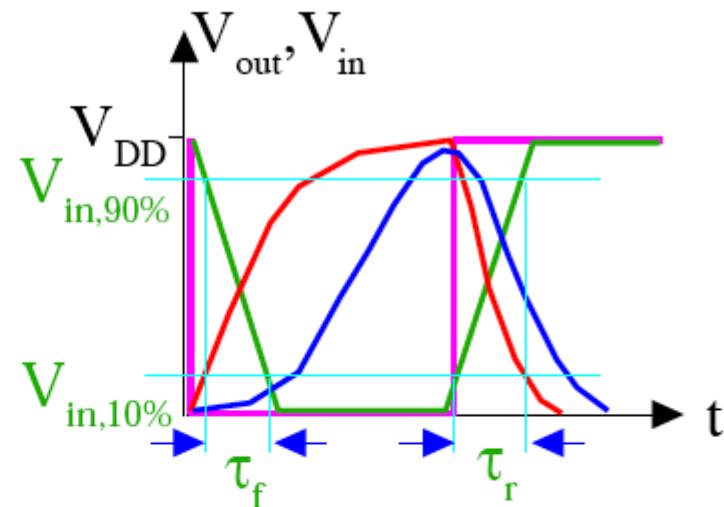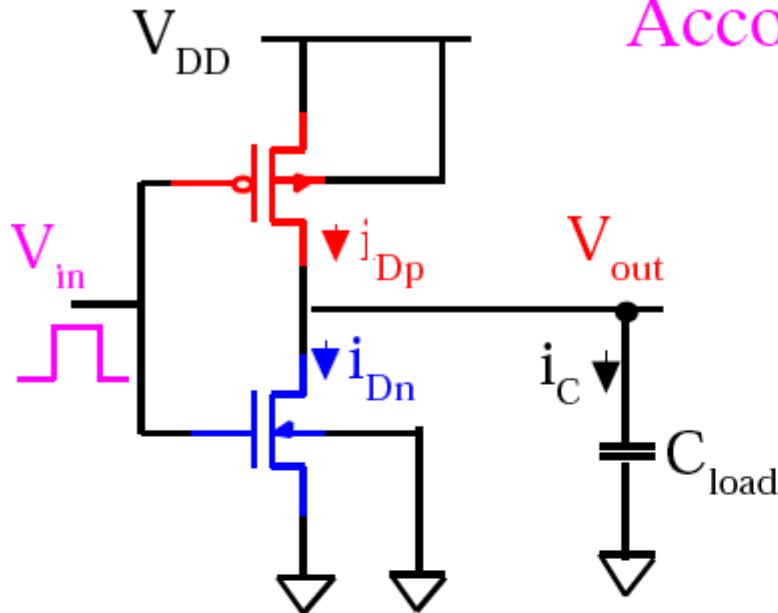

**EMPERICAL DELAY
CORRECTIONS FOR INPUT τ_r , τ_f :**

$$\tau_{PHL}(\text{actual}) = \sqrt{\tau_{PHL}^2(\text{step-input}) + \left(\frac{\tau_r}{2}\right)^2}$$

$$\tau_{PLH}(\text{actual}) = \sqrt{\tau_{PLH}^2(\text{step-input}) + \left(\frac{\tau_f}{2}\right)^2}$$

CMOS INVERTER DELAY DESIGN FORMULAS

$$\tau_{PHL} = \frac{C_{load}}{k_n(V_{DD} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

where $k_n = \mu_n C_{ox} \frac{W_n}{L_n}$

$$\frac{W_n}{L_n} = \frac{C_{load}}{\tau_{PHL} \mu_n C_{ox} (V_{DD} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH} = \frac{C_{load}}{k_p(V_{DD} - |V_{T0p}|)} \left[\frac{2|V_{T0p}|}{V_{DD} - |V_{T0p}|} + \ln \left(\frac{4(V_{DD} - |V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

where $k_p = \mu_p C_{ox} \frac{W_p}{L_p}$

$$\frac{W_p}{L_p} = \frac{C_{load}}{\tau_{PLH} \mu_p C_{ox} (V_{DD} - |V_{T0p}|)} \left[\frac{2|V_{T0p}|}{V_{DD} - |V_{T0p}|} + \ln \left(\frac{4(V_{DD} - |V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

EXAMPLE 6.3

Design a CMOS inverter by determining the W_n and W_p of the nMOS and PMOS transistors to meet the following specs:

-> $V_{th} = 2 \text{ V}$ for $V_{DD} = 5 \text{ V}$

-> Delay time of 2 ns for a V_{out} transition from 4 V to 1 V,
with $C_{load} = 1.0 \text{ pF}$.

The process and device parameters are specified as follows:

$$k_n' = \mu_n C_{ox} = 30 \mu\text{A}/\text{V}^2,$$

$$k_p' = \mu_p C_{ox} = 10 \mu\text{A}/\text{V}^2$$

$$L_n = L_p = 1.0 \mu\text{m}$$

$$V_{T0n} = 1.0 \text{ V}$$

$$V_{T0p} = -1.5 \text{ V}$$

$$W_{min} = 2 \mu\text{m} \text{ (limited by design rules)}$$

STEP #1: Satisfy the Delay Constraint: τ_{PHL} from 4 V to 1 V

HL => PULL-DOWN => τ_{PHL} determined by nMOS driver

NOTE $V_{in} = V_{OH}$ and $1 \leq V_{out} \leq 4 \text{ V} \Rightarrow$ nMOS LIN

$$C_{load} \frac{dV_{out}}{dt} = -\frac{\mu_n C_{ox}}{2} \frac{W_n}{L_n} [2(V_{OH} - V_{T0n}) V_{out} - V_{out}^2]$$

$$\begin{aligned}\tau_{delay} &= 2.0 \times 10^{-9} \text{ s} = -2 C_{load} \frac{1}{\mu_n C_{ox} \frac{W_n}{L_n}} \int_{V_{out}=4}^{V_{out}=1} \frac{dV_{out}}{[2(V_{OH} - V_{T0n}) V_{out} - V_{out}^2]} \\ &= -2 C_{load} \frac{1}{\mu_n C_{ox} \frac{W_n}{L_n}} \frac{1}{2(V_{OH} - V_{T0n})} \ln \left| \frac{V_{out}}{2(V_{OH} - V_{T0n}) - V_{out}} \right| \Big|_{V_{out}=4}^{V_{out}=1} \\ &= \frac{-C_{load}}{\mu_n C_{ox} \frac{W_n}{L_n} (V_{DD} - V_{T0n})} \left\{ \ln \left[\frac{1V}{2(5-1)V - 1V} \right] - \ln \left[\frac{4V}{2(5-1)V - 4V} \right] \right\} \\ 2.0 \times 10^{-9} \text{ s} &= \frac{-1 \times 10^{-12} \text{ F}}{(30 \times 10^{-6} \text{ A/V}^2) \frac{W_n}{L_n} (5-1)V} \left\{ \ln \left[\frac{1}{7} \right] - \ln \left[\frac{4}{4} \right] \right\}\end{aligned}$$

$$\frac{W_n}{L_n} = \frac{1 \times 10^{-12} \text{ F}}{(2.0 \times 10^{-9} \text{ s})(30 \times 10^{-6} \text{ A/V}^2)(4)} \ln(7) = \frac{1}{(2.0)(0.03)(4)} \ln(7) = 8.108$$

$$\frac{W_n}{L_n} = 8.108, L_n = 1\mu m \Rightarrow W_n = 8.108 (1 \mu m) = 8.1 \mu m$$

From τ_{delay} spec.

STEP #2: Satisfy the V_{th} constraint, where:

$$V_{th} = \frac{V_{T0n} + \sqrt{\frac{1}{k_R}}(V_{DD} + V_{T0p})}{\left(1 + \sqrt{\frac{1}{k_R}}\right)} = \frac{1.0V + \sqrt{\frac{1}{k_R}}(5 + (-1.5))V}{\left(1 + \sqrt{\frac{1}{k_R}}\right)}$$

$$= \frac{1.0V + \sqrt{\frac{1}{k_R}}(3.5)V}{\left(1 + \sqrt{\frac{1}{k_R}}\right)} = 2V \Rightarrow k_R = (1.5)^2 = \frac{9}{4}$$

$$k_R = \frac{\mu_n C_{ox} (W/L)_n}{\mu_p C_{ox} (W/L)_p} = \frac{30 W_n}{10 W_p} = 3 \frac{W_n}{W_p} = \frac{9}{4} \Rightarrow W_p = \frac{4}{9} (3) W_n$$

with $L_p = 1 \mu m$

$$W_p = \frac{4}{9} (3) 8.1 \mu m = 10.8 \mu m$$

LIMITS TO SCALING DEVICE DIMENSIONS TO REDUCE PROPAGATION DELAYS

30

$$\tau_{PHL} = \frac{C_{load}}{k_n(V_{DD} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH} = \frac{C_{load}}{k_p(V_{DD} - |V_{T0p}|)} \left[\frac{2|V_{T0p}|}{V_{DD} - |V_{T0p}|} + \ln \left(\frac{4(V_{DD} - |V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

$$k_n = \mu_n C_{ox} \frac{W_n}{L_n} \quad k_p = \mu_p C_{ox} \frac{W_p}{L_p}$$

If C_{load} = independent of L_n , W_n and L_p , W_p

$$\tau_{PHL} = \frac{C_{load} L_n}{\mu_n C_{ox} (V_{DD} - V_{T0n})} \left(\frac{1}{W_n} \right) \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right] = \frac{k_{PHL}}{W_n}$$

$$\tau_{PLH} = \frac{C_{load} L_p}{\mu_n C_{ox} (V_{DD} - |V_{T0p}|)} \left(\frac{1}{W_p} \right) \left[\frac{2|V_{T0p}|}{V_{DD} - |V_{T0p}|} + \ln \left(\frac{4(V_{DD} - |V_{T0p}|)}{V_{DD}} - 1 \right) \right] = \frac{k_{PLH}}{W_p}$$

Also

$$\tau_{fall} = \frac{k_{fall}}{W_n}$$

$$\tau_{rise} = \frac{k_{rise}}{W_p}$$

$$C_{load} \approx C_{dbn} + C_{dbp} + C_{int} + C_{gb}$$

For $C_{load} = \text{constant}$

$$\tau_{PHL} = \frac{k_{PHL}}{W_n}$$


$$\lim_{W_n \rightarrow \infty} \tau_{PHL} = \lim_{W_n \rightarrow \infty} \frac{k_{PHL}}{W_n} \rightarrow 0s$$

$$\tau_{PLH} = \frac{k_{PLH}}{W_p}$$


$$\lim_{W_p \rightarrow \infty} \tau_{PLH} = \lim_{W_p \rightarrow \infty} \frac{k_{PLH}}{W_p} \rightarrow 0s$$


Only when C_{load} is dominated by C_{int} is C_{load} a constant design parameter that is independent of the device dimensions.

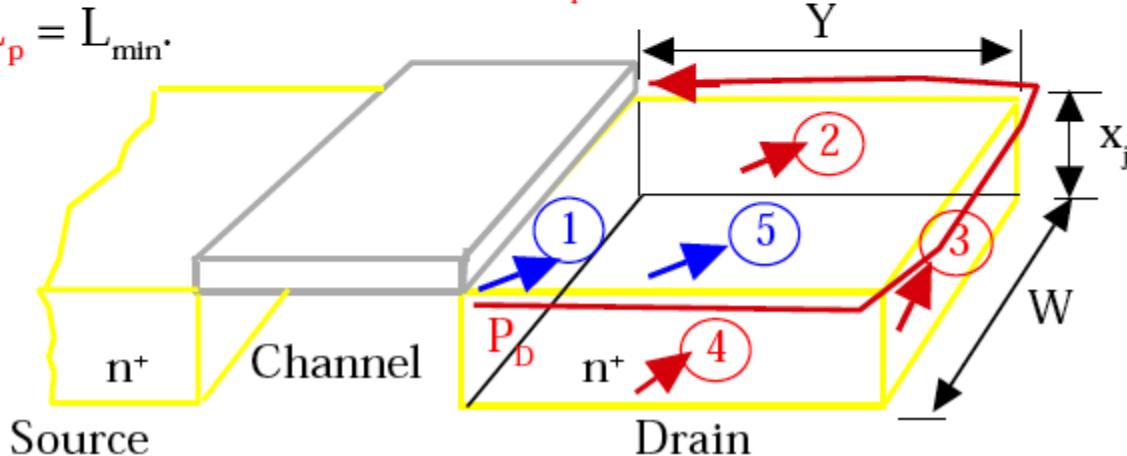In practice, to minimize area, L_n , L_p are set to the minimum dimension , i.e. $L_n = L_p = L_{min}$.


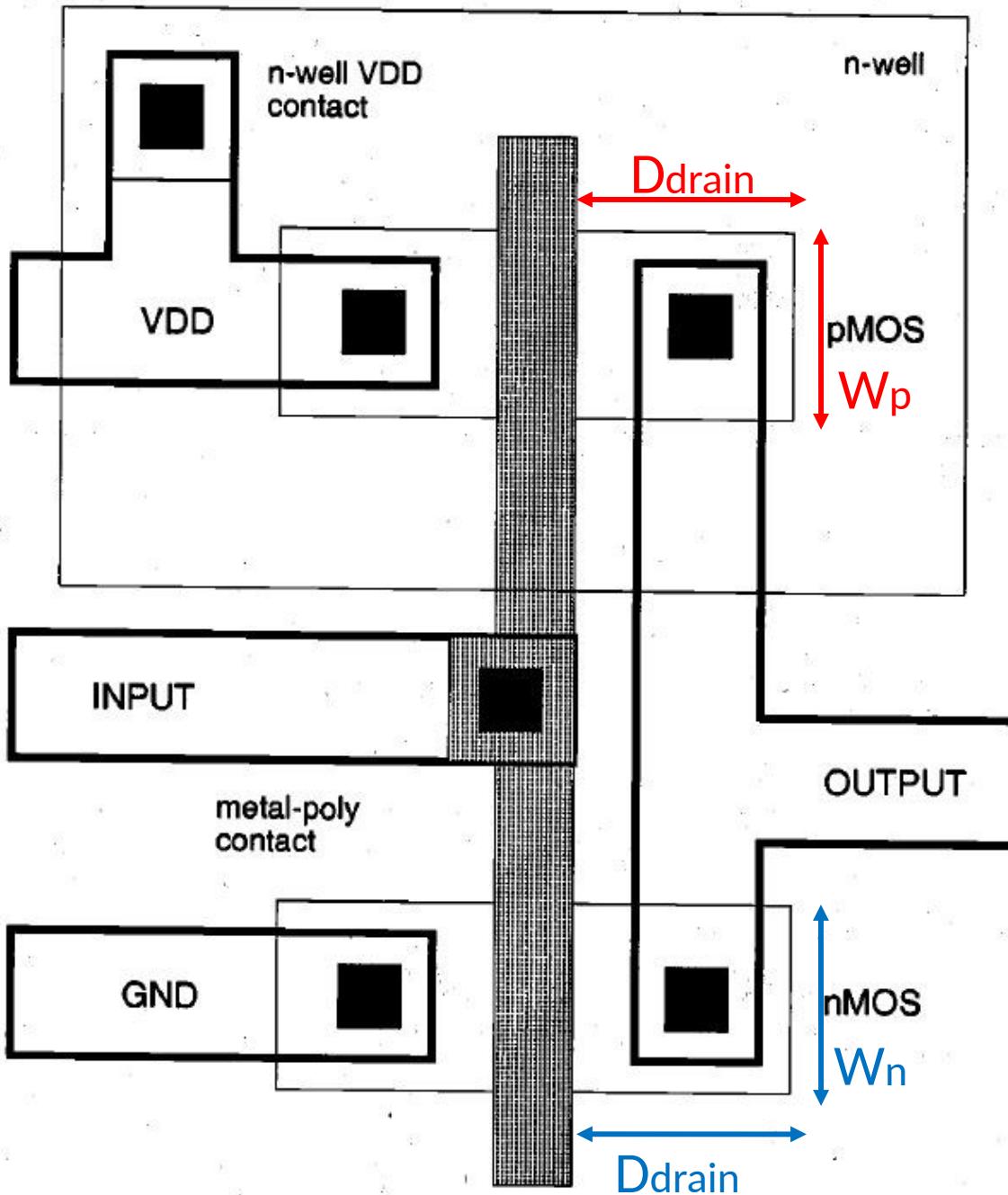
$$C_{load} \approx C_{dbn}(W_n) + C_{dbp}(W_p) + C_{int} + C_{gb}$$



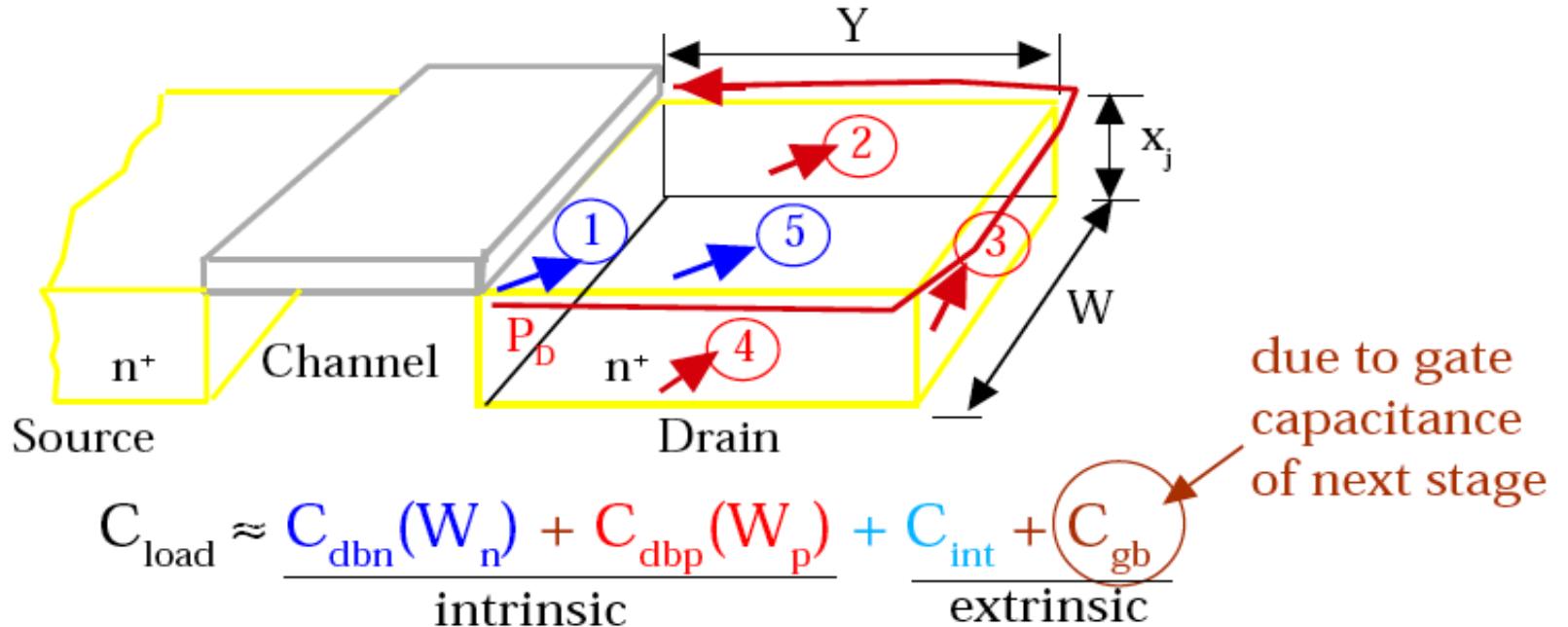

where

$$C_{\text{dbn}}(W_n) = W_n(Y + x_j)C_{j0n}K_{\text{eqn}} + (W_n + 2Y)C_{jswn}K_{\text{eqn}}$$

$$C_{\text{dbp}}(W_p) = W_p(Y + x_j)C_{j0p}K_{\text{eqp}} + (W_p + 2Y)C_{jswp}K_{\text{eqp}}$$

$$C_{\text{load}} = \alpha_n W_n + \alpha_p W_p + \alpha_0$$

$$\alpha_0 = 2Y(C_{jswn}K_{\text{eqn}} + C_{jswp}K_{\text{eqp}}) + C_{\text{int}} + C_{\text{gb}}$$

$$\alpha_n = K_{\text{eqn}} ((Y + x_j)C_{j0n} + C_{jswn})$$

$$\alpha_p = K_{\text{eqp}} ((Y + x_j)C_{j0p} + C_{jswp})$$

$$\tau_{PHL} = \frac{C_{load} L_n}{\mu_n C_{ox} (V_{DD} - V_{T0n})} \left(\frac{1}{W_n} \right) \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH} = \frac{C_{load} L_p}{\mu_n C_{ox} (V_{DD} - |V_{T0p}|)} \left(\frac{1}{W_p} \right) \left[\frac{2|V_{T0p}|}{V_{DD} - |V_{T0p}|} + \ln \left(\frac{4(V_{DD} - |V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

Let $C_{load} = \alpha_0 + \alpha_n W_n + \alpha_p W_p$

$$\tau_{PHL} = \Gamma_n \left(\frac{\alpha_0 + (\alpha_n + R\alpha_p)W_n}{W_n} \right)$$

$$\tau_{PLH} = \Gamma_p \left(\frac{\alpha_0 + \left(\frac{\alpha_n}{R} + \alpha_p \right) W_p}{W_p} \right)$$

where $R = \frac{W_p}{W_n}$ (set to static parameters, V_{th} in CMOS)

$$\Gamma_n = \left(\frac{L_n}{\mu_n C_{ox} (V_{DD} - V_{T0n})} \right) \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\Gamma_p = \left(\frac{L_p}{\mu_p C_{ox} (V_{DD} - |V_{T0p}|)} \right) \left[\frac{2|V_{T0p}|}{V_{DD} - |V_{T0p}|} + \ln \left(\frac{4(V_{DD} - |V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PHL} = \Gamma_n \left(\frac{\alpha_0 + (\alpha_n + R\alpha_p)W_n}{W_n} \right) \quad \tau_{PLH} = \Gamma_p \left(\frac{\alpha_0 + \left(\frac{\alpha_n}{R} + \alpha_p \right)W_p}{W_p} \right)$$

Hence, increasing W_p and W_n will have diminishing influence on τ_{PHL} and τ_{PLH} as they become large, i.e.

$$\tau_{PHL}^{\text{Limit}} = \lim_{W_n \rightarrow \infty} \tau_{PHL} = \Gamma_n (\alpha_n + R\alpha_p) \quad \text{absolute minimum delays}$$

$$\tau_{PLH}^{\text{Limit}} = \lim_{W_p \rightarrow \infty} \tau_{PLH} = \Gamma_p \left(\frac{\alpha_n}{R} + \alpha_p \right)$$

NOTE:


- $\tau_{PHL}^{\text{Limit}}$, $\tau_{PLH}^{\text{Limit}}$ are independent of $\alpha_0 = f(C_{int}, C_{gb})$.
- Achievement of ABSOLUTE MINIMUM DELAYS comes with maximum cost, i.e.

DIE AREA -> Maximized

POWER DISIPATION -> Maximized


Propagation Delay vs. W

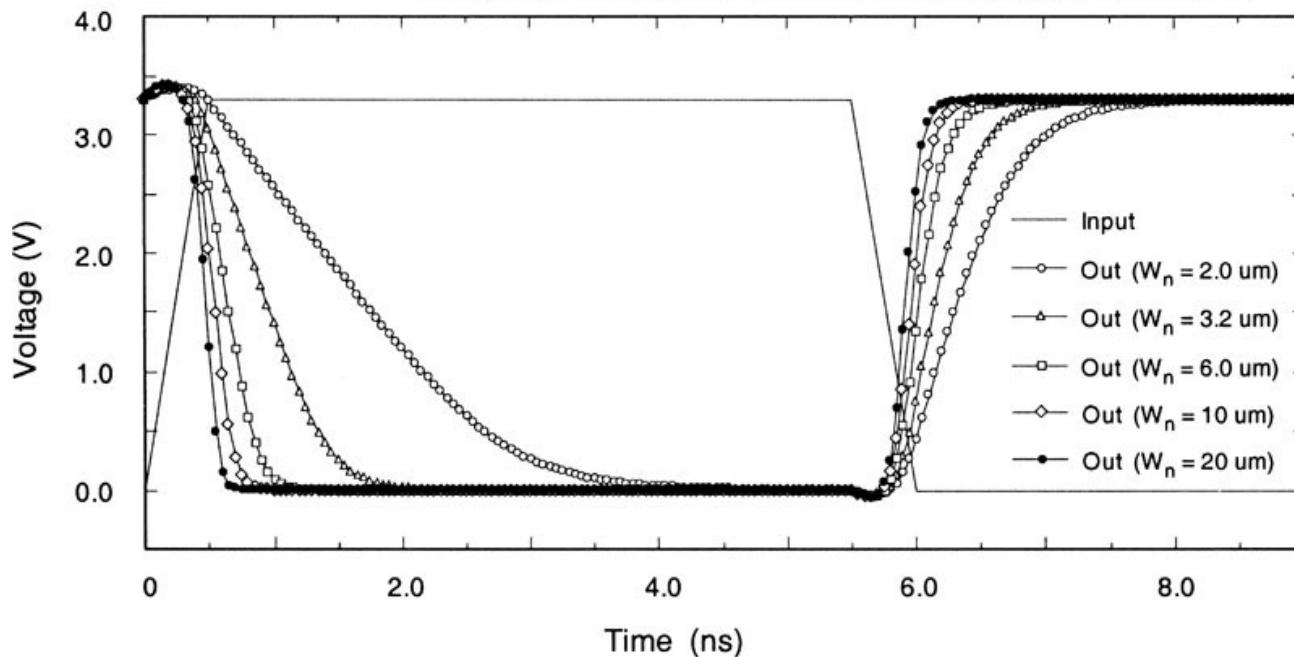Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Propagation Delay vs. Area

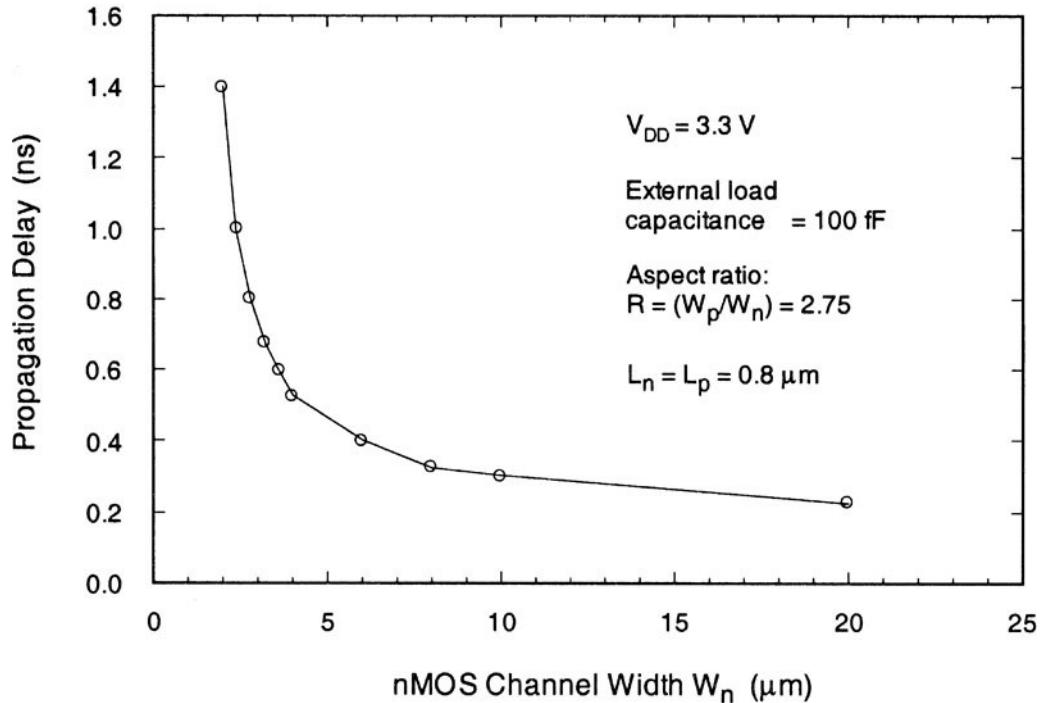
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



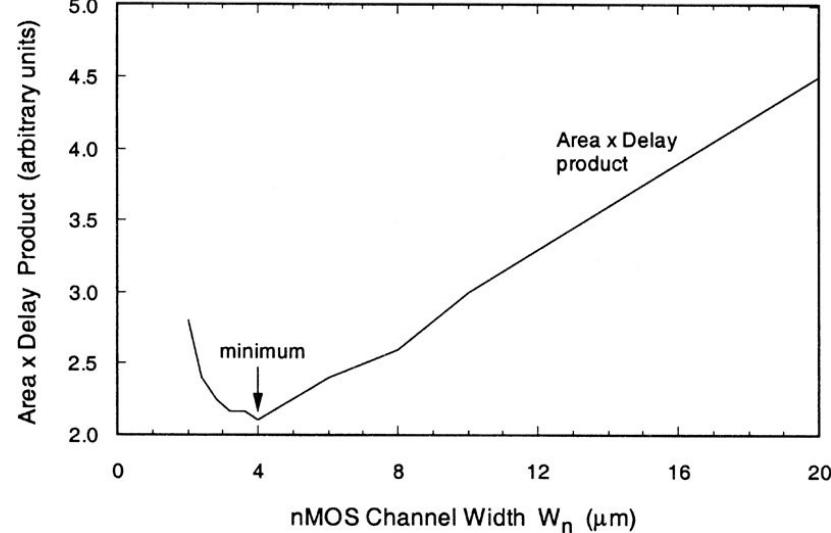
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




CMOS RING OSCILLATOR

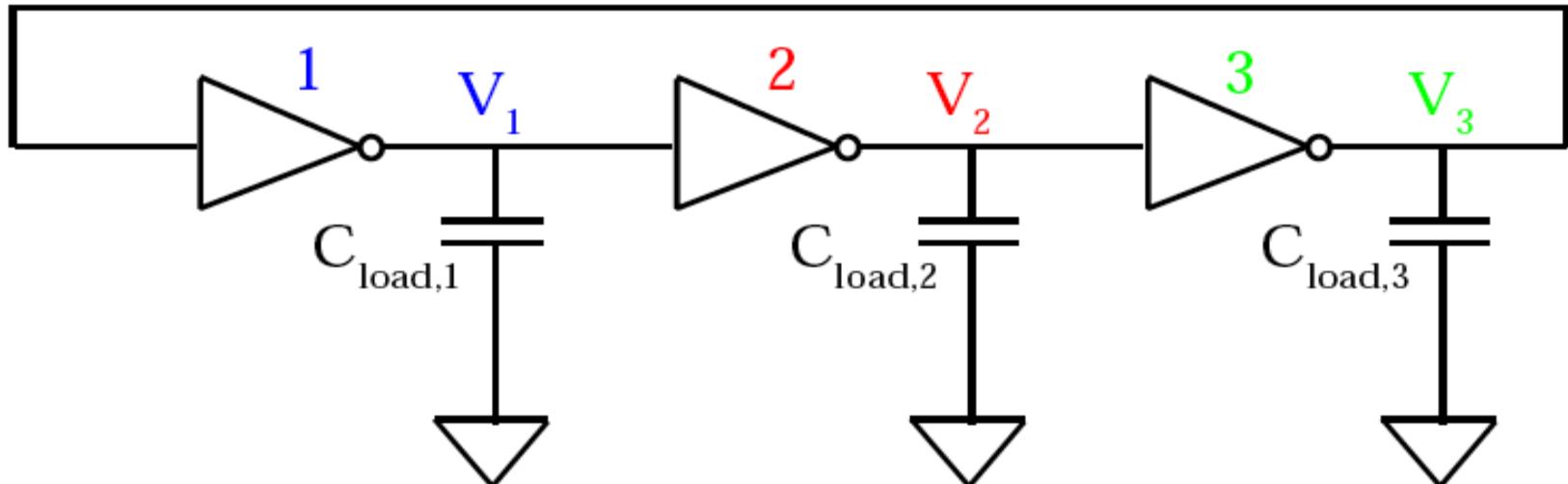

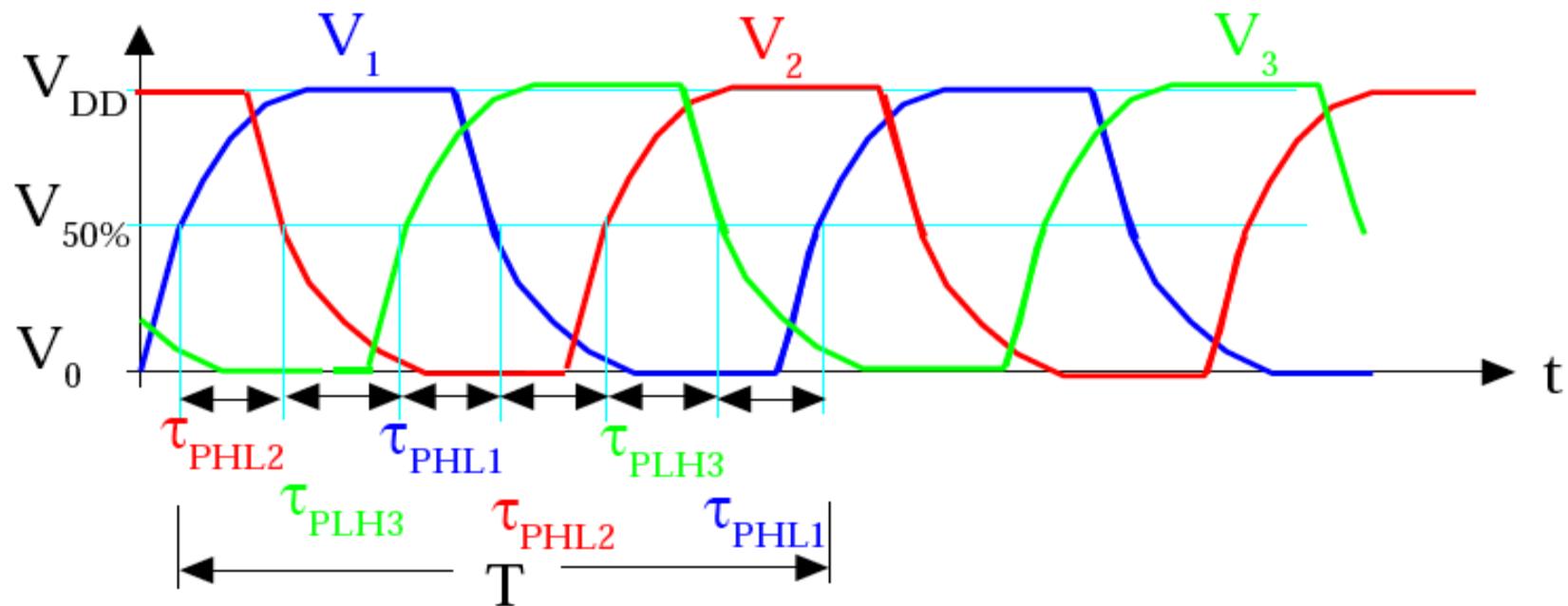$C_{load,1} = C_{load,2} = C_{load,3}$ and $\text{INV1} = \text{INV2} = \text{INV3}$



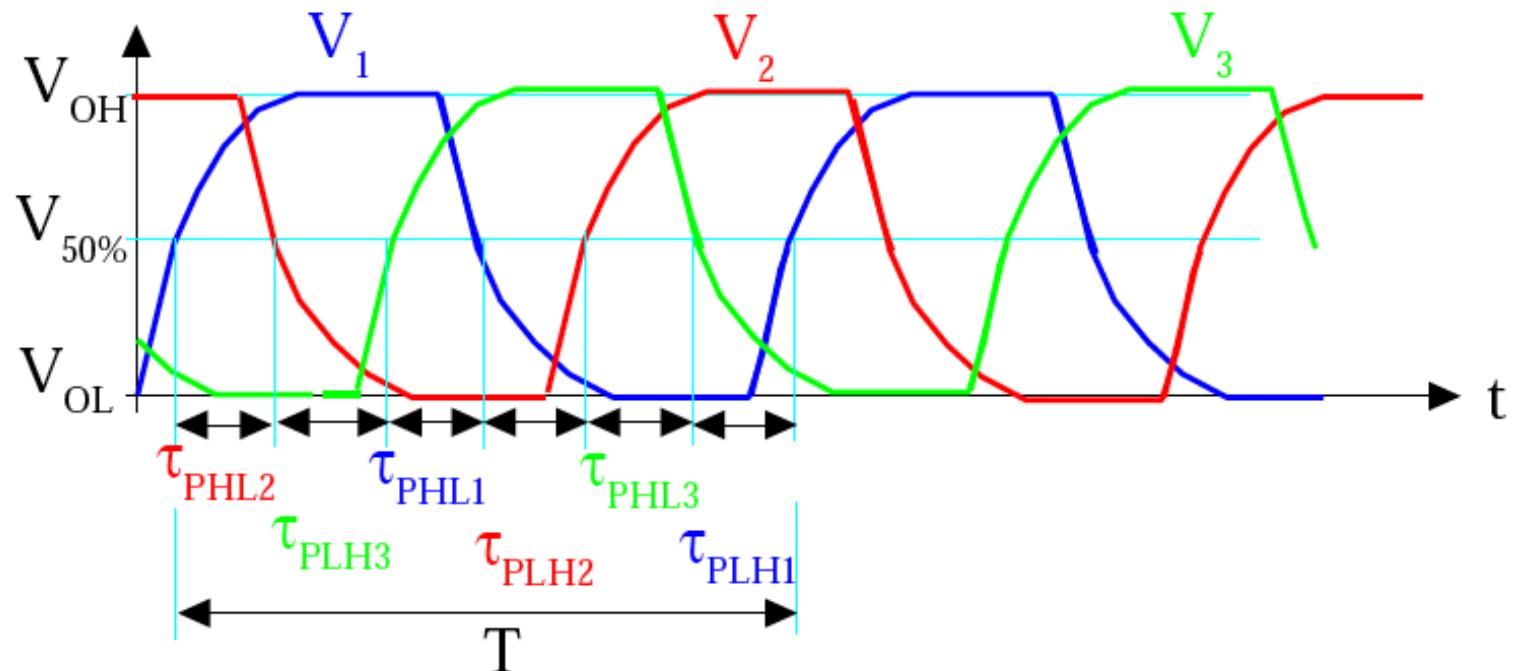

$$C_{\text{load},1} = C_{\text{load},2} = C_{\text{load},3} \quad \text{and} \quad \text{INV1} = \text{INV2} = \text{INV3}$$

$$T = \tau_{\text{PHL2}} + \tau_{\text{PLH3}} + \tau_{\text{PHL1}} + \tau_{\text{PLH2}} + \tau_{\text{PHL3}} + \tau_{\text{PLH1}} = 6\tau_p$$

where $2\tau_p = \tau_{\text{PHL}i} + \tau_{\text{PLH}i}$ for $i = 1, 2, 3$

$$f = \frac{1}{T} = \frac{1}{3 \times 2\tau_p} = \frac{1}{6\tau_p} \quad \text{Oscillation FREQ for 3 INVERTERS}$$


For n INVERTERS:
where $n = \text{odd}$

$$f = \frac{1}{T} = \frac{1}{2n\tau_p} \quad \text{or} \quad \tau_p = \frac{1}{2nf}$$

AMI 0.5 micron process

CIRCUIT PARAMETERS		UNITS	
Inverters	K		
Vinv	1.0	2.04	volts
Vinv	1.5	2.29	volts
Vol (100 uA)	2.0	0.12	volts
Voh (100 uA)	2.0	4.86	volts
Vinv	2.0	2.47	volts
Gain	2.0	-18.26	
Ring Oscillator Freq.			
DIV256 (31-stg,5.0V)		98.75	MHz
D256_WIDE (31-stg,5.0V)		153.47	MHz
Ring Oscillator Power			
DIV256 (31-stg,5.0V)		0.49	uW/MHz/gate
D256_WIDE (31-stg,5.0V)		1.00	uW/MHz/gate

Interconnection Capacitance

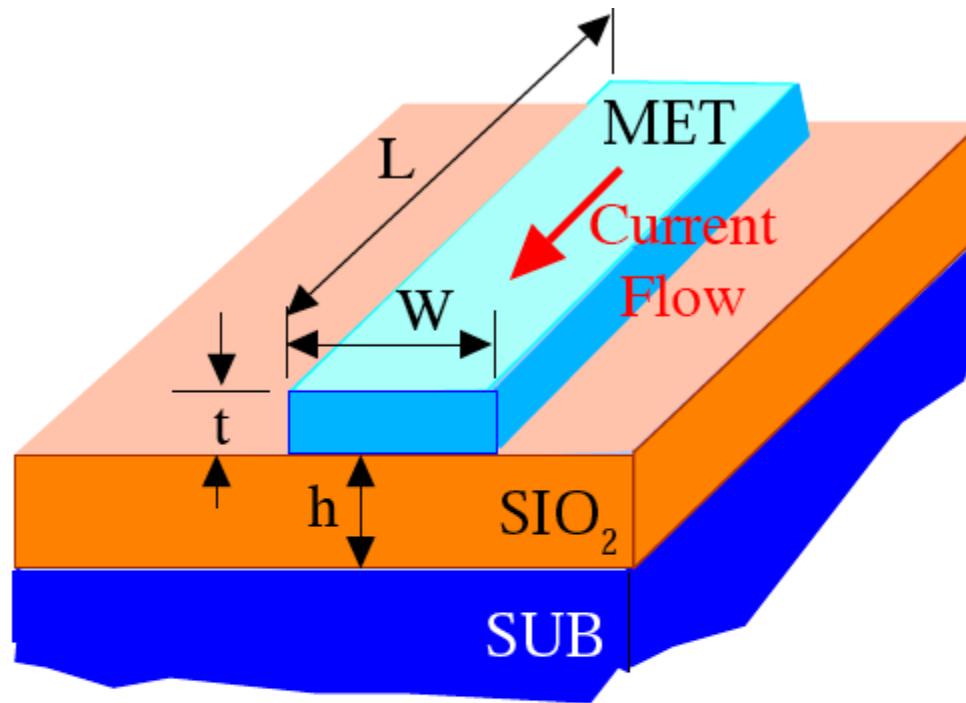


PARASITIC RESISTANCE:

$$R_{\text{metal}} = \rho \frac{L}{Wt} = R_{\text{sheet}} \frac{L}{W}$$

AMI 0.5 micron process


PROCESS PARAMETERS	N+	P+	POLY	PLY2_HR	POLY2	M1	M2	UNITS
Sheet Resistance	84.4	109.2	22.9	1102	41.9	0.09	0.09	ohms/sq
Contact Resistance	60.9	150.6	15.8		26.8		0.81	ohms
Gate Oxide Thickness	142							angstrom

Note: Polysilicon vs. Metal resistance!

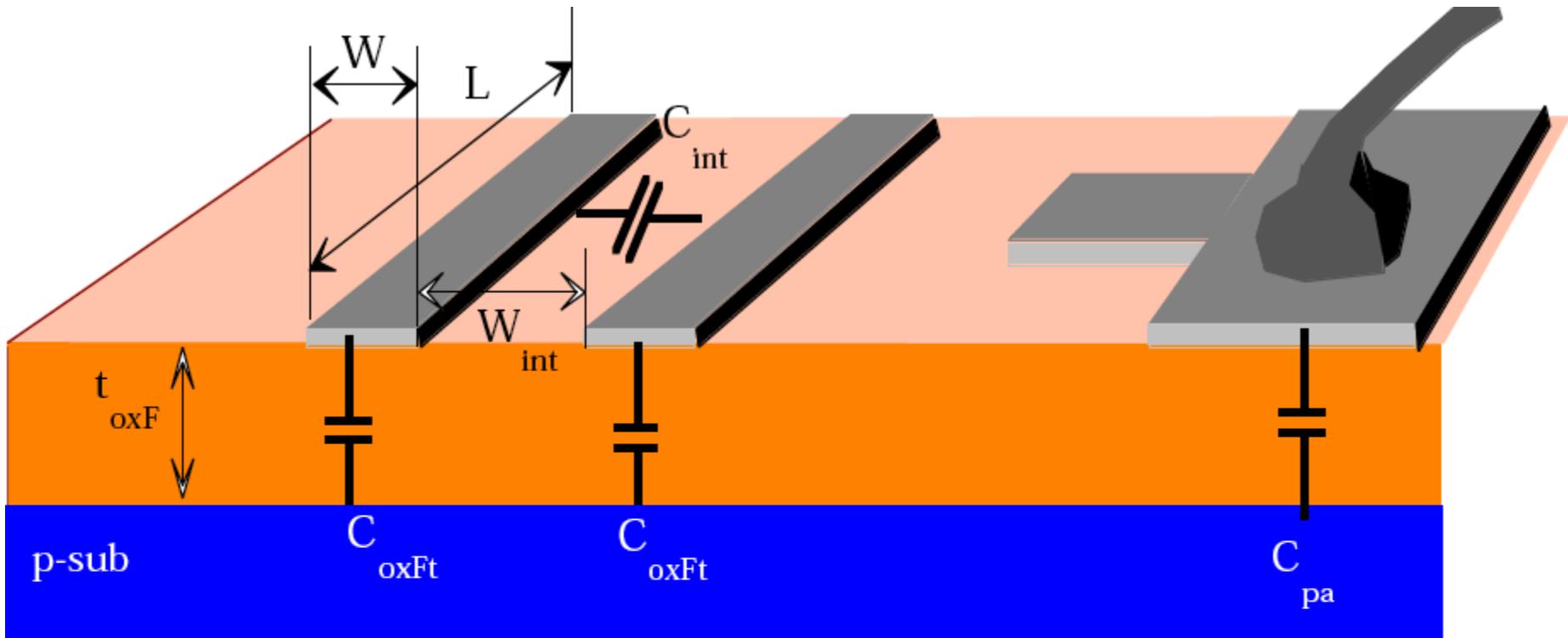



Double-metal double-poly n-well CMOS process

C_{mm}	$C_{\text{metal-to-metal}}$	=	2.5 nF/cm^2
C_{oxm}	$C_{\text{metal-to-substrate}}$	=	5.2 nF/cm^2
C_{oxp}	$C_{\text{poly-to-substrate}}$	=	6.5 nF/cm^2
C_{mp}	$C_{\text{metal-to-poly}}$	=	12.0 nF/cm^2

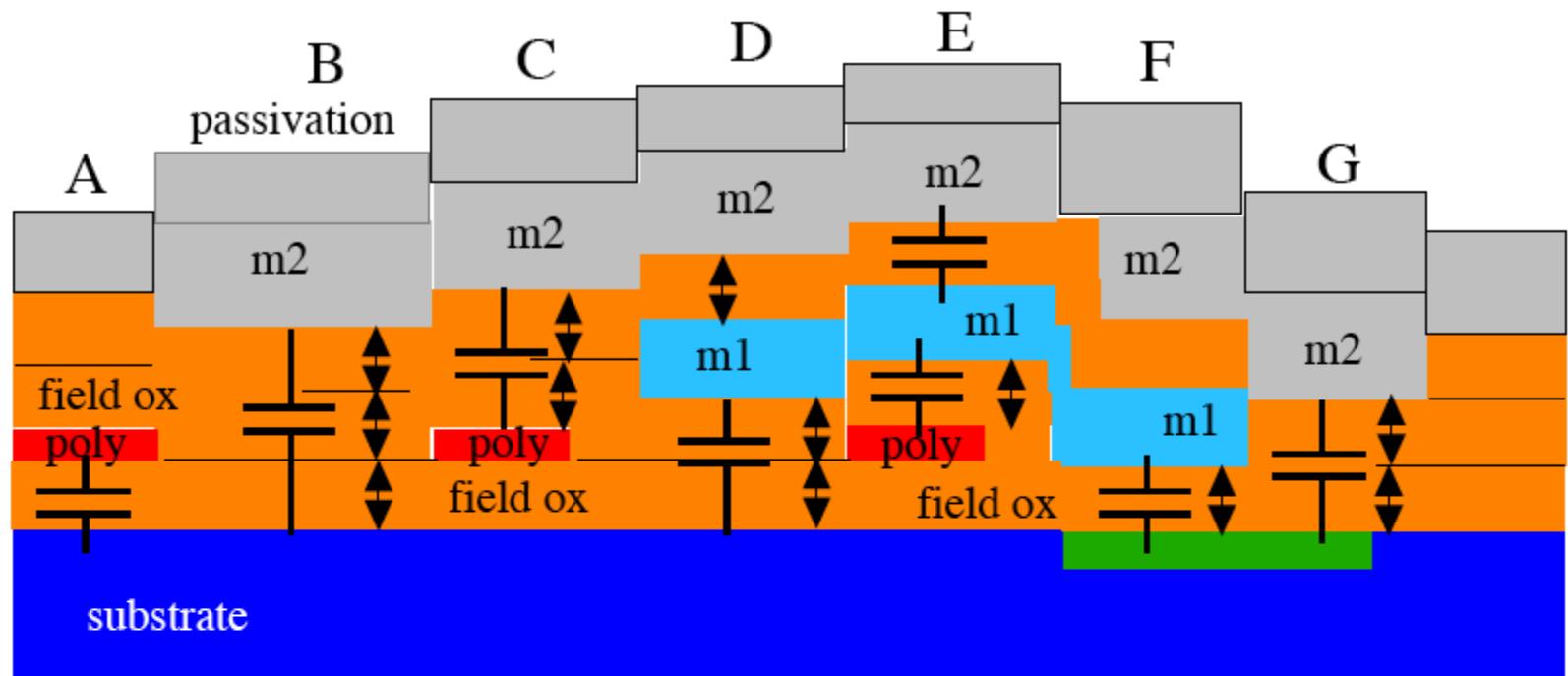


	Layer	Cap	Ox Thickness	Typ Value	
A	Poly-substrate	C_p	3000 Å	50 aF/ μm^2	1 μm CMOS Capacitances
B	Metal2-sub	C_{m2}	9000 Å	20 aF/ μm^2	$t_{\text{ox}} = 200\text{\AA}$
C	Poly-metal2	C_{m2p}	6000 Å	30 aF/ μm^2	$C_g = 1800 \text{ aF}/\mu\text{m}^2$
D	Metal1-sub	C_{m1}	6000 Å	30 aF/ μm^2	$a\text{F} = 10^{-18} \text{ F}$
E	Metal1-poly	C_{mlp}	3000 Å	60 aF/ μm^2	
F	Metal1-metall2	C_{m2m1}	6000 Å	50 aF/ μm^2	
F	Metal1-diffusion	C_{mld}	3000 Å	60 aF/ μm^2	
G	Metal2-diffusion	Passivation	6000 Å	30 aF/ μm^2	

Surface of an IC

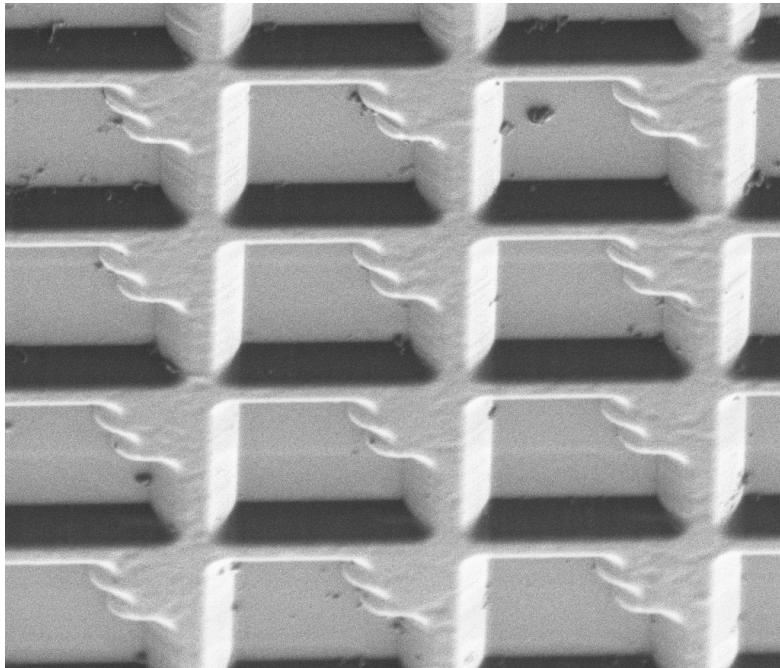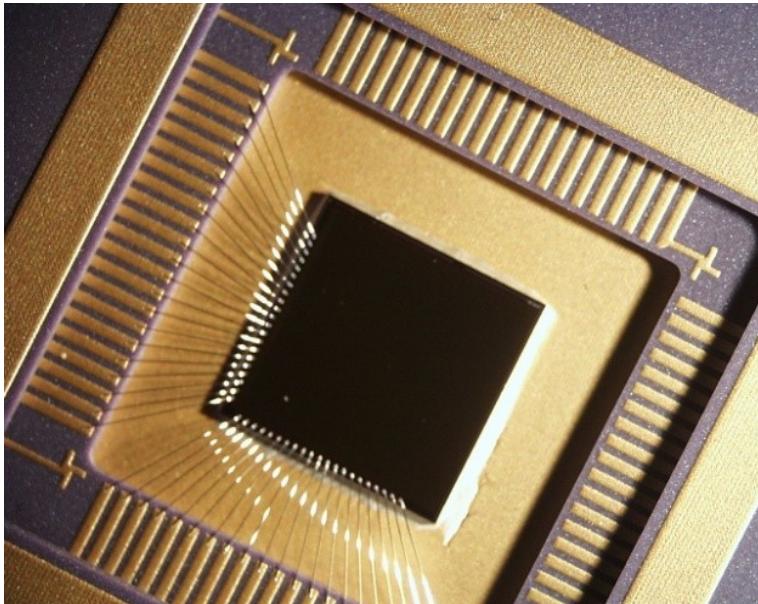

Mag 10.0 kX	Det SED	Tilt 0.0°	pA	I-Beam 30.0 kV	FWD 18.0	10 µm
----------------	------------	--------------	----	-------------------	-------------	-------

fringing fields

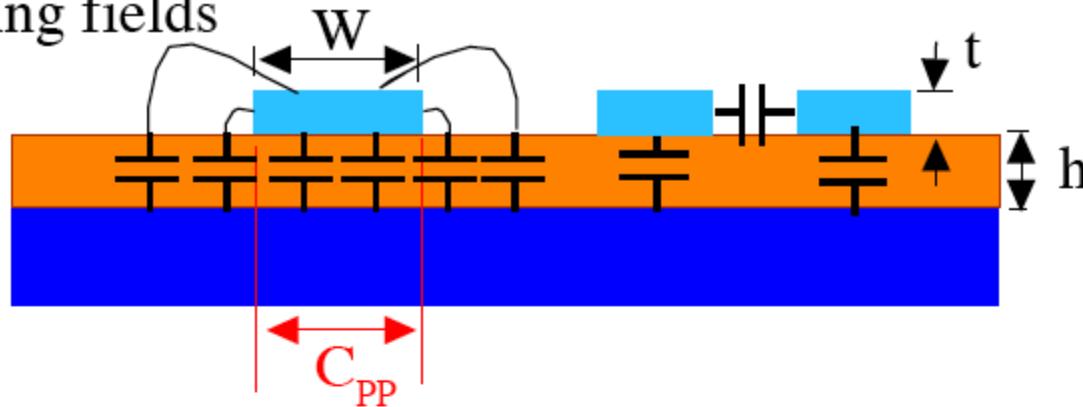

$$FF = C_{\text{total}} / C_{\text{PP}} \rightarrow \text{FRINGING-FIELD FACTOR}$$

FF \rightarrow INC as $t/h \rightarrow$ INC, $W/h <- \text{DEC}$, and $W/L \rightarrow$ INC

(SEE PLOT FF in FIG. 6.18 of TEXT)

$$C_{\text{total}} = \epsilon \left[\frac{W - \frac{t}{2}}{h} + \frac{2\pi}{\ln \left(1 + \frac{2h}{t} + \sqrt{\frac{2h}{t} \left(\frac{2h}{t} + 2 \right)} \right)} \right] \text{ pF}/\mu\text{m L} \quad \text{for } W \geq t/2$$

$$C_{\text{total}} = \epsilon \left[\frac{W}{h} + \frac{\pi \left(1 - 0.0543 \frac{t}{2h} \right)}{\ln \left(1 + \frac{2h}{t} + \sqrt{\frac{2h}{t} \left(\frac{2h}{t} + 2 \right)} \right)} + 1.47 \right] \text{ pF}/\mu\text{m L} \quad \text{for } W < t/2$$

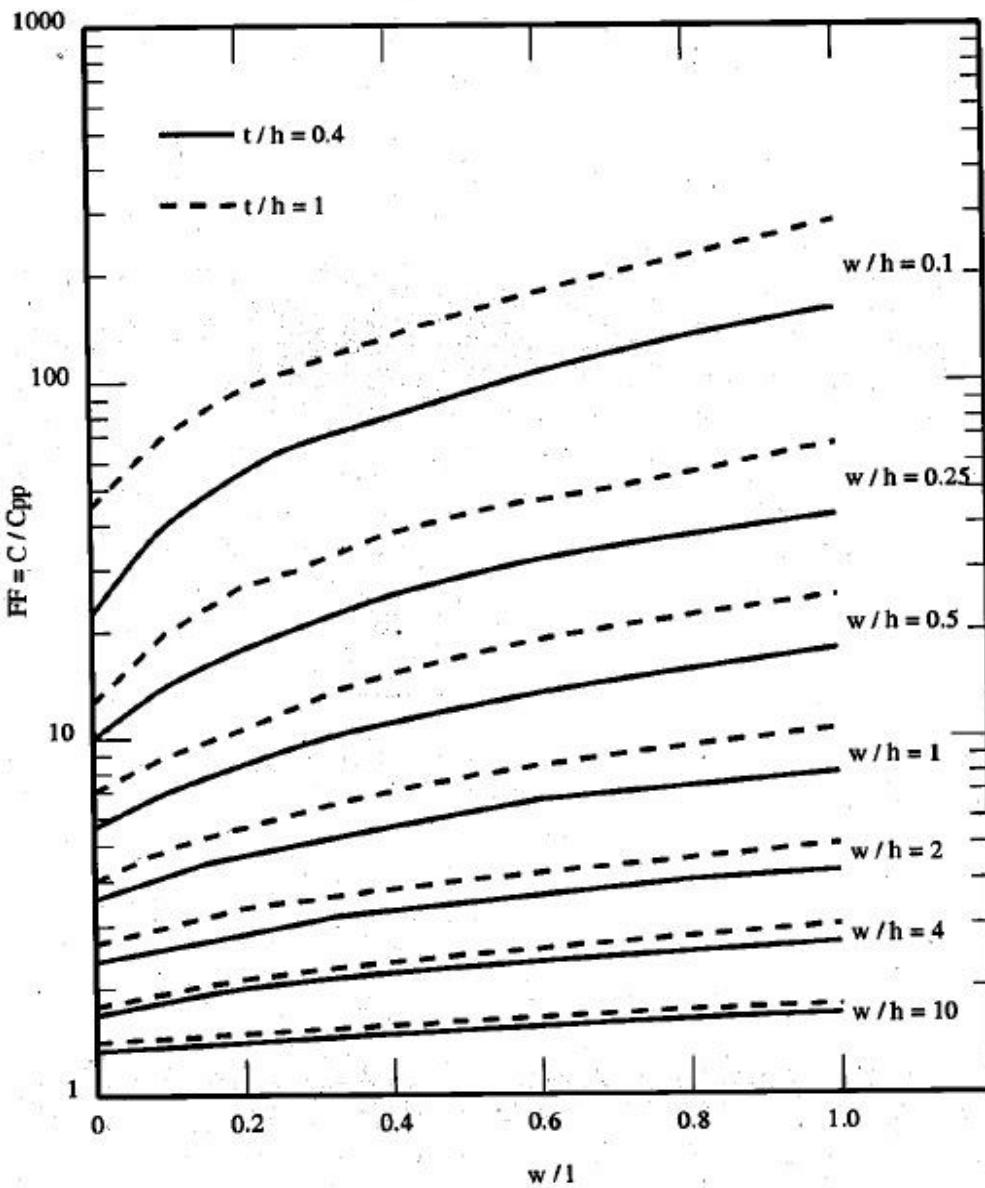



Figure 6.18. Variation of the fringing-field factor with the interconnect geometry.

AMI 0.5 micron process


CAPACITANCE PARAMETERS	N+	P+	POLY	POLY2	M1	M2	M3	N_W	UNITS
Area (substrate)	426	724	85		30	15	9	37	aF/um^2
Area (N+active)			2434		34	17	12		aF/um^2
Area (P+active)			2351						aF/um^2
Area (poly)				899	56	16	9		aF/um^2
Area (poly2)					46				aF/um^2
Area (metal1)						33	13		aF/um^2
Area (metal2)							32		aF/um^2
Fringe (substrate)	361	241			71	49	33		aF/um
Fringe (poly)					59	38	28		aF/um
Fringe (metal1)						46	34		aF/um
Fringe (metal2)							54		aF/um
Overlap (N+active)			292						aF/um
Overlap (P+active)			387						aF/um

Interconnection Delays in Sub-micron process

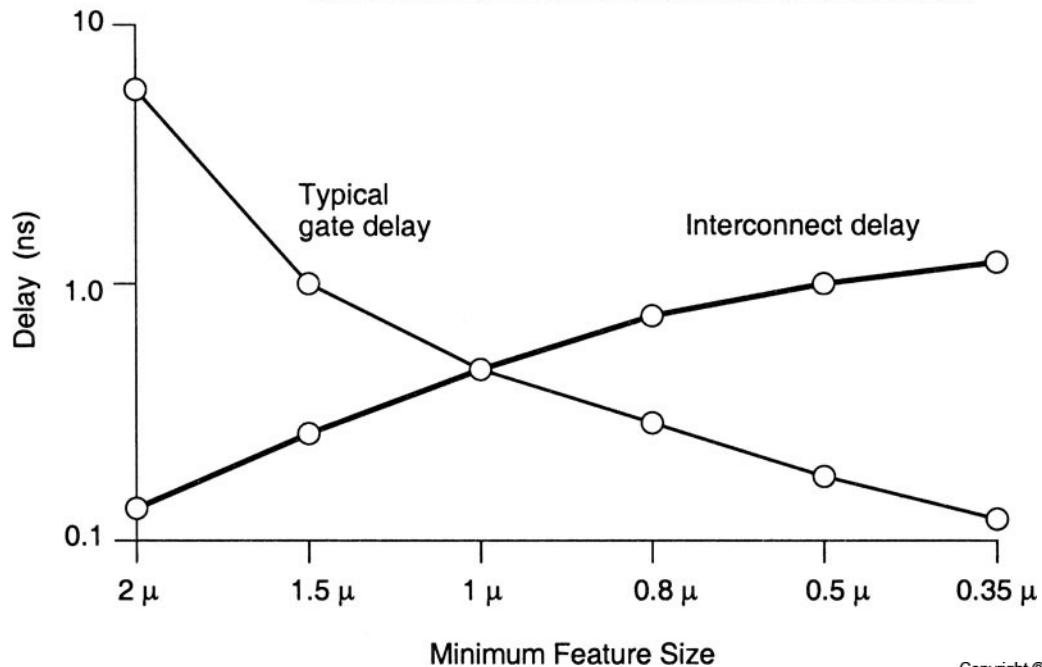Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



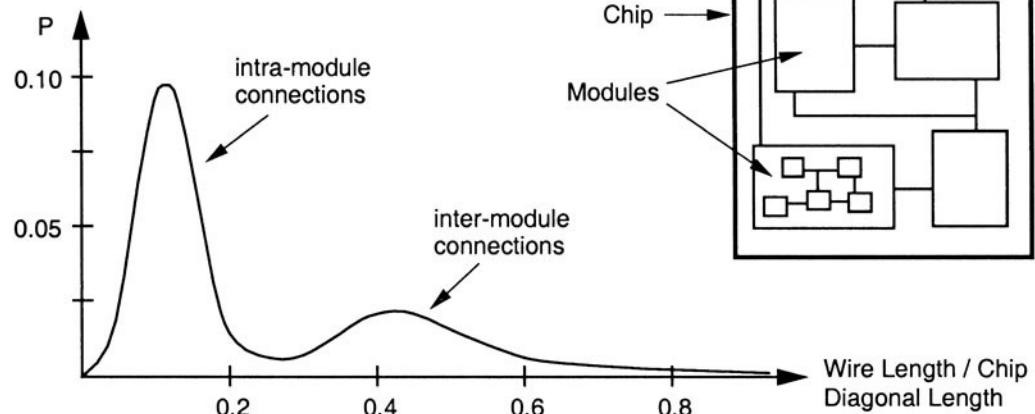Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Examples of Propagation Delay

Product	CMOS technology generation	Clock frequency, f	Fan-out=4 inverter delay
Pentium II	0.25 μm	600 MHz	\sim 100 ps
Pentium III	0.18 μm	1.8 GHz	\sim 40 ps
Pentium IV	0.13 μm	3.2 GHz	\sim 20 ps

Typical clock periods:

- high-performance μP : \sim 15 FO4 delays
- PlayStation 2: 60 FO4 delays



POWER DISSIPATION

P_s = Static power dissipation due to leakage current or other current drawn continuously from the power supply.

P_d = dynamic power dissipation due to charging and discharging load capacitances (v_{in} assumed to be square-like)

P_{sc} = short circuit power dissipation due to charging and discharging load capacitances during the finite rise and fall times of v_{in} .


DYNAMIC POWER DISSIPATION

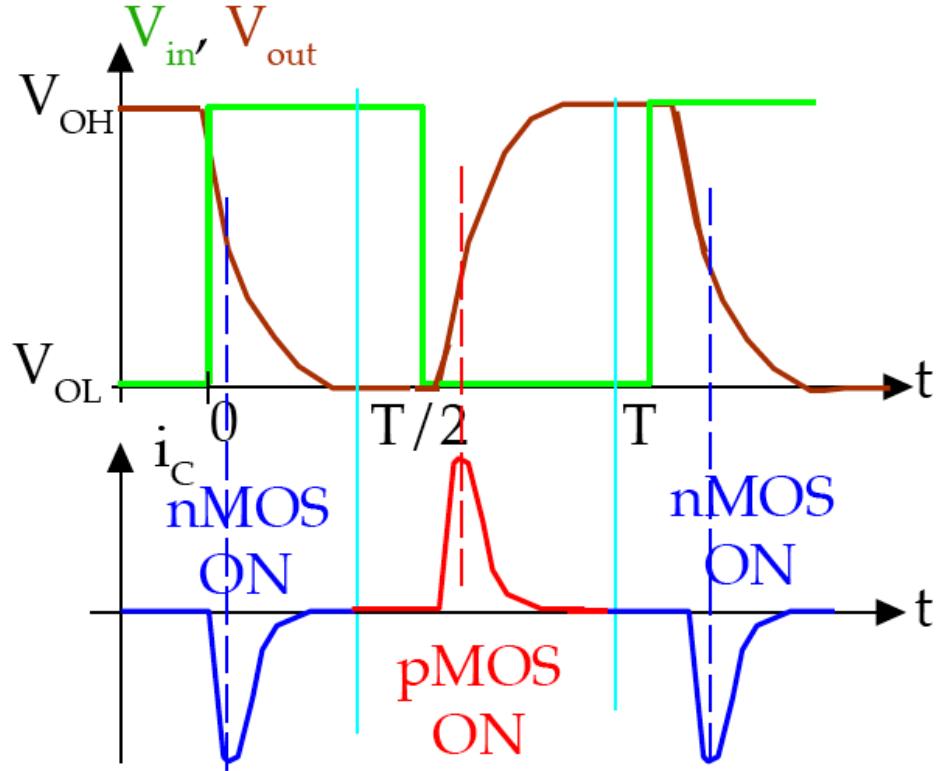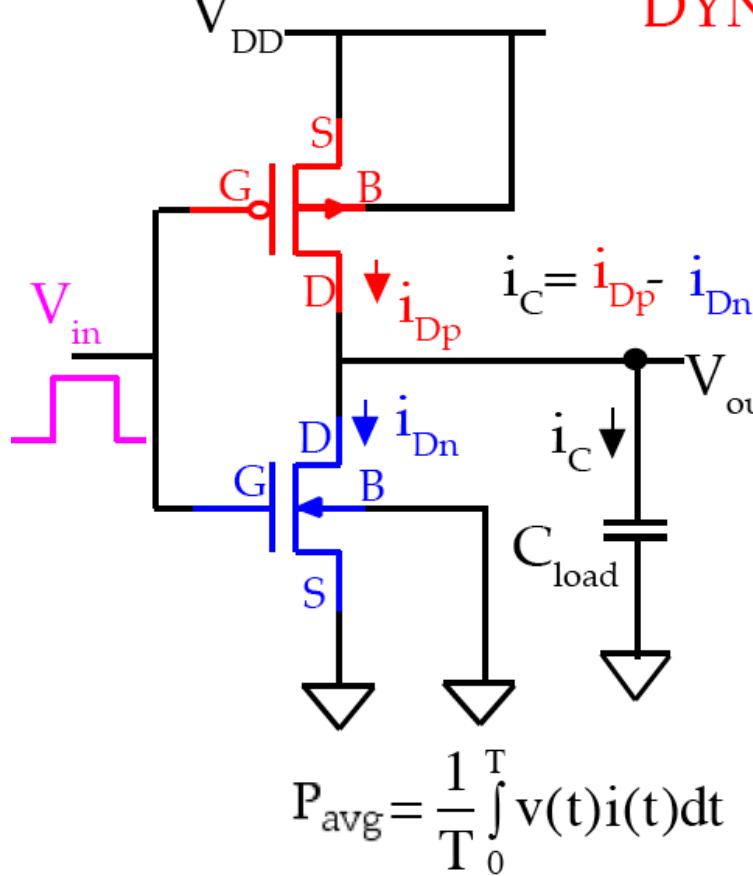

$$P_{avg} = \frac{1}{T} \int_0^{T/2} V_{out}(t)i_{Dn}(t)dt + \frac{1}{T} \int_{T/2}^T (V_{DD} - V_{out}(t))i_{Dp}(t)dt$$

where $i_{Dn}(t) = -C_{load} \frac{dV_{out}}{dt}$ $i_{Dp}(t) = C_{load} \frac{dV_{out}}{dt}$
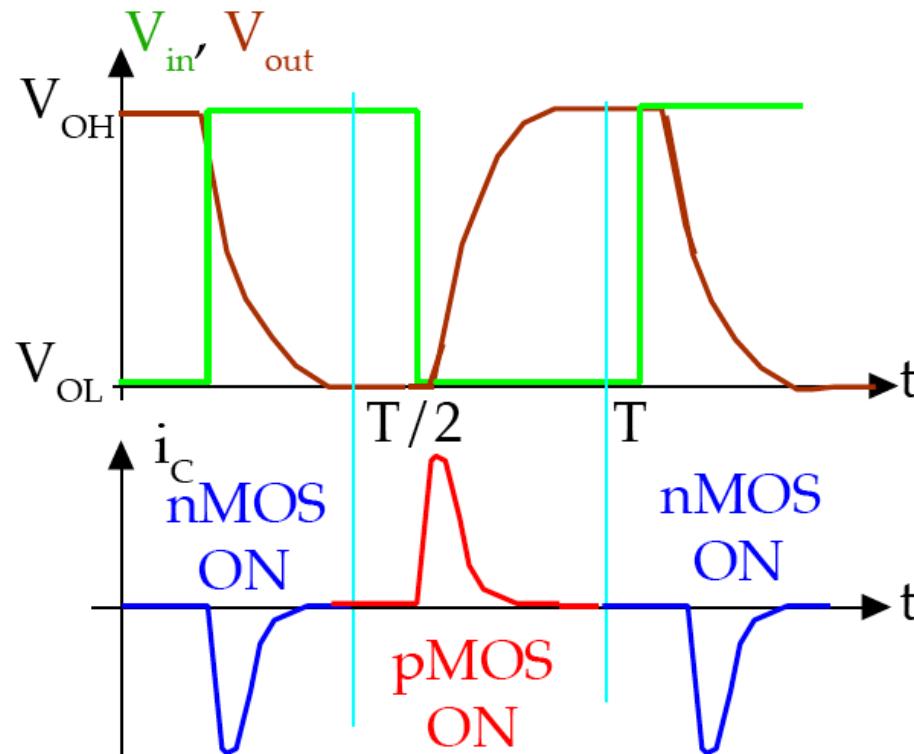
$$P_{avg} = \frac{1}{T} \int_0^{T/2} V_{out}(t) \left(-C_{load} \frac{dV_{out}}{dt} \right) dt + \frac{1}{T} \int_{T/2}^T (V_{DD} - V_{out}(t)) \left(C_{load} \frac{dV_{out}}{dt} \right) dt$$




$$\begin{aligned} P_{avg} &= \frac{1}{T} \int_{V_{DD}}^0 -C_{load} V_{out}(t) dV_{out} + \frac{1}{T} \int_0^{V_{DD}} C_{load} (V_{DD} - V_{out}(t)) dV_{out} \\ &= \frac{1}{T} \left[-C_{load} \frac{V_{out}^2}{2} \Big|_{V_{out}=0}^{V_{out}=V_{DD}} + C_{load} \left(V_{DD} V_{out} - \frac{V_{out}^2}{2} \right) \Big|_{V_{out}=0}^{V_{out}=V_{DD}} \right] \end{aligned}$$

$$P_{avg} = \frac{1}{T} \left[-C_{load} \frac{V_{out}^2}{2} \Big|_{V_{out}=0}^{V_{out}=V_{DD}} + C_{load} \left(V_{DD} V_{out} - \frac{V_{out}^2}{2} \right) \Big|_{V_{out}=0}^{V_{out}=V_{DD}} \right]$$



$$= \frac{1}{T} C_{load} V_{DD}^2$$

P_{avg} = C_{load} V_{DD}² f

APPLIES TO GENERAL CMOS LOGIC CIRCUITS

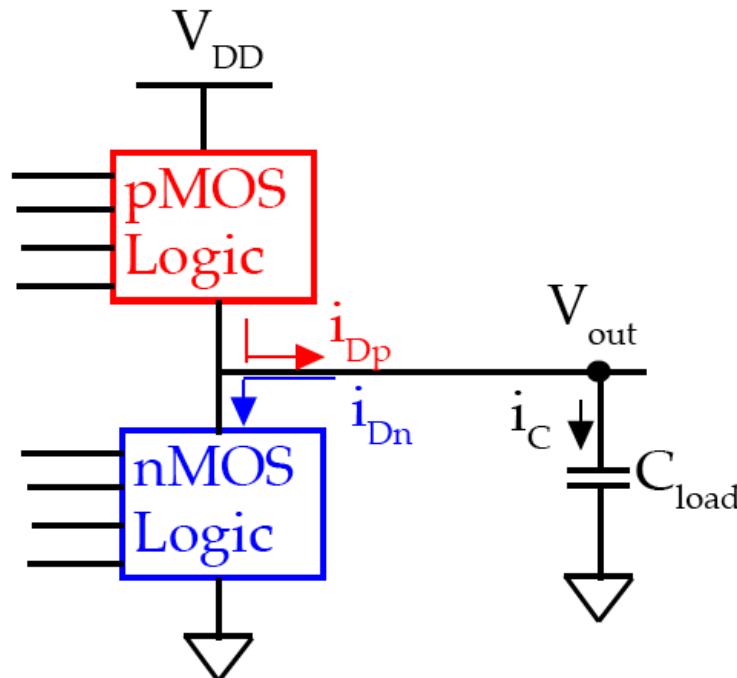


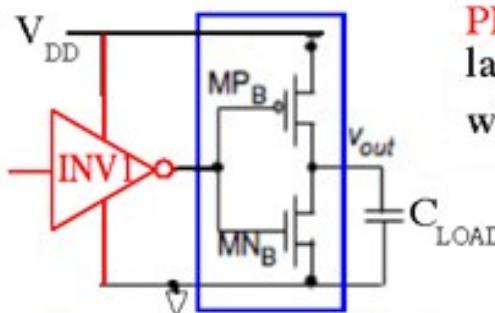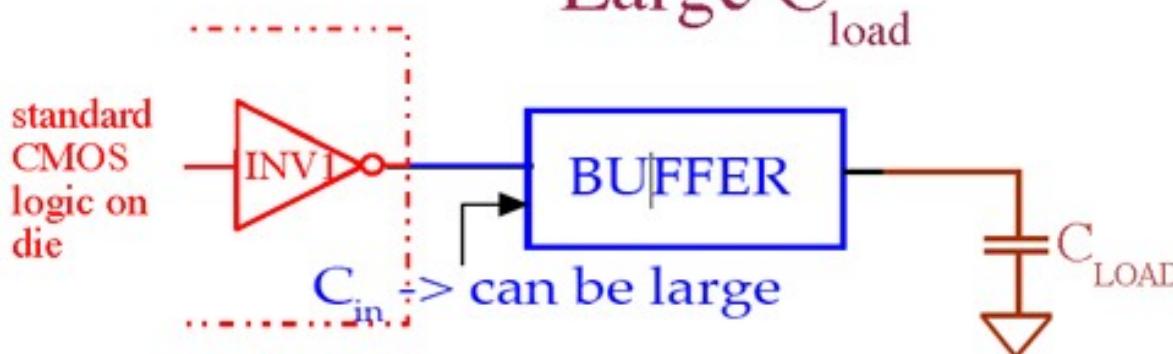Cascade of N Inverters or Super-Buffer to Drive Large C_{load}




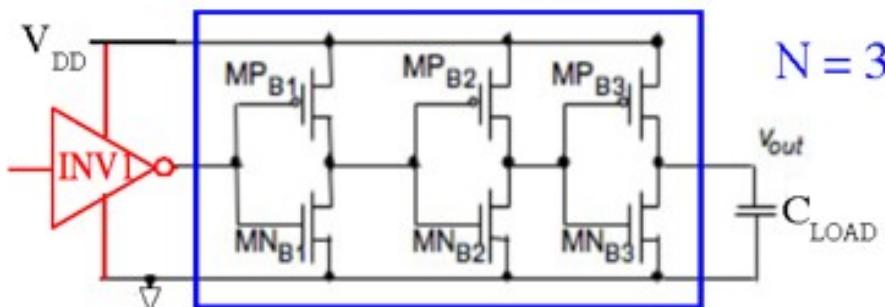PROBLEM: A minimum sized inverter drives a large load C_{LOAD} , leading to excessive delay, even with a large buffer (large W/L).

SOLUTION: Insert N inverter stages in cascade with increasing W/L between INV1 and load C_{LOAD} . The total delay through N stages will be less than the delay through a single stage driving C_{LOAD} .



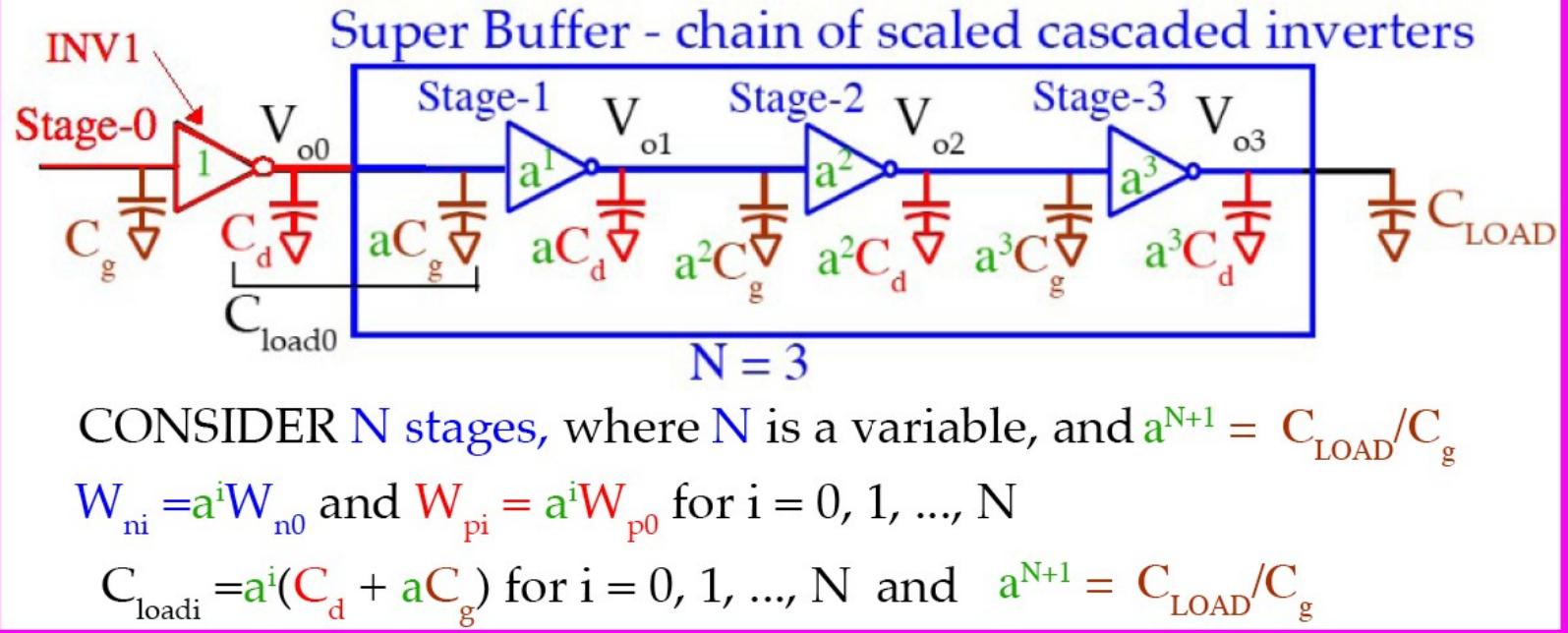Cascade of N Inverters or Super-Buffer to Drive Large C_{load} cont.



NOTE: ALL inverters have the same delay

$$t_d = \frac{\tau_0}{a^i} \frac{a^i (C_d + aC_g)}{C_d + C_g} = \tau_0 \frac{C_d + aC_g}{C_d + C_g} \quad \text{where } i = 1, \dots, N; \tau_0 \text{ is the gate delay for INV1 in a ring oscillator with load } C_d + C_g$$

$$t_{total} = (N+1) \cdot t_d = (N+1) \cdot \tau_0 \frac{C_d + aC_g}{C_d + C_g} \quad \text{Choose } N \text{ and } a \text{ to minimize } t_{total}$$

$$\text{where } a^{N+1} = C_{LOAD}/C_g \quad \& \quad N+1 = \frac{\ln(C_{LOAD}/C_g)}{\ln(a)}$$

Cascade of N Inverters or Super-Buffer to Drive Large C_{load} cont.

$$\left. \begin{aligned} t_{\text{total}} &= (N+1)\tau_0 \frac{C_d + aC_g}{C_d + C_g} \\ N+1 &= \frac{\ln(C_{\text{LOAD}}/C_g)}{\ln(a)} \end{aligned} \right] \Rightarrow t_{\text{total}} = \frac{\ln(C_{\text{LOAD}}/C_g)}{\ln(a)} \tau_0 \frac{C_d + aC_g}{C_d + C_g}$$

$W_{ni} = a^i W_{n0}$ and $W_{pi} = a^i W_{p0}$

TO MINIMIZE t_{total} :

$$\frac{dt_{\text{total}}}{da} = \tau_0 \ln\left(\frac{C_{\text{LOAD}}}{C_g}\right) \left[-\frac{1/a}{(\ln(a))^2} \left(\frac{C_d + aC_g}{C_d + C_g} \right) + \frac{1}{\ln(a)} \left(\frac{C_g}{C_d + C_g} \right) \right] = 0$$

$$a_{\text{opt}} \left[\ln(a_{\text{opt}}) - 1 \right] = \frac{C_d}{C_g} = 0$$

$a_{opt} \geq e = 2.718$

For the SPECIAL CASE $C_d = 0 \Rightarrow \ln(a_{\text{opt}}) = 1$ or $a_{\text{opt}} = e^1 = 2.718$


Since $C_d > C_g$, $C_d = 0$ is only an academic special case.

Cascade of N Inverters or Super-Buffer to Drive Large C_{load} cont.

EXAMPLE: Design a Buffer using a scaled cascade of inverters to achieve minimum total delay t_{total} when $C_{LOAD} = 100 C_g$. Consider the case where $C_d = 2C_g$.

$$C_d = 2C_g \Rightarrow \text{plot } a_{opt} \text{ as function of } C_d/C_g : a_{opt} = 4.35 \Rightarrow \ln(a_{opt}) = 1.47$$

Plot using Excel, MathCad, MatLab.

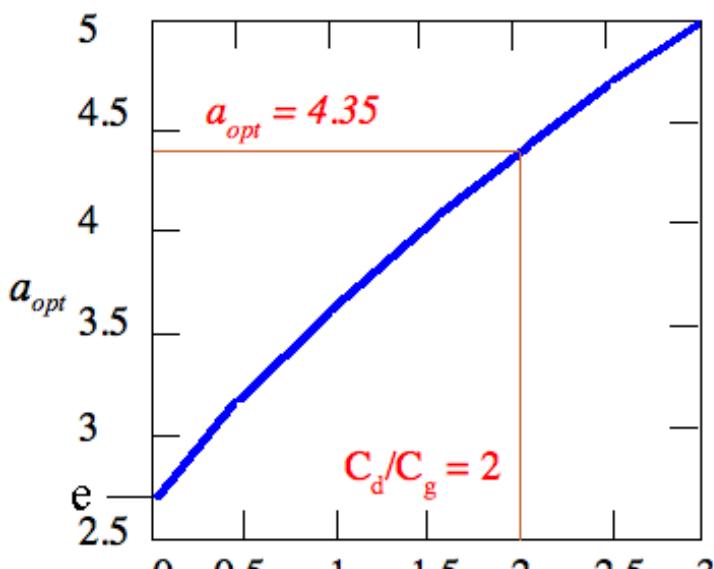

$$\frac{C_d}{C_g} = a_{opt} \cdot (\ln a_{opt} - 1)$$

$$N+1 = \frac{\ln(C_{LOAD}/C_g)}{\ln(a_{opt})}$$

$$\Rightarrow N = \frac{\ln(C_{LOAD}/C_g)}{1.47} - 1 = 2.13 \rightarrow N = 3$$

$$e^{3.13+1.47} = 100 \leq \frac{C_{LOAD}}{C_g} \leq e^{4+1.47} = 365$$

i	W_{ni}/W_{n0}	W_{pi}/W_{p0}
1	$(a_{opt})^1 = 4.35$	$(a_{opt})^1 = 4.35$
2	$(a_{opt})^2 = 18.92$	$(a_{opt})^2 = 18.92$
3	$(a_{opt})^3 = 82.31$	$(a_{opt})^3 = 82.31$

3rd stage can be eliminated with little impact.