

C
S
D
A
2/e

Appendix A: Digital Logic

By Miles Murdocca
Internet Institute USA

Chapter Contents

A.1 Combinational Logic

A.2 Truth Tables

A.3 Logic Gates

A.4 Boolean Algebra

A.5 SOP Forms, Logic Diagrams

A.6 POS Forms

A.7 Positive and Negative Logic

A.8 The Data Sheet

A.9 Digital Components

A.10 Simplification of Exprs.

A.11 Speed and Performance

A.12 Sequential Logic

A.13 JK and T Flip Flops

A.14 Design of Finite State

Machines

A.15 Mealy and Moore Machines

A.16 Registers

A.17 Counters

C

S

D

A

2/e

Some Definitions

- Combinational logic: a digital logic circuit in which logical decisions are made based only on combinations of the inputs. e.g. an adder.
- Sequential logic: a circuit in which decisions are made based on combinations of the current inputs as well as the past history of inputs. e.g. a memory unit.
- Finite state machine: a circuit which has an internal state, and whose outputs are functions of both current inputs and its internal state. e.g. a vending machine controller.

C

S

D

A

2/e

The Combinational Logic Unit

- translates a set of inputs into a set of outputs according to one or more mapping functions.
- Inputs and outputs for a CLU normally have two distinct (binary) values: high and low, 1 and 0, 0 and 1, or 5 v. and 0 v. for example.
- The outputs of a CLU are strictly functions of the inputs, and the outputs are updated immediately after the inputs change. A set of inputs $i_0 - i_n$ are presented to the CLU, which produces a set of outputs according to mapping functions $f_0 - f_m$

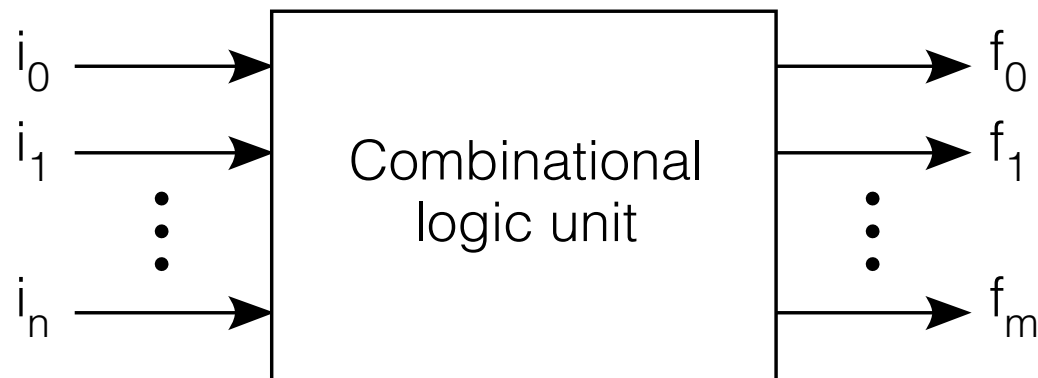


Fig A.1

C

S

D

A

2/e

Truth Tables


Developed in 1854 by George Boole

further developed by Claude Shannon (Bell Labs)

- Outputs are computed for all possible input combinations (how many input combinations are there?)

Consider a room with two light switches. How must they work†?

Fig. A.2

 

Inputs		Output
A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

†Don't show this to your electrician, or wire your house this way. This circuit definitely violates the electric code. The practical circuit never leaves the lines to the light "hot" when the light is turned off. Can you figure how?

Truth Tables Showing All Possible Functions of Two Binary Variables

<i>A</i>	<i>B</i>	<i>False</i>	<i>AND</i>	$\overline{A\overline{B}}$	<i>A</i>	$\overline{A}B$	<i>B</i>	<i>XOR</i>	<i>OR</i>
0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

<i>A</i>	<i>B</i>	<i>NOR</i>	<i>XNOR</i>	\overline{B}	$A + \overline{B}$	\overline{A}	$\overline{A} + B$	<i>NAND</i>	<i>True</i>
0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

- The more frequently used functions have names: AND, XOR, OR, NOR, XNOR, and NAND. (Always use upper case spelling.)

C

S


D

A

2/e

Logic Gates and Their Symbols

Fig. A.5 Logic symbols for AND, OR, buffer, and NOT Boolean functions

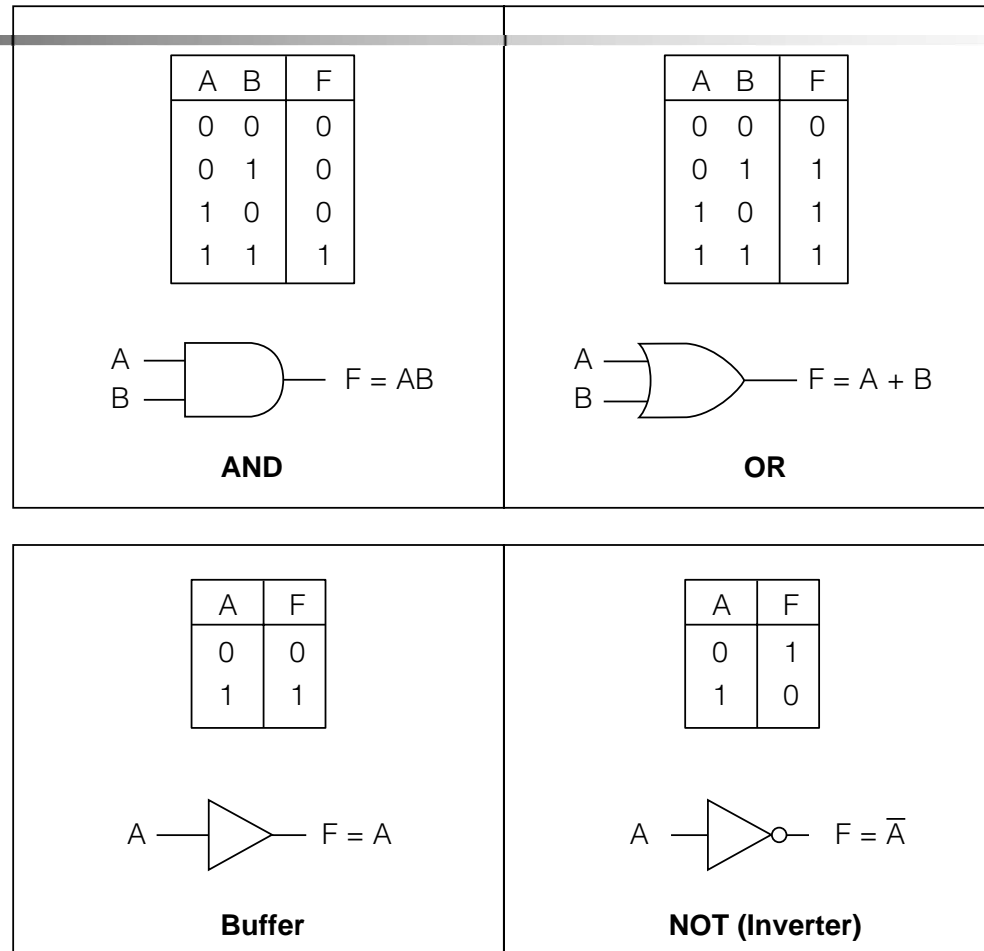

- Note the use of the “inversion bubble.”
- (Be careful about the “nose” of the gate when drawing AND vs. OR.)

C

S


D

A


2/e

Logic symbols for NAND, NOR, XOR, and XNOR Boolean functions

Fig A.6

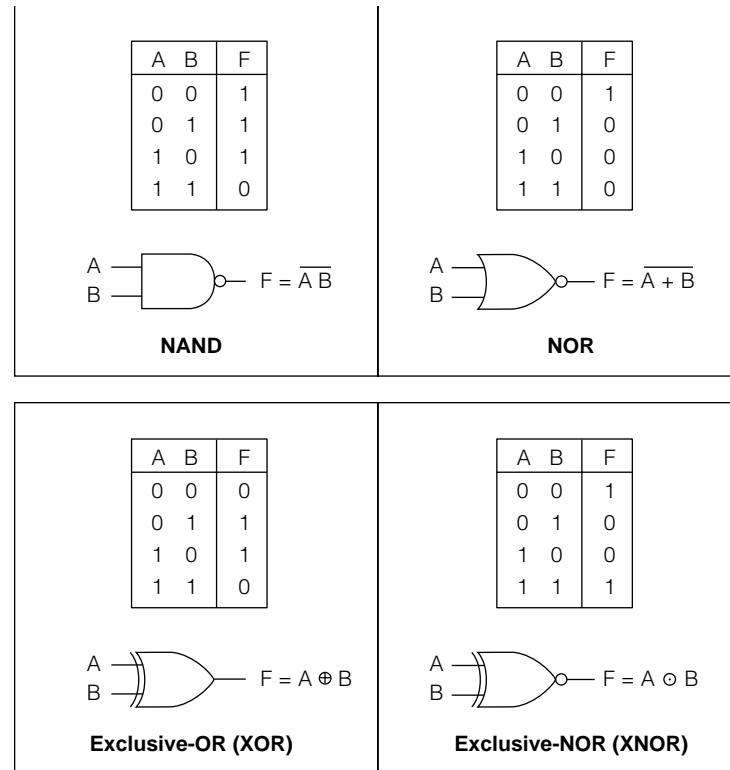


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

 


NOR

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

 


Exclusive-OR (XOR)

A	B	F
0	0	1
0	1	0
1	0	0
1	1	1

 


Exclusive-NOR (XNOR)


Fig A. 7 Variations of Basic Logic Gate Symbols

 

(a)

 

(b)

 


(c)

a) 3 inputs

b) A Negated Input


c) Complementary Outputs

Fig A.8 The Inverter at the Transistor Level

 


(a)

**Power
Terminals**

 


(b)

**Transistor
Symbol**

 

(c)

**A Transistor Used
as an Inverter**

 

(d)

**Inverter Transfer
Function**

C


S

D


A

2/e

Fig A.9 Allowable Voltages in Transistor-Transistor-Logic (TTL)

 


(a)

 


(b)

 A.10 Transistor-Level Circuits For 2-Input a) NAND and b) NOR Gates



(a)

 


(b)

Tbl A.1 The Basic Properties of Boolean Algebra

Principle of duality: The dual of a Boolean function is gotten by replacing AND with OR and OR with AND, constant 1s by 0s, and 0s by 1s

Relationship	Dual	Property
$A B = B A$	$A + B = B + A$	Commutative
$A (B + C) = A B + A C$	$A + B C = (A + B) (A + C)$	Distributive
$1 A = A$	$0 + A = A$	Identity
$A \bar{A} = 0$	$A + \bar{A} = 1$	Inverse
$0 A = 0$	$1 + A = 1$	Null
$A A = A$	$A + A = A$	Idempotence
$A (B C) = (A B) C$	$A + (B + C) = (A + B) + C$	Associative
$\overline{\bar{A}} = A$		Complement
$\overline{A B} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A} \bar{B}$	DeMorgan's Theorem
$AB + \bar{A}C + BC = AB + \bar{A}C$	$(A + B)(\bar{A} + C)(B + C) = (A + B)(\bar{A} + C)$	Consensus Theorem

Postulates

 

Theorems

A, B, etc. are Literals; 0 and 1 are constants.

C

S

D


A

2/e

A.11 and A. 12 DeMorgan's Theorem

A B	$\overline{A B} = \overline{A} + \overline{B}$	$\overline{A + B} = \overline{A} \overline{B}$
0 0	1 1	1 1
0 1	1 1	0 0
1 0	1 1	0 0
1 1	0 0	0 0

 DeMorgan's theorem: $A + B = \overline{\overline{A + B}} = \overline{\overline{A} \overline{B}}$



Discuss: Applying DeMorgan's theorem by “pushing the bubbles,” and “bubble tricks.”

C

S

D


A

2/e

The Sum-of-Products (SOP) Form

Fig. A.14—Truth Table for The Majority Function

Minterm Index	A	B	C	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

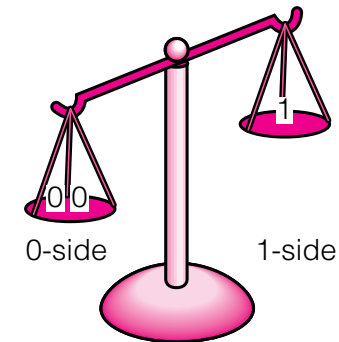

A balance tips to the left or right depending on whether there are more 0's or 1's.

- transform the function into a two-level AND-OR equation
- implement the function with an arrangement of logic gates from the set {AND, OR, NOT}
- M is true when $A=0, B=1, \text{ and } C=1$, or when $A=1, B=0, \text{ and } C=1$, and so on for the remaining cases.
- Represent logic equations by using the sum-of-products (SOP) form

C

S

D

A

2/e


The SOP Form of the Majority Gate

- The SOP form for the 3-input majority gate is:

- $$M = \bar{A}BC + A\bar{B}C + ABC\bar{C} + ABC = m_3 + m_5 + m_6 + m_7 = \sum (3, 5, 6, 7)$$

- Each of the 2^n terms are called minterms, running from 0 to $2^n - 1$
- Note the relationship between minterm number and boolean value.
- Discuss: common-sense interpretation of equation.

Fig A.15 A 2-Level AND-OR Circuit that Implements the Majority Function

 

Discuss: What is the Gate Count?

C


S

D


A

2/e


Fig A.16 Notation Used at Circuit Intersections

 


Connection

 

No connection

 


Connection

 

No connection

Fig A.17 A 2-Level OR-AND Circuit that Implements the Majority Function

 

C
S
D
A
2/e

Positive vs. Negative Logic

- Positive logic: truth, or assertion is represented by logic 1, higher voltage; falsity, de- or unassertion, logic 0, is represented by lower voltage.
- Negative logic: truth, or assertion is represented by logic 0, lower voltage; falsity, de- or unassertion, logic 1, is represented by higher voltage

Gate Logic: Positive vs. Negative Logic

Normal Convention: Positive Logic/Active High
 Low Voltage = 0; High Voltage = 1

Alternative Convention sometimes used: Negative Logic/Active Low

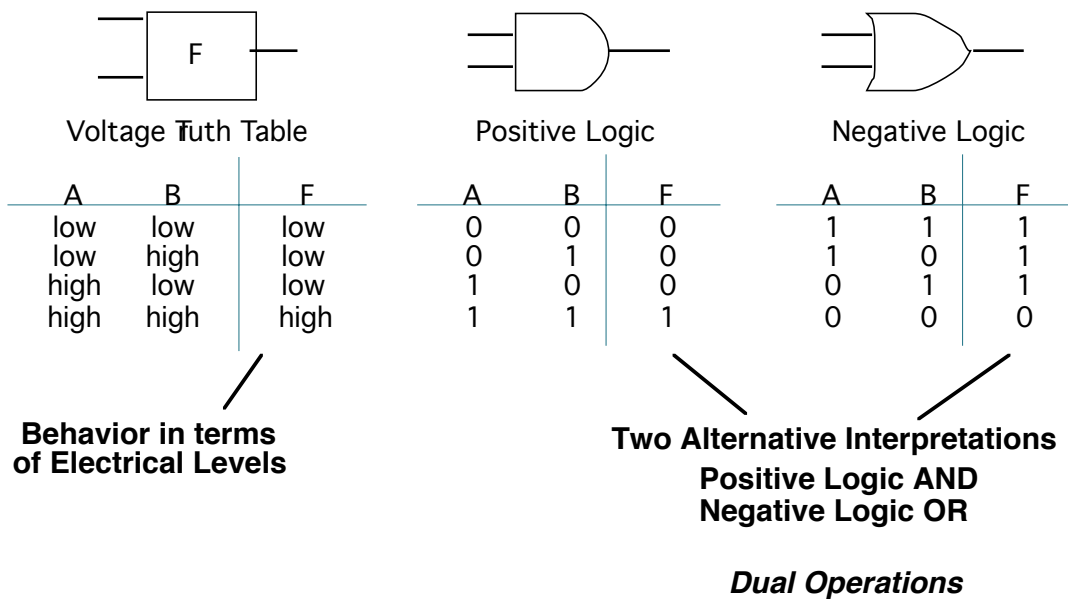


Fig A.18 Positive and Negative Logic (Cont'd.)


Voltage levels

A	B	F
low	low	low
low	high	low
high	low	low
high	high	high




Positive logic levels

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

 


Negative logic levels

A	B	F
1	1	1
1	0	1
0	1	1
0	0	0

 


Voltage levels

A	B	F
low	low	high
low	high	high
high	low	high
high	high	low

 


Positive logic levels

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

 

Negative logic levels

A	B	F
1	1	0
1	0	0
0	1	0
0	0	1

 

C

S

D


A

2/e


Bubble Matching

- Active low signals are signified by a prime or overbar or /.
- Active high: enable _____
- Active low: enable', enable, enable/
- Discuss microwave oven control:
- Active high: Heat = DoorClosed • Start
- Active low: ? (hint: begin with AND gate as before.)


Fig. A.19 Bubble Matching (Cont'd.)

 


(a)

 

(b)

 

(c)

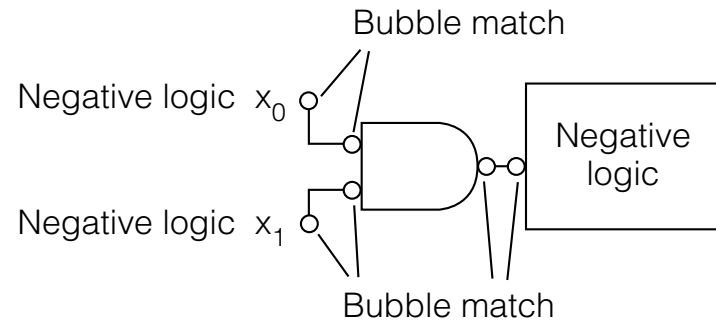

(d)

C

S

D

A

2/e

Digital Components

- High level digital circuit designs are normally made using collections of logic gates referred to as components, rather than using individual logic gates. The majority function can be viewed as a component.
- Levels of integration (numbers of gates) in an integrated circuit (IC):
 - small scale integration (SSI): 10-100 gates.
 - medium scale integration (MSI): 100 to 1000 gates.
 - Large scale integration (LSI): 1000-10,000 logic gates.
 - Very large scale integration (VLSI): 10,000-upward.
 - These levels are approximate, but the distinctions are useful in comparing the relative complexity of circuits.
 - Let us consider several useful MSI components:

SN7400 QUADRUPLE 2-INPUT POSITIVE-NAND GATES

description

These devices contain four independent 2-input NAND gates.


function table (each gate)

INPUTS		OUTPUT
A	B	Y
H	H	L
L	X	H
X	L	H

absolute maximum ratings

Supply voltage, V_{CC} 7 V
 Input voltage: 5.5 V
 Operating free-air temperature range: 0°C to 70°C
 Storage temperature range: -65°C to 150°C

package (top view)

 

schematic (each gate)


 


Fig A.20 The Data Sheet

recommended operating conditions

	MIN	NOM	MAX	UNIT
V_{CC} Supply voltage	4.75	5	5.25	V
V_{IH} High-level input voltage	2			V
V_{IL} Low-level input voltage			0.8	V
I_{OH} High-level output current			-0.4	mA
I_{OL} Low-level output current			16	mA
T_A Operating free-air temperature	0		70	°C

logic diagram (positive logic)

 


electrical characteristics over recommended operating free-air temperature range

VALUE	OPERATING CONDITIONS	MIN	TYP	MAX	UNIT
V_{OH}	$V_{CC} = \text{MIN}, V_{IL} = 0.8 \text{ V}, I_{OH} = -0.4 \text{ mA}$	2.4	3.4		V
V_{OL}	$V_{CC} = \text{MIN}, V_{IH} = 2 \text{ V}, I_{OL} = 16 \text{ mA}$		0.2	0.4	V
I_{IH}	$V_{CC} = \text{MAX}, V_I = 2.4 \text{ V}$			40	μA
I_{IL}	$V_{CC} = \text{MAX}, V_I = 0.4 \text{ V}$			-1.6	mA
I_{CCH}	$V_{CC} = \text{MAX}, V_I = 0 \text{ V}$		4	8	mA
I_{CCL}	$V_{CC} = \text{MAX}, V_I = 4.5 \text{ V}$		12	22	mA

switching characteristics, $V_{CC} = 5 \text{ V}, T_A = 25^\circ \text{ C}$


PARAMETER	FROM (input)	TO (output)	TEST CONDITIONS	MIN	NOM	MAX	UNIT
t_{PLH}	A or B	Y	$R_L = 400 \Omega$ $C_L = 15 \text{ pF}$	11	22		ns
t_{PHL}				7	15		ns

Figs A.21, A.22 The Multiplexer

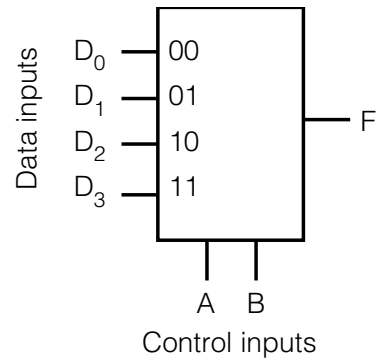

A	B	F
0	0	D ₀
0	1	D ₁
1	0	D ₂
1	1	D ₃

 
$$F = \bar{A} \bar{B} D_0 + \bar{A} B D_1 + A \bar{B} D_2 + A B D_3$$



C
S
D
A
2/e


Fig A.23 Implementing the Majority Function with an 8-1 Mux

A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

Principle: Use the mux select to pick out the selected minterms of the function.

Fig. A.24 More Efficiency: Using a 4-1 Mux to Implement the Majority F'n.

 

Principle: Use the A and B inputs to select a pair of minterms. The value applied to the MUX input is selected from {0, 1, C, C} to pick the desired behavior of the minterm pair.

C


S

D

A

2/e

Fig. A.25 The Demultiplexer (DEMUX)

 

$$F_0 = D \bar{A} \bar{B}$$

$$F_2 = D A \bar{B}$$

$$F_1 = D \bar{A} B$$

$$F_3 = D A B$$

D	A	B	F ₀	F ₁	F ₂	F ₃
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

C

S



D

A

2/e

Fig's. A.26 and A.27: The Demultiplexer is a Decoder with an Enable Input

Compare to
Fig A.28

  

		Enable = 1			
A	B	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

		Enable = 0			
A	B	D ₀	D ₁	D ₂	D ₃
0	0	0	0	0	0
0	1	0	0	0	0
1	0	0	0	0	0
1	1	0	0	0	0

$$D_0 = \bar{A} \bar{B}$$

$$D_1 = \bar{A} B$$

$$D_2 = A \bar{B}$$

$$D_3 = A B$$

C


S

D

AA-27


2/e

Fig A.28 A 2-4 Decoder

 

C
S
D
A
2/e


Fig A.29 Using a Decoder to Implement the Majority Function

 

C**S****D****A****2/e**

Figs A.30, 31, The Priority Encoder

 - An encoder translates a set of inputs into a binary encoding,
- Can be thought of as the converse of a decoder.
- A priority encoder imposes an order on the inputs.
- A_i has a higher priority than A_{i+1}



$$F_0 = \bar{A}_0 \bar{A}_1 A_3 + \bar{A}_0 \bar{A}_1 A_2$$

$$F_1 = \bar{A}_0 \bar{A}_2 A_3 + \bar{A}_0 A_1$$

A_0	A_1	A_2	A_3	F_0	F_1
0	0	0	0	0	0
0	0	0	1	1	1
0	0	1	0	1	0
0	0	1	1	1	0
0	1	0	0	0	1
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	0	1
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0

 


Fig A.32 Programmable Logic Arrays (PLAs)

- A PLA is a customizable AND matrix followed by a customizable OR matrix:


 


Fig. A.33 Using a PLA to Implement the Majority Function

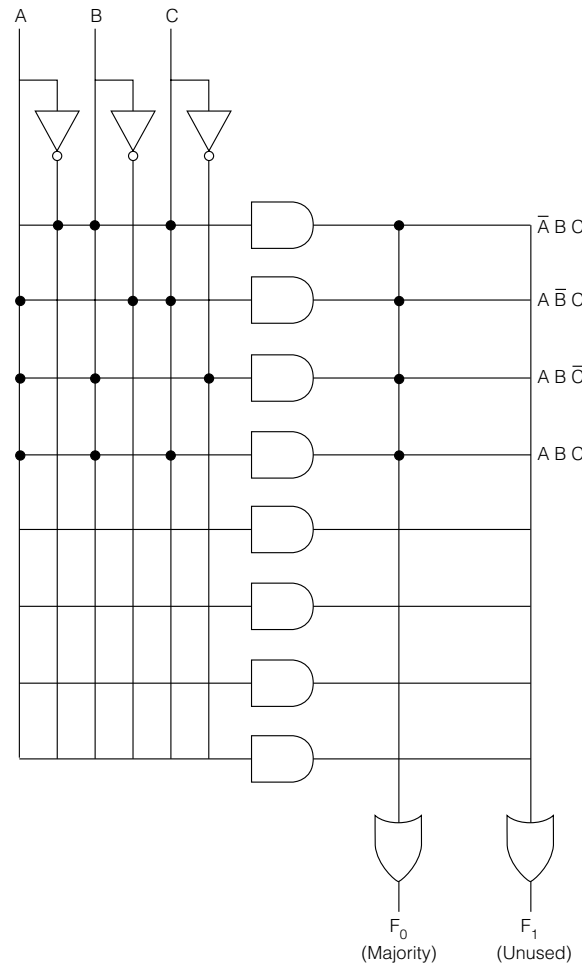

Using PLAs to Implement an Adder

Carry In	→	0	0	0	0	1	1	1	1
Operand A	→	0	0	1	1	0	0	1	1
Operand B	→	+ 0	+ 1	+ 0	+ 1	+ 0	+ 1	+ 0	+ 1
		<hr/>	<hr/>	<hr/>	<hr/>	<hr/>	<hr/>	<hr/>	<hr/>
		0 0	0 1	0 1	1 0	0 1	1 0	1 0	1 1
		↑ ↑							
		Carry	Sum						
		Out							

Example:

Carry		1	0	0	0
Operand A		0	1	0	0
Operand B	+	0	1	1	0
		<hr/>	<hr/>	<hr/>	<hr/>
Sum		1	0	1	0

Figs A.34-36



A _i	B _i	C _i	S _i	C _{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Fig A.37 A Multi-Bit Ripple-Carry Adder


 


Fig A.38 PLA Realization of a FA

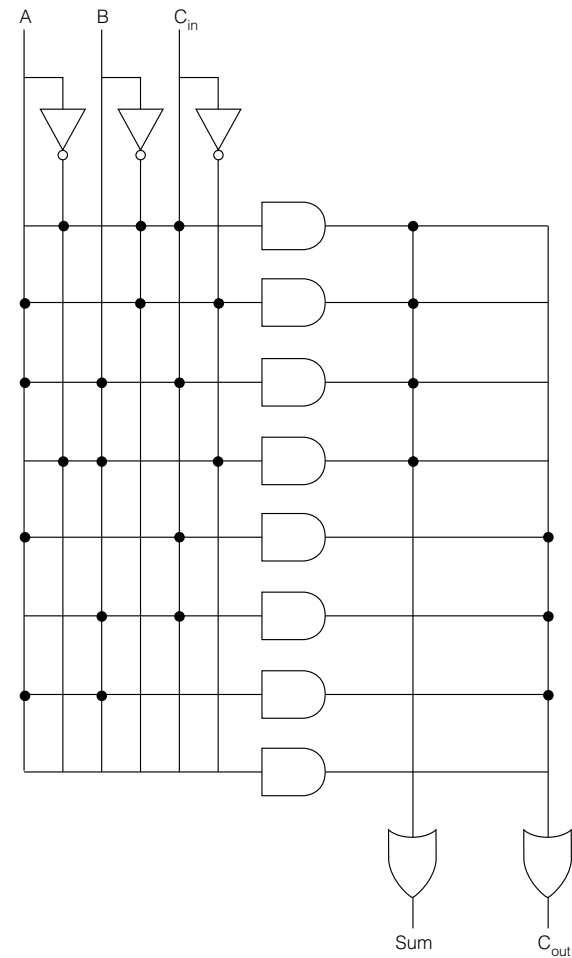

Reduction (Simplification) of Boolean Expressions

- It may be possible to simplify the canonical SOP or POS forms.
- A smaller Boolean equation translates to a lower gate count in the target circuit.
- We discuss two methods: algebraic reduction and Karnaugh map reduction.

C

S

D

A

2/e

The Algebraic Method

Consider the majority function, F:

$$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$F = \bar{A}BC + A\bar{B}C + AB(\bar{C} + C) \quad \text{Distributive Property}$$

$$F = \bar{A}BC + A\bar{B}C + AB(1) \quad \text{Complement Property}$$

$$F = \bar{A}BC + A\bar{B}C + AB \quad \text{Identity Property}$$

$$F = \bar{A}BC + A\bar{B}C + AB + ABC \quad \text{Idempotence}$$

$$F = \bar{A}BC + AC(\bar{B} + B) + AB \quad \text{Identity Property}$$

$$F = \bar{A}BC + AC + AB \quad \text{Complement and Identity}$$

$$F = \bar{A}BC + AC + AB + ABC \quad \text{Idempotence}$$

$$F = BC(\bar{A} + A) + AC + AB \quad \text{Distributive}$$

$$F = BC + AC + AB \quad \text{Complement and Identity}$$

C



S

D

A

2/e

Fig A.40 Venn Diagrams

  


**Each distinct region in the “Universe” represents a minterm.
This diagram can be transformed into a Karnaugh Map.**

C**S****D****A****2/e**

Fig A.41 A K-Map of the Majority Function

Place a “1” in each cell that has a that minterm.
Cells on the outer edge of the map “wrap around”


Minterm Index	A	B	C	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

 

The map contains all the minterms. Adjacent 1's in the K-Map satisfy the Complement property of Boolean Algebra.

C
S
D
A
2/e


Fig A.42 Adjacency Groupings for the Majority Function

 

$$M = BC + AC + AB$$

C
S
D
A
2/e

 A.43 Minimized AND OR Circuit for the Majority Function



$$M = BC + AC + AB$$

C


S

D


A

2/e

Fig A.44 Minimal and not Minimal Groupings

 
 
$$F = \bar{A}\bar{B}\bar{C} + \bar{A}CD + ABC + A\bar{C}\bar{D}$$



$$F = BD + \bar{A}\bar{B}\bar{C} + \bar{A}CD + ABC + A\bar{C}\bar{D}$$

C


S

D

A

2/e

Fig A.45 The Corners are Logically Adjacent

 

$$F = BCD + \bar{B}\bar{D} + \bar{A}B$$

A.46 Two Different Minimized Equations

CD \ AB		00	01	11	10
		00	01	11	10
00	1			d	
01		1	1		
11		1	1		
10	d				

$$F = \bar{B}\bar{C}\bar{D} + BD$$

CD \ AB		00	01	11	10
		00	01	11	10
00	1			d	
01		1	1		
11		1	1		
10	d				

$$F = \bar{A}\bar{B}\bar{D} + BD$$

C

S

D


A

2/e


Speed and Performance

- The speed of a digital system is governed by
 - the propagation delay through the logic gates and
 - the propagation across interconnections.

Fig A.47 Propagation Delay for a NOT Gate (From Hamacher et. al. 1990)



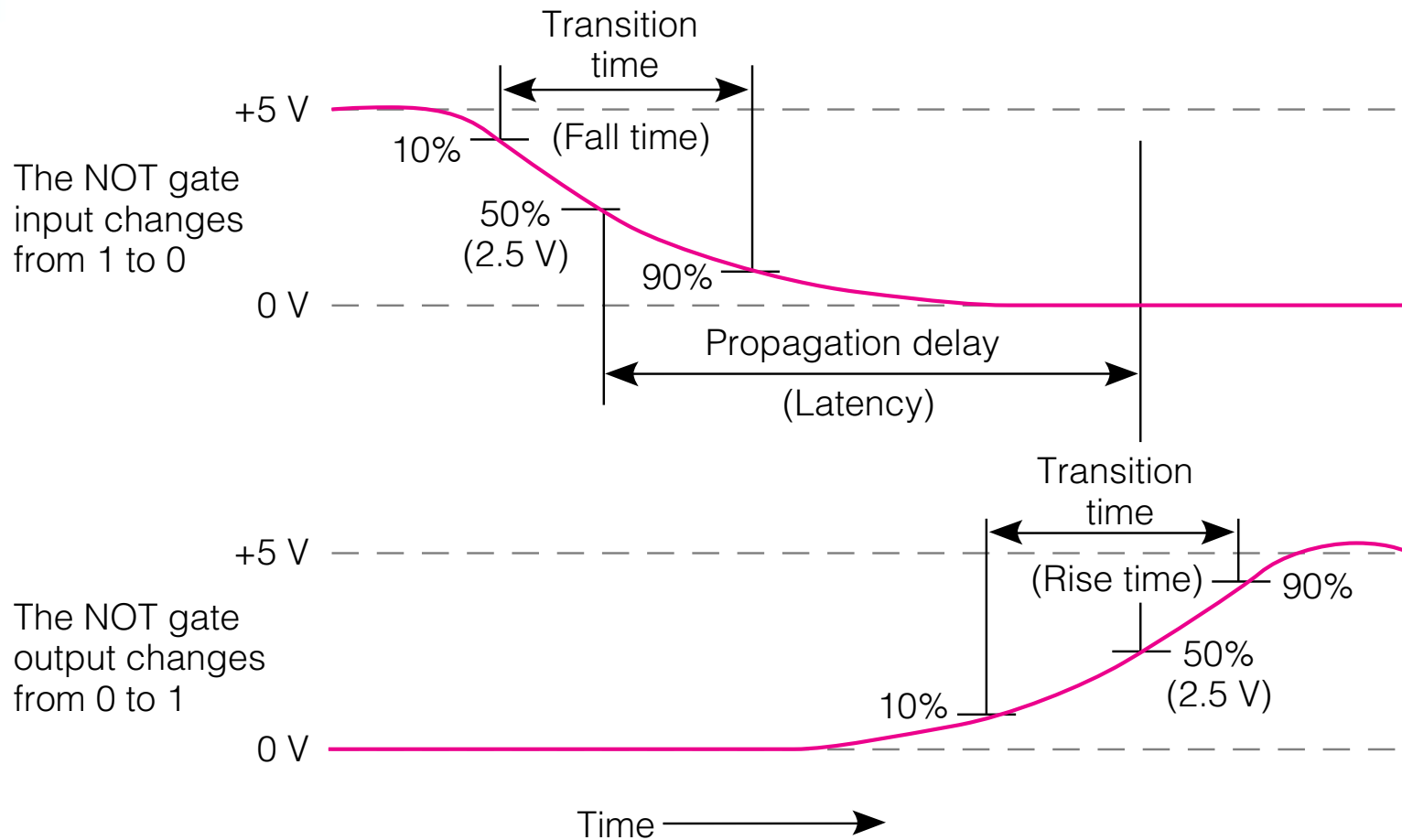


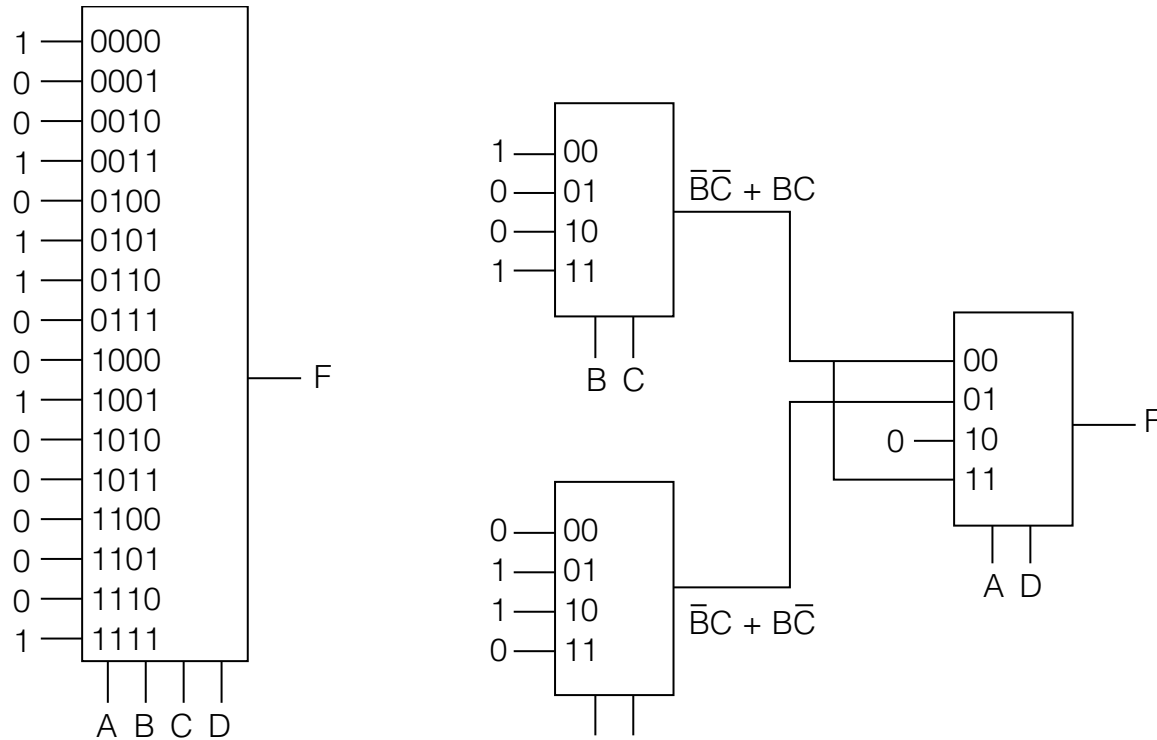Circuit Depth Affects Propagation Delay—Fig A.48



$$\begin{aligned}
 F(ABCD) &= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} + A\bar{B}\bar{C}D + ABCD \\
 &= (\bar{B}\bar{C} + BC)AD + (\bar{B}C + B\bar{C})\bar{A}D + (\bar{B}\bar{C} + BC)
 \end{aligned}$$

Fig A.49 Fanin may Affect Circuit Depth

   

Associative law of Boolean algebra:
 $A + B + C + D = (A + B) + (C + D)$

$((A + B) + C) + D$
 Degenerate tree

C

S

D


A

2/e

Sequential Logic

- The combinational logic circuits we have been studying so far have no memory. The outputs always follow the inputs.
- There is a need for circuits with a memory, which behave differently *depending upon their previous state*.
- An example is the vending machine, which must remember how many and what kinds of coins have been inserted, and which behave according to not only the current coin inserted, but also upon how many and what kind of coins have been deposited previously.
- These are referred to as *finite state machines*, because they can have at most a finite number of states.

Fig A.50 Classical Model of a Finite State Machine (FSM)

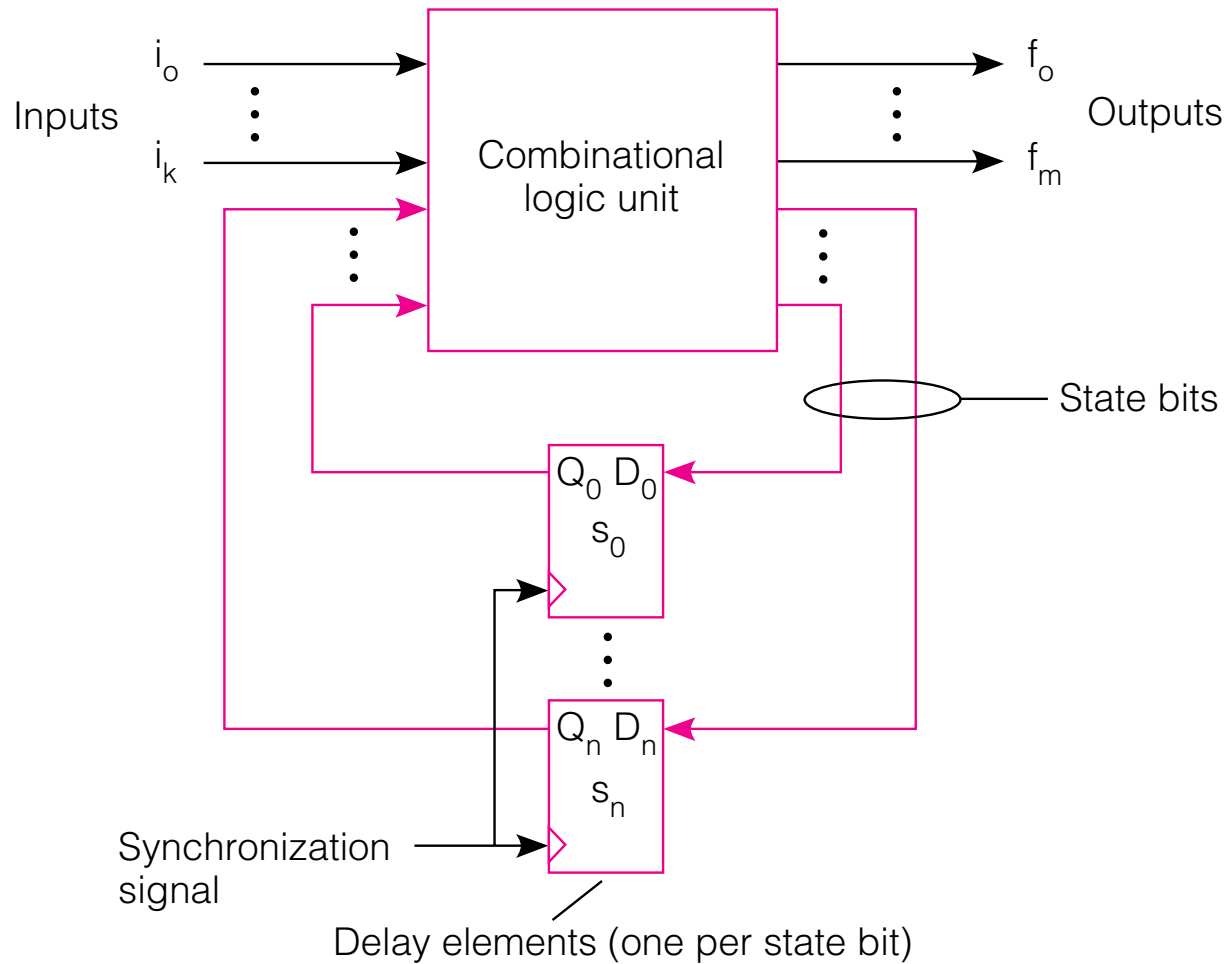

C



S

D

A

2/e

A.51 A NOR Gate with a Lumped Delay

  

Timing behavior

This delay between input and output is at the basis of the functioning of an important memory element, the *flip-flop*.

C


S

D


A

2/e

A.52 The S-R (Set-Reset) Flip-Flop

 


Q_t	S_t	R_t	Q_{i+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	(disallowed)
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	(disallowed)

 

Timing behavior

The S-R flip-flop is an active high (positive logic) device.

Fig A.53 Converting a NOR S-R to an NAND S-R

 

Active High
NOR Impl.

Push Bubbles
(DeMorgan's)

Rearrange
Bubbles

Convert
from Bubbles
to Active Low
Signal Names

C


S

D


A

2/e

Fig A.54 A Circuit with a Hazard

 

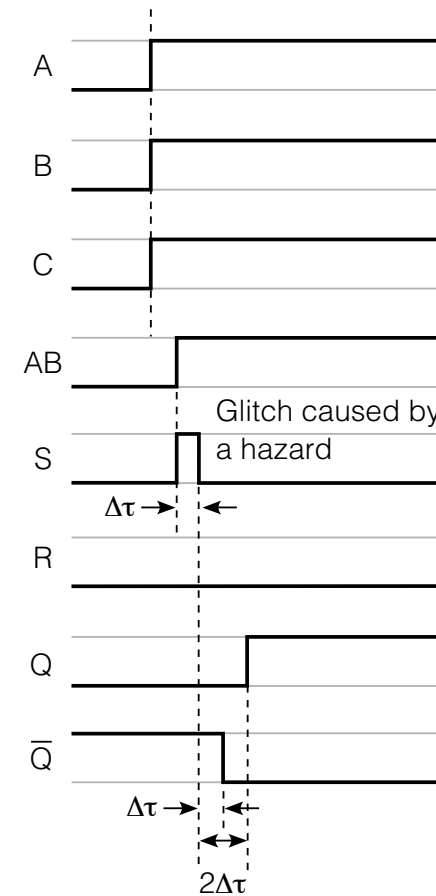It is desirable to be able to “turn off” the flip-flop so it does not respond to such hazards.



Timing behavior

C


S

D

A

2/e



Fig A.55 The Clock Paces the System

 

In a positive logic system, the “action” happens when the clock is high, or positive. The low part of the clock cycle allows propagation between subcircuits, so their inputs are stable at the correct value when the clock next goes high.

C
S
D
A
2/e

A.56 A Clocked S-R Flip-Flop

  

Timing behavior

The clock signal, CLK, turns on the inputs to the flip-flop.

C




S

D

A

2/e



Fig A.57 The Clocked D (Data) Flip-Flop

   

Timing behavior

The clocked D flip-flop, sometimes called a latch, has a potential problem: If D changes while the clock is high, the output will also change. The Master-Slave flip-flop solves this problem:

A.58 The Master-Slave Flip-Flop

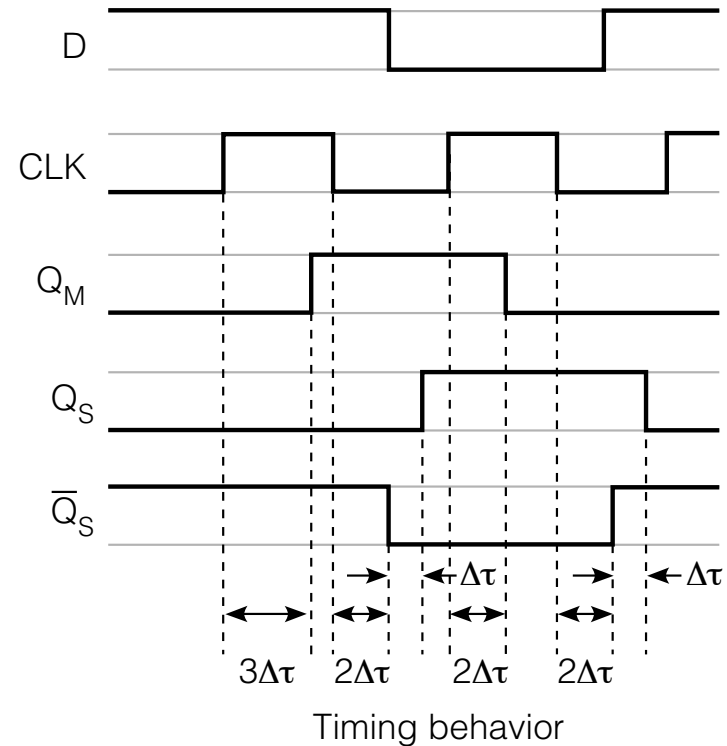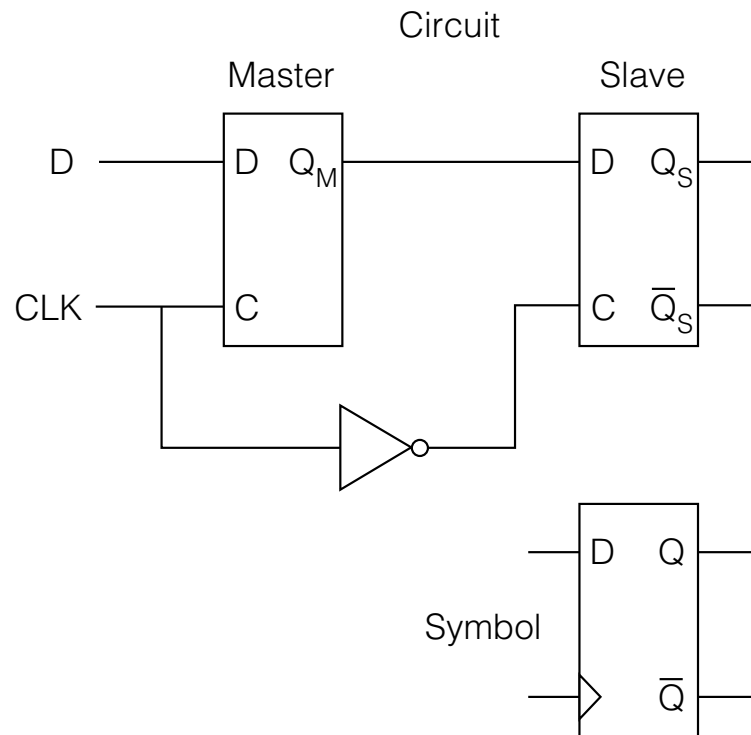

The rising edge of the clock clocks new data into the Master, while the slave holds previous data. The falling edge clocks the new Master data into the Slave.

C


S

D

A

2/e

Fig A.59 The Basic J-K Flip-Flop

 

- The J-K flip-flop eliminates the $S=R=1$ problem of the S-R flip-flop, because Q enables J while Q' disables K, and vice-versa.
- However there is still a problem. If J goes momentarily to 1 and then back to 0 while the flip-flop is active and in the reset, the flip-flop will “catch” the 1.
- This is referred to as “1’s catching.”
- The J-K Master-Slave flip-flop solves this problem.

C


S

D

A

2/e

Fig A.61 The Master-Slave J-K Flip-Flop

 

C


S

D


A

2/e

Fig A.60 The T (Toggle) Flip-Flop

 

Circuit


 


Symbol

- The presence of a constant 1 at J and K means that the flip-flop will change its state from 0-1 or 1-0 each time it is clocked by the T (Toggle) input.

C
S
D
A
2/e

Fig A.62 The Negative Edge-Triggered D Flip-Flop

 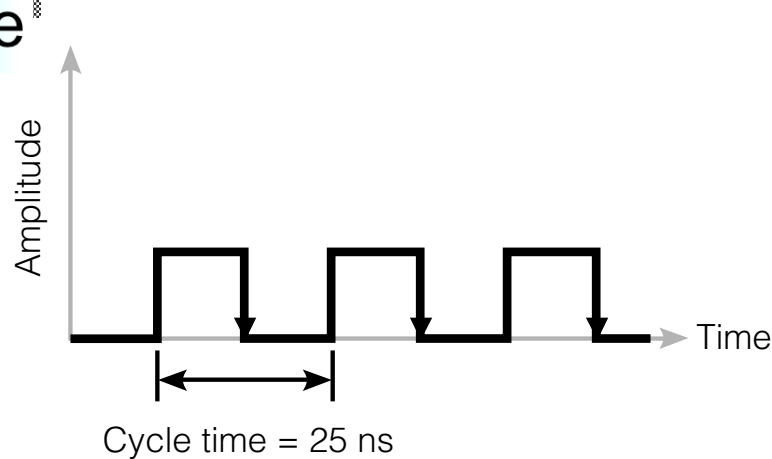

- When the clock is high, the two input latches output 0, so the Main latch remains in its previous state, regardless of changes in D.
- When the clock goes high-low, values in the two input latches will affect the state of the Main latch.
- While the clock is low, D cannot affect the Main latch.

C
S
D
A
2/e

Fig A.63 Finite State Machine Design Example: The Modulo-4 Counter

Counter has a clock input, CLK, and a RESET input.

- Has two output lines, which must take values of 00, 01, 10, and 11 on subsequent clock cycles.

It requires two flip-flops to store the state.


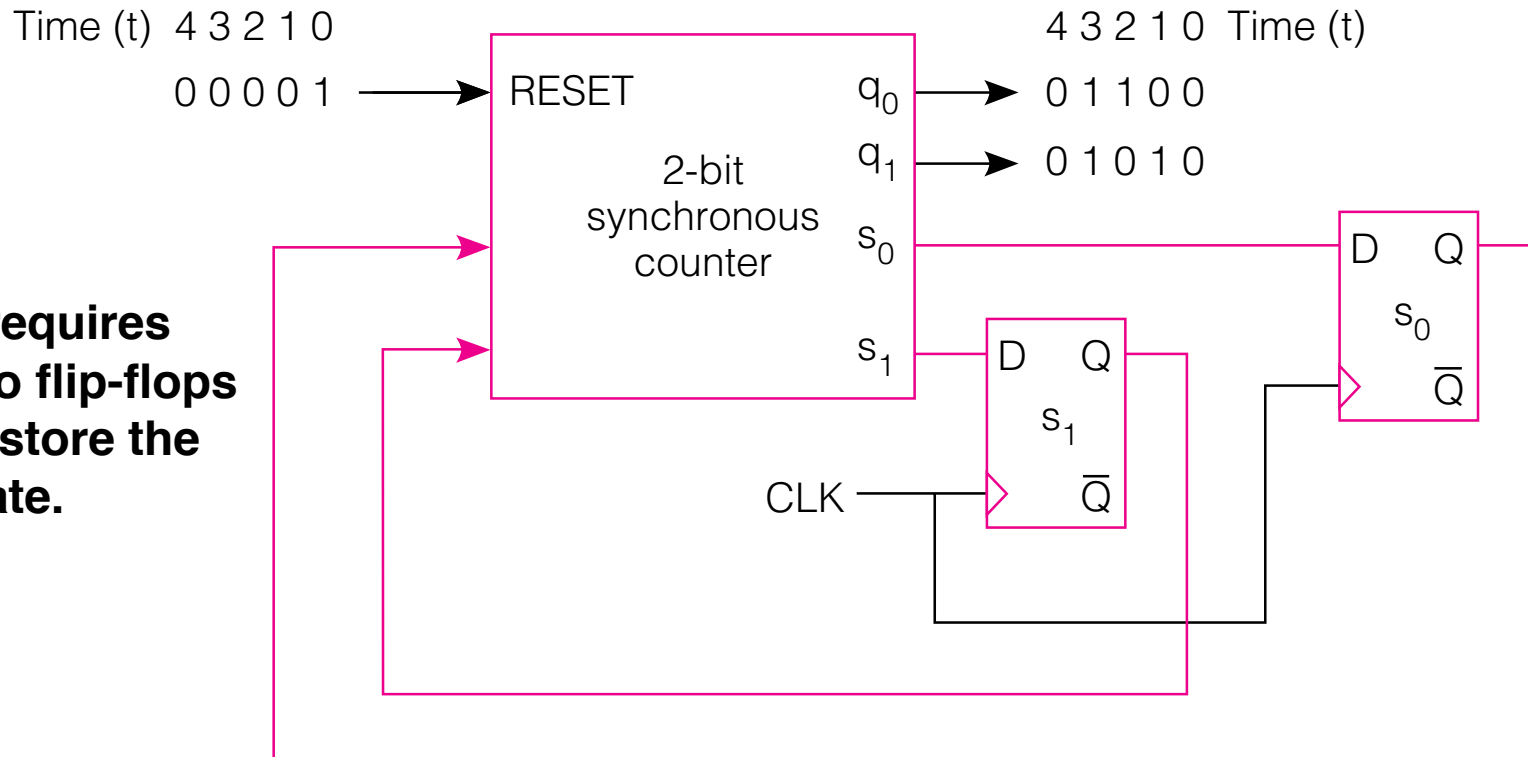


Fig A.64 State Transition Diagram for a Modulo(4) Counter

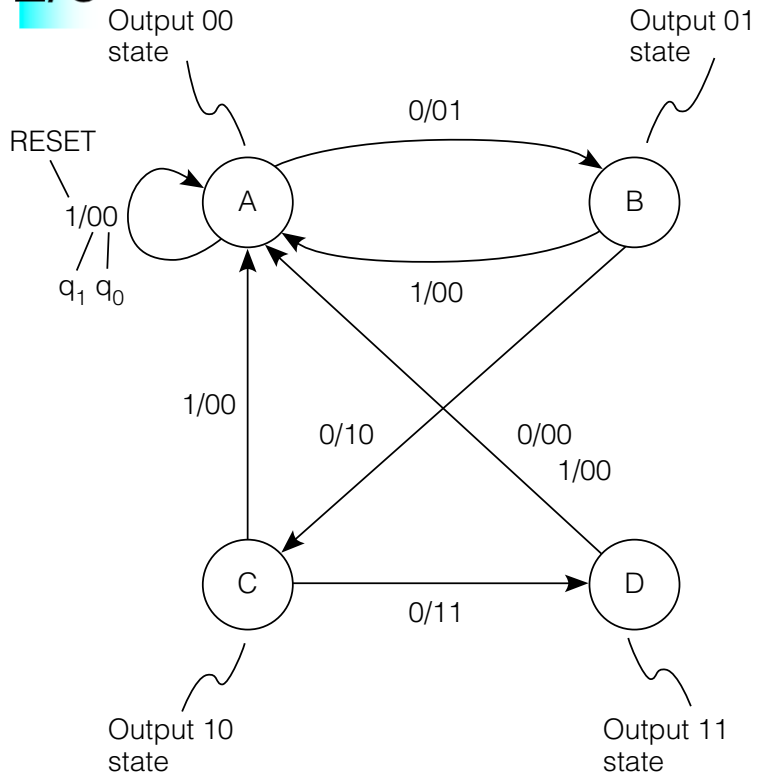

State Table

Present State	Next State	
	RESET 0	1
A	B/01	A/00
B	C/10	A/00
C	D/11	A/00
D	A/00	A/00

State Table With States Assigned

Present State	RESET	
	0	1
A:00	01	00
B:01	10	00
C:10	11	00
D:11	00	00

- The state diagram and state table tell “all there is to know” about the FSM, and are the basis for a provably correct design.

Fig A.67a

C
S
D
A
2/e

$r(t)$	$s_1(t)s_0(t)$	$s_1s_0(t+1)$	$q_1q_0(t+1)$
0	00	01	01
0	01	10	10
0	10	11	11
0	11	00	00
1	00	00	00
1	01	00	00
1	10	00	00
1	11	00	00

- Develop equations from this truth table for $s_0(t+1)$, $s_1(t+1)$, $q_0(t+1)$, and $q_1(t+1)$ from inputs $r(t)$, $s_0(t)$ and $s_1(t)$

C

S

D

A

2/e

Fig A.67b

$$s_0(t + 1) = \overline{r(t)s_1(t)s_0(t)} + \overline{r(t)}s_1(t)\overline{s_0(t)}$$

$$s_1(t + 1) = \overline{r(t)s_1(t)s_0(t)} + \overline{r(t)}s_1(t)\overline{s_0(t)}$$


$$q_0(t + 1) = \overline{r(t)s_1(t)s_0(t)} + \overline{r(t)}s_1(t)\overline{s_0(t)}$$

$$q_1(t + 1) = \overline{r(t)s_1(t)s_0(t)} + \overline{r(t)}s_1(t)\overline{s_0(t)}$$

Implement these equations

Fig A.68

Circuit for a 2-bit counter:

 

There are many simpler techniques for implementing counters.

C

S

D

A

2/e

Example A.2: A Sequence Detector

- Design a machine that outputs a 1 when exactly 2 of the last 3 inputs are 1.
- e.g. input sequence of 011011100 produces an output sequence of 001111010
- Assume input is a 1-bit serial line.
- Use D flip-flops and 8-1 Multiplexers
- Begin by constructing a state transition diagram:

C


S

D

Design a machine that outputs a 1 when exactly 2 of the last 3 inputs are 1.

2/e

Fig A.69 State Transition Diagram for Sequence Detector

 


Pres. State	X	
	0	1
$S_2S_1S_0$	$S_2S_1S_0Z$	$S_2S_1S_0Z$
A=000	001/0	010/0
B=001	011/0	100/0
C=010	101/0	110/0
D=011	011/0	100/0
E=100	101/0	110/1
F=101	011/0	100/1
G=110	101/1	110/0

• Discuss: the “meaning” of each state.

• Convert table to truth table (how?).

• Solve for $s_2 s_1 s_0$ and Z.

Fig A.72 Logic Diagram for Seq. Det.

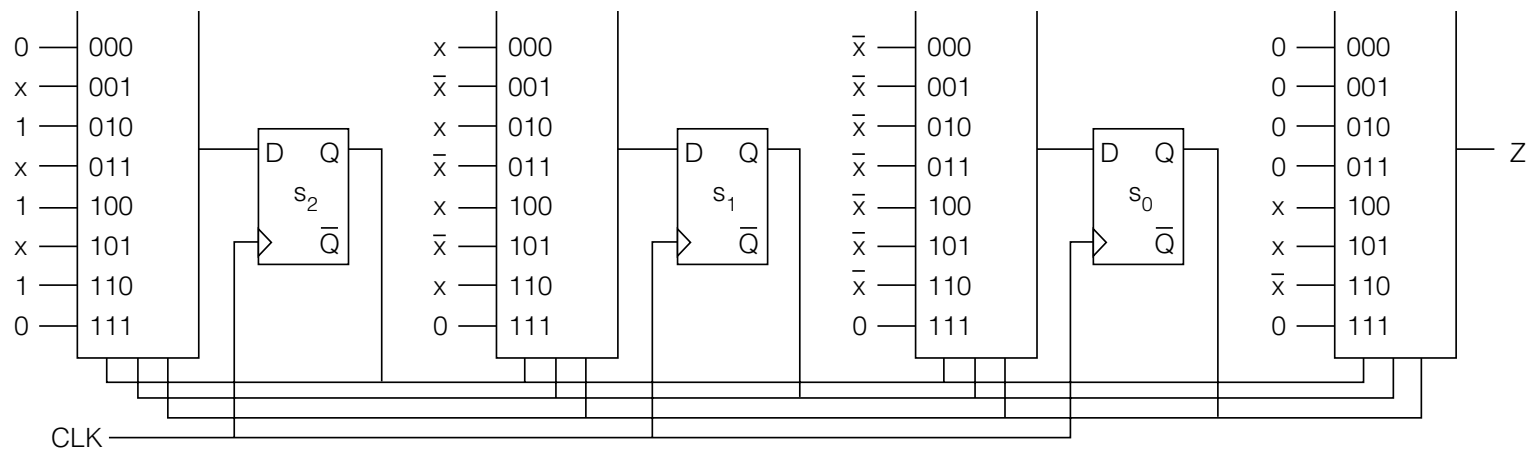

C

S

D


A

2/e

Ex A.3 A Vending Machine Controller

- Accepts nickel, dime, and quarter. When value of money inserted equals or exceeds twenty cents, machine vends item and returns change if any, and waits for next transaction.
- Implement with PLA and D flip-flops.

Fig A.73 State Trans. Diagram for Vending Machine Controller

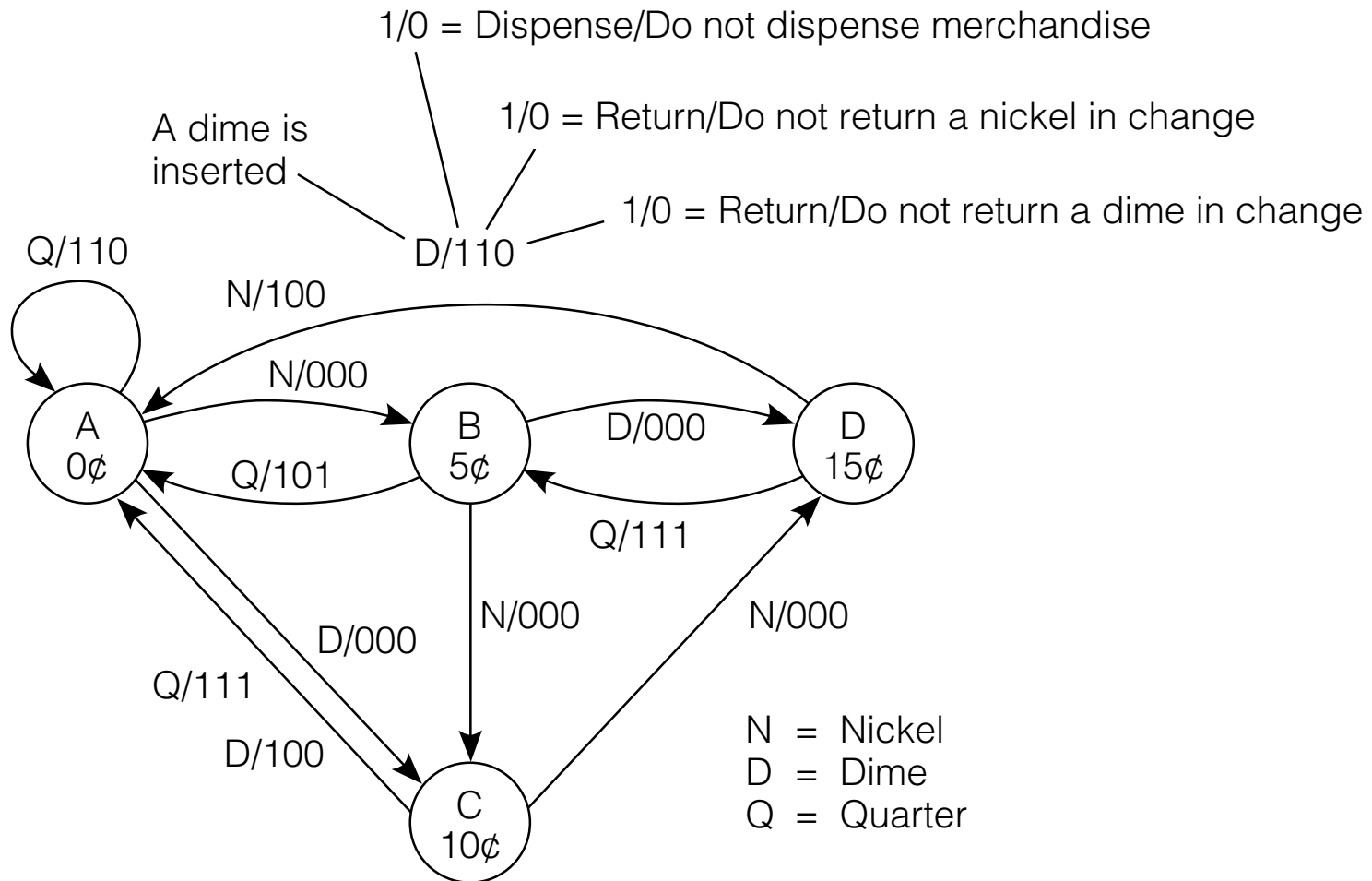

C

S

D

A


2/e

Fig A.75b Truth Table for Vending Machine

Base 10 equivalent	Present state				Next state		Dispense		
	state		Coin		state		Return nickel z_2	Return dime z_1	Return dime z_0
	s_1	s_0	x_1	x_0	s_1	s_0			
0	0	0	0	0	0	1	0	0	0
1	0	0	0	1	1	0	0	0	0
2	0	0	1	0	0	0	1	1	0
3	0	0	1	1	d	d	d	d	d
4	0	1	0	0	1	0	0	0	0
5	0	1	0	1	1	1	0	0	0
6	0	1	1	0	0	0	1	0	1
7	0	1	1	1	d	d	d	d	d
8	1	0	0	0	1	1	0	0	0
9	1	0	0	1	0	0	1	0	0
10	1	0	1	0	0	0	1	1	1
11	1	0	1	1	d	d	d	d	d
12	1	1	0	0	0	0	1	0	0
13	1	1	0	1	0	0	1	1	0
14	1	1	1	0	0	1	1	1	1
15	1	1	1	1	d	d	d	d	d


(b)

Fig A.75 a)FSM, b)Truth Table, c)PLA realization

 

Base 10 equivalent	Present state		Coin		Next state		Dispense		
	s_1	s_0	x_1	x_0	s_1	s_0	Z_2	Z_1	Z_0
0	0	0	0	0	0	1	0	0	0
1	0	0	0	1	1	0	0	0	0
2	0	0	1	0	0	0	1	1	0
3	0	0	1	1	d	d	d	d	d
4	0	1	0	0	1	0	0	0	0
5	0	1	0	1	1	1	0	0	0
6	0	1	1	0	0	0	1	0	1
7	0	1	1	1	d	d	d	d	d
8	1	0	0	0	1	1	0	0	0
9	1	0	0	1	1	0	0	1	0
10	1	0	1	0	0	0	1	1	1
11	1	0	1	1	d	d	d	d	d
12	1	1	0	0	0	0	1	0	0
13	1	1	0	1	0	0	1	1	0
14	1	1	1	0	0	1	1	1	1
15	1	1	1	1	d	d	d	d	d

(b)

 


(c)


Mealy vs. Moore Machines

Mealy Model: Outputs are functions of Inputs and Present State.

 - Previous FSM designs were Mealy Machines, because next state was computed from present state and inputs.



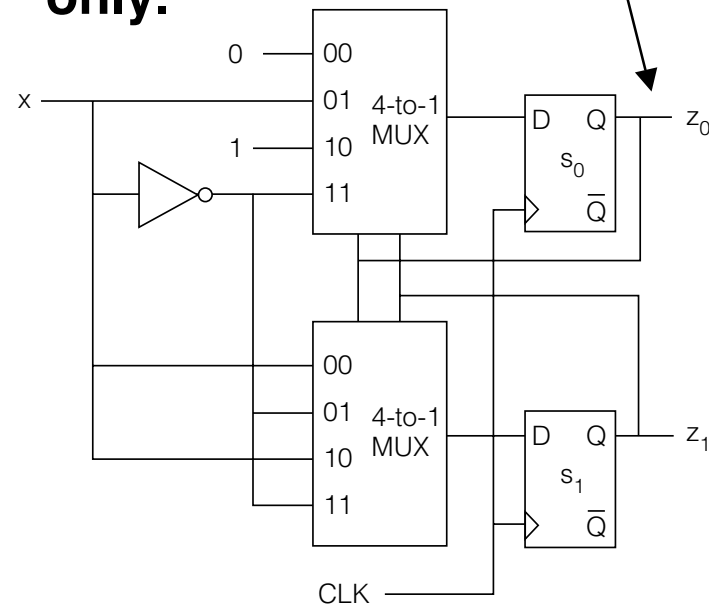- Moore Model: Outputs are functions of Present State only.**




- Both are equally powerful.**


Fig A.77 Tri-state Buffers

C	A	F
0	0	∅
0	1	∅
1	0	0
1	1	1

C	A	F
0	0	0
0	1	1
1	0	∅
1	1	∅

 

Tri-state buffer

 


Tri-state buffer, inverted control

- There is a third state: High impedance. This means the gate output is essentially disconnected from the circuit.
- This state is indicated by ∅ in the figure.

Fig A78, A79 Registers

Gate-Level View

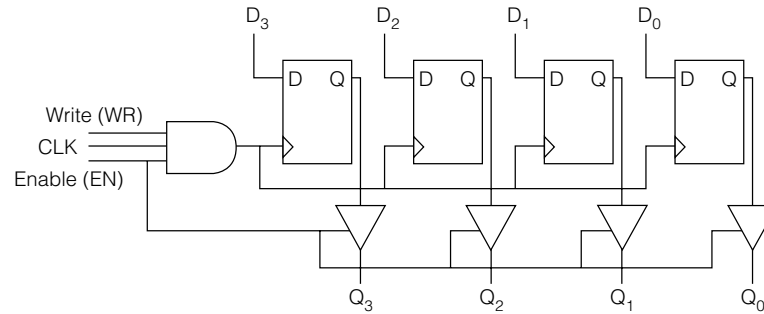

Chip-Level View



 


Fig A.80 A Left-Right Shift Register with Parallel Read and Write

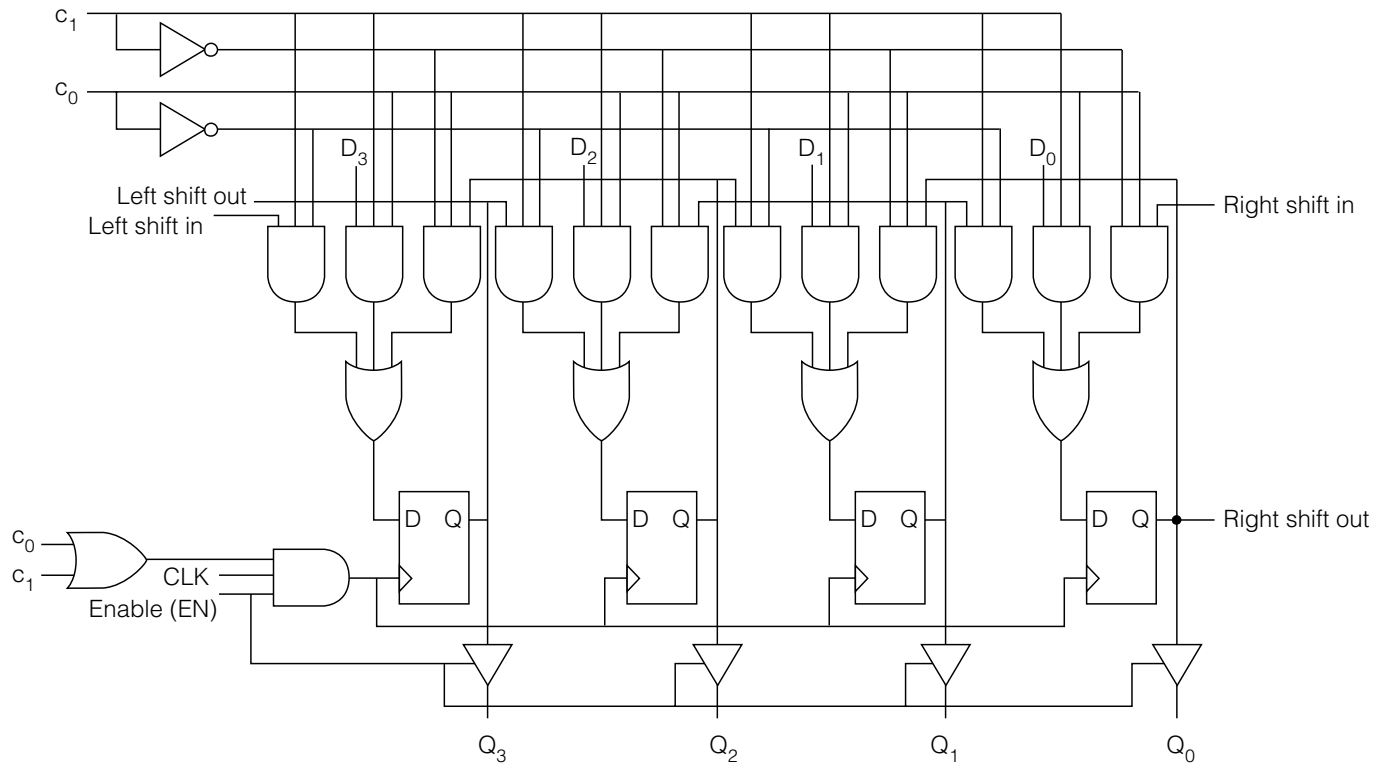

Control		Function
c ₁	c ₀	
0	0	No change
0	1	Shift left
1	0	Shift right
1	1	Parallel load

 

C
S
D
A
2/e

Fig A.81 A Modulo 8 (3-bit) Ripple Counter

Note the use of the T flip-flops. They are used to toggle the input of the next flip-flop when its output is 1.

