

LOOKAHEAD CARRY ADDER INTRODUCTION

Let A, B, and C be the inputs to a full adder. Then, finding the Sum, S, and Carry Out, Cout, we have:

		AB	00	01	11	10
		C	0	1		1
		0	1		1	
		1		1		
		1				

$$S = A \text{ XOR } B \text{ XOR } C$$

		AB	00	01	11	10
		C	0		1	
		0			1	
		1		1	1	1
		1				

$$\text{Cout} = A^*B + A^*C + B^*C = A^*B + (A + B)^*C, \text{ or}$$

$$\text{Cout} = G + P^*C, \text{ where } G = A^*B, P = A + B$$

Generalizing the result above to n bits, we have the following:


$$C_1 = G_0 + P_0^*C_0$$

$$C_2 = G_1 + P_1^*C_1 = G_1 + P_1^*(G_0 + P_0^*C_0) = G_1 + P_1^*G_0 + P_1^*P_0^*C_0$$

$$C_3 = G_2 + P_2^*C_2 = G_2 + P_2^*G_1 + P_2^*P_1^*G_0 + P_2^*P_1^*P_0^*C_0$$

$$C_4 = G_3 + P_3^*C_3 = G_3 + P_3^*G_2 + P_3^*P_2^*G_1 + P_3^*P_2^*P_1^*G_0 + P_3^*P_2^*P_1^*P_0^*C_0$$

$$C_5 = G_4 + P_4^*C_4 = \dots$$

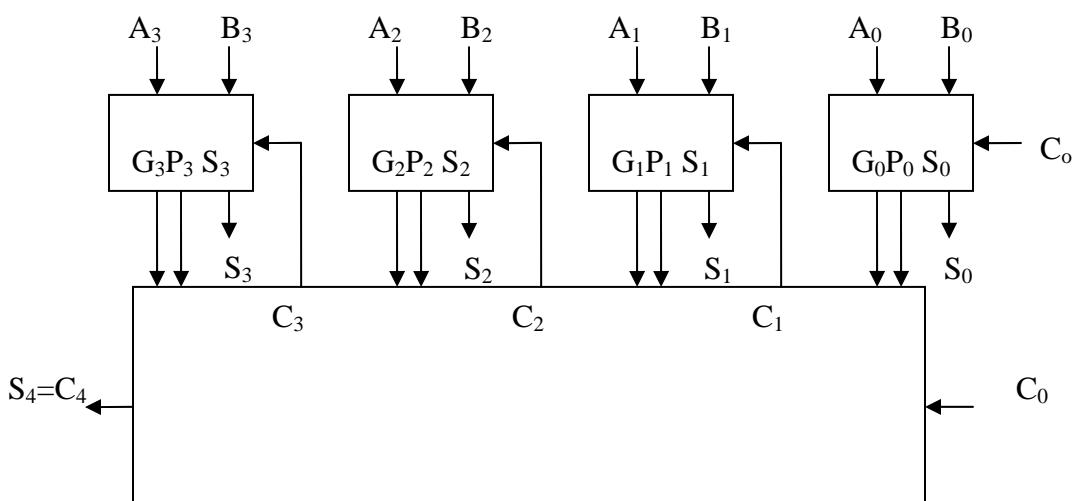

An n-bit Ripple-Carry Adder (RCA) takes $2n$ gate delays to compute an n-bit sum.

With carry lookahead, we can theoretically compute an n-bit sum in 5 gate delays!

The theoretical limit for an n-bit sum (full parallel implementation) is 2 gate delays.