
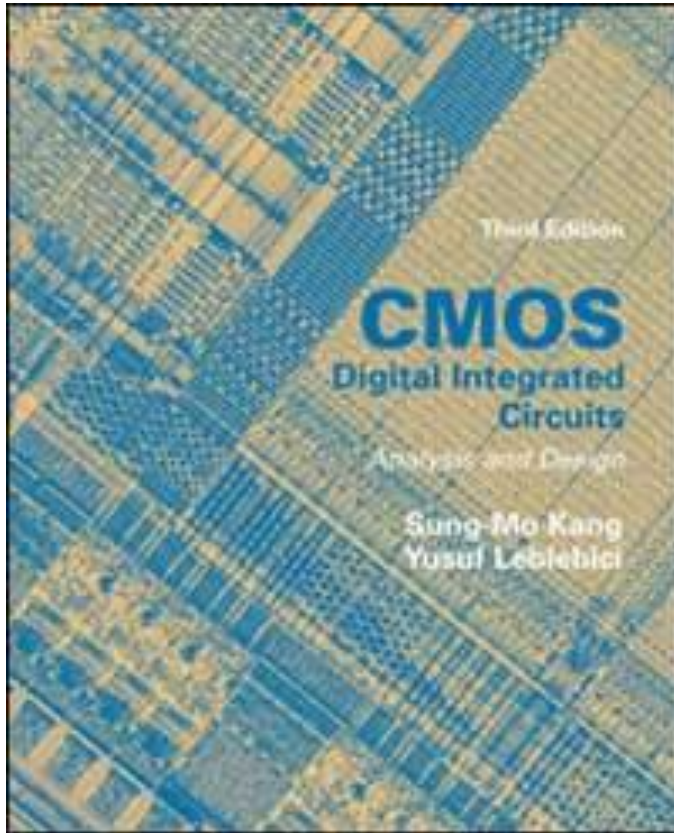


Digital IC Design and Architecture

 


MOS Inverter Static Characteristics


IDEAL INVERTER VOLTAGE TRANSFER CHARACTERISTIC (VTC)



A	B
0	1
1	0

 

 ACTUAL INVERTER VOLTAGE TRANSFER CHARACTERISTIC (VTC)




V_{OH} -> max output voltage when output is "1"

V_{OL} -> min output voltage when output is "0"

V_{IL} -> max input voltage which can be interpreted as "0"

 V_{IH} -> min input voltage which can be interpreted as "1"




NOISE IMMUNITY AND NOISE MARGINS

V_{OH} -> max output voltage when output is "1"

V_{OL} -> min output voltage when output is "0"

V_{IL} -> max input voltage which can be interpreted as "0"

 V_{IH} -> min input voltage which can be interpreted as "1"




NOISE IMMUNITY AND NOISE MARGINS

V_{OH} -> max output voltage when output is "1"

V_{OL} -> min output voltage when output is "0"

V_{IL} -> max input voltage which can be interpreted as "0"

 V_{IH} -> min input voltage which can be interpreted as "1"



$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

JUSTIFICATION FOR V_{IL} , V_{IH} :

LET: $V_{out} = f(V_{in})$, $V'_{out} = f(V_{in} + \Delta V_{noise})$

$$V'_{out} = f(V_{in}) + \frac{dV_{out}}{dV_{in}} \Delta V_{noise} + \text{H.O. term}$$

Using first-order Taylor series expansion

Perturbed Output = Nominal Output + Gain x Ext. Perturbation

FIVE CRITICAL VOLTAGES: V_{OL} , V_{OH} , V_{IL} , V_{IH} , V_{th} determine:

- > DC Output Voltage Behavior
- > Noise Margins
- > Width and Location of Transition Region

POWER DISSIPATION AND DIE AREA

Power Dissipation -> **HEAT**

$$T_j = T_a + \Theta P$$

$$P \text{ --> } P_{DC}, P_{dynamic}$$

$$P_{DC} = V_{DD} I_{DC}$$

T_j -> junction Temp

T_a -> ambient Temp

Θ -> Thermal Resistance


P -> Power Dissipated

ASSUME: $V_{in} = "1"$ 50% of Op Time, $"0"$ 50% of Op Time

$$P_{DC} = \frac{V_{DD}}{2} [I_{DC}(V_{in} = "0") + I_{DC}(V_{in} = "1")]$$


DIE AREA --> MIN W x L and routing --> limited by design rules

Digital IC Design and Architecture

 


CMOS Inverter

CMOS Inverter Circuit

 





(a)

 


(b)

CMOS Inverter Circuit

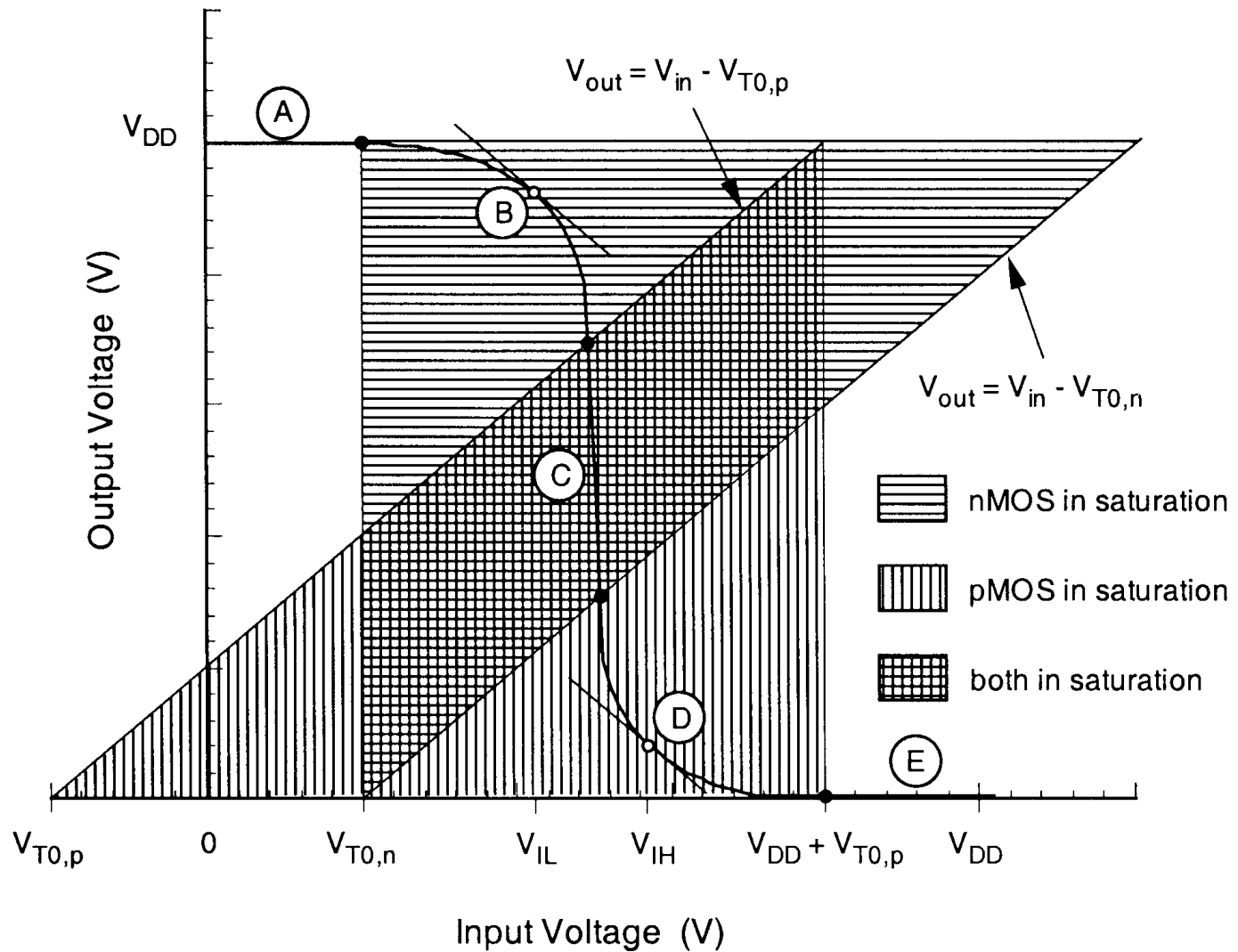

  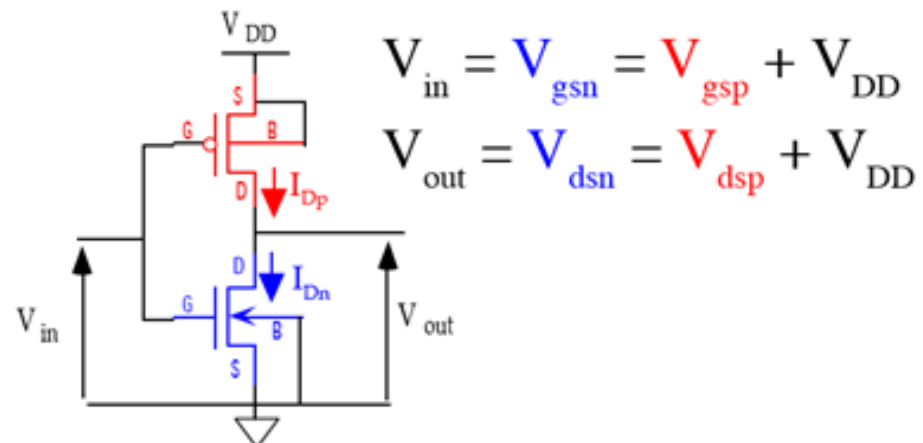

CALCULATE V_{OH}

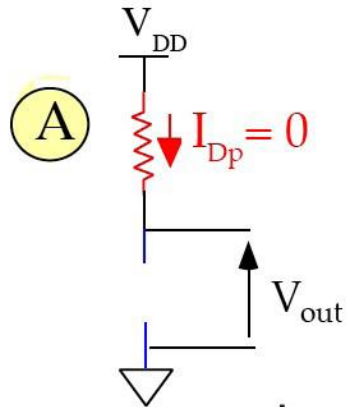


$$I_{Dp} = I_{Dn} = 0$$

$$V_{OH} = V_{DD}$$

$$\frac{k'_p}{2} \left(\frac{W}{L} \right)_p \left[2(V_{in} - V_{DD} - V_{T0p})(V_{out} - V_{DD}) - (V_{out} - V_{DD})^2 \right] = 0$$

CALCULATE V_{OL}

 


$$I_{Dp} = I_{Dn} = 0$$

$$V_{OL} = 0$$

$$0 = \frac{k'_n}{2} \left(\frac{W}{L} \right)_n \left[2(V_{in} - V_{T0n})(V_{out}) - (V_{out})^2 \right]$$

CALCULATE V_{OH}

 


$$I_{Dp} = I_{Dn} = 0$$

- nMOS is off
- pMOS is on and in linear region

$$V_{OH} = V_{DD}$$

$$\frac{k'_p}{2} \left(\frac{W}{L} \right)_p \left[2(V_{in} - V_{DD} - V_{T0p})(V_{out} - V_{DD}) - (V_{out} - V_{DD})^2 \right] = 0$$

CALCULATE V_{OL}

 


$$I_{Dp} = I_{Dn} = 0$$

$$V_{OL} = 0$$

$$0 = \frac{k'_n}{2} \left(\frac{W}{L} \right)_n \left[2(V_{in} - V_{T0n})(V_{out}) - (V_{out})^2 \right]$$

CALCULATE V_{OH}

 


$$I_{Dp} = I_{Dn} = 0$$

- nMOS is off
- pMOS is on and in linear region

$$V_{OH} = V_{DD}$$

$$\frac{k'_p}{2} \left(\frac{W}{L} \right)_p \left[2(V_{in} - V_{DD} - V_{T0p})(V_{out} - V_{DD}) - (V_{out} - V_{DD})^2 \right] = 0$$

CALCULATE V_{OL}

 



$$I_{Dp} = I_{Dn} = 0$$

- nMOS is on and in linear region
- pMOS is off

$$V_{OL} = 0$$

$$0 = \frac{k'_n}{2} \left(\frac{W}{L} \right)_n \left[2(V_{in} - V_{T0n})(V_{out}) - (V_{out})^2 \right]$$

CALCULATE V_{IL}

  

$$I_{Dp} = I_{Dn}$$



$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n (V_{GSn} - V_{T0n})^2 = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p [2(V_{GSp} - V_{T0p})V_{DSp} - V_{DSp}^2]$$

$$V_{GSn} = V_{in}, \quad V_{GSp} = V_{in} - V_{DD}, \quad V_{DSp} = V_{out} - V_{DD}$$

$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n (V_{in} - V_{T0n})^2$$

$$= \frac{k'_p}{2} \left(\frac{W}{L} \right)_p [2(V_{in} - V_{DD} - V_{T0p})(V_{out} - V_{DD}) - (V_{out} - V_{DD})^2]$$

CALCULATE V_{IL}

  

- nMOS is in saturation region
- pMOS is in linear region

$$I_{Dp} = I_{Dn}$$

$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n (V_{GSn} - V_{T0n})^2 = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p [2(V_{GSp} - V_{T0p})V_{DSp} - V_{DSp}^2]$$

$$V_{GSn} = V_{in}, \quad V_{GSp} = V_{in} - V_{DD}, \quad V_{DSp} = V_{out} - V_{DD}$$

$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n (V_{in} - V_{T0n})^2$$

$$= \frac{k'_p}{2} \left(\frac{W}{L} \right)_p [2(V_{in} - V_{DD} - V_{T0p})(V_{out} - V_{DD}) - (V_{out} - V_{DD})^2]$$

$$\begin{aligned} & \frac{k'_n}{2} \left(\frac{W}{L} \right)_n (V_{in} - V_{T0n})^2 \\ & = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p \left[2(V_{in} - V_{DD} - V_{T0p})(V_{out} - V_{DD}) - (V_{out} - V_{DD})^2 \right] \end{aligned} \quad (5.59)$$

DIFFERENTIATING wrt V_{in}

$$\begin{aligned} k'_n \left(\frac{W}{L} \right)_n (V_{in} - V_{T0n}) & = k'_p \left(\frac{W}{L} \right)_p \left[(V_{out} - V_{DD}) + (V_{in} - V_{DD} - V_{T0p}) \frac{dV_{out}}{dV_{in}} \right] \\ & - (V_{out} - V_{DD}) \frac{dV_{out}}{dV_{in}} \end{aligned} \quad (-1)$$



$$k'_n \left(\frac{W}{L} \right)_n (V_{IL} - V_{T0n}) = k'_p \left(\frac{W}{L} \right)_p [2V_{out} - V_{IL} + V_{T0p} - V_{DD}]$$

SOLVING FOR V_{IL}

$$V_{IL} = \frac{2V_{out} + V_{T0p} - V_{DD} + k_R V_{T0n}}{1 + k_R} \quad \text{where} \quad k_R = \frac{k'_n (W/L)_n}{k'_p (W/L)_p} \quad (5.62)$$

SOLVE Eqs (5.59) and (5.62) for V_{out} and V_{IL}

CALCULATE V_{IH}

  


$$I_{Dp} = I_{Dn}$$

$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n [2(V_{GSn} - V_{T0n})V_{DSn} - V_{DSn}^2] = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p (V_{GSp} - V_{T0p})^2$$


$$V_{GSn} = V_{in}, V_{DSn} = V_{out}, V_{GSp} = V_{in} - V_{DD}$$

$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n [2(V_{in} - V_{T0n})V_{out} - V_{out}^2] = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p (V_{in} - V_{DD} - V_{T0p})^2$$

CALCULATE V_{IH}

 

(D)

 

- nMOS is in linear region
- pMOS is in saturation region

$$I_{Dp} = I_{Dn}$$

$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n [2(V_{GSn} - V_{T0n})V_{DSn} - V_{DSn}^2] = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p (V_{GSp} - V_{T0p})^2$$

$$V_{GSn} = V_{in}, V_{DSn} = V_{out}, V_{GSp} = V_{in} - V_{DD}$$

$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n [2(V_{in} - V_{T0n})V_{out} - V_{out}^2] = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p (V_{in} - V_{DD} - V_{T0p})^2$$

$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n [2(V_{in} - V_{T0n})V_{out} - V_{out}^2] = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p (V_{in} - V_{DD} - V_{T0p})^2 \quad (5.64)$$

DIFFERENTIATING wrt V_{in}

$$k'_n \left(\frac{W}{L} \right)_n \left[(V_{in} - V_{T0n}) \frac{dV_{out}}{dV_{in}} + V_{out} - V_{out} \frac{dV_{out}}{dV_{in}} \right] = k'_p \left(\frac{W}{L} \right)_p (V_{in} - V_{DD} - V_{T0p})$$

$$k'_n \left(\frac{W}{L} \right)_n [-V_{IH} + V_{T0n} + 2V_{out}] = k'_p \left(\frac{W}{L} \right)_p (V_{IH} - V_{DD} - V_{T0p})$$

SOLVING FOR V_{IH}



$$V_{IH} = \frac{V_{DD} + V_{T0p} + k_R (2V_{out} + V_{T0n})}{1 + k_R} \quad (5.67)$$

where

$$k_R = \frac{k'_n (W/L)_n}{k'_p (W/L)_p}$$

SOLVE Eqs. (5.64) and (5.67) for V_{out} and V_{IH}

CALCULATE V_{th}

  



$$I_{Dp} = I_{Dn}$$

$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n (V_{GSn} - V_{T0n})^2 = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p (V_{GSp} - V_{T0p})^2$$

$$V_{GSn} = V_{in}, \quad V_{GSp} = V_{in} - V_{DD}$$

$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n (V_{in} - V_{T0n})^2 = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p (V_{in} - V_{DD} - V_{T0p})^2$$

CALCULATE V_{th}

  

- nMOS is in saturation region
- pMOS is in saturation region


$$I_{Dp} = I_{Dn}$$

$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n (V_{GSn} - V_{T0n})^2 = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p (V_{GSp} - V_{T0p})^2$$

$$V_{GSn} = V_{in}, \quad V_{GSp} = V_{in} - V_{DD}$$


$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n (V_{in} - V_{T0n})^2 = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p (V_{in} - V_{DD} - V_{T0p})^2$$

POWER SUPPLY CURRENT VS V_{IN}

 

$I_D = 0, V_{in} < V_{T0n}$
 $I_D = 0, V_{in} > V_{DD} + V_{T0p}$
 $I_D = \text{MAX}, V_{in} = V_{th}$

POWER SUPPLY CURRENT VS V_{IN}

 

$$I_D = 0, V_{in} < V_{T0n}$$

$$I_D = 0, V_{in} > V_{DD} + V_{T0p}$$

$$I_D = \text{MAX}, V_{in} = V_{th}$$

Almost all power is dissipated during the switching!

DESIGN OF CMOS INVERTERS

$$V_{in} = V_{th} = \frac{V_{T0n} + \sqrt{\frac{1}{k_R}} (V_{DD} + V_{T0p})}{\left(1 + \sqrt{\frac{1}{k_R}}\right)}$$

SOLVING FOR k_R

$$k_R = \left(\frac{V_{DD} + V_{T0p} - V_{th}}{V_{th} - V_{T0n}} \right)^2$$

FOR IDEAL INVERTER $V_{th} = \frac{1}{2} V_{DD}$

$$(k_R)_{ideal} = \left(\frac{0.5 V_{DD} + V_{T0p}}{0.5 V_{DD} - V_{T0n}} \right)^2$$

IF $V_{T0} = V_{T0n} = -V_{T0p} \Rightarrow (k_R)_{symmetric\ inverter} = 1$

$$k_R = \frac{k'_n (W/L)_n}{k'_p (W/L)_p} = \frac{\mu_n C_{ox} (W/L)_n}{\mu_p C_{ox} (W/L)_p} = \frac{\mu_n (W/L)_n}{\mu_p (W/L)_p}$$

FOR SYMMETRIC INVERTER $V_{T0} = V_{T0n} = -V_{T0p}$ $(k_R)_{\text{symmetric inverter}} = 1$

$$\frac{(W/L)_n}{(W/L)_p} = k_R \frac{\mu_p}{\mu_n} \xrightarrow{k_R=1} \frac{(W/L)_n}{(W/L)_p} = \frac{\mu_p}{\mu_n}$$

$$\frac{(W/L)_n}{(W/L)_p} = \frac{\mu_p}{\mu_n} = \frac{230 \text{ cm}^2/\text{Vs}}{580 \text{ cm}^2/\text{Vs}} \rightarrow \frac{(W/L)_p}{(W/L)_n} = 2.5$$

$$V_{IL} = \frac{1}{8}(3V_{DD} + 2V_{T0})$$

solve eqs. (5.59) and (5.62)

$$V_{IH} = \frac{1}{8}(5V_{DD} - 2V_{T0})$$


solve eqs. (5.64) and (5.67)

NOTE: $V_{IL} + V_{IH} = V_{DD}$



$$NM_H = V_{OH} - V_{IH} = V_{DD} - V_{IH} = (3/8)V_{DD} + (2/8)V_{T0}$$

$$NM_L = V_{IL} - V_{OL} = V_{IL} = (3/8)V_{DD} + (2/8)V_{T0}$$

 VTC for three CMOS inverters with different nMOS-pMOS ratios



POWER DISSIPATION CONSIDERATIONS

  

$$P_{DC} = \frac{V_{DD}}{2} [I_{DC}(V_{in} = "0") + I_{DC}(V_{in} = "1")] = \frac{P(V_{in} = 0) + P(V_{in} = 1)}{2}$$

WHEN $V_{in} = V_{OL}$: $I_L = I_D = 0 \Rightarrow P(V_{in} = 0) = 0$

WHEN $V_{in} = V_{OH}$: $I_L = I_D = 0 \Rightarrow P(V_{in} = 1) = 0$


$P_{DC} = 0$

Minimum Area MOS Transistor Layouts

COLOR LEGEND


- n-Well
- p-Well
- n⁺
- Polysilicon
- p⁺
- Gate Oxide
- Field Oxide
- Metal 1
- Metal 2
- Metal 3
- Contact/via

Minimum pMOS Layout

 


$$Area = 24 \cdot 13 \lambda^2 = 312 \lambda^2$$


Minimum nMOS Layout

 
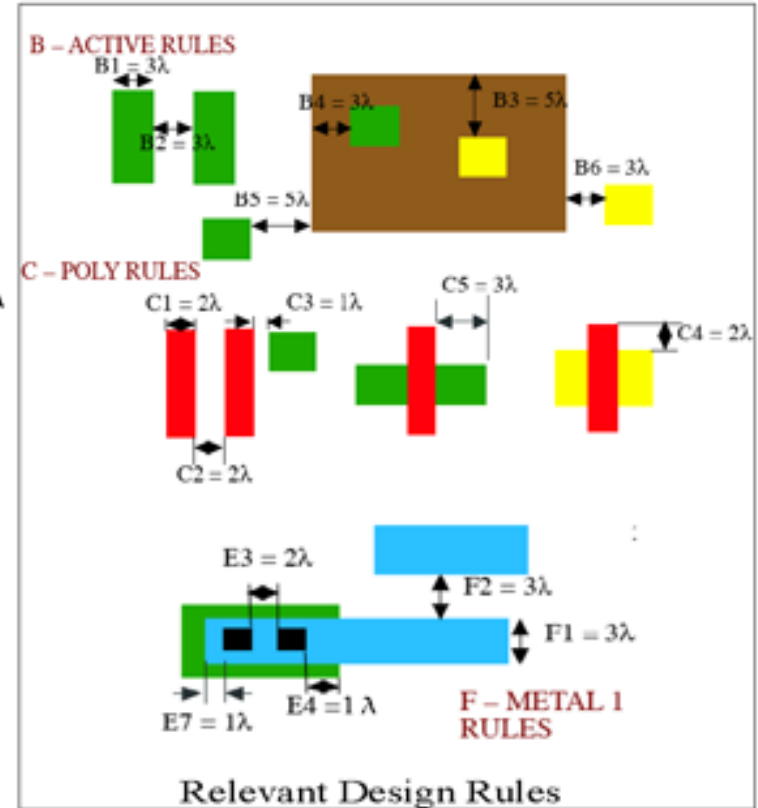
$$Area = 16 \cdot 7 \lambda^2 = 112 \lambda^2$$




Digital IC Design and Architecture

 

Resistive Load Inverter

RESISTIVE-LOAD INVERTER

 

$$V_{BS} = 0 \Rightarrow V_{T,n} = V_{T0,n}$$

Let (for hand calculations) $\lambda = 0$

Units

$$k_n = \left(\frac{\text{cm}^2}{\text{Vsec}} \right) \left(\frac{\text{F}}{\text{cm}^2} \right) = \left(\frac{\text{cm}^{-1}}{\text{Vsec}} \right) \left(\frac{\text{C}}{\text{Vcm}^2} \right)$$

$$= \left(\frac{\text{C/sec}}{\text{V}^2} \right) = \frac{\text{A}}{\text{V}^2}$$

CUTOFF: $V_{in} = V_{GS} < V_{T0,n}$, $I_D = 0$

LINEAR: $V_{in} = V_{GS} \geq V_{T0,n}$
 $V_{out} = V_{DS} \leq V_{in} - V_{T0,n}$

$$I_D = \frac{k_n}{2} \left[2(V_{in} - V_{T0,n}) V_{out} - V_{out}^2 \right]$$

SATURATION:

$$V_{in} = V_{GS} \geq V_{T0,n}$$



$$V_{out} = V_{DS} > V_{in} - V_{T0,n}$$

$$I_D = \frac{k_n}{2} (V_{in} - V_{T0,n})^2$$

Where: $k_n = \mu_n C_{ox} \frac{W}{L}$

RESISTOR R_L :

$$I_L = \frac{V_{DD} - V_{out}}{R_L}$$

 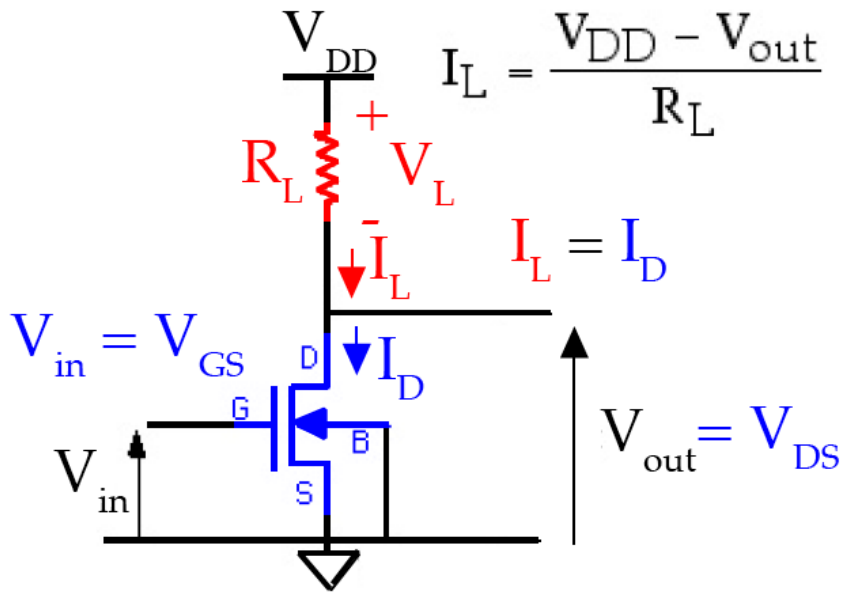




CALCULATION OF V_{OH} : (A)

$$V_{out} = V_{DD} - R_L I_L$$


$V_{in} < V_{T0,n} \Rightarrow$ nMOS Cut-off
 
$$I_D = I_L = 0 \Rightarrow V_{OH} = V_{DD}$$



  


CALCULATION OF V_{OL} : (C)

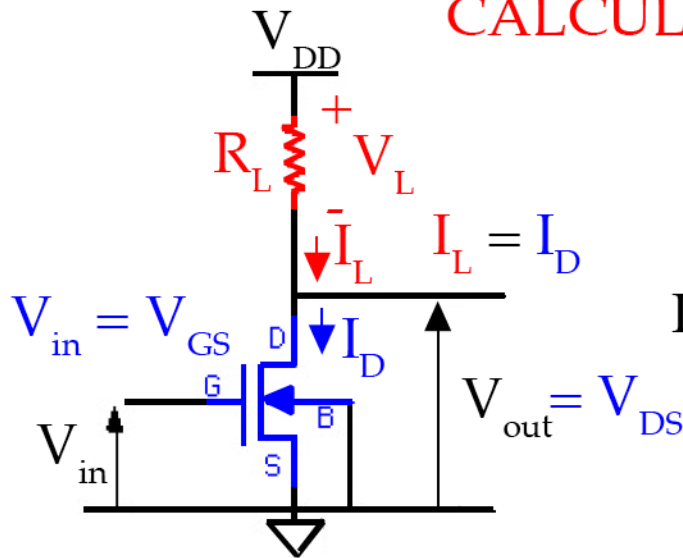

$$I_L = \frac{V_{DD} - V_{out}}{R_L}$$
 
$$I_D = \frac{k_n}{2} [2(V_{in} - V_{T0,n}) V_{out} - V_{out}^2]$$



$$I_L = I_D$$


$$\frac{V_{DD} - V_{OL}}{R_L} = \frac{k_n}{2} [2(V_{DD} - V_{T0,n}) V_{OL} - V_{OL}^2] \quad \begin{array}{l} \text{where } V_{in} = V_{OH} = V_{DD} \\ \text{where } V_{out} = V_{OL} \end{array}$$

$$V_{OL}^2 - 2 \left(V_{DD} - V_{T0,n} + \frac{1}{k_n R_L} \right) V_{OL} + \frac{2}{k_n R_L} V_{DD} = 0$$

$$\underline{0 < V_{OL} < V_{T0,n}}$$

$$V_{OL} = V_{DD} - V_{T0,n} + \frac{1}{k_n R_L} \pm \sqrt{\left(V_{DD} - V_{T0,n} + \frac{1}{k_n R_L} \right)^2 - \frac{2}{k_n R_L} V_{DD}}$$

CALCULATION OF V_{IL} : (B)

 

$I_L = I_D$

$$\frac{V_{DD} - V_{out}(V_{in})}{R_L} = \frac{k_n}{2} (V_{in} - V_{T0,n})^2$$


Differentiate wrt to V_{in} , i.e.

$$-\frac{1}{R_L} \frac{dV_{out}}{dV_{in}} = k_n (V_{in} - V_{T0,n})$$

$$\frac{dV_{out}}{dV_{in}} = -1 \quad @ \quad V_{in} = V_{IL} \quad \longrightarrow \quad -\frac{1}{R_L} (-1) = k_n (V_{IL} - V_{T0,n})$$

$\Rightarrow V_{out} \approx V_{OH}$
 
$$V_{IL} = V_{T0,n} + \frac{1}{k_n R_L}$$





Find V_{out} (when $V_{in} = V_{IL}$):

$$\frac{V_{DD} - V_{out}(V_{in} = V_{IL})}{R_L} = \frac{k_n}{2} (V_{IL} - V_{T0,n})^2$$

$$V_{out}(V_{in} = V_{IL}) = V_{DD} - \frac{1}{2k_n R_L}$$

CALCULATION OF V_{IH} : (C)

  

$$\frac{dV_{out}}{dV_{in}} = -1 \quad @ \quad V_{in} = V_{IH}$$

$$\Rightarrow V_{out} \approx V_{OL}$$


$$I_L = I_D \rightarrow \frac{V_{DD} - V_{out}}{R_L} = \frac{k_n}{2} [2(V_{in} - V_{T0,n}) V_{out} - V_{out}^2]$$

Differentiate wrt to V_{in} , i.e.

$$-\frac{1}{R_L} \frac{dV_{out}}{dV_{in}} = \frac{k_n}{2} \left[2(V_{in} - V_{T0,n}) \frac{dV_{out}}{dV_{in}} + 2V_{out} - 2V_{out} \frac{dV_{out}}{dV_{in}} \right]$$

$$V_{IH} = V_{T0,n} + 2V_{out} - \frac{1}{k_n R_L}$$

CALCULATION OF V_{IH} : (C)

 

Find V_{out} ($V_{in} = V_{IH}$):

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{k_n}{2} [2(V_{IH} - V_{T0,n}) V_{out} - V_{out}^2]$$

where

$$V_{IH} = V_{T0,n} + 2V_{out} - \frac{1}{k_n R_L}$$

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{k_n}{2} \left[2(V_{T0,n} + 2V_{out} - \frac{1}{k_n R_L} - V_{T0,n}) V_{out} - V_{out}^2 \right]$$

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{k_n}{2} \left[3V_{out}^2 - \frac{2V_{out}}{k_n R_L} \right]$$

$$\frac{V_{DD}}{R_L} = \frac{3}{2} k_n V_{out}^2$$

$$V_{out} (V_{in} = V_{IH}) = \sqrt{\frac{2}{3} \frac{V_{DD}}{k_n R_L}}$$

$$V_{IH} = V_{T0,n} + 2 \sqrt{\frac{2}{3} \frac{V_{DD}}{k_n R_L}} - \frac{1}{k_n R_L}$$

CALCULATION OF V_{th} :

$$V_{in} = V_{out} = V_{th} \Rightarrow V_{DS} = V_{GS} > V_{GS} - V_{T0,n} \longrightarrow \textcircled{B}$$

$$I_L = I_D \rightarrow \frac{V_{DD} - V_{out}}{R_L} = \frac{k_n}{2} (V_{in} - V_{T0,n})^2$$

$$\frac{V_{DD} - V_{th}}{R_L} = \frac{k_n}{2} (V_{th} - V_{T0,n})^2$$

$$V_{th}^2 - 2 \left(V_{T0,n} - \frac{1}{k_n R_L} \right) V_{th} + V_{T0,n}^2 - \frac{2V_{DD}}{k_n R_L} = 0$$

$$V_{th} = V_{T0,n} - \frac{1}{k_n R_L} \pm \sqrt{\left(V_{T0,n} - \frac{1}{k_n R_L} \right)^2 + \frac{2V_{DD}}{k_n R_L} - V_{T0,n}^2}$$

SUMMARY - RESISTIVE LOAD INVERTER

$$\rightarrow V_{th} = V_{T0,n} - \frac{1}{k_n R_L} + \sqrt{\left(V_{T0,n} - \frac{1}{k_n R_L} \right)^2 + \frac{2 V_{DD}}{k_n R_L} - V_{T0,n}^2}$$

$$\rightarrow V_{IL} = V_{T0,n} + \frac{1}{k_n R_L} \quad V_{out}(V_{in} = V_{IL}) = V_{DD} - \frac{1}{2 k_n R_L}$$

$$\rightarrow V_{IH} = V_{T0,n} + 2 \sqrt{\frac{2}{3} \frac{V_{DD}}{k_n R_L} - \frac{1}{k_n R_L}} \quad V_{out}(V_{in} = V_{IH}) = \sqrt{\frac{2}{3} \frac{V_{DD}}{k_n R_L}}$$

$$\rightarrow V_{OL} = V_{DD} - V_{T0,n} + \frac{1}{k_n R_L} \pm \sqrt{\left(V_{DD} - V_{T0,n} + \frac{1}{k_n R_L} \right)^2 - \frac{2}{k_n R_L} V_{DD}}$$


$$\rightarrow V_{OH} = V_{DD}$$

$$V_{DD} = 5V$$

$$V_{T0,n} = 1V$$

Units
 
$$k_n R_L = \left(\frac{A}{V^2} \right) \left(\frac{V}{A} \right) = V^{-1}$$



$$P_{DC} = \frac{V_{DD}}{2} [I_{DC}(V_{in} = "0") + I_{DC}(V_{in} = "1")]$$

WHEN $V_{in} = V_{OL}$: DRIVER nMOS in CUT-OFF


$$I_L = I_D = 0 \Rightarrow P(V_{in} = 0) = 0$$

WHEN $V_{in} = V_{OH}$:

$$I_{DC}(V_{in} = "1") = I_L = I_D = \frac{V_{DD} - V_{OL}}{R_L}$$

$$P(V_{in} = "1") = \frac{V_{DD}}{2} \frac{V_{DD} - V_{OL}}{R_L}$$
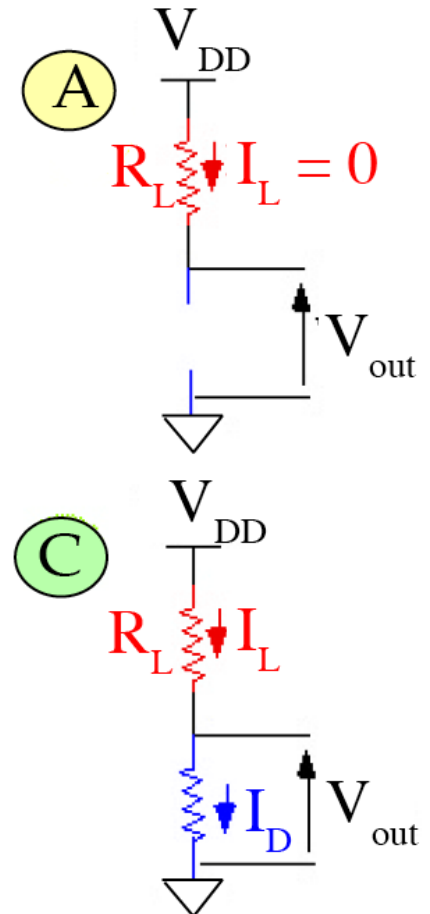
$$P_{DC}(\text{average}) = \frac{V_{DD}}{2} \frac{V_{DD} - V_{OL}}{R_L}$$



Two examples of resistive load inverter layout are shown below:


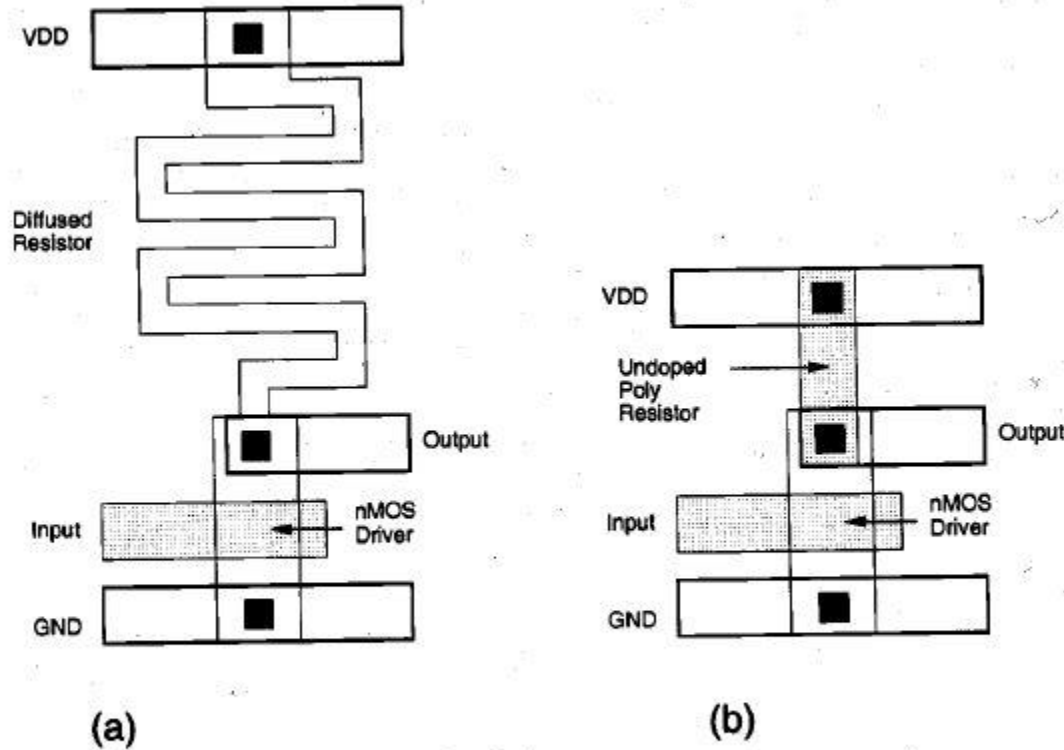




Figure 5.10. Sample layout of resistive-load inverter circuits with (a) diffused resistor and (b) undoped polysilicon resistor.

Digital IC Design and Architecture

 

Saturated Enhancement Load Inverter



SATURATED ENHANCEMENT-LOAD INVERTER

  

LOAD:

$V_{GS,L} = V_{DS,L} \Rightarrow V_{DS,L} > V_{GS,L} - V_{T,L}$ SAT cond. is ALWAYS SATISFIED
 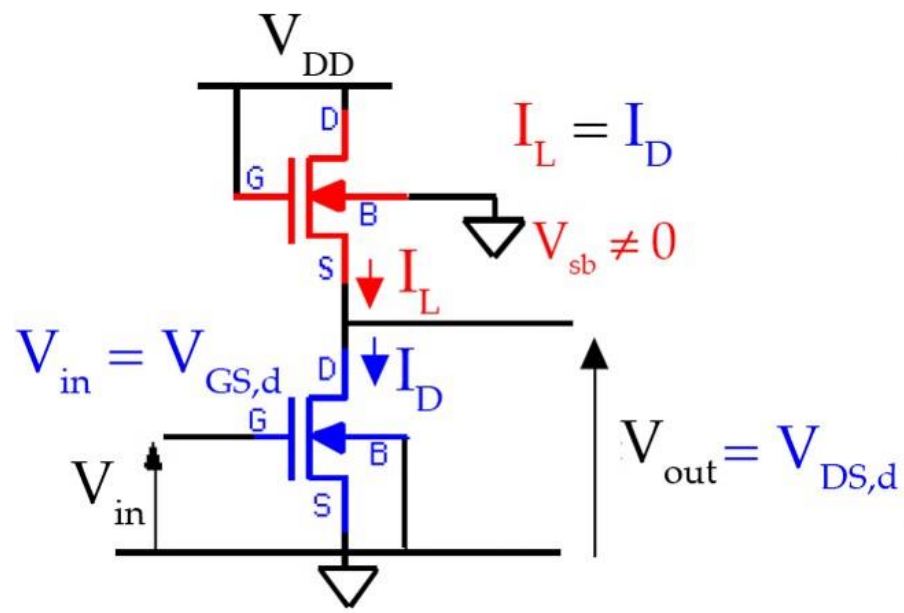
$$I_L = \frac{k'_n}{2} \left(\frac{W}{L} \right)_L (V_{GS,L} - V_{T,L})^2 = \frac{k'_n}{2} \left(\frac{W}{L} \right)_L (V_{DD} - V_{out} - V_{T,L})^2$$



Load -> Sat, Driver -> Cutoff (A)

$$\frac{k'_n}{2} \left(\frac{W}{L}\right)_L (V_{DD} - V_{out} - V_{T.L})^2 = 0$$

Load -> Sat, Driver -> Sat (B)

$$\frac{k'_n}{2} \left(\frac{W}{L}\right)_L (V_{DD} - V_{out} - V_{T.L})^2 = \frac{k'_n}{2} \left(\frac{W}{L}\right)_d (V_{in} - V_{T0,n})^2$$

Load -> Sat, Driver -> Lin (C)

$$\frac{k'_n}{2} \left(\frac{W}{L}\right)_L (V_{DD} - V_{out} - V_{T.L})^2 = \frac{k'_n}{2} \left(\frac{W}{L}\right)_d (2[V_{in} - V_{T0,n}]V_{out} - V_{out}^2)$$

$$\begin{aligned} V_{OH} &< V_{DD} \\ V_{OL} &> 0 \end{aligned}$$

- Saturated Enhancement Load Inverters require relatively high stand-by DC power dissipation
- Because of this high stand-by DC power dissipation the Enhancement-load nMOS inverters are not used in any large-scale digital applications

Textbook examples to be reviewed:

Examples 5.1 and 5.2 – Resistive Load Inverter

Example 5.4 – nMOS with pMOS Load Inverter