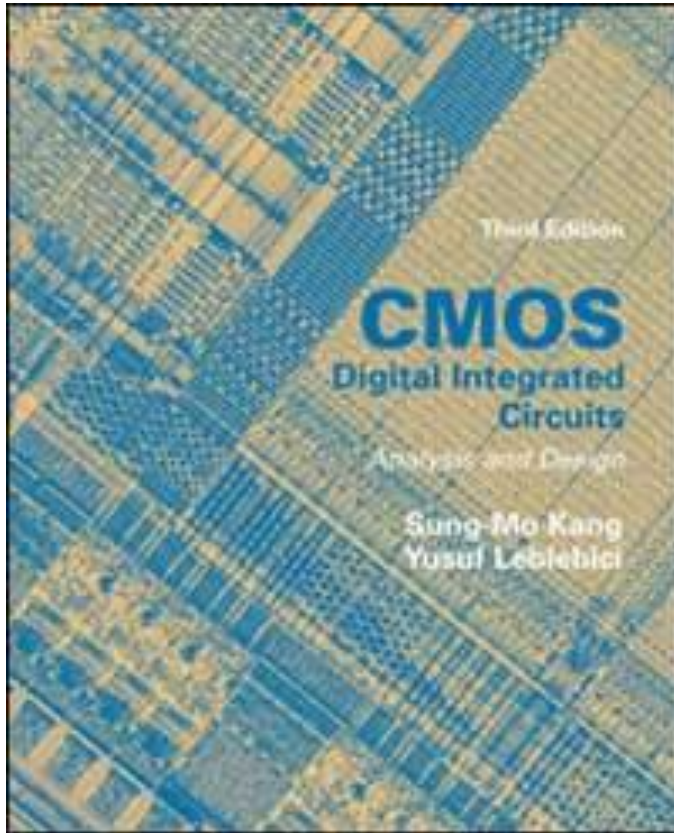


# Digital IC Design and Architecture




## Combinational Logic and Circuits

# Static CMOS Circuit

At every point in time (except during the switching transients) each **gate output is connected to either  $V_{DD}$  or  $V_{SS}$**  via a low-resistive path.


The outputs of the gates **assume at all times the value of the Boolean function**, implemented by the circuit (ignoring, once again, the transient effects during switching periods).

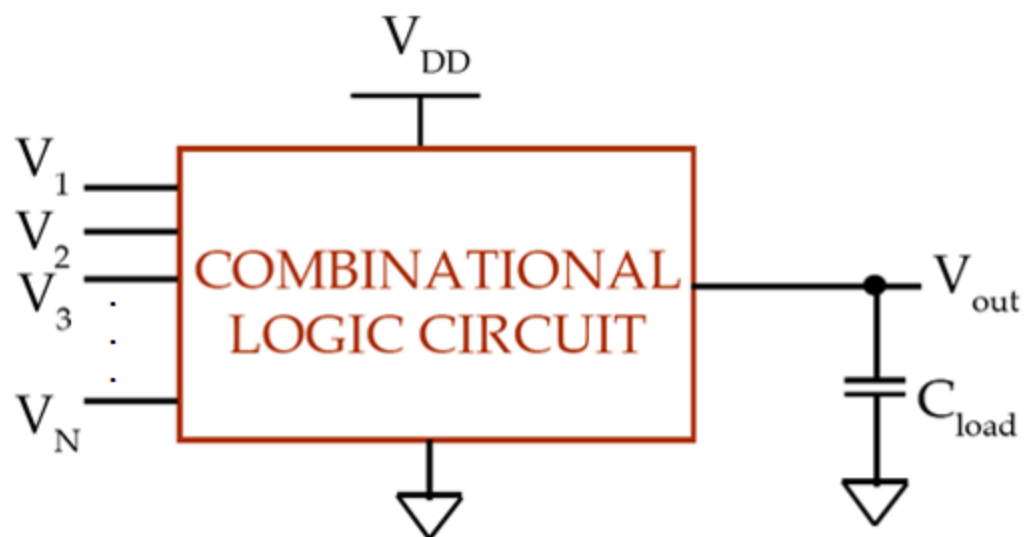This is in contrast to the **dynamic** circuit class, which relies on temporary storage of signal values on the capacitance of high impedance circuit nodes.




$V_{out}$  is Boolean function of inputs,  $V_1, V_2, V_3, \dots, V_N$ .

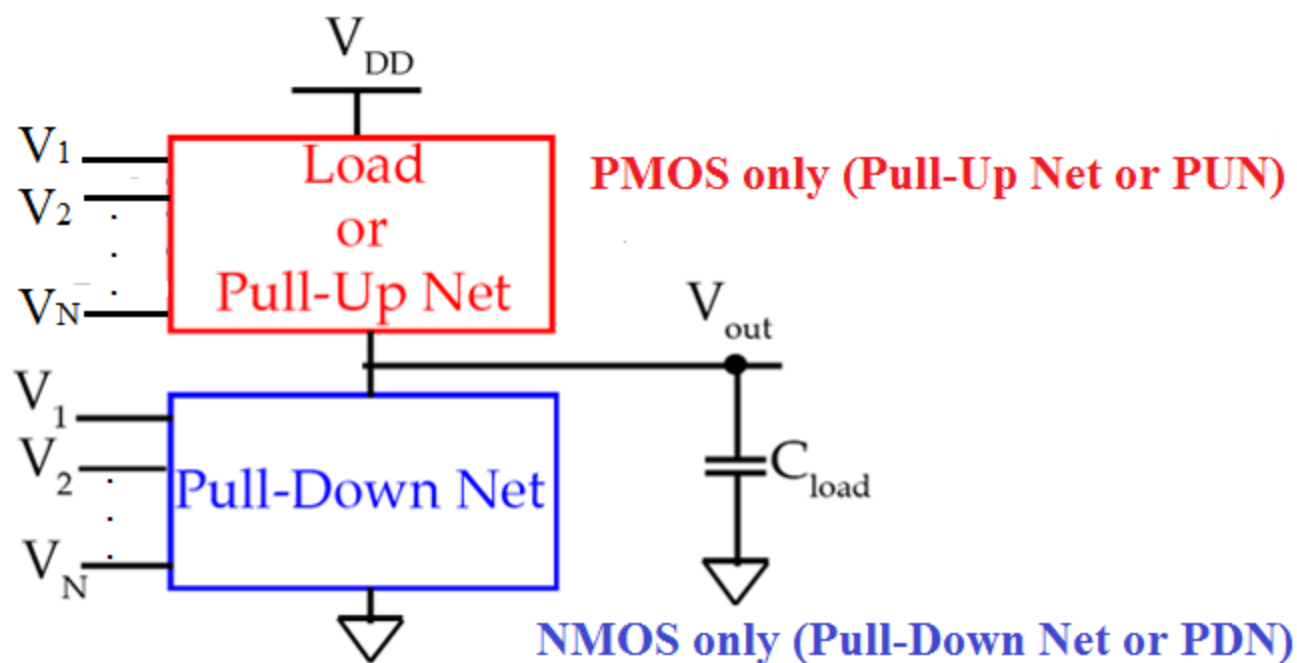"1"  $\Rightarrow V_{DD}$   
 "0"  $\Rightarrow 0$



# Static Complementary CMOS


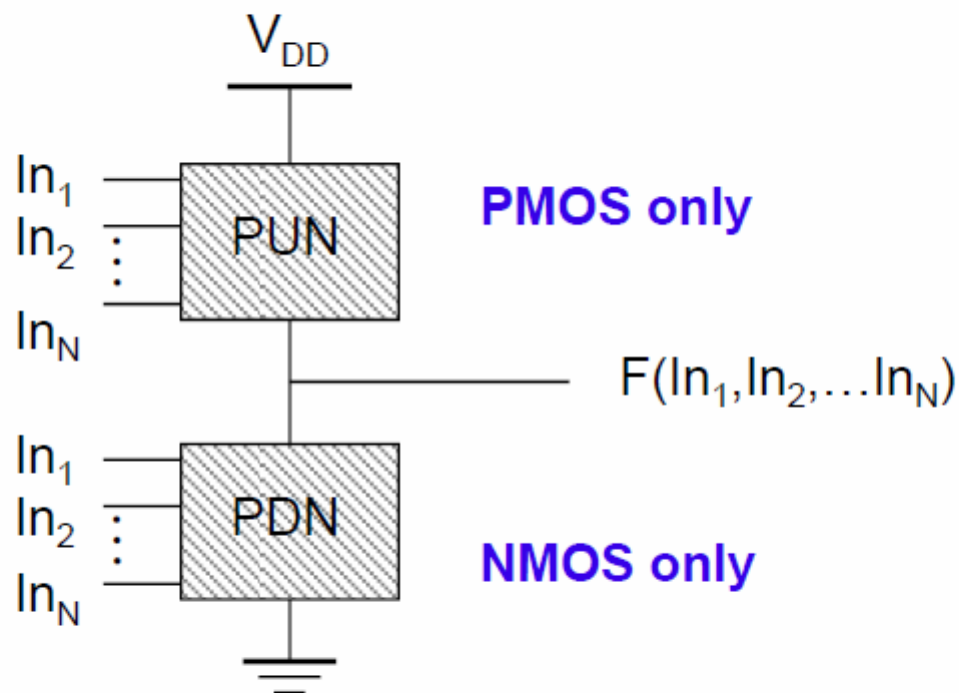


- ◆ PUN and PDN are **dual** logic networks
- ◆ PUN and PDN functions are **complementary**

# NMOS Transistors in Series/Parallel Connection

**Transistors can be thought as a switch controlled by its gate signal**

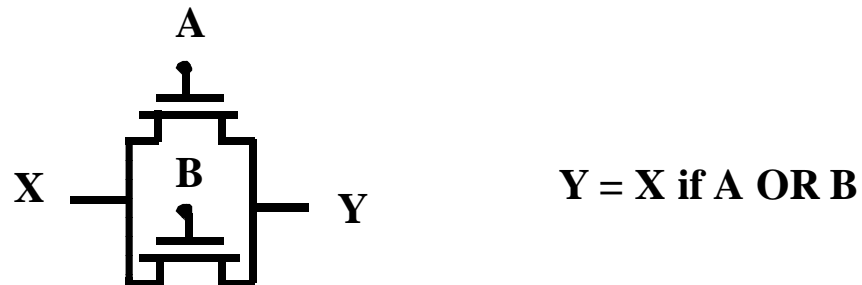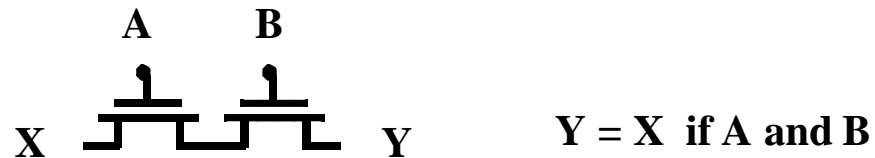**NMOS switch closes when switch control input is high**





**NMOS Transistors pass a “strong” 0 but a “weak” 1**

# PMOS Transistors
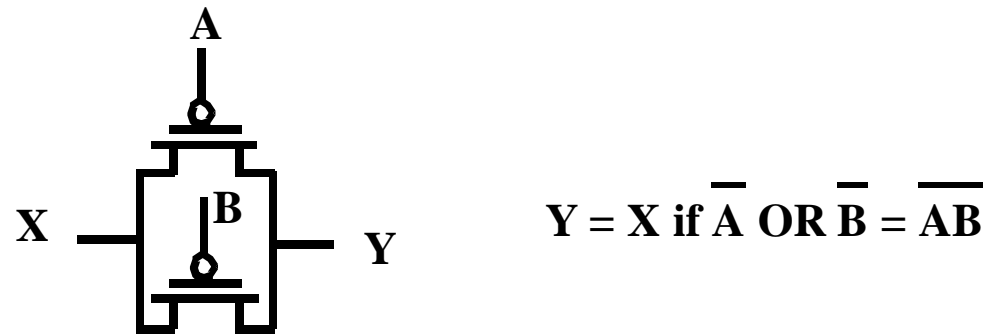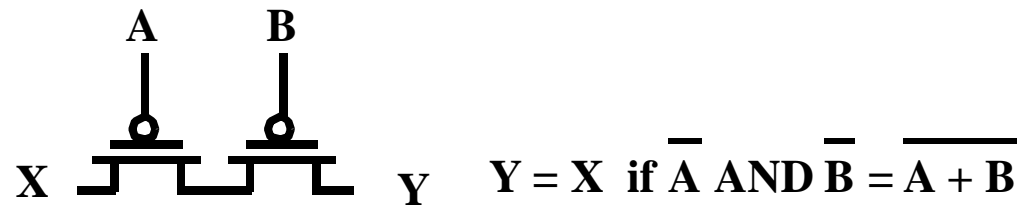
## in Series/Parallel Connection



PMOS switch closes when switch control input is low





PMOS Transistors pass a “strong” 1 but a “weak” 0

# Threshold Drops

## PUN – Pull Up Network

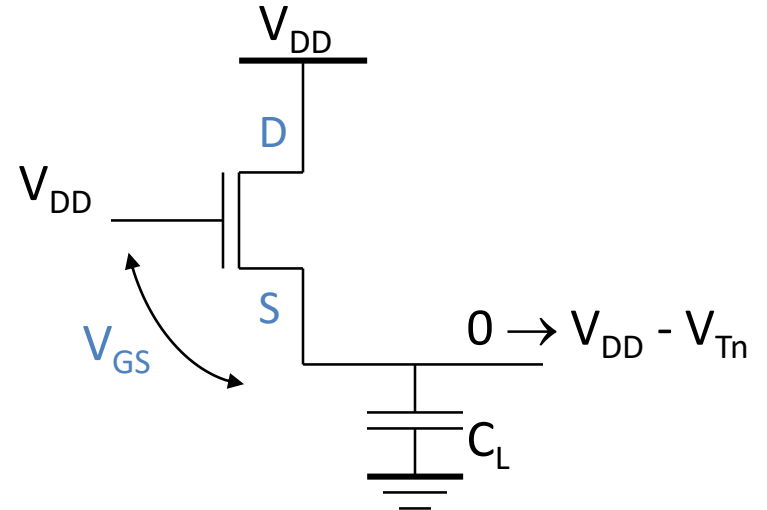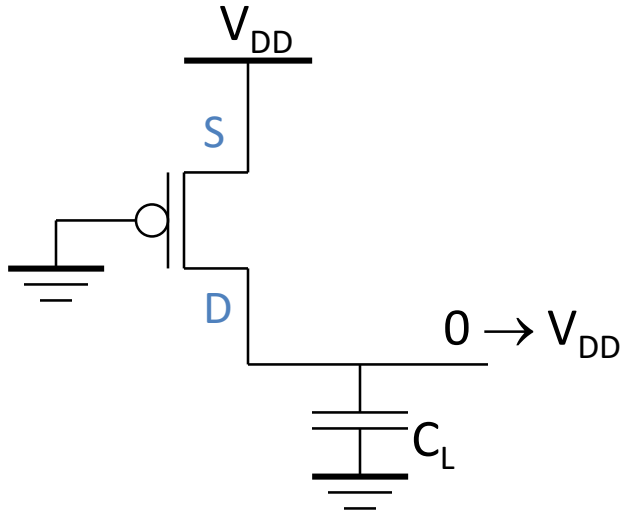

## PDN – Pull Down Network

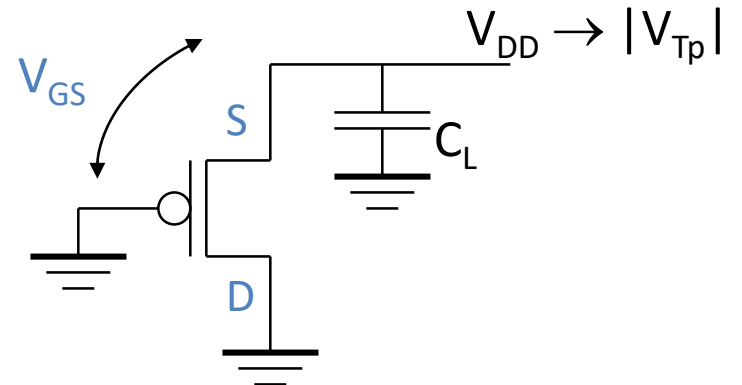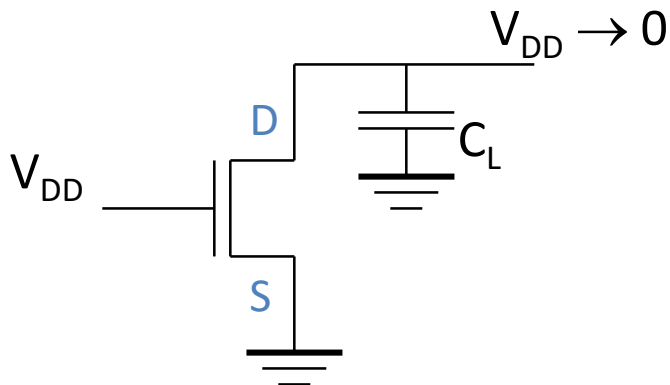


# Complementary CMOS Logic Style

- **PUP is the DUAL of PDN**  
(can be shown using DeMorgan's Theorem's)

$$\overline{A + B} = \bar{A}\bar{B}$$

$$\overline{AB} = \bar{A} + \bar{B}$$

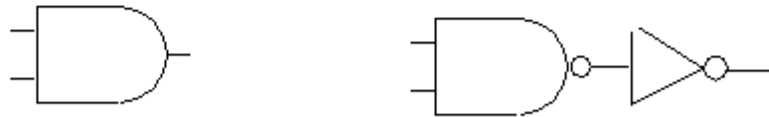- **The complementary gate is inverting**




**AND = NAND + INV**



# Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

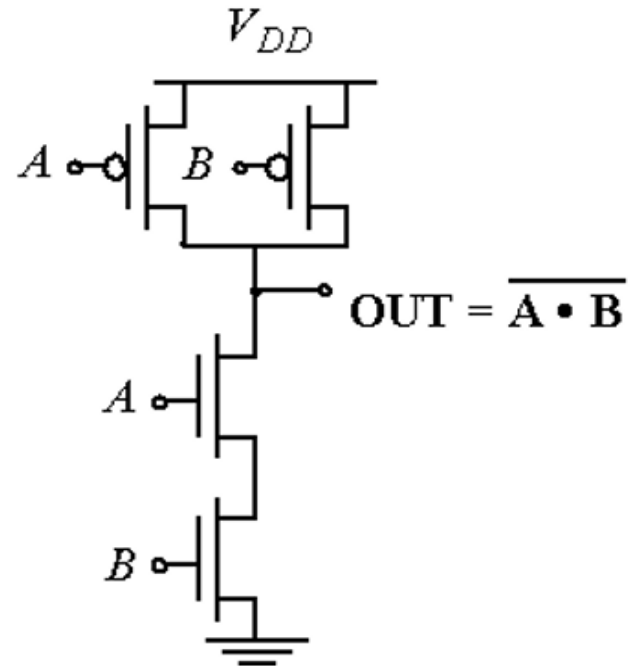

**PDN:**  $G = A B \Rightarrow$  Conduction to GND


**PUN:**  $F = \overline{A} + \overline{B} = \overline{AB} \Rightarrow$  Conduction to  $V_{DD}$

$$\overline{G(In_1, In_2, In_3, \dots)} \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$$


# Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


Truth Table of a 2 input NOR gate

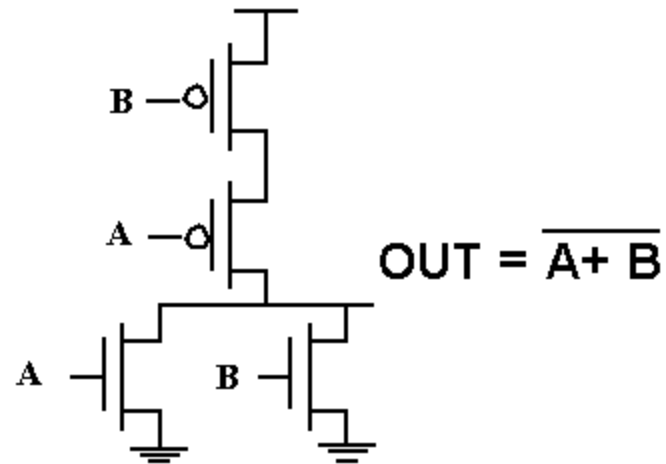

# Complex CMOS Gate

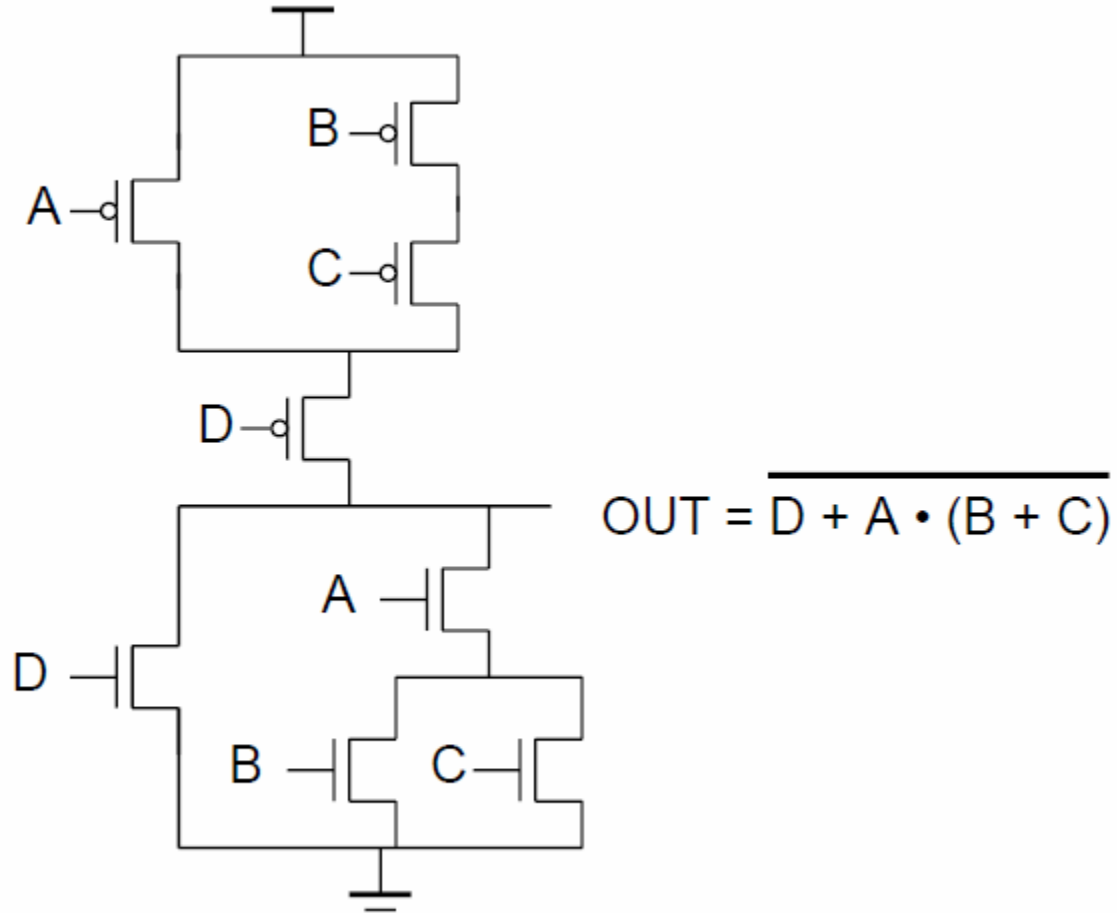



# Digital IC Design and Architecture

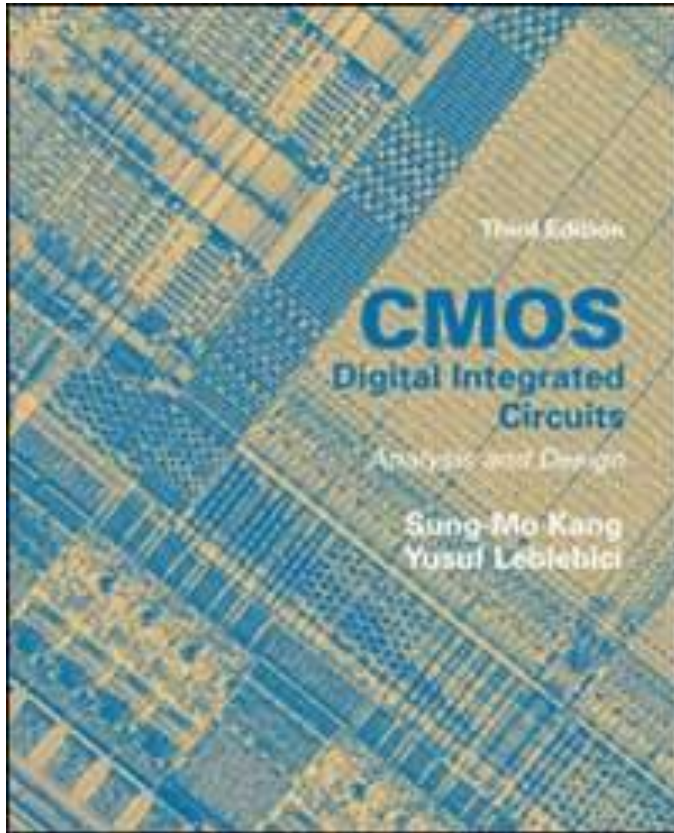

## Combinational Logic: CMOS Implementation


# CMOS LOGIC GATES

## 2-INPUT NOR (NR2)

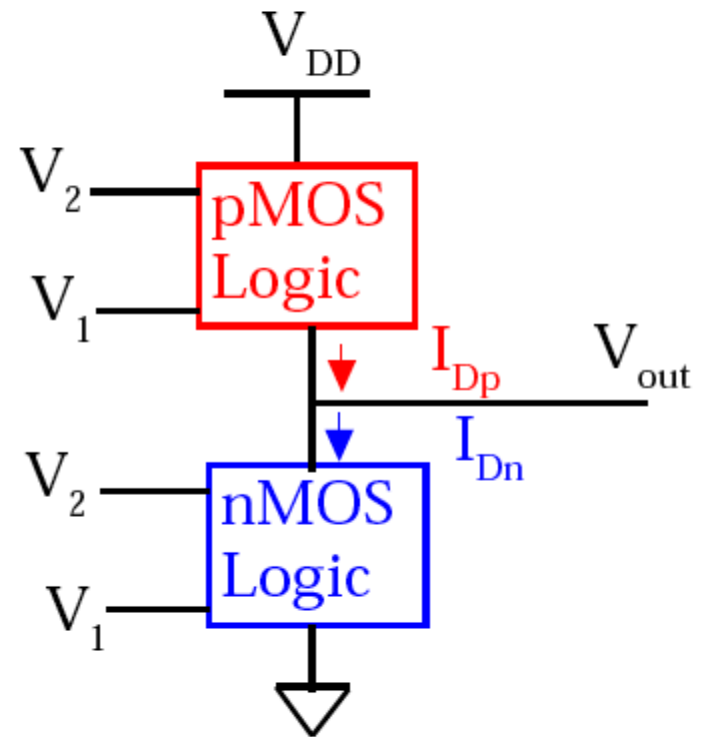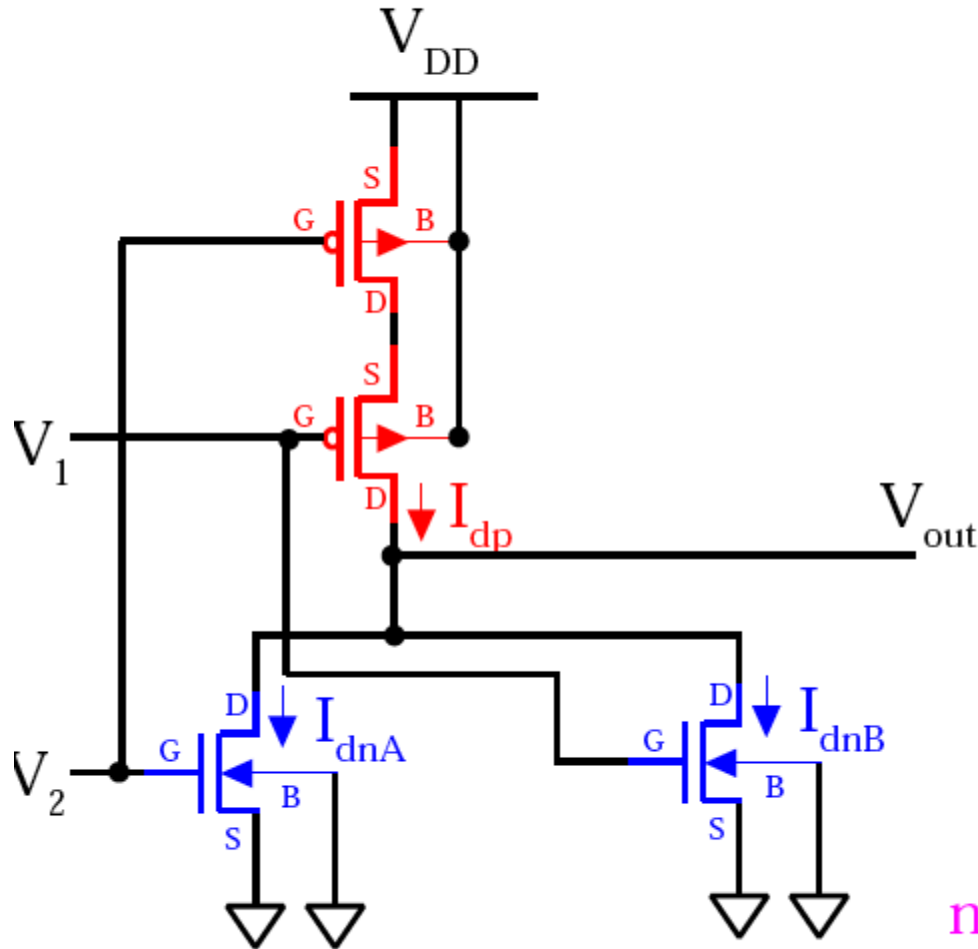


nMOS Net ON, pMOS Net OFF  
or  
nMOS Net OFF, pMOS Net ON

# CMOS NR2

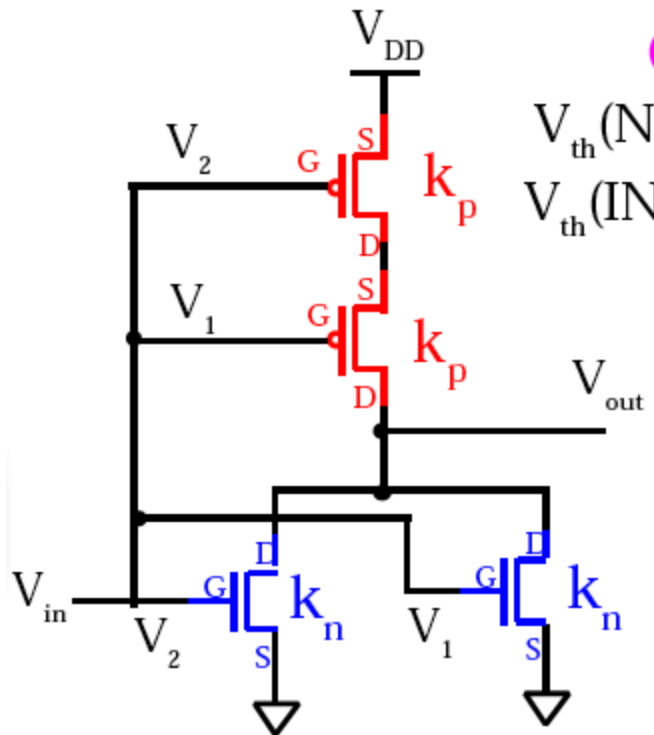

$$V_{th}(NR2) \Rightarrow V_1 = V_2 = V_{out}$$

$$V_{th}(INV) = V_{in} = V_{out}$$

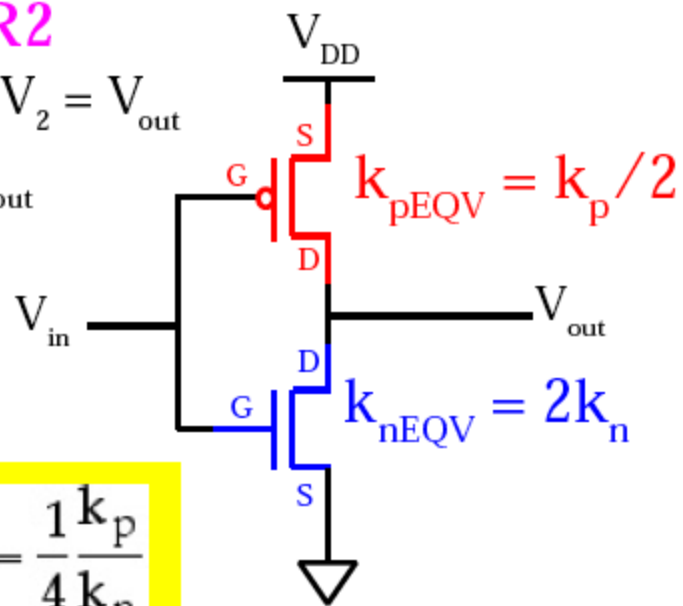

$$\frac{k_{pEQV}}{k_{nEQV}} = \frac{1 k_p}{4 k_n}$$

$$V_{th}(NOR2) = \frac{V_{Tn} + \frac{1}{2} \sqrt{\frac{k_p}{k_n}} (V_{DD} + V_{Tp})}{1 + \frac{1}{2} \sqrt{\frac{k_p}{k_n}}}$$


$$V_{th}(INV) = \frac{V_{Tn} + \sqrt{\frac{k_{pEQV}}{k_{nEQV}}} (V_{DD} + V_{Tp})}{1 + \sqrt{\frac{k_{pEQV}}{k_{nEQV}}}}$$

## Symmetrical EQUIV INV

$$k_{pEQV} = k_{nEQV} \text{ or } k_{pEQV}/k_{nEQV} = 1 \text{ and } V_{Tn} = |V_{Tp}| \Rightarrow V_{th}(INV) = V_{DD}/2$$

$$V_{th}(NR2) = V_{DD}/2 \Rightarrow k_p = 4k_n$$
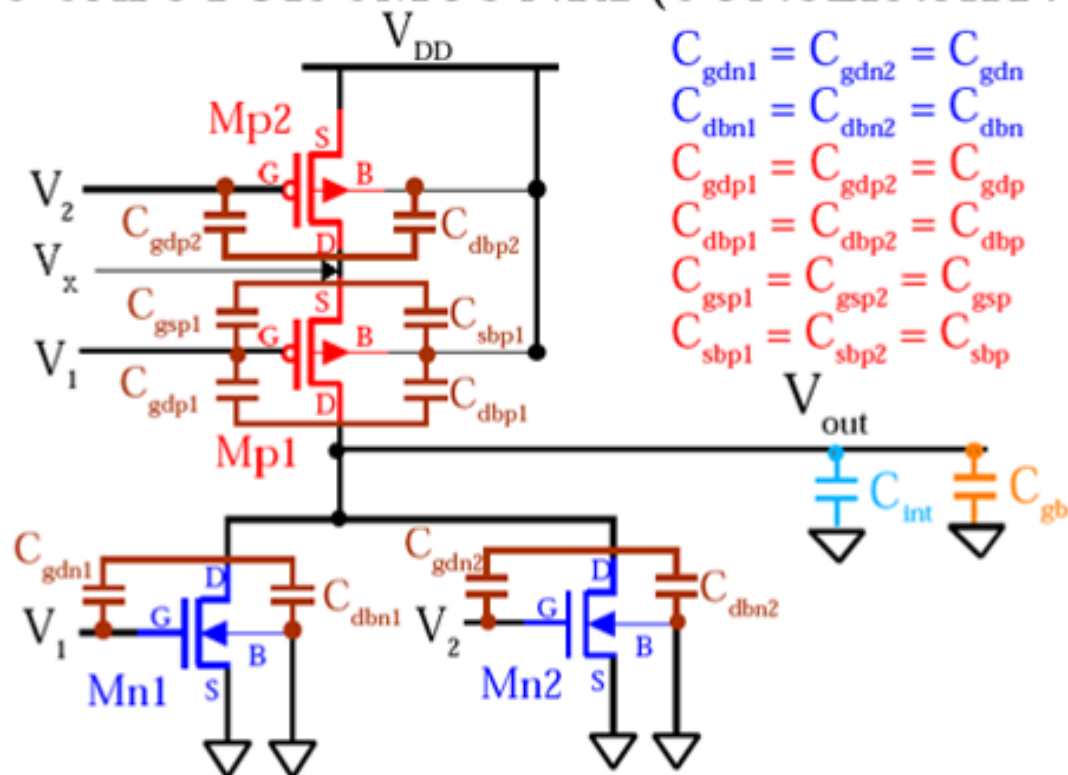
# PARASITIC CAPS FOR CMOS NR2 (CONSERVATIVE)



WORST CASE for PULL-UP  $\Rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$  &  $V_x = \text{low} \rightarrow \text{high}$

$$C_{\text{load-NR2}} \approx 2C_{dbn} + 2C_{dbp} + C_{sbp} + C_{\text{int}} + C_{gb} = 2C_{dbn} + 3C_{dbp} + C_{\text{int}} + C_{gb}$$

WORST CASE for PULL-DOWN  $\Rightarrow V_1 = 0, V_2 = 0 \rightarrow V_{DD}$  &  $V_x = \text{high} \rightarrow \text{low}$

$$C_{\text{load-NR2}} \approx 2C_{dbn} + 2C_{dbp} + C_{sbp} + C_{\text{int}} + C_{gb} = 2C_{dbn} + 3C_{dbp} + C_{\text{int}} + C_{gb}$$

NRn:  $C_{\text{load-NRn}} \approx nC_{dbn} + (2n-1)C_{dbp} + C_{\text{int}} + C_{gb}$

NR2:

1. Symmetric Inverter  $V_{th} = V_{DD}/2$ :

$$V_{th}(NR2) = V_{DD}/2 \Rightarrow k_p = 4k_n$$

2. Propagation delay  $\tau_{PHL}$  or  $\tau_{PLH}$ :

$$\tau_{PHL-NR2} \approx \frac{C_{load-NR2}}{2k_n(V_{DD}-V_{T0n})} \left[ \frac{2V_{T0n}}{V_{DD}-V_{T0n}} + \ln \left( \frac{4(V_{DD}-V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH-NR2} \approx \frac{C_{load-NR2}}{\frac{k_p(V_{DD}-|V_{T0p}|)}{2}} \left[ \frac{2|V_{T0p}|}{V_{DD}-|V_{T0p}|} + \ln \left( \frac{4(V_{DD}-|V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

NRn:

1. Symmetric Inverter  $V_{th} = V_{DD}/2$ :

$$V_{th}(NRn) = V_{DD}/2 \Rightarrow k_p = n^2k_n$$


2. Propagation delay  $\tau_{PHL}$  or  $\tau_{PLH}$ :

$$\tau_{PHL-NRn} \approx \frac{C_{load-NRn}}{nk_n(V_{DD}-V_{T0n})} \left[ \frac{2V_{T0n}}{V_{DD}-V_{T0n}} + \ln \left( \frac{4(V_{DD}-V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH-NRn} \approx \frac{C_{load-NRn}}{\frac{k_p(V_{DD}-|V_{T0p}|)}{n}} \left[ \frac{2|V_{T0p}|}{V_{DD}-|V_{T0p}|} + \ln \left( \frac{4(V_{DD}-|V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$




## CMOS ND2

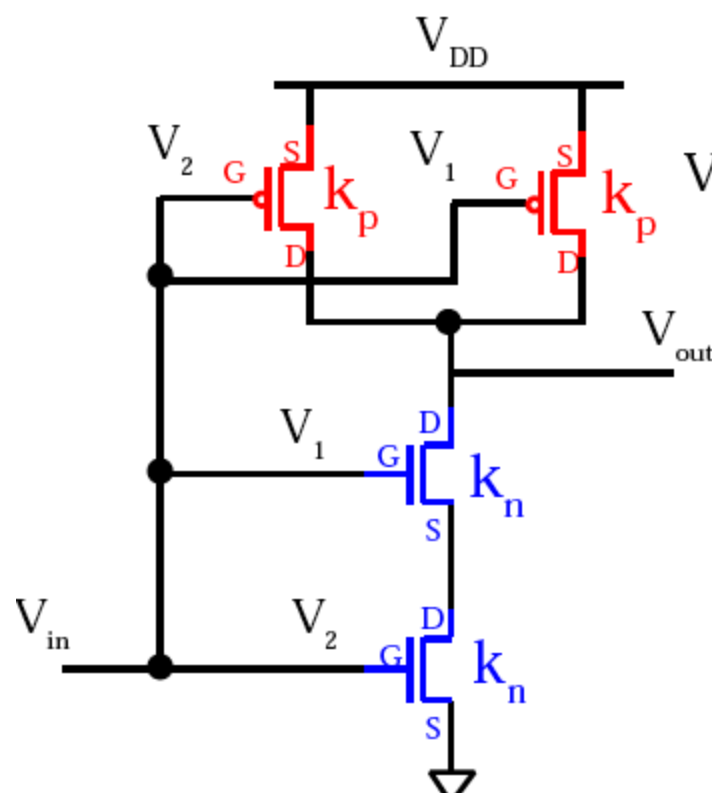

$V_{th}(ND2) \Rightarrow V_1 = V_2 = V_{out}$   
 $V_{th}(INV) = V_{in} = V_{out}$
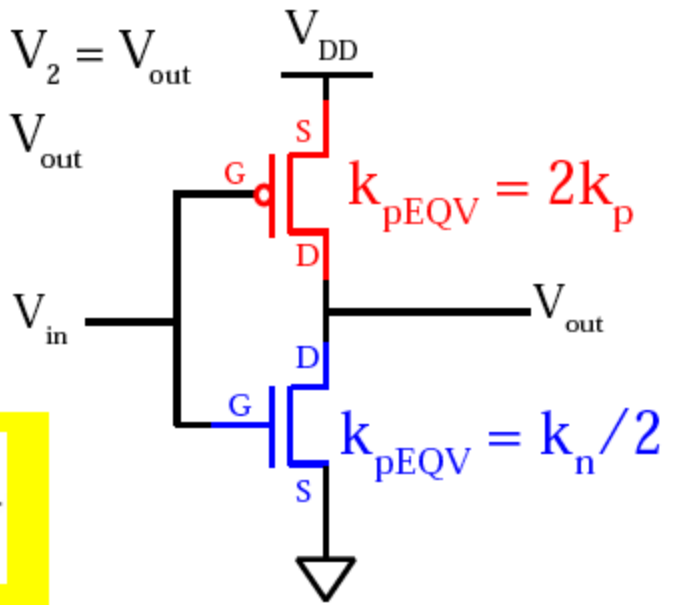
$$\frac{k_{pEQV}}{k_{nEQV}} = 4 \frac{k_p}{k_n}$$



$$V_{th}(NAND2) = \frac{V_{Tn} + 2\sqrt{\frac{k_p}{k_n}}(V_{DD} + V_{Tp})}{1 + 2\sqrt{\frac{k_p}{k_n}}}$$


$$V_{th}(INV) = \frac{V_{Tn} + \sqrt{\frac{k_{pEQV}}{k_{nEQV}}}(V_{DD} + V_{Tp})}{1 + \sqrt{\frac{k_{pEQV}}{k_{nEQV}}}}$$

### Symmetrical EQUIV INV

$k_{pEQV} = k_{nEQV}$  and  $V_{Tn} = |V_{Tp}| \Rightarrow V_{th}(INV) = V_{DD}/2$

$V_{th}(ND2) = V_{DD}/2 \Rightarrow k_n = 4k_p$
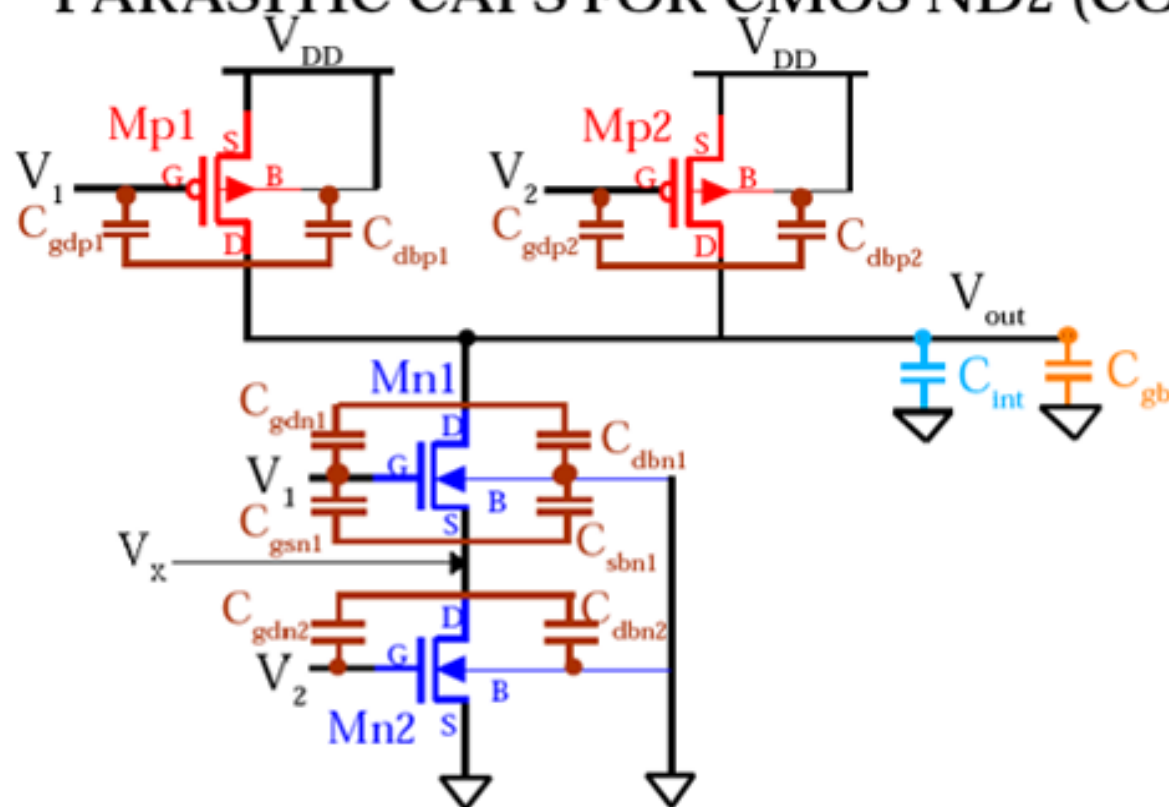
# PARASITIC CAPS FOR CMOS ND2 (CONSERVATIVE) 25



$$\begin{aligned}
 C_{gdn1} &= C_{gdn2} = C_{gdn} \\
 C_{dbn1} &= C_{dbn2} = C_{dbn} \\
 C_{gdp1} &= C_{gdp2} = C_{gdp} \\
 C_{dbp1} &= C_{dbp2} = C_{dbp} \\
 C_{gsp1} &= C_{gsp2} = C_{gsp} \\
 C_{sbp1} &= C_{sbp2} = C_{sbp}
 \end{aligned}$$

**WORST CASE for PULL-UP**  $\Rightarrow V_1 = V_{DD}, V_2 = V_{DD} \rightarrow 0$  &  $V_x = \text{low} \rightarrow \text{high}$

$$C_{\text{load-ND2}} \approx 2C_{dbn} + C_{sbn} + 2C_{dbp} + C_{\text{int}} + C_{gb} = 3C_{dbn} + 2C_{dbp} + C_{\text{int}} + C_{gb}$$

**WORST CASE for PULL-DOWN**  $\Rightarrow V_1 = V_{DD}, V_2 = 0 \rightarrow V_{DD}$  &  $V_x = \text{high} \rightarrow \text{low}$

$$C_{\text{load-ND2}} \approx 2C_{dbn} + C_{sbn} + 2C_{dbp} + C_{\text{int}} + C_{gb} = 3C_{dbn} + 2C_{dbp} + C_{\text{int}} + C_{gb}$$

**NDn:**  $C_{\text{load-NDn}} \approx (2n-1)C_{dbn} + nC_{dbp} + C_{\text{int}} + C_{gb}$

**ND2:**

**1. Symmetric Inverter  $V_{th} = V_{DD}/2$ :**

$$V_{th}(ND2) = V_{DD}/2 \Rightarrow k_n = 4k_p$$

**2. Propagation delay  $\tau_{PHL}$  or  $\tau_{PLH}$ :**

$$\tau_{PHL-ND2} \approx \frac{C_{load-ND2}}{\frac{k_n(V_{DD}-V_{T0n})}{2}} \left[ \frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left( \frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH-ND2} \approx \frac{C_{load-ND2}}{2k_p(V_{DD}-|V_{T0p}|)} \left[ \frac{2|V_{T0p}|}{V_{DD} - |V_{T0p}|} + \ln \left( \frac{4(V_{DD} - |V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

**NDn:**

**1. Symmetric Inverter  $V_{th} = V_{DD}/2$ :**

$$V_{th}(NDn) = V_{DD}/2 \Rightarrow k_n = n^2k_p$$

**2. Propagation delay  $\tau_{PHL}$  or  $\tau_{PLH}$ :**





$$\tau_{PHL-NDn} \approx \frac{C_{load-NDn}}{\frac{k_n(V_{DD}-V_{T0n})}{n}} \left[ \frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left( \frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH-NDn} \approx \frac{C_{load-NDn}}{nk_p(V_{DD}-|V_{T0p}|)} \left[ \frac{2|V_{T0p}|}{V_{DD} - |V_{T0p}|} + \ln \left( \frac{4(V_{DD} - |V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

# TYPICAL CMOS NAND AND NOR DELAYS

Delays for a Family of **NAND & NOR** gates

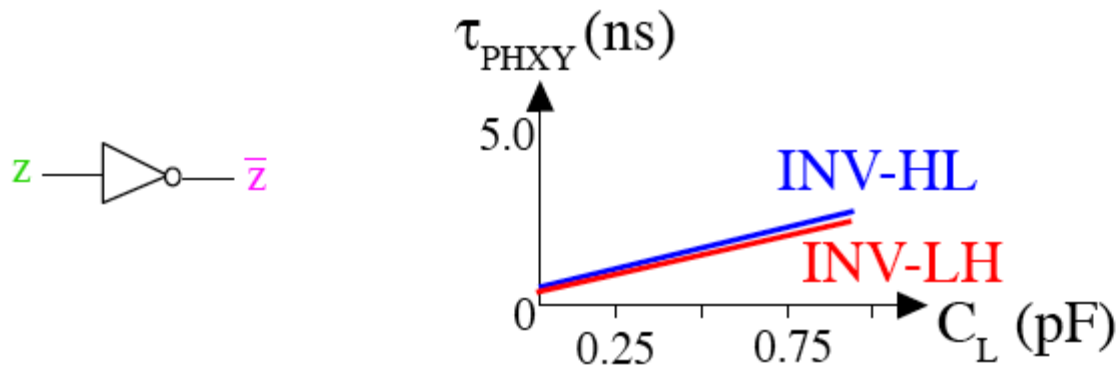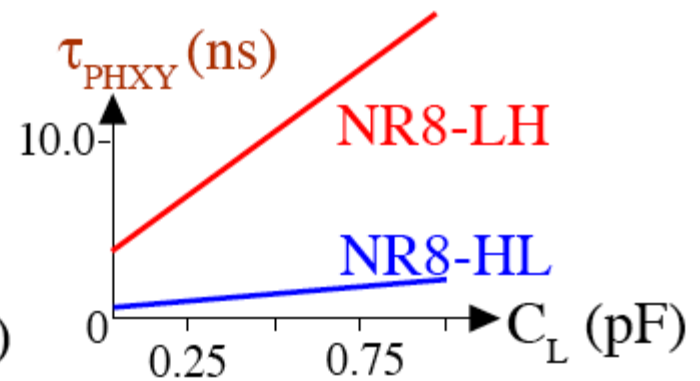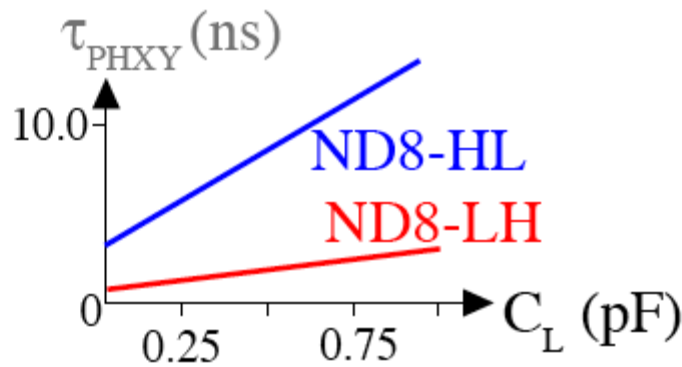
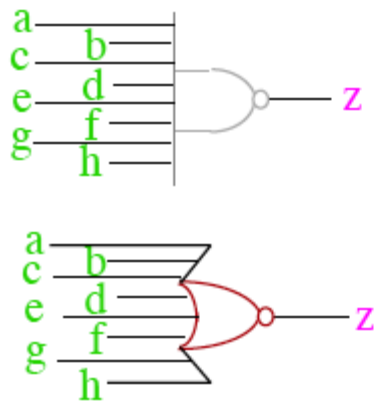
1.  $W_n = 6.4 \mu\text{m}$ ,  $L_n = 1 \mu\text{m}$ , and  $W_p = 12.8 \mu\text{m}$ ,  $L_p = 1 \mu\text{m}$ .
2.  $t_{\text{input-rise/fall}} = 0.1 \text{ ns}$  and  $C_{\text{load}} = 0 \rightarrow 1 \text{ pF}$ .




# NR2 Layout Example
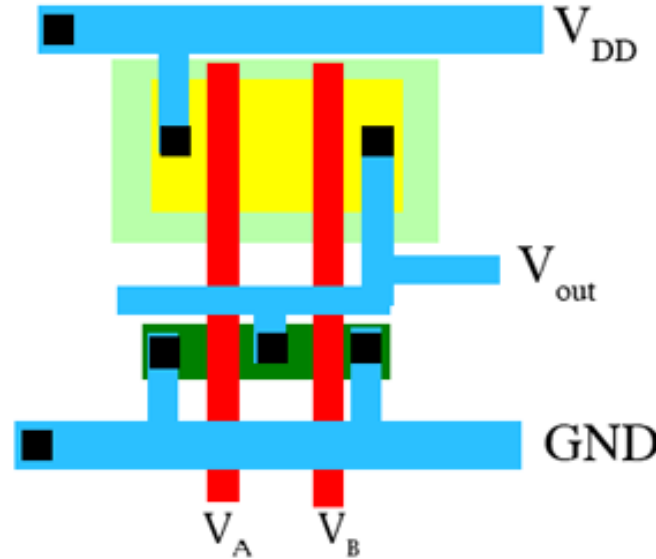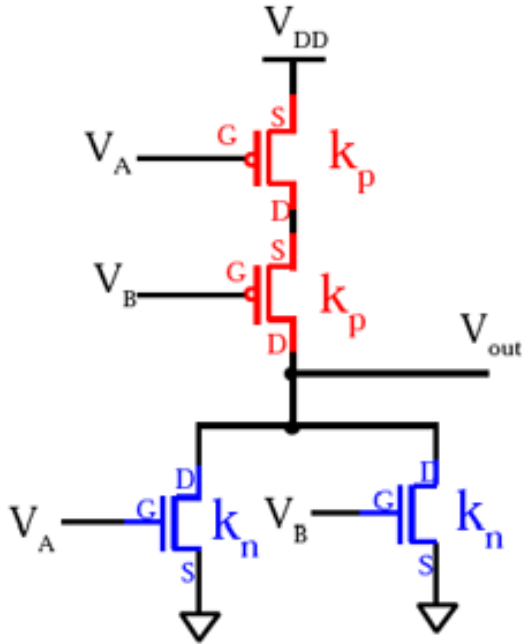
## COLOR LEGEND


- n-Well
- p-Well
- n<sup>+</sup>
- Polysilicon
- p<sup>+</sup>
- Gate Oxide
- Field Oxide
- Metal 1
- Metal 2
- Metal 3
- Contact/via



STICK DIAGRAM →

 


# ND2 Layout Example

 

COLOR LEGEND 30

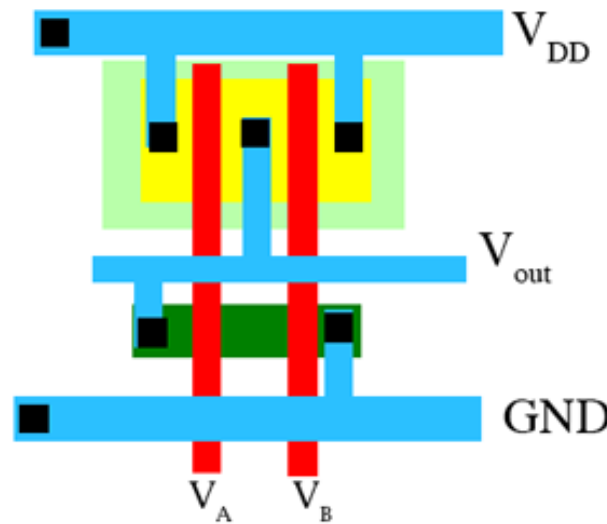
- n-Well
- p-Well
- n<sup>+</sup>
- Polysilicon
- p<sup>+</sup>
- Gate Oxide
- Field Oxide
- Metal 1
- Metal 2
- Metal 3
- Contact/via



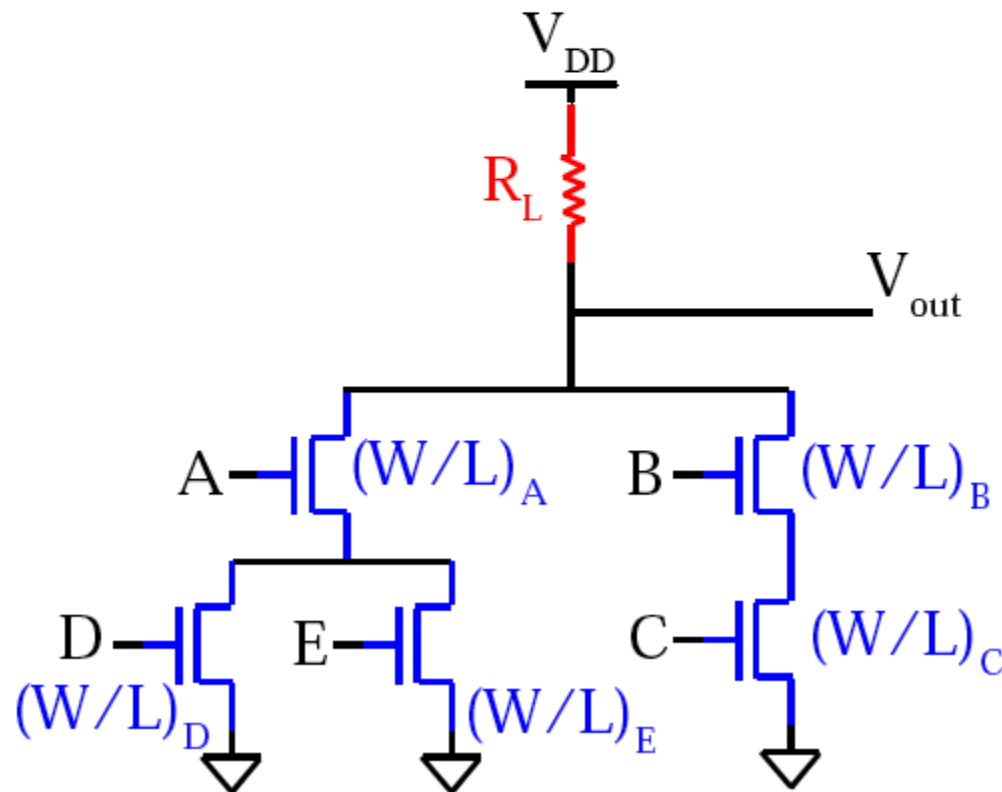
## COMPLEX LOGIC GATES

$$Z = \overline{A(D + E) + BC}$$

- “OR” OPS PERFORMED BY PARALLEL CONNECTED DRIVERS.
- “AND” OPS PERFORMED BY SERIES CONNECTED DRIVERS.
- “INVERSION” IS PROVIDED BY NATURE OF MOS CIRCUIT OP.



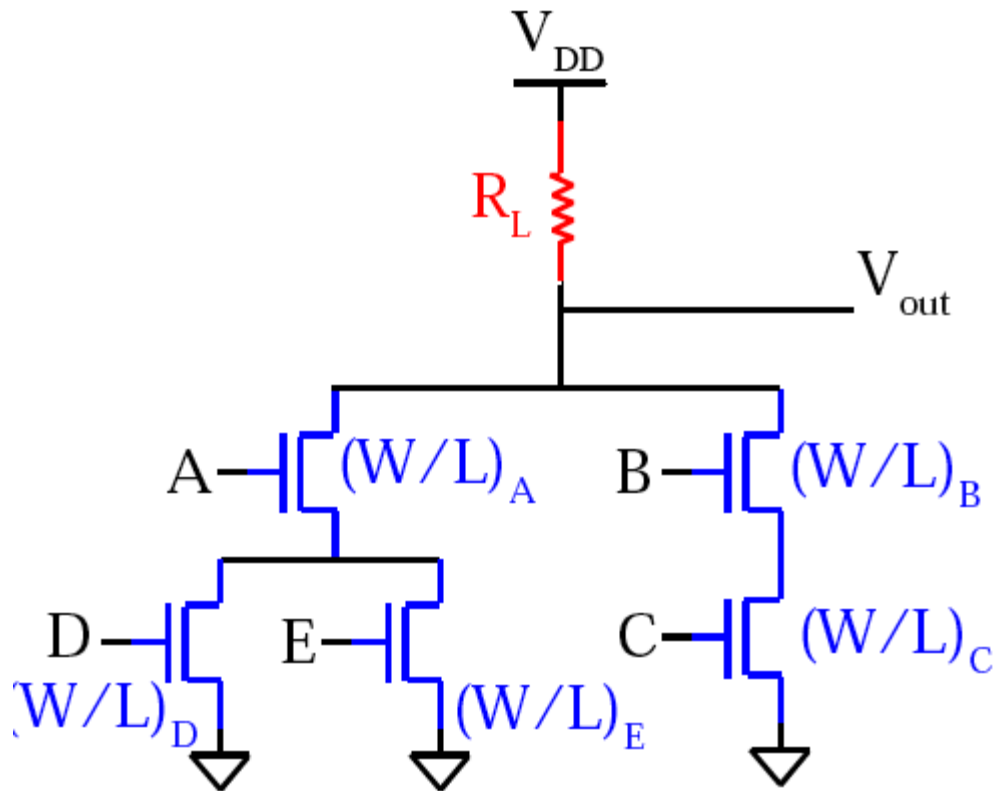


ON Drivers	Out-GND Path
A-D	Class 1
A-E	Class 1
B-C	Class 1
A-D-E	Class 2
A-D-B-C	Class 3
A-E-B-C	Class 3
A-D-E-B-C	Class 4
$G1 < G2 < G3 < G4$	
$V_{OL1} > V_{OL2} > V_{OL3} > V_{OL4}$	

**EQV INVERTER** (for case  $G4$  where  $A = B = C = D = E = 1$ )
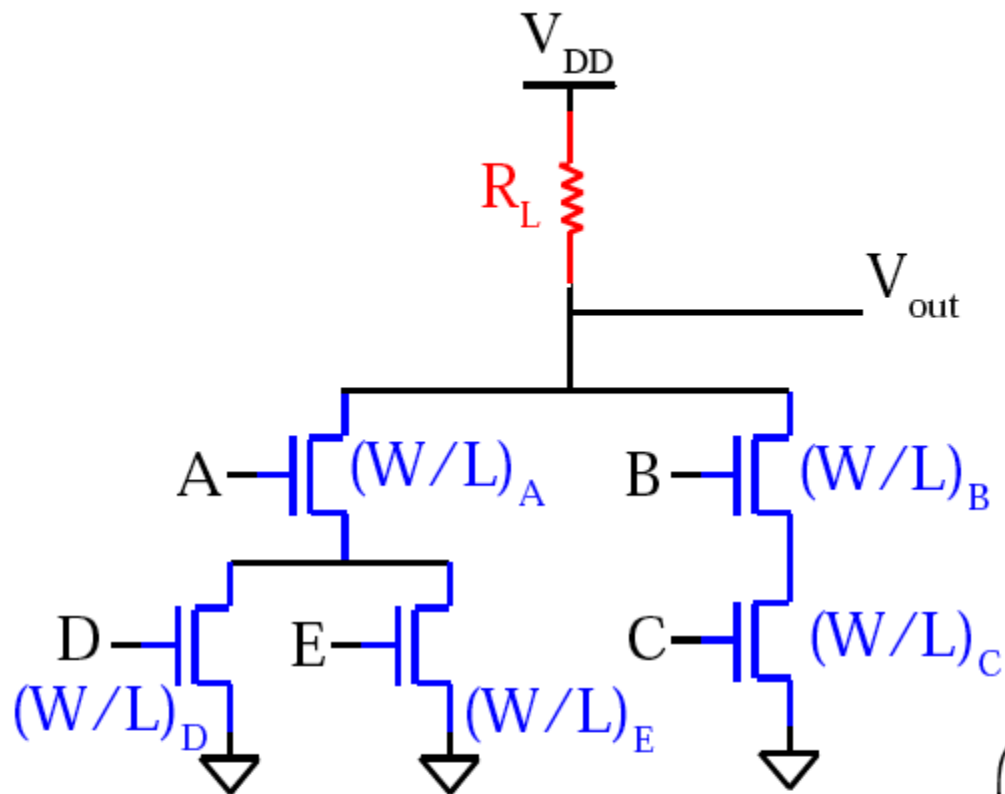
$$\left(\frac{W}{L}\right)_{EQV} = \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_B} + \frac{1}{\left(\frac{W}{L}\right)_C}} + \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_A} + \frac{1}{\left(\frac{W}{L}\right)_D + \left(\frac{W}{L}\right)_E}}$$





$$\left(\frac{W}{L}\right)_{\text{EQV-ND2}} = \frac{1}{2} \left(\frac{W}{L}\right)$$

## DESIGN STRATEGY:


1. Identify all WORST CASE Paths (e.g. Class 1).
2. Determine nMOS transistor sizes such that each Class 1 path has  $(W/L)_{\text{EQV}}$

$$\left(\frac{W}{L}\right)_A = \left(\frac{W}{L}\right)_D = 2 \left(\frac{W}{L}\right)_{\text{EQV}}$$


$$\left(\frac{W}{L}\right)_A = \left(\frac{W}{L}\right)_E = 2 \left(\frac{W}{L}\right)_{\text{EQV}}$$

$$\left(\frac{W}{L}\right)_B = \left(\frac{W}{L}\right)_C = 2 \left(\frac{W}{L}\right)_{\text{EQV}}$$



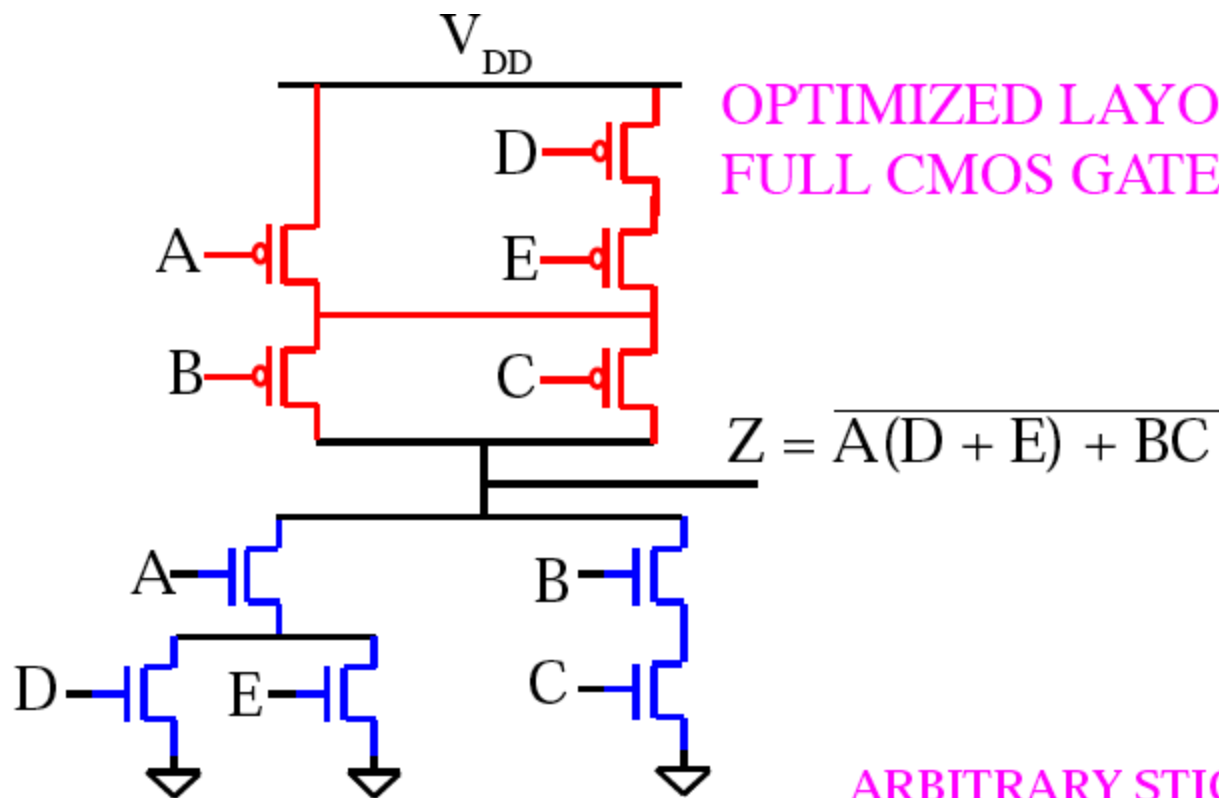
# OPTIMIZED LAYOUT OF COMPLEX FULL CMOS GATES







## ARBITRARY STICK LAYOUT

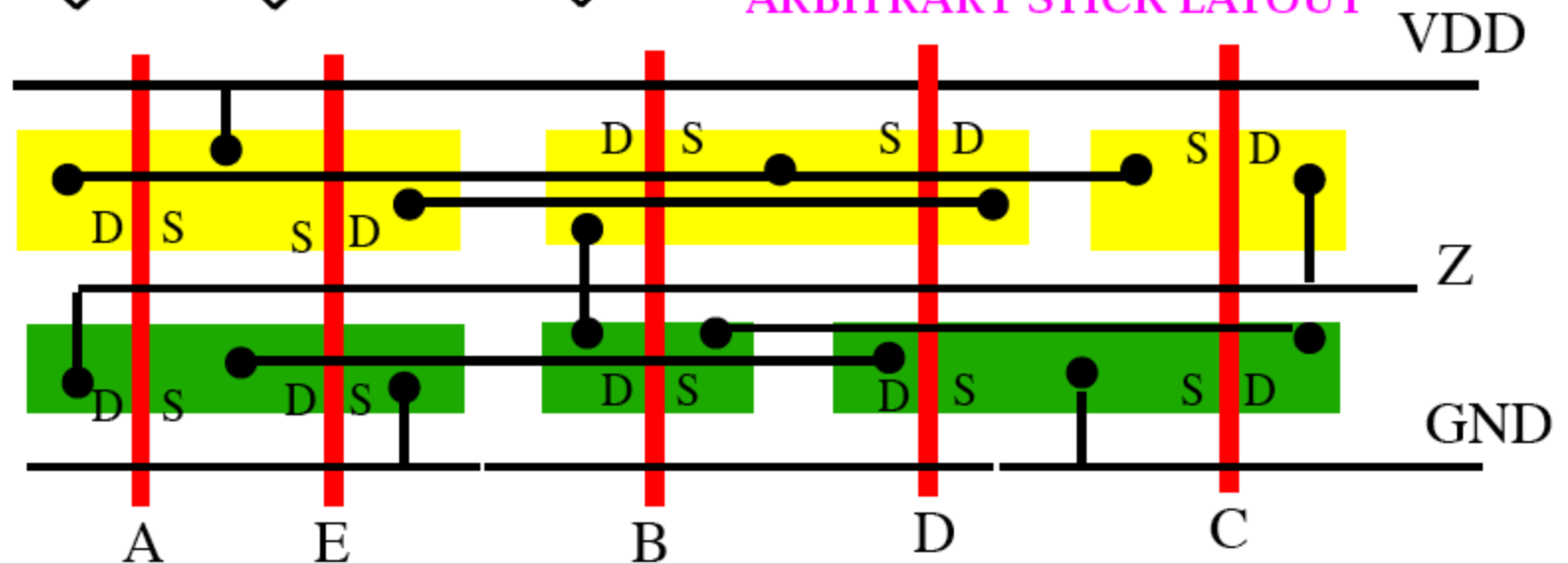
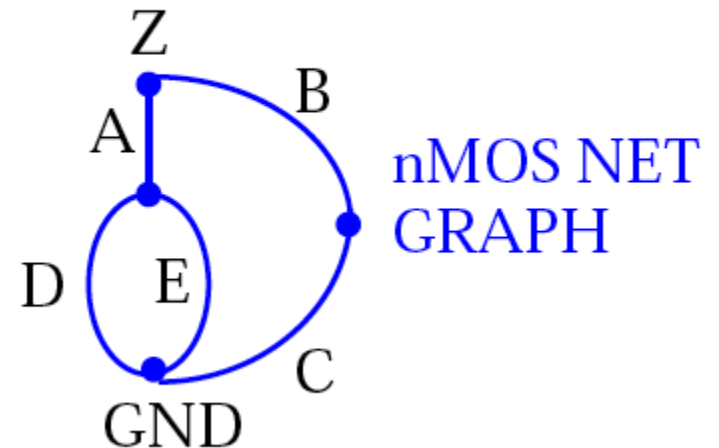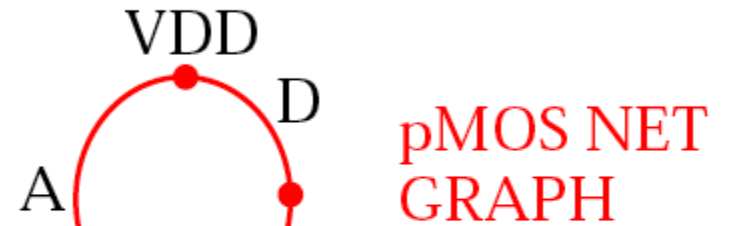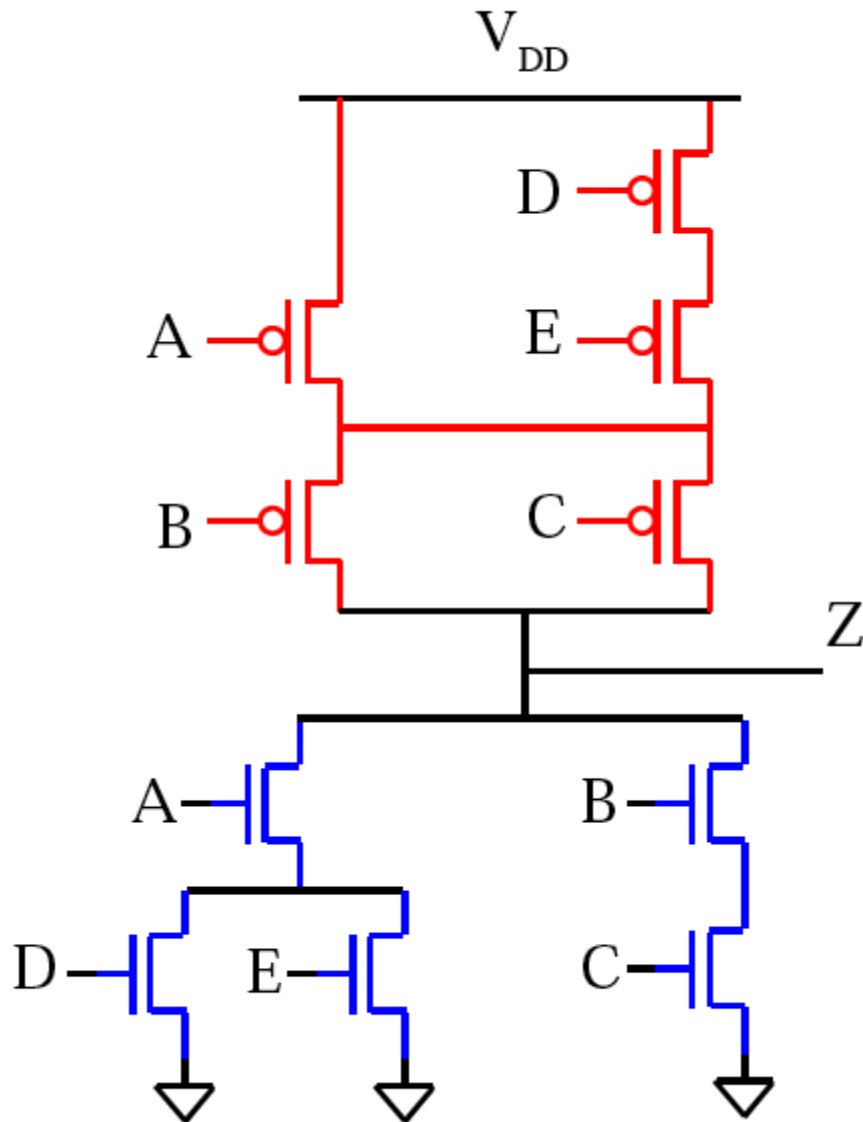
# OPTIMIZED LAYOUT OF COMPLEX FULL CMOS GATES




# ARBITRARY ORDERING OF GATE COLUMNS

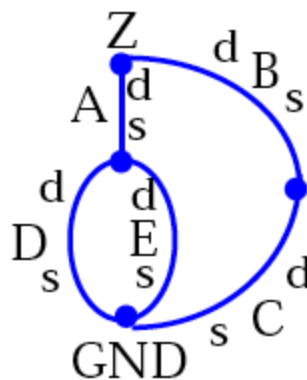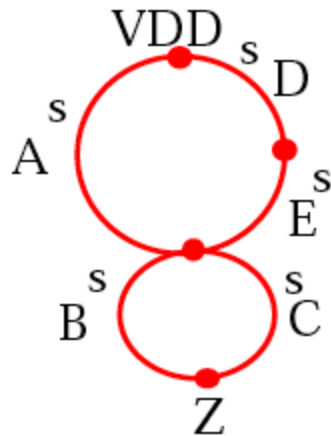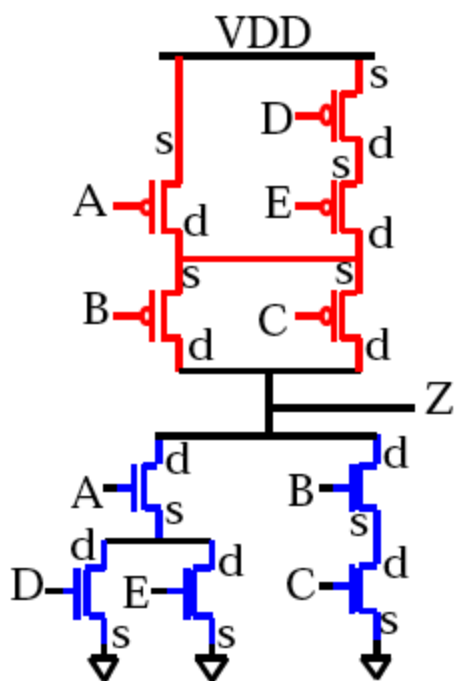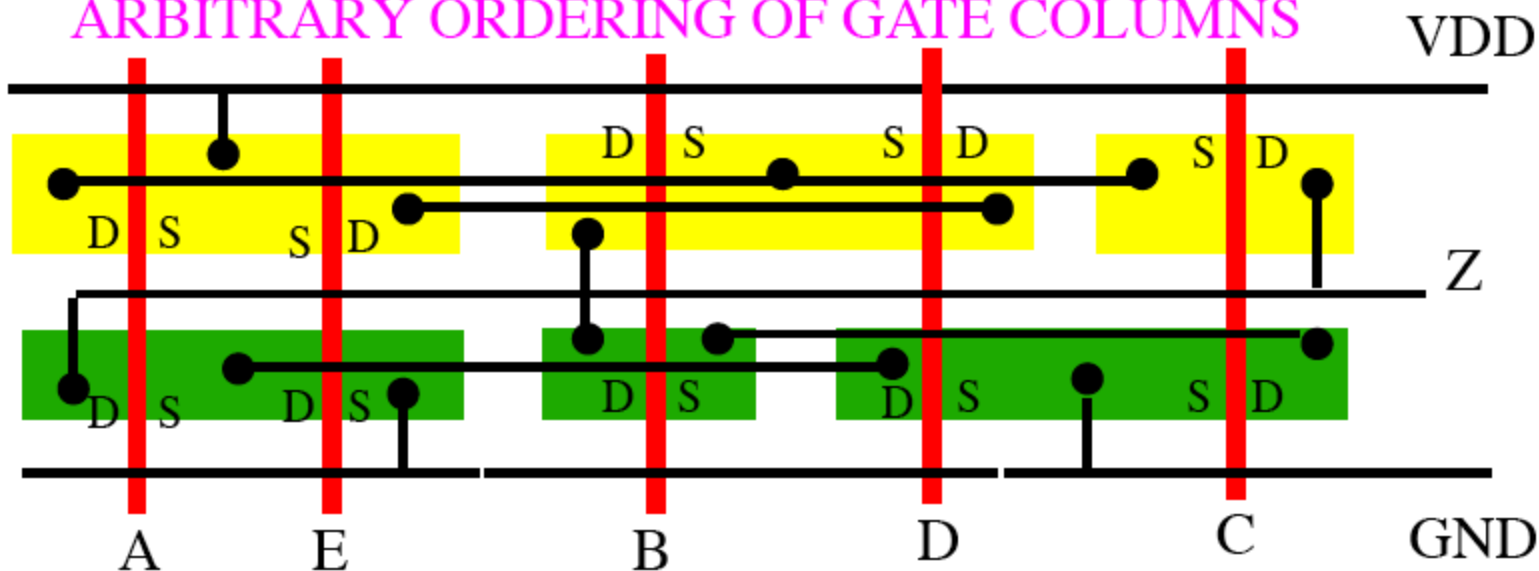

**Euler path** - connected sequence of edges




**n, p** diffusions for common **Euler paths** have layouts with no diffusion breaks.

# MINIMIZE NUMBER OF DIFFUSION BREAKS

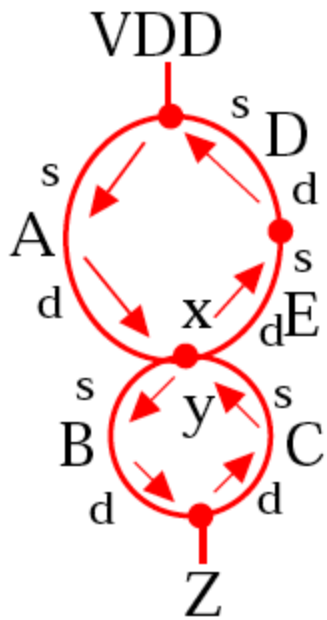


COMMON  
EULER PATH:  
E-D-A-B-C


Is A-D-E-C-B a  
common Euler  
path?

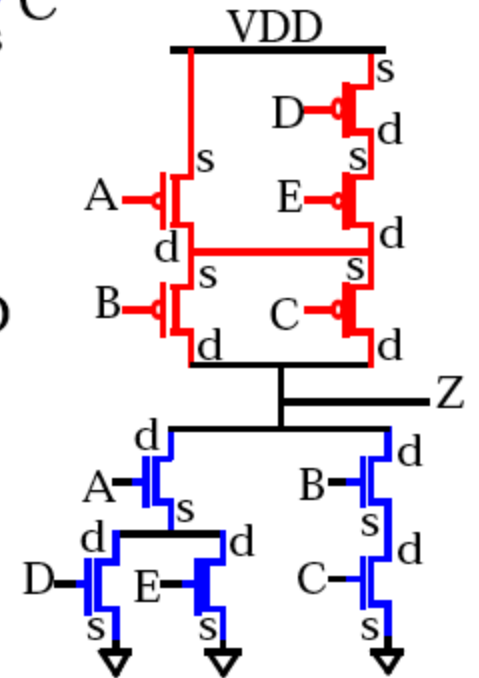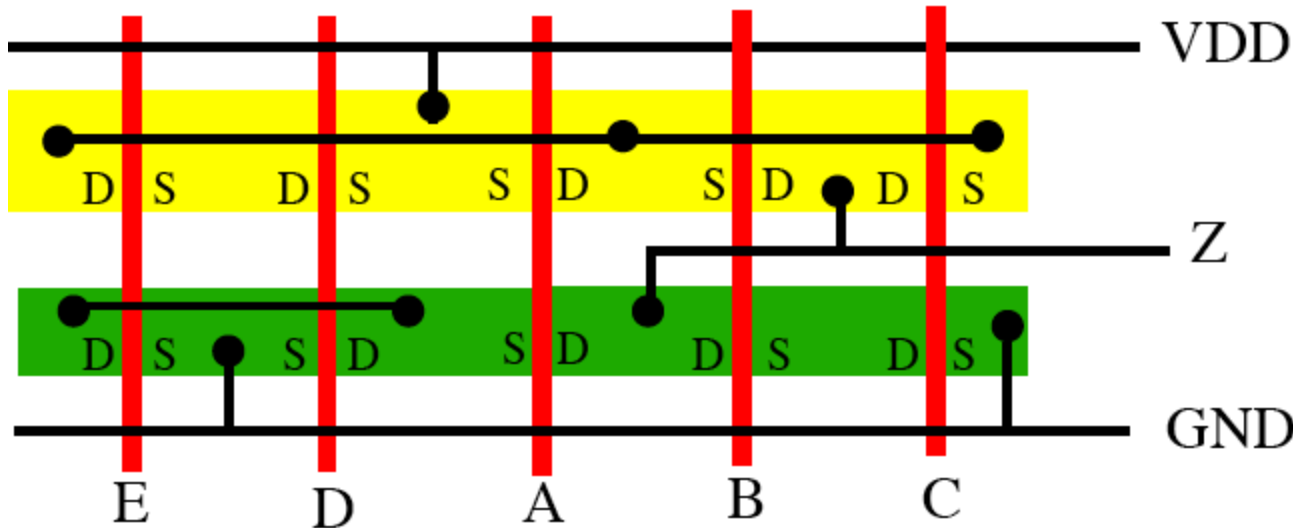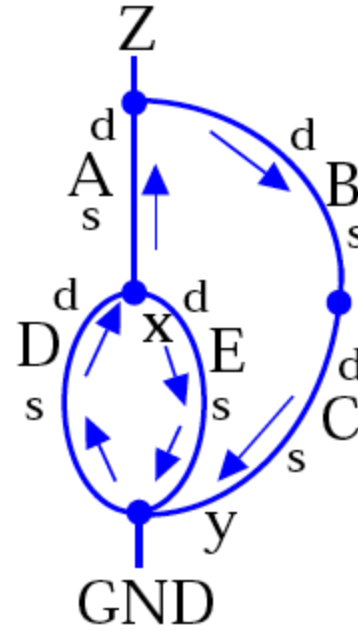

Arbitrary Stack

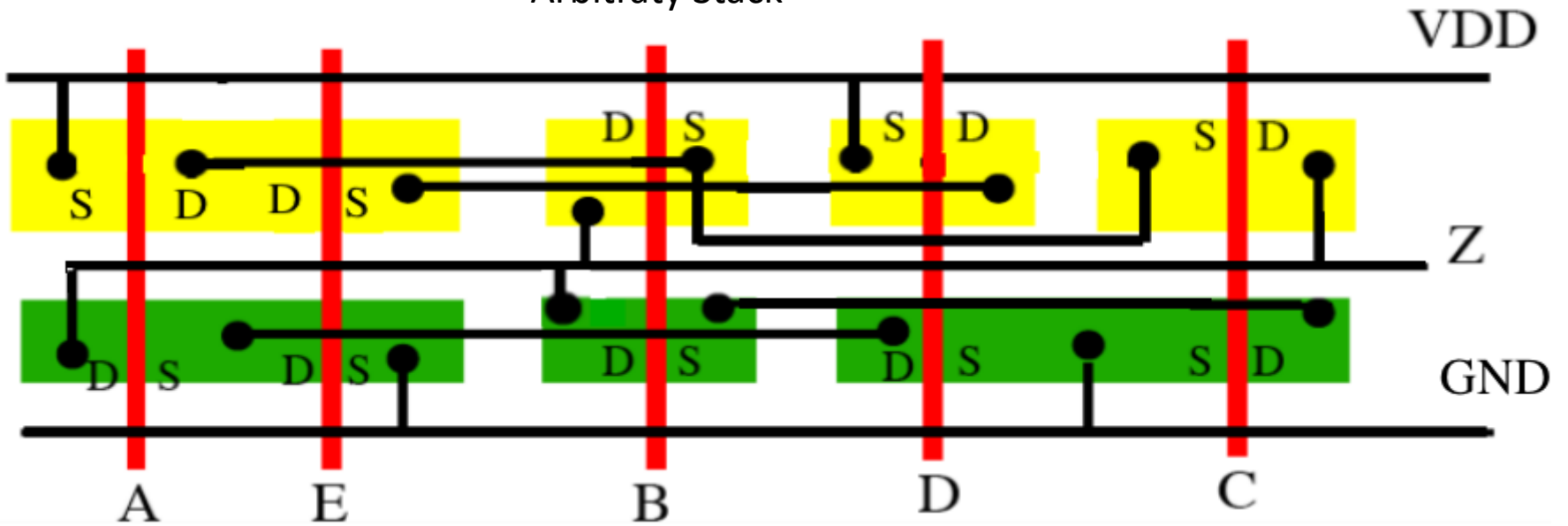


Optimized Stack

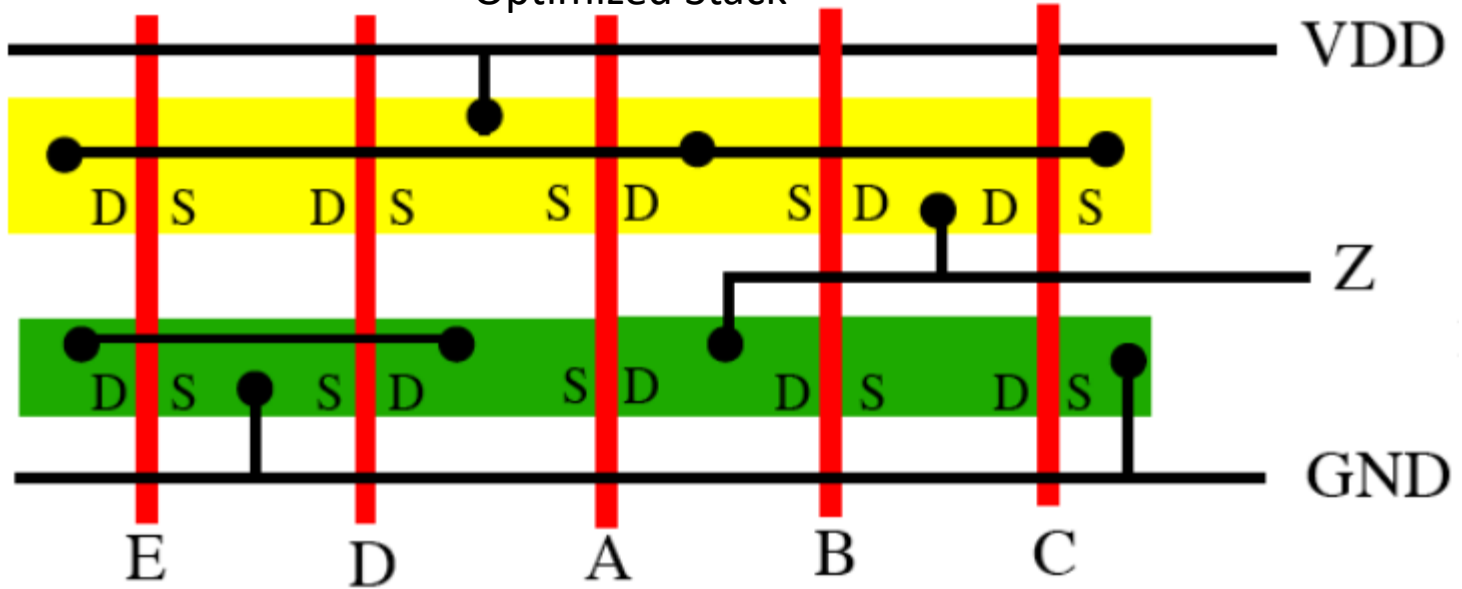

## ALGORITHM FOR LINE OF GATES LAYOUT STYLE

1. Find all **Euler paths** that cover the graph.
2. Find common **n-** and **p- Euler paths**.
3. If no **Euler paths** are found in step 2, break the gate in the minimum number of places that to achieve step 2 with separate common **Euler paths**.

## FULL CMOS XOR GATE

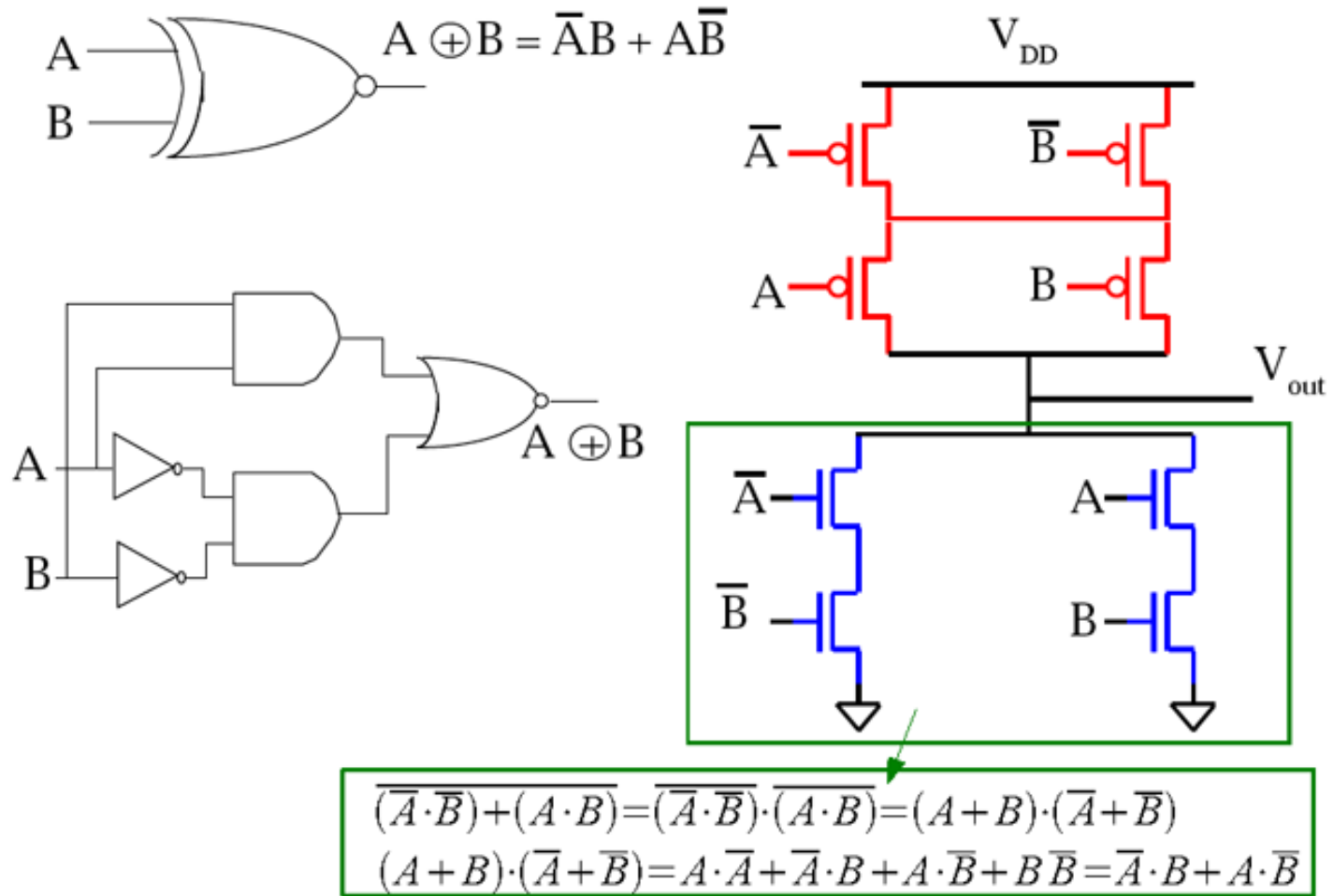




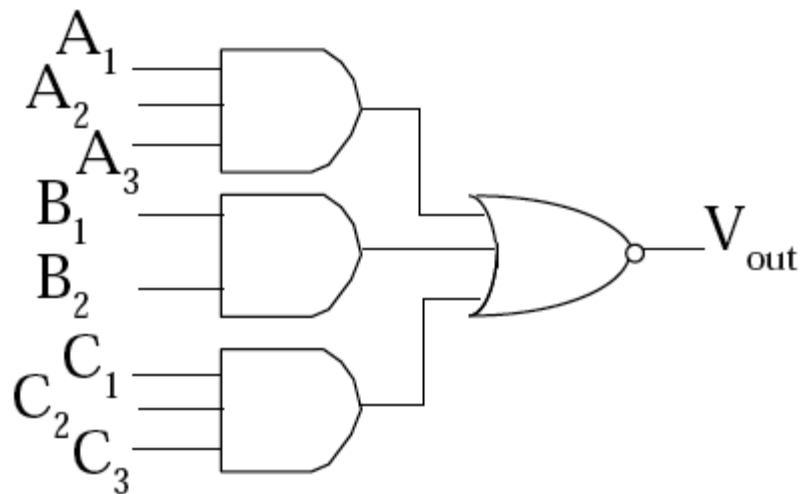
## AOI & OAI GATES

AOI -> AND-OR-INVERT (for SUM - of - PRODUCTS Realization)



OAI -> OR-AND-INVERT (for PRODUCT - of - SUMS Realization)




AOI

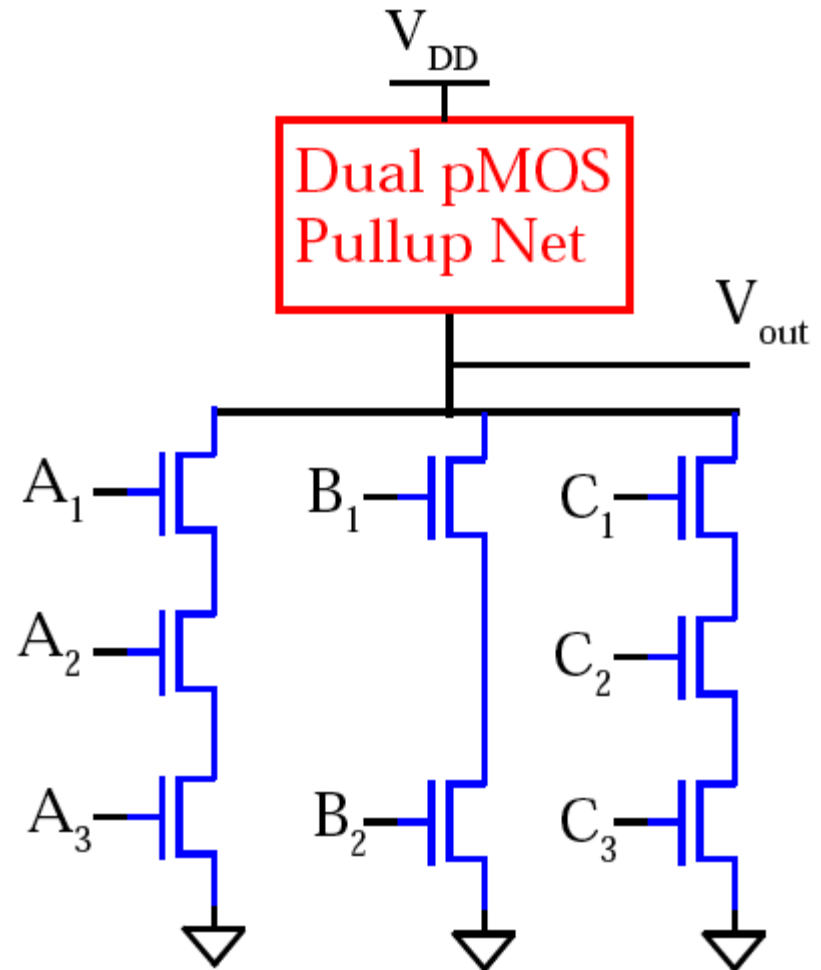
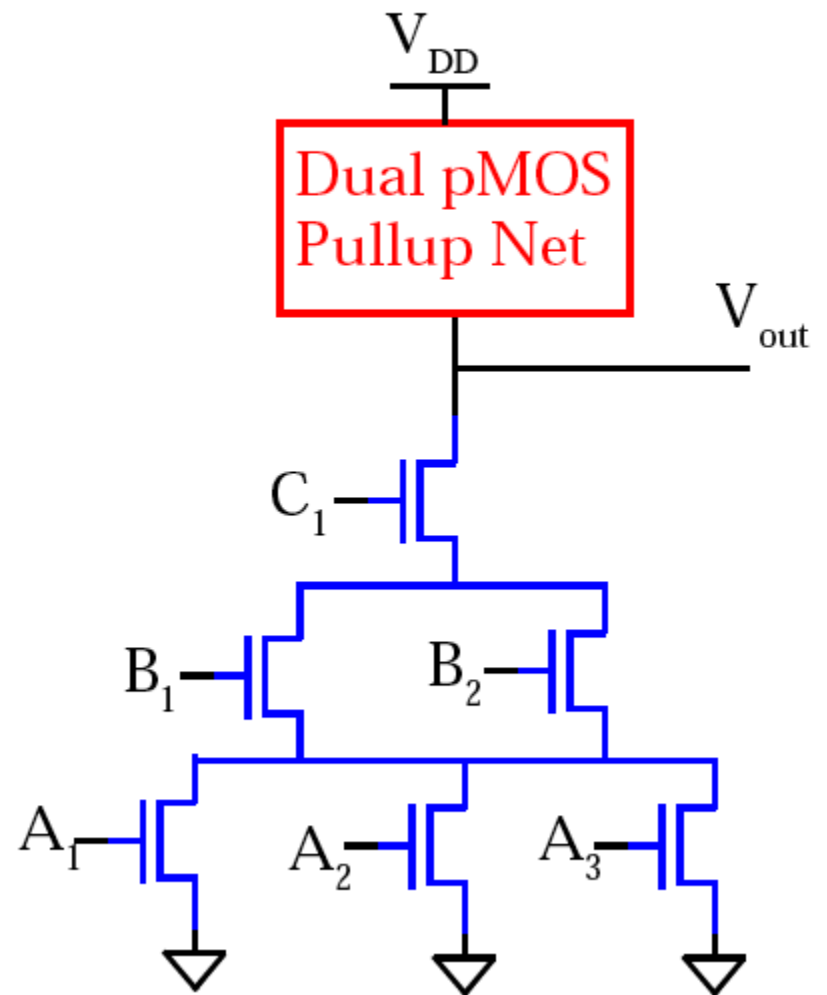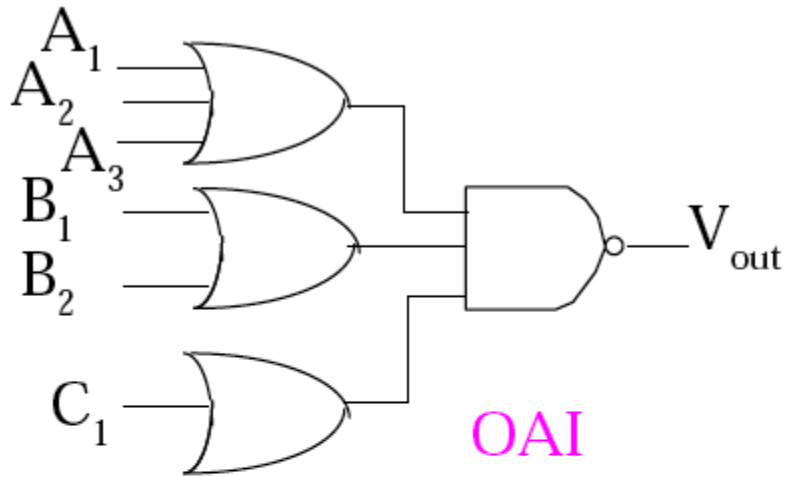
# OAI -> OR-AND-INVERT (for PRODUCT - of - SUMS Realization)




# Pseudo-nMOS OAI Realization

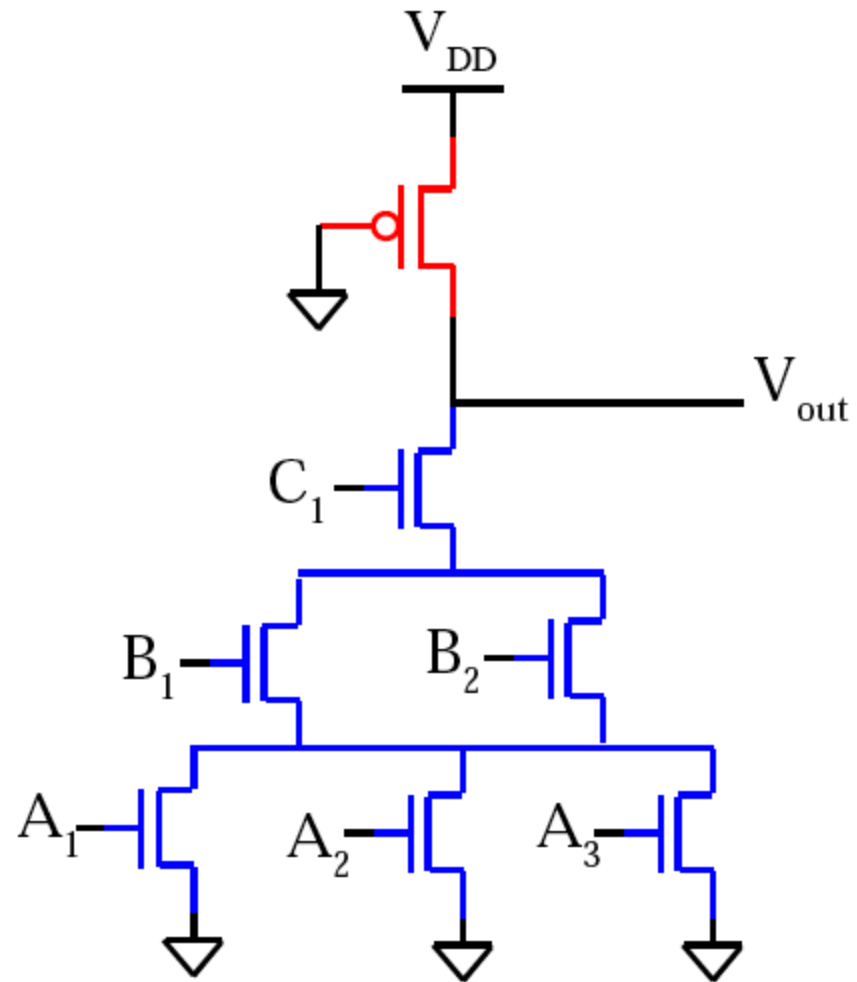

# CMOS Transmission Gates (TGs) & TG Logic

## SYMBOLS

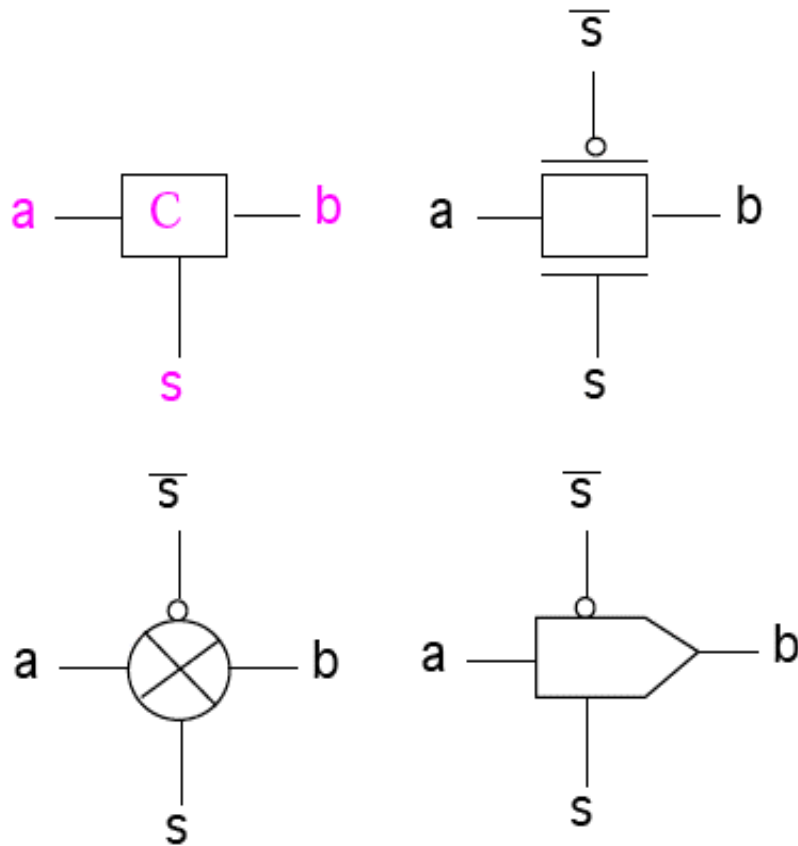



## SWITCH CHARACTERISTICS

Input

Output

0 a — o —▶— o — b Strong 0

1 a — o —▶— o — b Strong 1

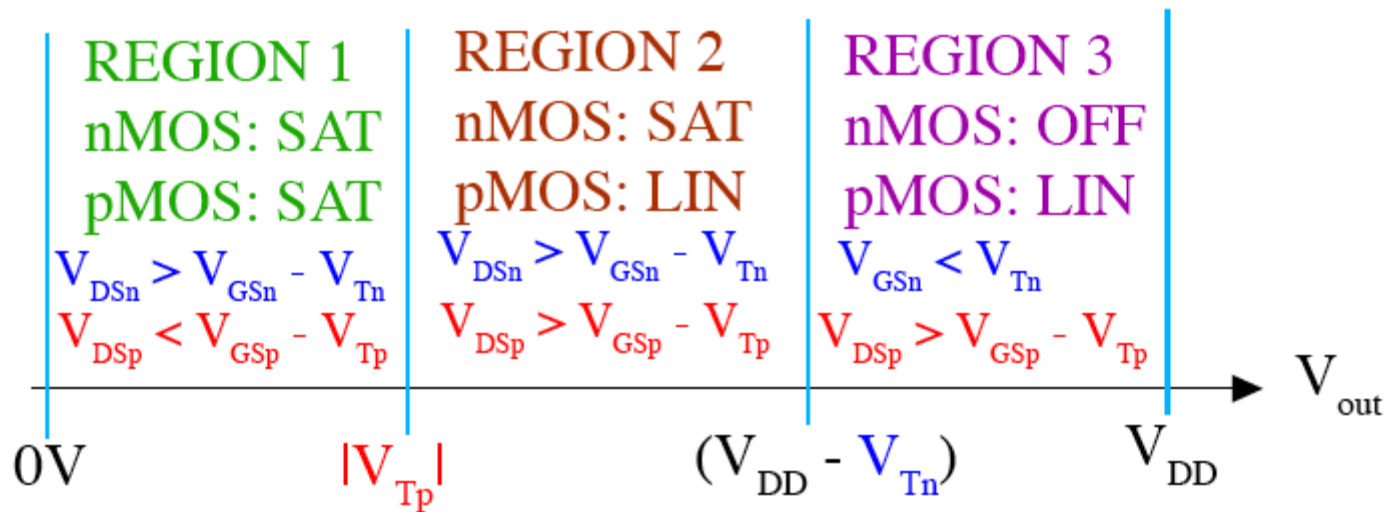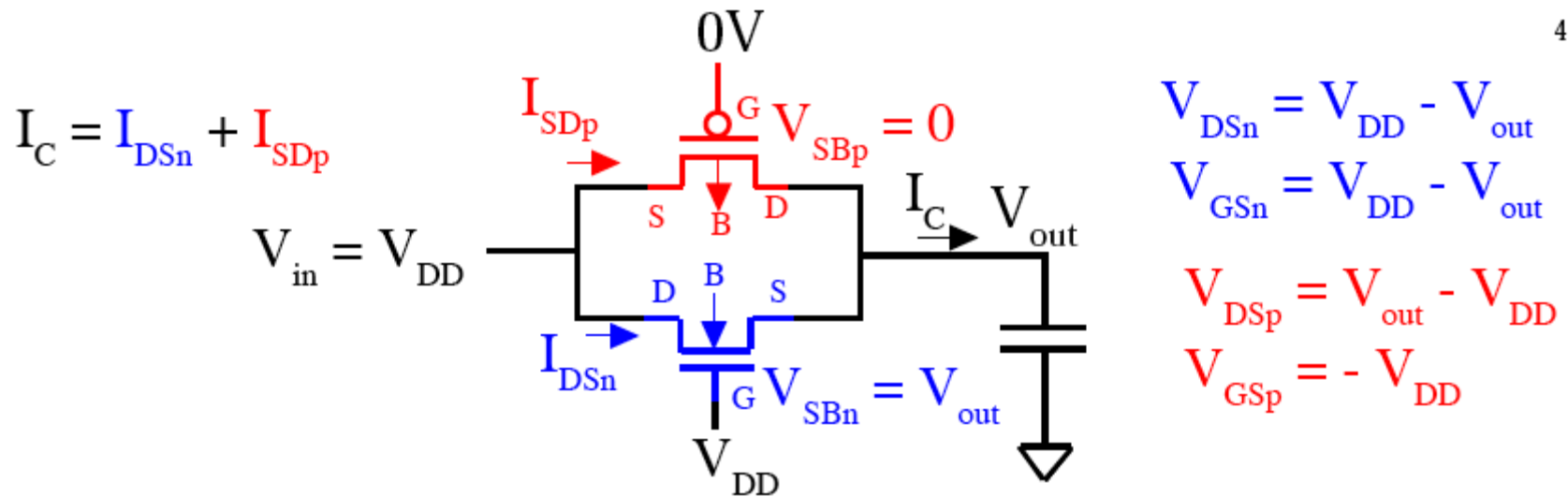

$$R_{eqn} = \frac{V_{DD} - V_{out}}{I_{DSn}}$$

$$R_{eqp} = \frac{V_{DD} - V_{out}}{I_{SDp}}$$

$$R_{eqTOT} = R_{eqn} \parallel R_{eqp}$$

REGION 1:  
nMOS: SAT  
pMOS: SAT

$$R_{\text{eqn}} = \frac{2(V_{\text{DD}} - V_{\text{out}})}{k_n (V_{\text{DD}} - V_{\text{out}} - V_{\text{Tn}})^2}$$

$$R_{\text{eqp}} = \frac{2(V_{\text{DD}} - V_{\text{out}})}{k_p (V_{\text{DD}} - |V_{\text{Tp}}|)^2}$$

REGION 2  
nMOS: SAT  
pMOS: LIN

$$R_{\text{eqn}} = \frac{2(V_{\text{DD}} - V_{\text{out}})}{k_n (V_{\text{DD}} - V_{\text{out}} - V_{\text{Tn}})^2}$$


$$R_{\text{eqp}} = \frac{2(V_{\text{DD}} - V_{\text{out}})}{k_p \left[ 2(V_{\text{DD}} - |V_{\text{Tp}}|)(V_{\text{DD}} - V_{\text{out}}) - (V_{\text{DD}} - V_{\text{out}})^2 \right]}$$



$$= \frac{2}{k_p \left[ 2(V_{\text{DD}} - |V_{\text{Tp}}|) - (V_{\text{DD}} - V_{\text{out}}) \right]}$$

REGION 3  
nMOS: OFF  
pMOS: LIN

$$R_{\text{eqn}} = \infty$$

$$R_{\text{eqp}} = \frac{2}{k_p \left[ 2(V_{\text{DD}} - |V_{\text{Tp}}|) - (V_{\text{DD}} - V_{\text{out}}) \right]}$$

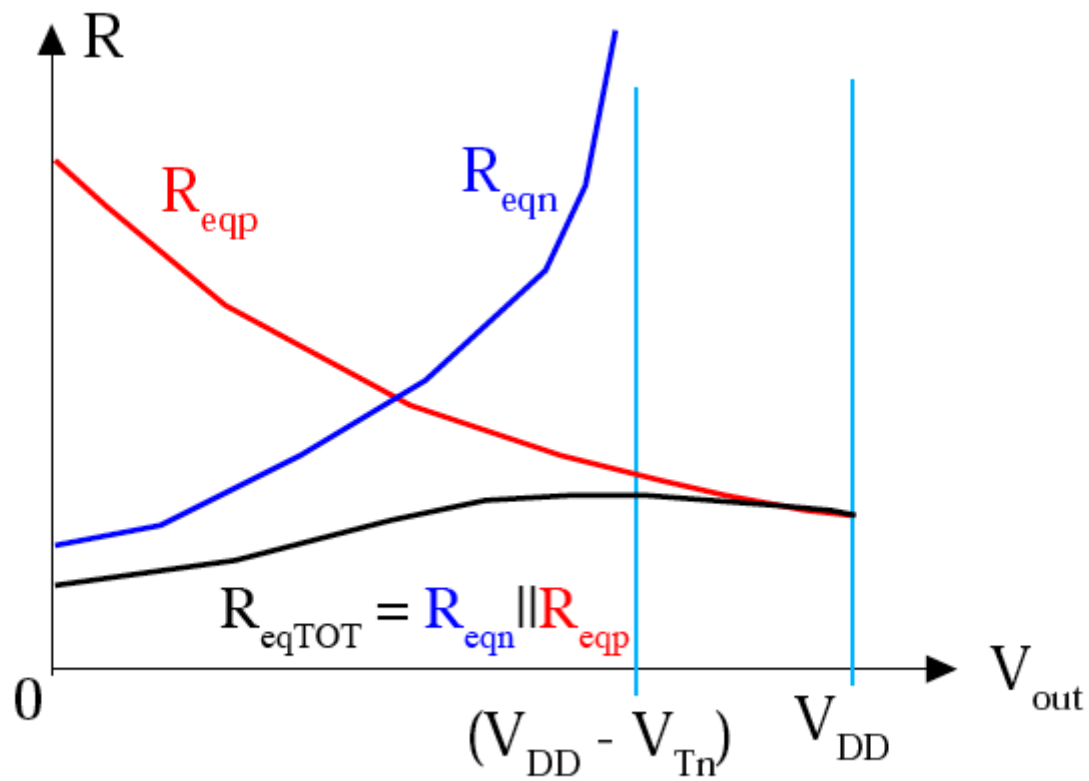

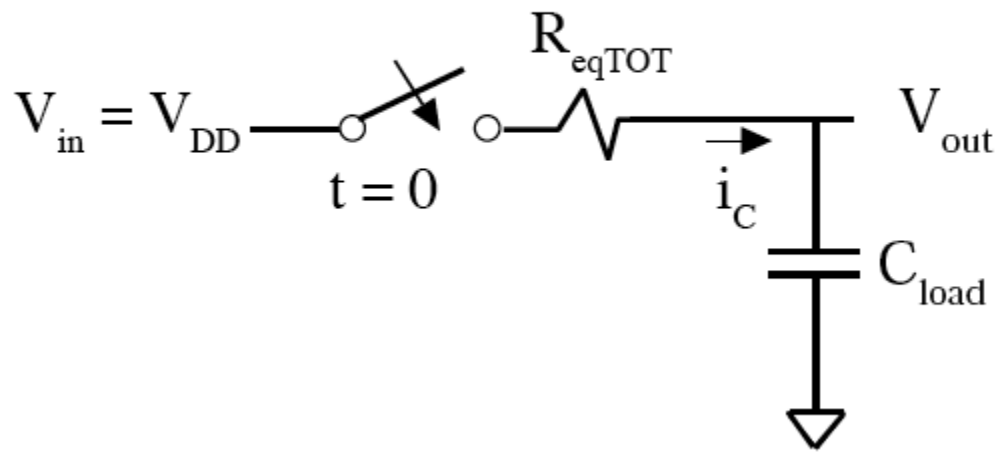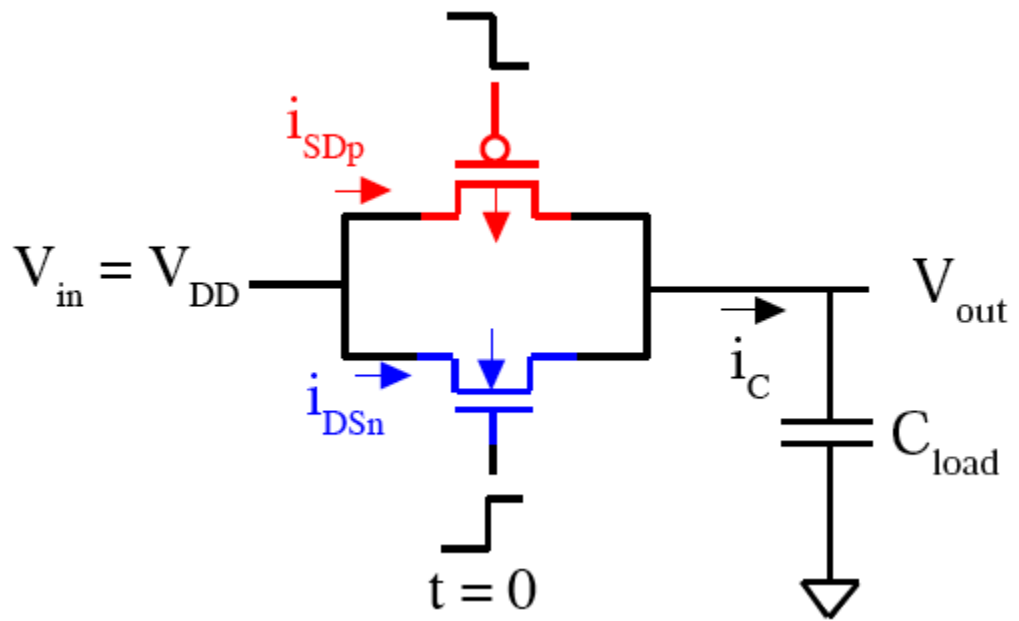



## TRANSMISSION GATE LAYOUTS



Simple and small,  
but no metal lines  
can pass  
horizontally



poly used to achieve  
horizontal metal1  
transparency



metal2 used to  
achieve  
horizontal metal1  
transparency

## Routing Gate Signals to Transmission Gate



horizontal, via  
metal1




vertical, via poly



vertical, via metal1 straps  
metal2 used to achieve vertical  
metal1 transparency




## 2-INPUT MULTIPLEXER

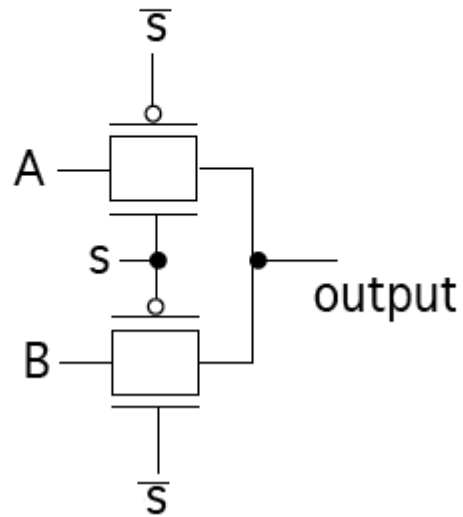


output =  $As + B \cdot \bar{s}$

A	B	s	$\bar{s}$	output
x	0	0	1	0 (B)
x	1	0	1	1 (B)
0	x	1	0	0 (A)
1	x	1	0	1 (A)
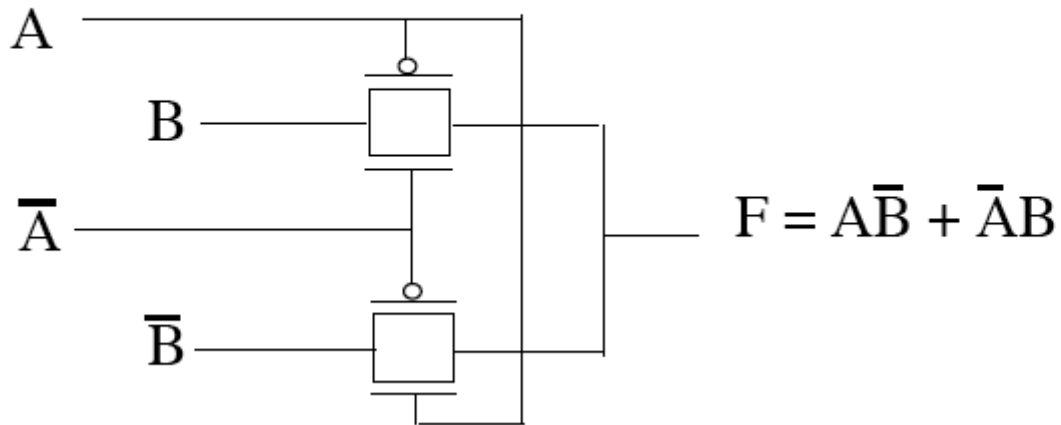
## XOR (COMPLEMENTARY PASS-TRANSISTOR LOGIC OR CPL)



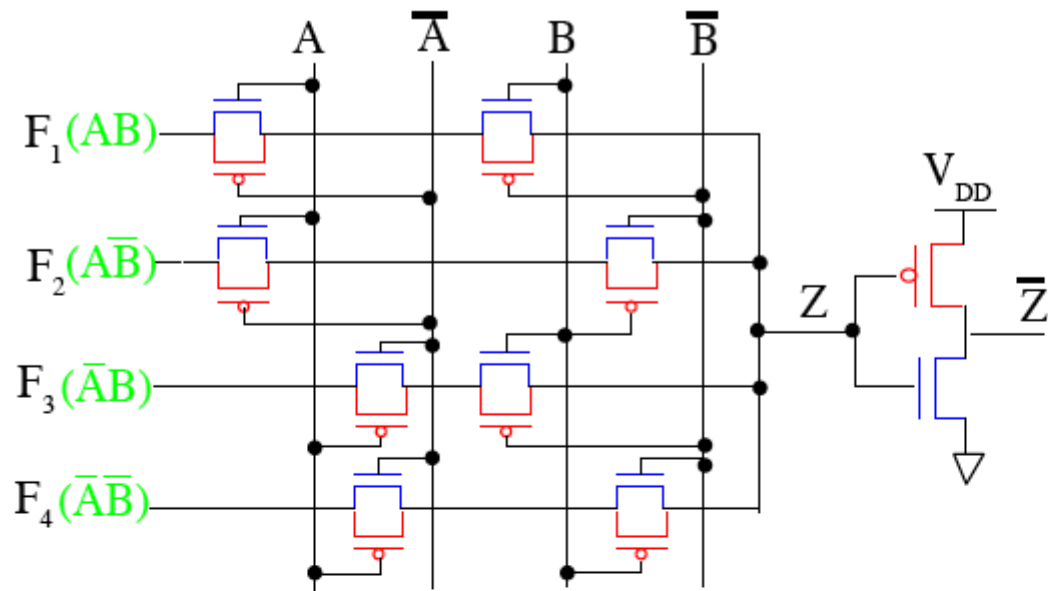

## SOME OF THE FUNCTIONS REALIZED BY THE BOOLEAN FUNCTION UNIT (CPL)

OPERATION (Z)	$F_1$	$F_2$	$F_3$	$F_4$
NOR(A,B)	0	0	0	1
XOR(A,B)	0	1	1	0
NAND(A,B)	0	1	1	1
AND(A,B)	1	0	0	0
OR(A,B)	1	1	1	0