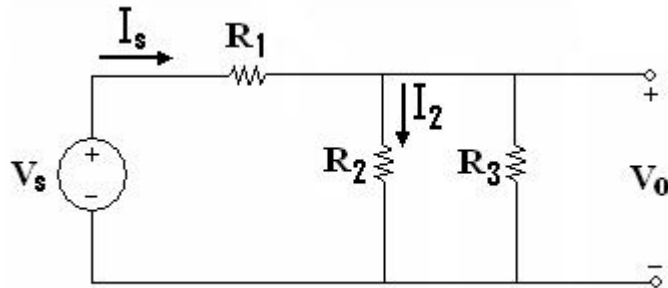


JEE2330 – Spring 2025

Lab #1 Problem

A DC circuit similar to that of Figure 1.10 of the lab manual is shown below. In this circuit, $R_1 = 2.2 \text{ k}\Omega$, $R_2 = 1.5 \text{ k}\Omega$, and $R_3 = 1.5 \text{ k}\Omega$.



1. Calculate the source voltage V_s if $I_s = 4 \text{ mA}$. $V_s = \underline{\hspace{2cm}}$

2. Calculate the current I_2 through R_2 if $I_s = 4 \text{ mA}$. $I_2 = \underline{\hspace{2cm}}$

3. Calculate the open circuit output voltage V_{OC} for this circuit. $V_{OC} = \underline{\hspace{2cm}}$

4. Calculate the short circuit current I_{SC} . $I_{SC} = \underline{\hspace{2cm}}$

5. Calculate the Thevenin resistance R_T . $R_T = \underline{\hspace{2cm}}$

6. Use the Thevenin equivalent circuit to calculate the expected reading of a laboratory DMM set to the 20 V scale if it is used to measure the output voltage V_o . Be sure to consider the resistance of the DMM on the 20 V scale. $V_o = \underline{\hspace{2cm}}$

7. Use the Thevenin equivalent circuit to calculate the expected reading of a laboratory DMM set to the 20 mA scale if it is used to measure the short circuit current I_{SC} . Be sure to consider the resistance of the DMM on the 20 mA scale. $I_{SC} = \underline{\hspace{2cm}}$

8. Calculate the Thevenin resistance based on the DMM readings. $R_T = \underline{\hspace{2cm}}$