
JEE2330 – Spring 2025 Lab #2B Problem

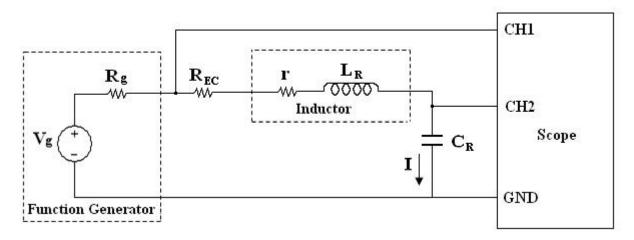In the laboratory, you are to construct the RLC circuit shown below. Assume the following: $v_g(t)=6~u(t),~R_g=50~\Omega,~R_{EC}=450~\Omega,~L_R=500~mH,~C_R=1~\mu F,$ and that the coil resistance r of the inductor L_R is 150 Ω . Note that u(t) is the unit-step function.



1. What is the final value of the capacitor voltage?

$$v_{\rm C}(\infty) = \underline{\hspace{1cm}}$$

2. What is the final value of the current in this circuit?

$$I(\infty) =$$

3. What is the neper frequency?

$$\alpha =$$

4. What is the undamped natural frequency?

$$\omega_{o} = \underline{\hspace{1cm}}$$

5. What is the damped natural frequency?

$$\omega_d = \underline{\hspace{1cm}}$$

6. Is the circuit overdamped, critically damped, or underdamped?

7. Based on your answers above, what is the mathematical expression for the capacitor voltage $v_c(t)$ for t > 0?