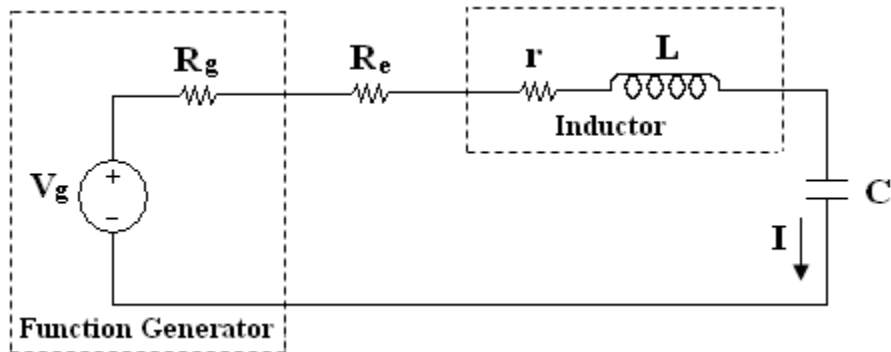


JEE2330 – Spring 2025 Lab #5 Problem

A series RLC circuit like the one shown here will be constructed in the lab this week. Assume that the generator resistance $R_g = 50 \Omega$, the external resistor $R_e = 200 \Omega$, $L = 47 \text{ mH}$, $r = 327 \Omega$. Also, assume that $v_g(t) = 6 \cos(2\pi ft)$ volts, where $f = 15 \text{ kHz}$.



1. Compute the quality factor of the inductor at $f = 15 \text{ kHz}$. $Q = \underline{\hspace{2cm}}$
2. Compute the value of the capacitor needed to resonate with the inductor at 15 kHz . $C = \underline{\hspace{2cm}}$
3. Compute the bandwidth of the resonant circuit in Hz. $BW = \underline{\hspace{2cm}}$
4. Compute the quality factor for the circuit at resonance. $Q_C = \underline{\hspace{2cm}}$
5. Define the phasor voltage V_g provided by the function generator. $V_g = \underline{\hspace{2cm}}$
6. Compute the corresponding phasor current I in the circuit at resonance. $I = \underline{\hspace{2cm}}$
7. Compute the corresponding phasor voltage V_C across the capacitor at resonance. $V_C = \underline{\hspace{2cm}}$
8. Compute the power dissipated by the external resistor R_e at resonance. $P_{R_e} = \underline{\hspace{2cm}}$
9. Compute the real power dissipated in the inductor at resonance. $P_r = \underline{\hspace{2cm}}$