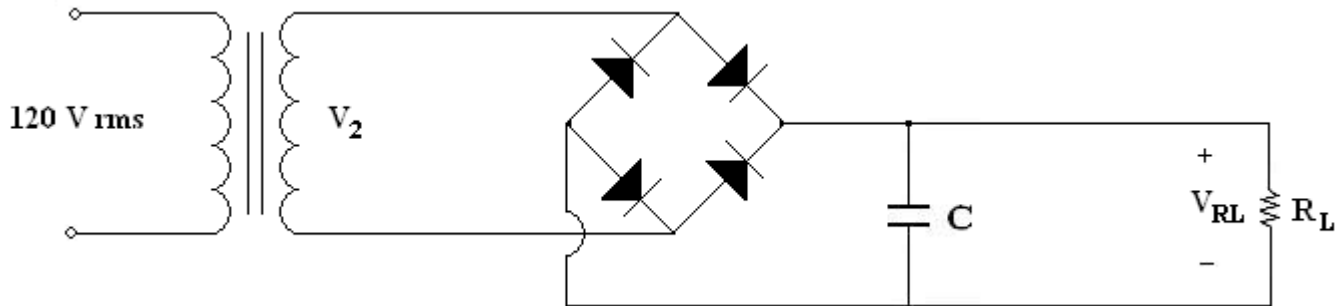


# JEE2330 – Spring 2025

## Lab #8 Problem

A DC power supply consisting of a transformer and a full-wave bridge rectifier with a capacitor filter is shown. The output voltage of the transformer is  $V_2 = 24$  V rms at a frequency of 60 Hz, and the output resistance  $R_L = 4.3$  k $\Omega$ . Assume that the voltage drop across each forward biased diode is 0.7 volts.



1. What is the peak positive voltage seen across the capacitor C and loaded resistor  $R_L$ ?

$$V_C = \underline{\hspace{2cm}}$$

2. What is the value of the capacitor needed for the peak-to-peak ripple voltage across the load resistor to be 0.2 volts?

$$C = \underline{\hspace{2cm}}$$

3. What is the DC voltage across the load resistor  $R_L$  considering both the drop across the diodes and the effect of the ripple voltage?

$$V_{RL} = \underline{\hspace{2cm}}$$

4. What is the DC power delivered to the load resistor?

$$P_{RL} = \underline{\hspace{2cm}}$$

5. What is the ripple factor for this power supply?

$$RF = \underline{\hspace{2cm}}$$